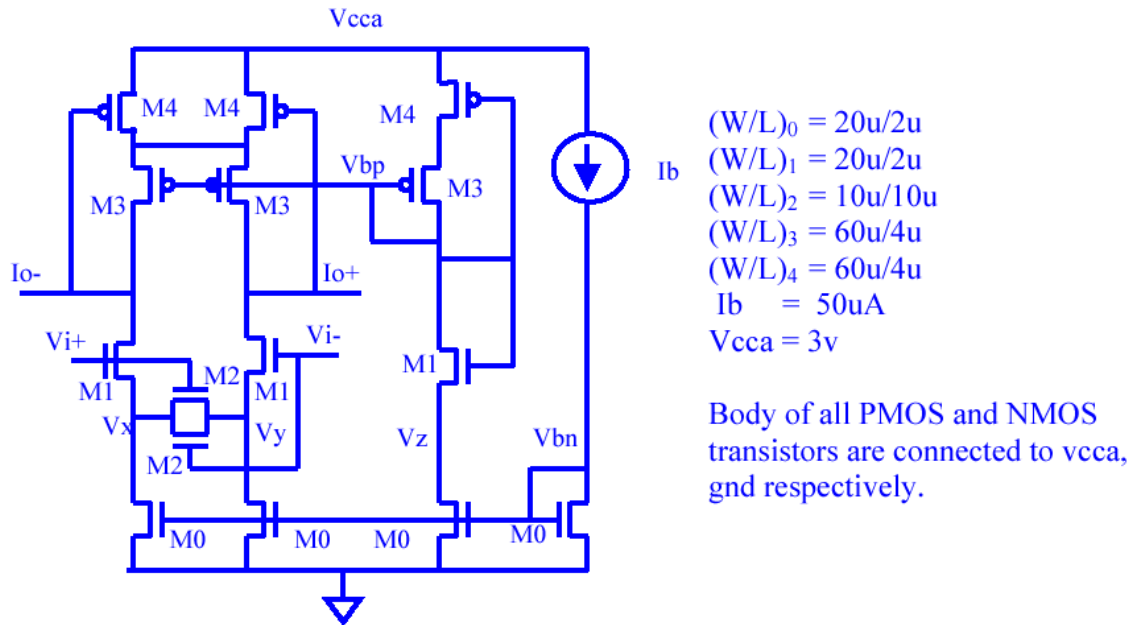


**EEE598D Homework #3**  
 Instructor: Dr. Hongjiang Song

Fuding Ge,  
 Register at ASU EAST

A fully differential CMOS transconductor circuit is shown in Fig.1.



**Fig.1 Fully differential CMOS transconductor circuit**

**Problem 1.** Derive the expression of differential transconductance  $g_m$  of this circuit and calculate  $g_m$  for the 0.5 $\mu m$  CMOS process (given in Homework#1). (Assuming 1.5v input common-mode voltage and neglecting body effects)

**Problem 2.** Simulate the differential  $g_m$  for the 1V peak-to-peak input voltage and a 1k resistive load across  $I^+$  and  $I^-$ . Plot  $I$  (across  $R$ ) and  $g_m$  vs.  $(v_i^+ - v_i^-)$ . Extract  $a_2$  and  $a_3$  from your simulation data using the curve fitting technique. Where  $a_2$  and  $a_3$  are non-linearity parameters defined as:

$$I^+ - I^- = g_m (V_i^+ - V_i^-) + a_2 (V_i^+ - V_i^-)^2 + a_3 (V_i^+ - V_i^-)^3$$

**Problem 1:**

This transconductor is first proposed by *Krummenacher and Joehl* (A 4-MHz CMOS continuous-time filter with on-chip automatic tuning, *IEEE JSSC*, Vol.23(3), 1988).

The following figure shows their original schematics.

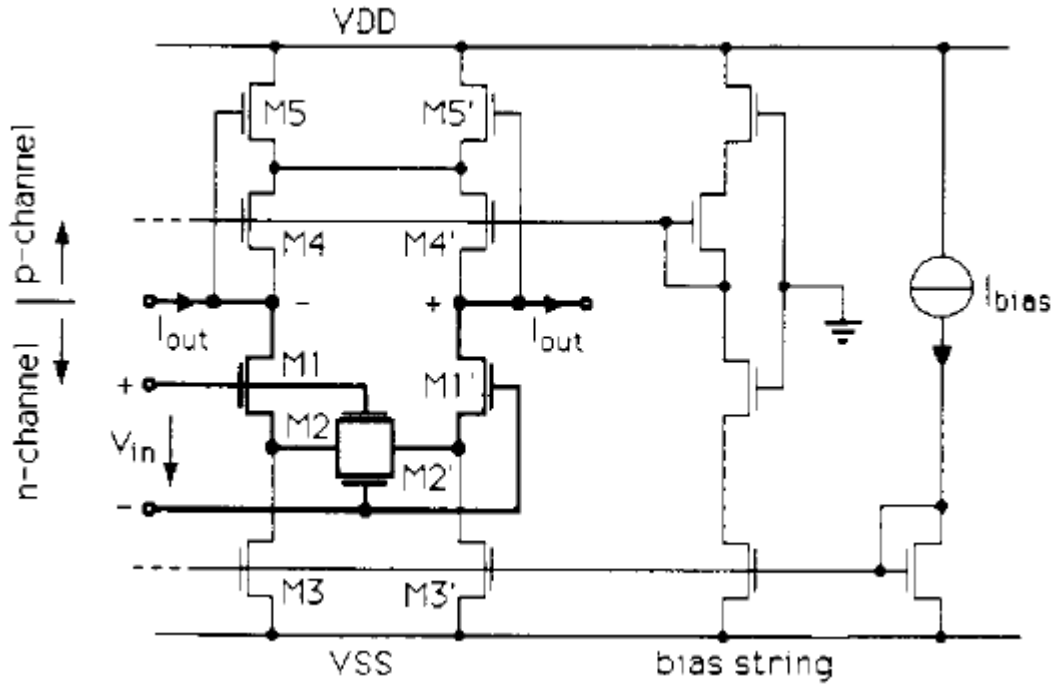


Figure.2 Original schematics proposed by *Krummenacher and Joehl*.

Its can be simplified as the following figure:

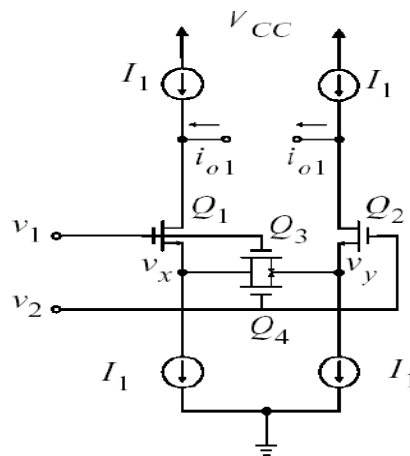


Figure.3 Simplified schematic shows the operation principle  
The current pass through transistor Q1 is:

$$I_1 + I_0 = \frac{\beta_1}{2}(v_i^+ - v_x - v_T)^2 \quad (1)$$

The current pass through transistor Q2 is (assuming  $\beta_1 = \beta_2$ ):

$$I_1 - I_0 = \frac{\beta_1}{2}(v_i^- - v_y - v_T)^2 \quad (2)$$

Then we have:

$$2I_0 = \frac{\beta_1}{2}[v_i^- - v_i^+ - (v_x - v_y)][v_i^- + v_i^+ - 2v_T - (v_x + v_y)] \quad (3)$$

The current pass through transistors Q3 and Q4 is equal to  $I_0$ , so we have:

$$\begin{aligned} I_0 &= \beta_3 \left\{ [v_i^+ - v_T - \frac{(v_x + v_y)}{2}](v_x - v_y) + [v_i^- - v_T - \frac{(v_x + v_y)}{2}](v_x - v_y) \right\} \\ &= \beta_3 (v_x - v_y) [v_i^+ + v_i^- - 2v_T - (v_x + v_y)] \end{aligned} \quad (4)$$

Using (3) and (4) we have:

$$\frac{\beta_1}{4}[v_i^+ - v_i^- - (v_x - v_y)] = \beta_3 (v_x - v_y) \quad (5)$$

We have:

$$v_x - v_y = \frac{\beta_1}{\beta_1 + 4\beta_3}(v_i^+ - v_i^-) \quad (6)$$

Now if we assume  $I_0$  is very small compared to  $I_1$ , then we can write the equations of Q1 and Q2 as:

$$\begin{aligned} \sqrt{\frac{2I_1}{\beta_1}} &= v_i^+ - v_x - v_T \\ \sqrt{\frac{2I_1}{\beta_1}} &= v_i^- - v_y - v_T \end{aligned} \quad (7)$$

From (7) we have:

$$2\sqrt{\frac{2I_1}{\beta_1}} = v_i^+ + v_i^- - (v_x + v_y) - 2v_T \quad (8)$$

Plug (6) and (8) into (4) we have:

$$I_0 = \beta_3 \frac{\beta_1}{\beta_1 + 4\beta_3} 2\sqrt{\frac{2I_1}{\beta_1}} (v_i^+ - v_i^-) \quad (9)$$

So the transconductance can be written as:

$$G_m = \frac{I_0}{(v_i^+ - v_i^-)} = \frac{2\beta_1\beta_3}{\beta_1 + 4\beta_3} \sqrt{\frac{2I_1}{\beta_1}} \quad (10)$$

$$G_m = \frac{I_0}{(v_i^+ - v_i^-)} = \frac{2\sqrt{\beta_1}\beta_3}{\beta_1 + 4\beta_3} \sqrt{2I_1} \quad (11)$$

We introduce the following parameter:

$$\alpha = 1 + \beta_1 / 4\beta_3 \quad (12)$$

Equation (11) can be written as:

$$G_m = \frac{I_0}{(v_i^+ - v_i^-)} = \frac{1}{1 + \frac{\beta_1}{4\beta_3}} \sqrt{\frac{I_1\beta_1}{2}} = \frac{1}{\alpha} \sqrt{\frac{I_1\beta_1}{2}} \quad (13)$$

From equation (7) we know:

$$\sqrt{\frac{I_1\beta_1}{2}} = \frac{I_b}{(V_{gs} - v_T)_{Q1}} \quad (14)$$

So we have:

$$G_m = \frac{I_b}{\alpha(V_{gs} - v_T)_{Q1}} \quad (15)$$

$\beta = u_n C_{ox} (W/L)$ . In this example, we have  $(W/L)_1 = 20\mu/2\mu$ ;  $(W/L)_2 = 10\mu/2\mu$ ;

For the 0,5 um process, form the MOSIS web we know:

$T_{ox} = 1.4E-8 \text{ m} = 1.4E-2 \text{ um}$

$$\mu_n = 452.9910821 \text{ cm}^2/\text{V S}$$

$$\epsilon_{ox} = 3.97 \times 8.85 \times 10^{-14} = 34.5 \text{ aF}/\mu\text{m}$$

$$C_{ox} = \epsilon_{ox}/T_{ox} = 2.46 \text{ fF}/\mu\text{m}^2.$$

$$\mu_n C_{ox} = 111 \text{ uA}/\text{V}^2.$$

We have:  $\beta_1 = \mu_n C_{ox} (W/L)_1 = 1110 \text{ uA}/\text{V}^2$  and  $\beta_3 = \mu_n C_{ox} (W/L)_3 = 111 \text{ uA}/\text{V}^2$

$$I_1 = 50 \text{ uA}.$$

Plug these parameters into equation (12) we get  $\alpha = 3.5$ .


Using equation (13) we get

$$\mathbf{gm = 47.5 \text{ uS}} \quad \mathbf{(16)}$$

See the simulation results in the next problem. The simulated results is about 48uS. The calculated result is in good agreement with the simulated results.

**More about this circuit:**

There is a optimum value of the  $\beta_1 / \beta_3$  for the best linearity performance. It appears to be about 7 (see the following figure). More detailed results please see *Krummenacher and Joehl (A 4-MHz CMOS continuous-time filter with on-chip automatic tuning, IEEE JSSC, Vol.23(3), 1988)*.

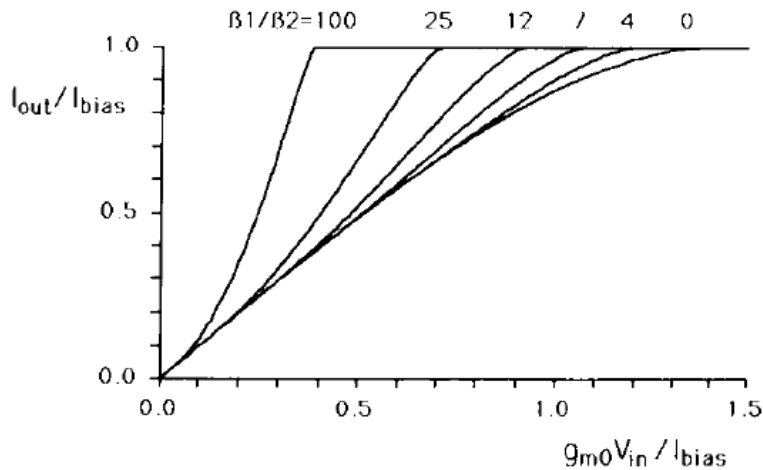

**Problem 2**

The following schematics is the simulation circuit.

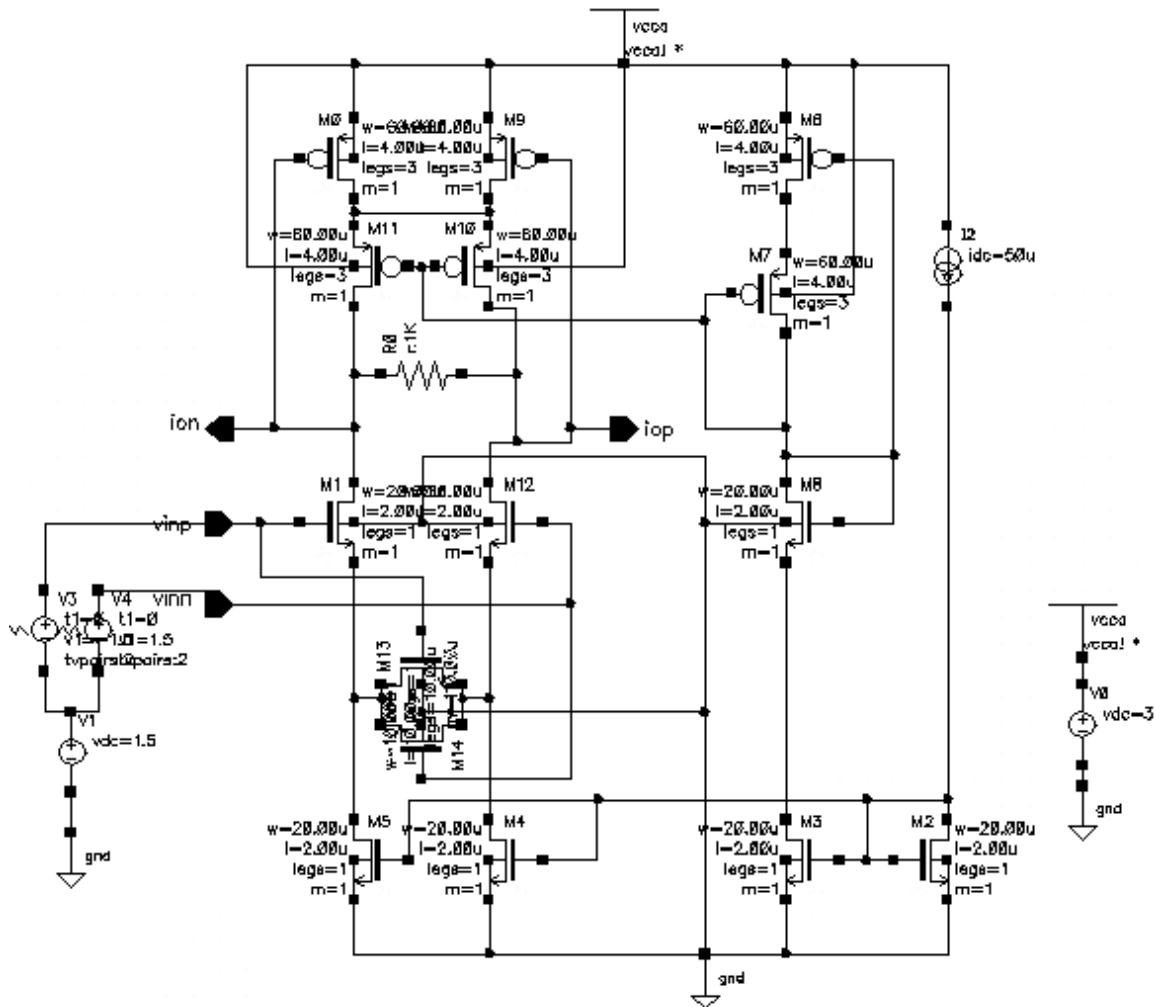


Figure.4 Simulation schematics used in this homework

The transistors M4 in figure.1 (or M5 and M5' in figure.2) operate in the triode region. See the following figure.

# Fuding Ge: Analog signal processing and filter circuits design

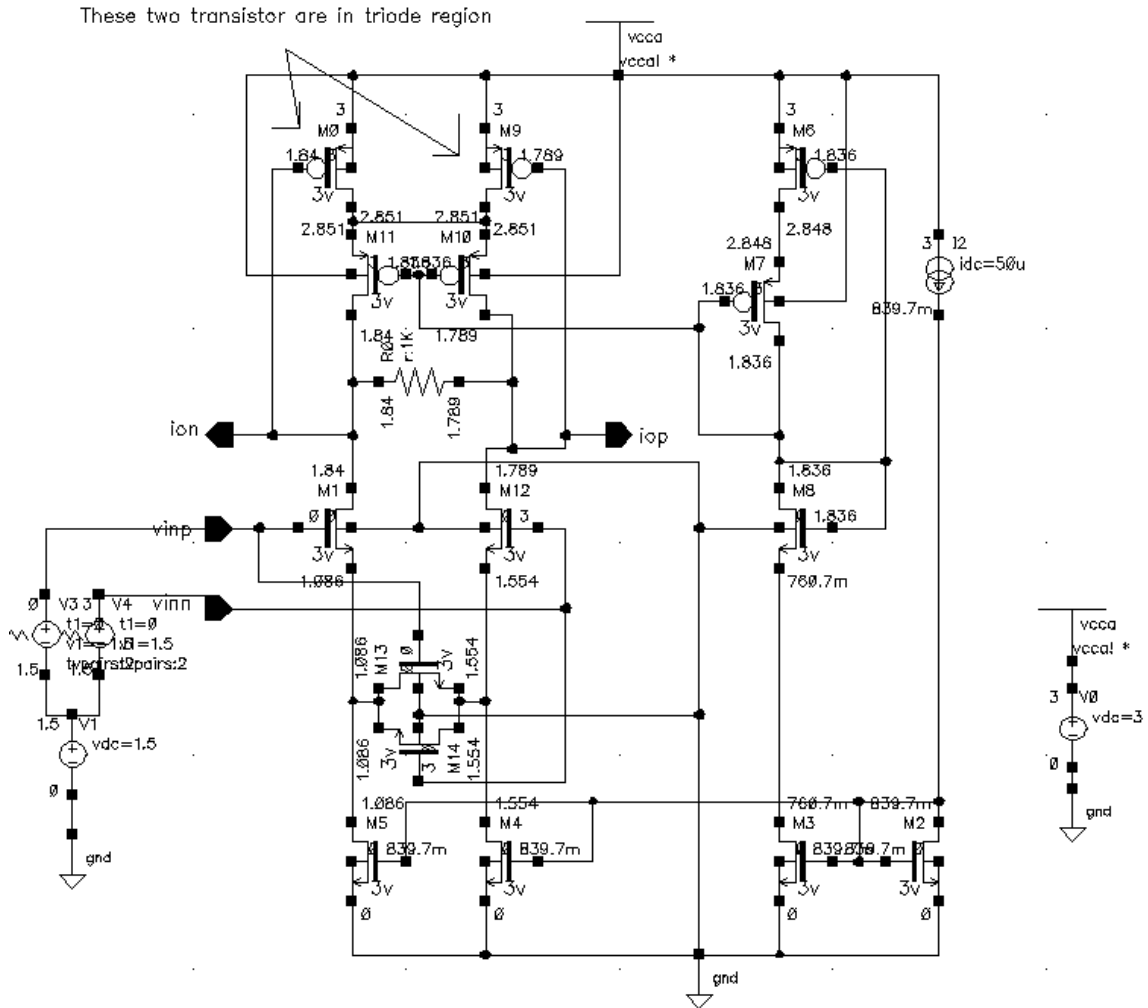


Figure.5 The DC node voltage of the circuit. It can be seen that the transistors of M4 in figure is in triode region.

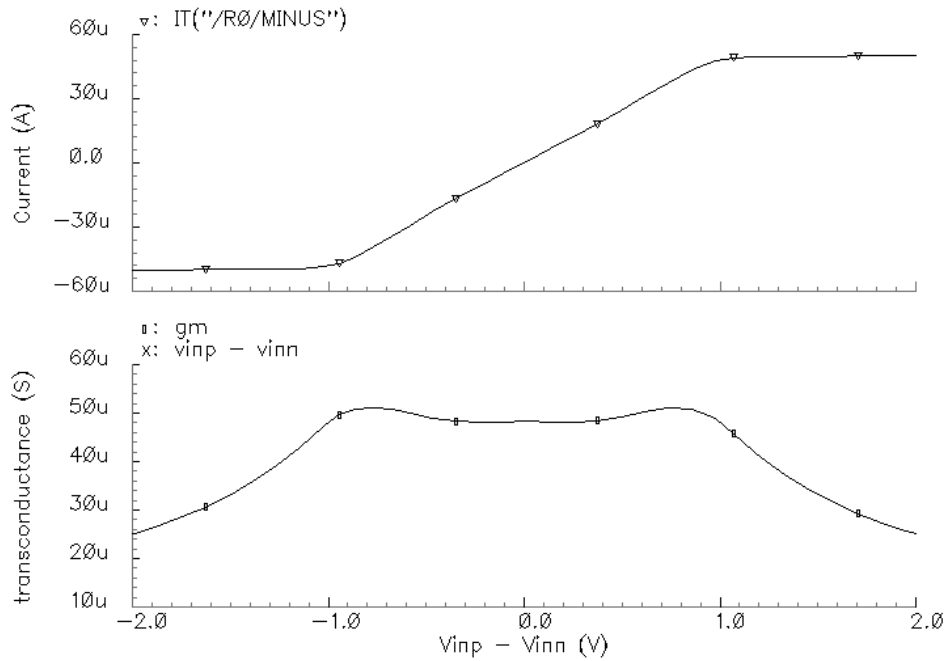


Figure.6 The simulation results: I (across R) and gm vs. the differential iunput.

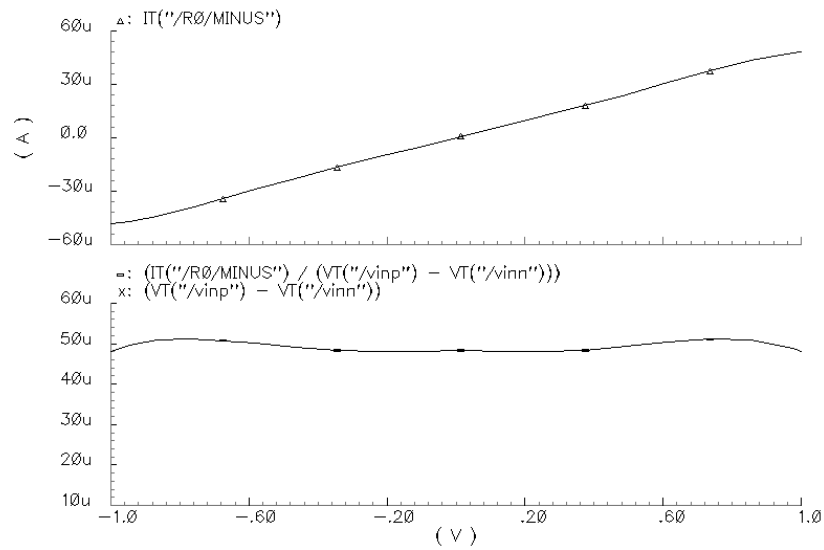


Figure.7 Detailed I and gm vs differential input in the region of -1V to 1V.

Note that the maximum output current is  $I_b=50uA$ .



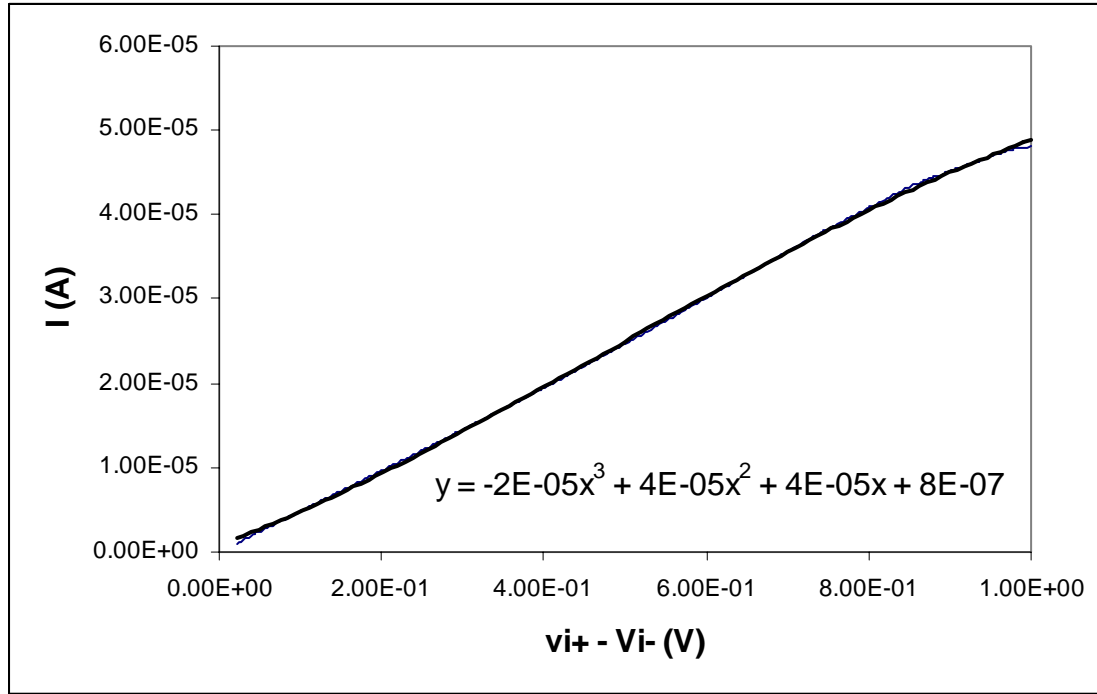


Figure.7 Curve fitting. This figure shows the value of  $g_m$  is about 40uS.  
 $\alpha_1=4E-5$ ,  $\alpha_2=4E-5$  and  $\alpha_3=2E-5$ .

Now we characterize its nonlinearity distortion.

### Harmonic distortion:

For a memoryless, time-variant system, assume:

$$y(t) = \alpha_1 x(t) + \alpha_2 x(t)^2 + \alpha_3 x(t)^3 \quad (17)$$

If the input  $x(t)$  is a sinusoidal signal given by:

$$x(t) = A \cos(\omega t) \quad (18)$$

The output is:

$$\begin{aligned} y(t) &= \alpha_1 A \cos(\omega t) + \alpha_2 A^2 \cos^2(\omega t) + \alpha_3 A^3 \cos^3(\omega t) \\ &= \alpha_1 A \cos(\omega t) + \alpha_2 A^2 \frac{1 + \cos(2\omega t)}{2} + \alpha_3 A^3 \frac{3 \cos(\omega t) + \cos(3\omega t)}{4} \\ &= \frac{\alpha_2 A^2}{2} + \left[ \alpha_1 A \cos(\omega t) + \frac{3\alpha_3 A^3}{4} \right] \cos(\omega t) + \frac{\alpha_2 A^2}{2} \cos(2\omega t) + \frac{\alpha_3 A^3}{4} \cos(3\omega t) \end{aligned} \quad (19)$$

## Fuding Ge: Analog signal processing and filter circuits design

It can be seen that the amplitude of the  $n$ th harmonic grows approximately in proportional  $A^n$ . For a fully differential system, all even terms are small, so typically  $\alpha_3$  dominates and the output signal can be approximately expressed as:

$$y(t) = \alpha_1 A \cos(\omega t) + \frac{\alpha_3 A^3}{4} \cos(3\omega t) \quad (20)$$

The fundamental is:

$$H_{D1} = \alpha_1 A \quad (21)$$

The 3<sup>rd</sup> order harmonic is:

$$H_{D3} = \frac{\alpha_3 A^3}{4} \quad (22)$$

The 3<sup>rd</sup> order harmonic distortion is defined as:

$$HD_3 = \frac{H_{D3}}{H_{D1}} = \frac{A^2}{4} \frac{\alpha_3}{\alpha_1} \quad (23)$$

Note that this distortion lies at  $3\omega t$  for a single sinusoidal input at  $\omega t$ .

For the circuit configuration we just simulated, we  $A=1V$ ,  $\alpha_3=2E-5$  and  $\alpha_1=4E-5$ . Use this data we find that:

$$HD_3 = -18dB \quad (24)$$

## **Intermodulation:**

If the input signal consists of two equally sized sinusoidal signals:

$$x(t) = A \cos(\omega_1 t) + A \cos(\omega_2 t) \quad (25)$$

The output signal is:

$$\begin{aligned} y(t) &= \alpha_1 x(t) + \alpha_2 x(t)^2 + \alpha_3 x(t)^3 \\ &= (\alpha_1 A + \frac{9\alpha_3}{4} A^3) [\cos(\omega_1 t) + \cos(\omega_2 t)] \\ &\quad + \frac{\alpha_3}{4} A^3 [\cos(3\omega_1 t) + \cos(3\omega_2 t)] \\ &\quad + \frac{\alpha_3}{4} A^3 [\cos(2\omega_1 t + \omega_2 t) + \cos(2\omega_2 t + \omega_1 t)] \\ &\quad + \frac{\alpha_3}{4} A^3 [\cos(2\omega_1 t - \omega_2 t) + \cos(2\omega_2 t - \omega_1 t)] \end{aligned} \quad (26)$$

Define:

$$I_{D1} = \alpha_1 A \quad (27)$$

$$I_{D3} = \frac{3\alpha_3}{4} A^3 \quad (28)$$

The 3rd intermodulation is defined as:

$$ID_3 = \frac{I_{D3}}{I_{D1}} = \frac{3A^2}{4} \frac{\alpha_3}{\alpha_1} \quad (29)$$

Use the simulated data we can get:

$$ID_3 = \frac{I_{D3}}{I_{D1}} = \frac{3A^2}{4} \frac{\alpha_3}{\alpha_1} = -8.5dB \quad (30)$$

### More simulation results:

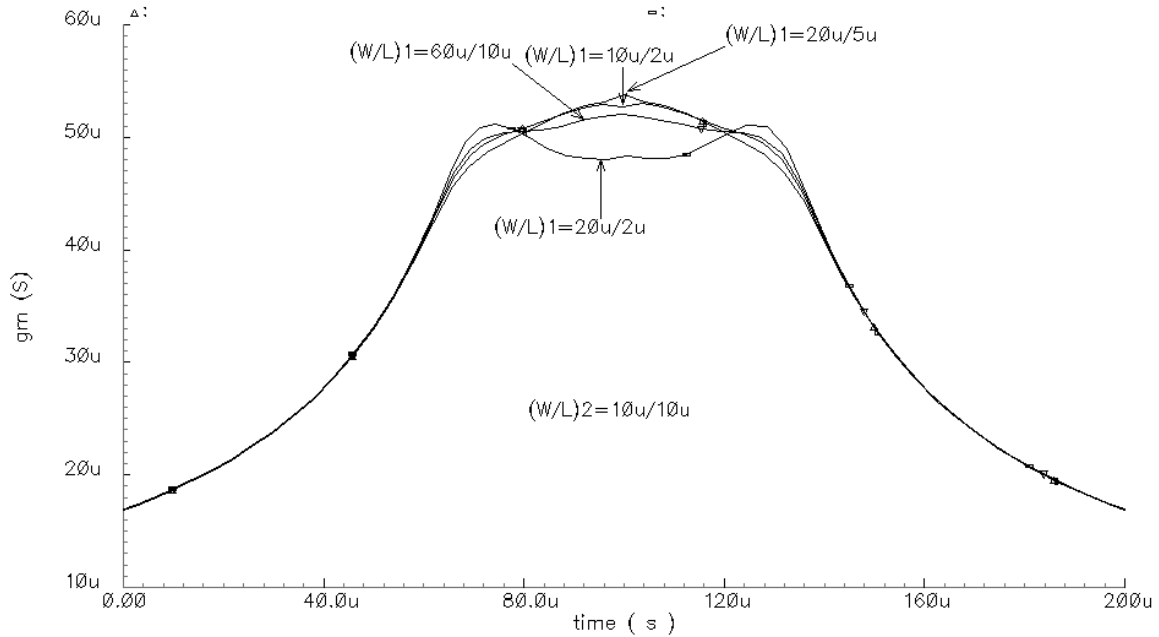


Figure 8: gm vs  $\beta_1/\beta_2$ . In this figure,  $\beta_2$  is kept to be constant and  $\beta_1$  changes.