

Spring 2002



**EEE598D: Analog Filter & Signal
Processing Circuits**

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering

Arizona State University

Thursday January 17, 2002



Today: Continuous-Time Filter Fundamental


- Fourier Transformation
- Laplace Transformation
- Transfer Function (TF)

RLC Network and Response



- The traditional question:

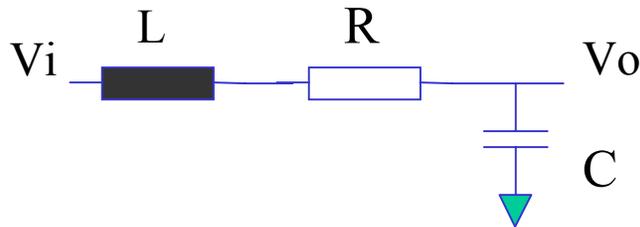For a given input $v_i(t)$ signal and a RLC network, what is the output signal $v_o(t)$?



$$\left\{ \begin{array}{l} LC \frac{d^2 v_o(t)}{dt^2} + RC \frac{dv_o(t)}{dt} + v_o(t) = v_i(t) \\ v_o(t) \Big|_{t=0} = v_o(0) \\ \frac{dv_o(t)}{dt} \Big|_{t=0} = \frac{dv_o(0)}{dt} \end{array} \right. \quad (1.1)$$

- The solution:

It is a differential equation.

– Solvable but not trivial!!

Steady State Response



- Sometimes we only interest in the steady state responses of the form:

$$\left\{ \begin{array}{l} v_i(t) = V_i e^{j\omega t} \text{ and} \\ v_o(t) = V_o e^{j\omega t} \end{array} \right. \quad (1.2)$$

- Equation (1.1) can be simplified as:

$$(1 - LC\omega^2 + j\omega RC)V_o = V_i \quad \text{or} \quad (1.3)$$
$$H(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 - LC\omega^2 + j\omega RC}$$

Frequency Response



- The magnitude (gain) response of the network is

$$|H(j\omega)| = \frac{1}{\sqrt{(1 - LC\omega^2)^2 + (RC\omega)^2}} \quad (1.5)$$


- We have:

$$|H(j\omega)|_{\omega \rightarrow 0} = 1$$

$$|H(j\omega)|_{\omega \rightarrow \infty} = 1/\omega^2 \Big|_{\omega \rightarrow \infty} = 0$$

$$|H(j\omega)|_{\omega \rightarrow 1/\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}} \equiv Q$$

Gain Response

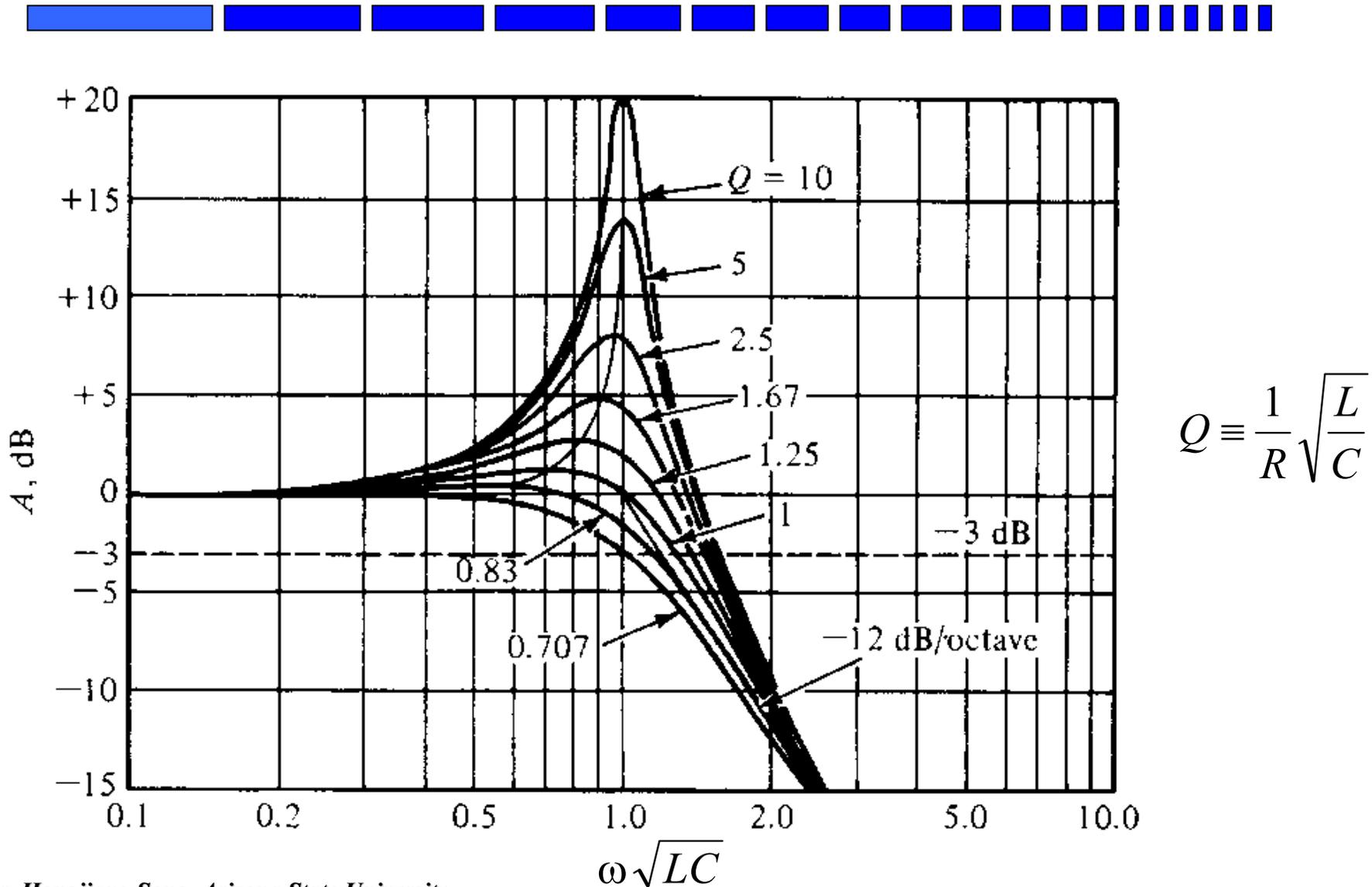

Frequency Response



- The phase response of the network is

$$\theta(j\omega) = \tan^{-1}\left(\frac{RC\omega}{(1-LC\omega^2)}\right) \quad (1.6)$$


- We have:

$$\theta(j\omega) \Big|_{\omega \rightarrow 0} = 0$$

$$\theta(j\omega) \Big|_{\omega \rightarrow 1/\sqrt{LC}} = -\pi / 2$$

$$\theta(j\omega) \Big|_{\omega \rightarrow \infty} = -\pi$$

Phase Response

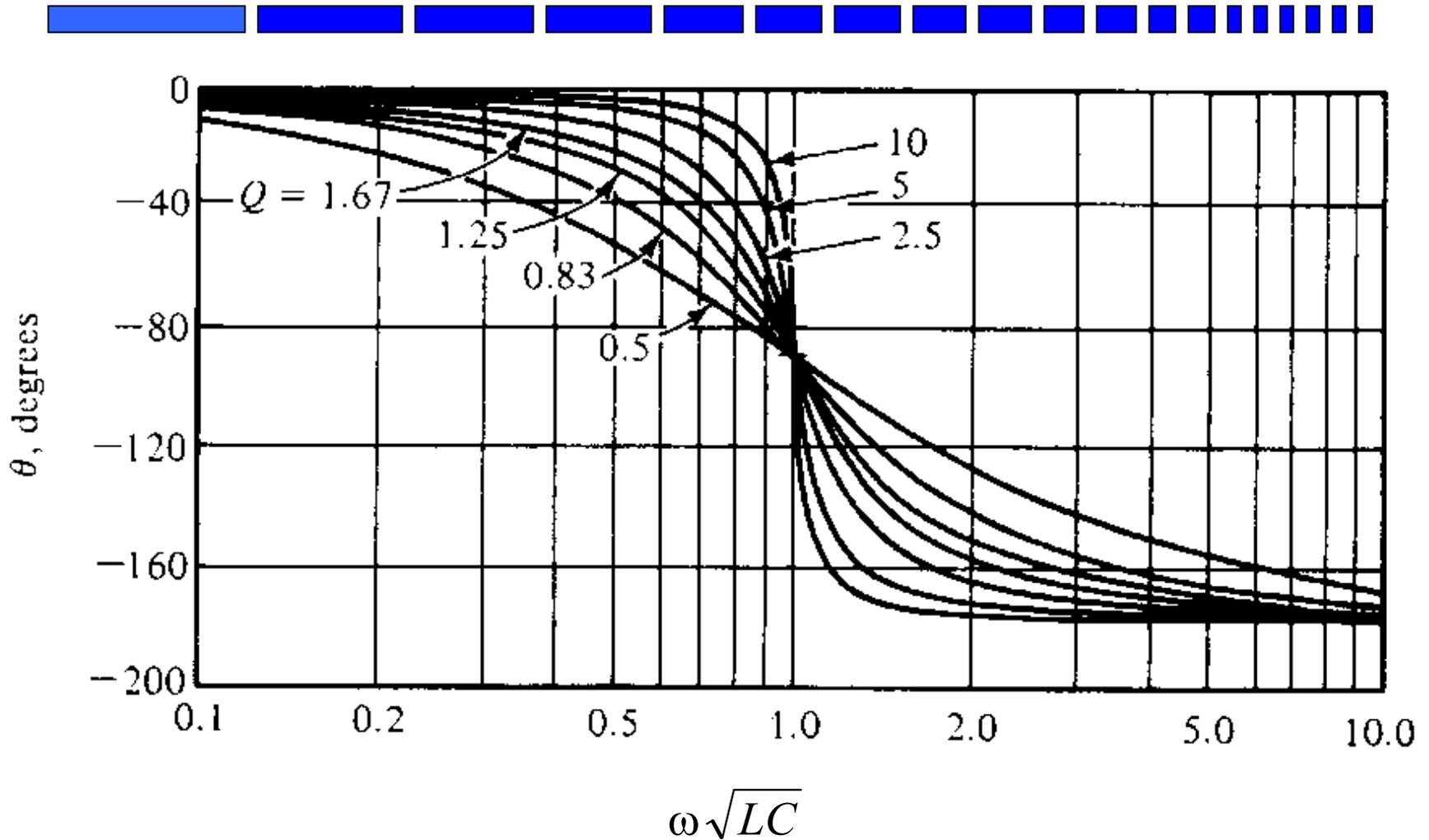

General Network Responses



- Question 1: How is the network response to a general input (non-sinusoidal) signal?
- Question 2: What is the network's transient response (non-steady-state response)?

Answer to Q1: Fourier Transformation



- A generic input signal can be expressed by combination of sinusoidal signal using Fourier transformation

The Fourier Transformation




- The Fourier Transform pair is defined as

$$F(j\omega) = \int_{-\infty}^{\infty} f(t)e^{-j\omega t} dt \quad (1.7)$$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega)e^{j\omega t} dt$$


Spectrum of $f(t)$

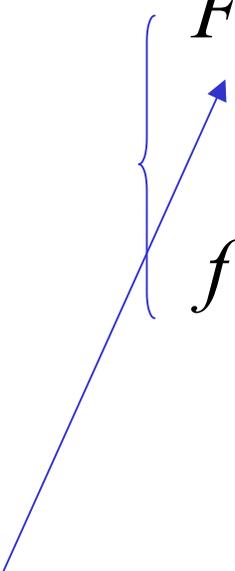

Useful *Fourier* Transform Pairs



$f(t)$	$F(j\omega)$
$df(t)/dt$	$j\omega F(j\omega)$
$\int_{-\infty}^t f(\tau) d\tau$	$\frac{1}{j\omega} F(j\omega) + \pi F(0)\delta(\omega)$
$f_1(t) * f_2(t)$	$F_1(j\omega)F_2(j\omega)$
$\int_{-\infty}^{\infty} f(t) ^2 dt$	$\frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) ^2 d\omega$
$f(t - t_0)$	$F(j\omega)e^{-j\omega t_0}$
$f(t)e^{j\omega_0 t}$	$F(j\omega - j\omega_0)$
$k_1 f_1(t) + k_2 f_2(t)$	$k_1 F_1(j\omega) + k_2 F_2(j\omega)$

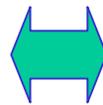

(1.8)

Useful *Fourier* Transform Pairs



$\delta(t)$		1	
$u(t)$		$\pi\delta(\omega) + \frac{1}{j\omega}$	
$e^{-a t }$		$\frac{2a}{\omega^2 + a^2}$	
$\left. \begin{array}{l} 1, \quad t < t_0 \\ 0, \quad t > t_0 \end{array} \right\}$		$(2/\omega) \sin \omega t_0$	
$\frac{\sin \omega_0 t}{\pi t}$		$\begin{cases} 1, & \omega < \omega_0 \\ 0, & \omega > \omega_0 \end{cases}$	
$e^{j\omega_0 t}$		$2\pi \delta(\omega - \omega_0)$	
1		$2\pi \delta(\omega)$	
$\cos \omega_0 t$		$\pi \delta(\omega - \omega_0) + \pi \delta(\omega + \omega_0)$	
$\sin \omega_0 t$		$-j\pi \delta(\omega - \omega_0) + j\pi \delta(\omega + \omega_0)$	

(1.9)

Response by Fourier Transformation



- Apply Fourier Transform to (1.1), we have

$$-LC\omega^2 V_o(j\omega) + j\omega RC V_o(j\omega) + V_o(j\omega) = V_i(j\omega)$$

$$\Rightarrow H(j\omega) \equiv \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{1 - LC\omega^2 + j\omega RC}$$

Answer to Q2: Laplace Transformation



- The transient response of the network can be calculated by using the Laplace Transformation

Laplace Transformation



- *The (one side) Laplace Transform* is defined as:

$$\left\{ \begin{array}{l} F(s) \equiv L(f(t)) \equiv \int_0^{\infty} f(t)e^{-st} dt \\ f(t) = L^{-1}(F(s)) = \frac{1}{2\pi j} \int_{\sigma - j\infty}^{\sigma + j\infty} F(s)e^{-st} dt \end{array} \right. \quad (1.10)$$


Useful *Laplace* Transform Pairs



$f(t)$		$F(s)$
$df(t)/dt$		$sF(s) - f(0)$
$\int_0^t f(\tau) d\tau$		$\frac{1}{s} F(s)$
$f_1(t) * f_2(t)$		$F_1(s) F_2(s) \quad (1.11)$
$f(t - a)u(t - a), a \geq 0$		$e^{-as} F(s)$
$tf(t)$		$-\frac{dF(s)}{ds}$
$e^{at}f(t)$		$F(s - a)$
$k_1 f_1(t) + k_2 f_2(t)$		$k_1 F_1(s) + k_2 F_2(s)$

Useful *Laplace* Transform Pairs

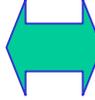

$\delta(t)$		1
K or $Ku(t)$		$\frac{K}{s}$
t^n		$\frac{n!}{s^{n+1}}$
e^{at}		$\frac{1}{s - a}$
$e^{at} \cos bt$		$\frac{s - a}{(s - a)^2 + b^2}$
$e^{at} \sin bt$		$\frac{b}{(s - a)^2 + b^2}$

(1.12)

General Continuous-Time Linear Filter



- A general continuous-time (CT) linear filter can be expressed as a differential equation:

$$\left\{ \begin{array}{l} \sum_{k=0}^n b_k \frac{d^k v_o(t)}{dt^k} = \sum_{k=0}^m a_k \frac{d^k v_i(t)}{dt^k} \\ \frac{d^k v_o(t)}{dt^k} \Big|_{t=0} = \frac{d^k v_o(0)}{dt^k} \quad k = 0, 1, \dots, n-1 \end{array} \right. \quad (1.13)$$

Filter Response using *Laplace* Transform



- The response of the above filter can be solved using Laplace Transform:

$$L\left(\sum_{k=0}^n b_k \frac{d^k v_o(t)}{dt^k}\right) = L\left(\sum_{k=0}^m a_k \frac{d^k v_i(t)}{dt^k}\right) \quad (1.14)$$

$$V_o(s) = \frac{\sum_{k=0}^m a_k s^k}{\sum_{k=0}^n b_k s^k} V_i(s) + T(s)$$


$$v_o(t) = L^{-1}\left[\left(\frac{\sum_{k=0}^m a_k s^k}{\sum_{k=0}^n b_k s^k}\right)V_i(s)\right] + L^{-1}[T(s)] \quad (1.15)$$

Initial condition

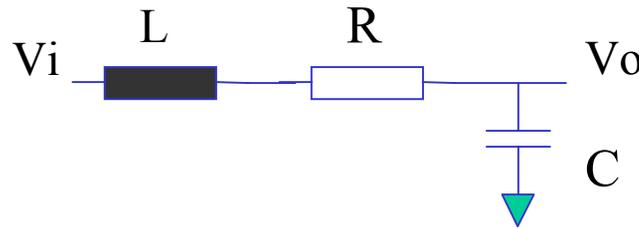Example of *Laplace* Transform



- Look at filter response of the above filter for given initial condition



$$\left\{ \begin{array}{l} LC \frac{d^2 v_o(t)}{dt^2} + RC \frac{dv_o(t)}{dt} + v_o(t) = Ae^{-j\omega t} \\ v_o(t) \Big|_{t=0} = 0 \\ \frac{dv_o(t)}{dt} \Big|_{t=0} = 0 \end{array} \right. \quad (1.16)$$

Example of *Laplace* Transform



- Using (1.5), we have

$$V_o(s) = \frac{1}{(LCs^2 + RCs + 1)} \frac{V_m}{(s + j\omega)} \quad (1.17)$$

- Let
$$\begin{cases} \alpha \equiv \frac{R}{2L} \\ \beta \equiv \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \end{cases} \quad (1.18)$$

- We have

$$V_o(s) = \frac{1}{(s + \alpha + j\beta)(s + \alpha - j\beta)} \frac{V_m}{(s + j\omega)} \quad (1.19)$$

Example of *Laplace* Transform



- With partial-fraction expansion, we have

$$V_o(s) = \frac{A}{(s + j\omega)} + \frac{B}{(s + \alpha + j\beta)} + \frac{C}{(s + \alpha - j\beta)} \quad (1.20)$$

- where
$$\left\{ \begin{aligned} A &= \frac{V_m}{s^2 LC + sRC + 1} \Big|_{s=j\omega} \\ B &= \frac{V_m}{(s + \alpha - j\beta)(s + j\omega)} \Big|_{s=\alpha + j\beta} \\ C &= \frac{V_m}{(s + \alpha + j\beta)(s + j\omega)} \Big|_{s=\alpha - j\beta} \end{aligned} \right. \quad (1.21)$$

Example of *Laplace* Transform



- Using (1.3) the response can be solved as:

$$v_i(t) = Ae^{-j\omega t} + \underbrace{Be^{-\alpha t - j\beta t} + Ce^{-\alpha t + j\beta t}}_{\text{transient response}} \quad (1.22)$$

transient response
($\rightarrow 0$ as $t \rightarrow \infty$)

$$A = \frac{V_o(s)}{V_i(s)} \Big|_{s=j\omega} \quad \text{steady-state response}$$

Transfer Function



- For steady-state response, the s-domain ratio of the output signal to input signal is known as the transfer function (TF) of the filter:

$$H(s) = \frac{V_o(s)}{V_i(s)} \quad (1.23)$$

- For the given example above, TF is given as:

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 LC + sRC + 1} \quad (1.24)$$

S-Domain Representation of Operators



- By using the Laplace Transform, we have:

Integrator:

$$y(t) = \int_{t_0}^t x(\tau) d\tau \Rightarrow Y(s) = \frac{1}{s} X(s) \Rightarrow \int dt \Leftrightarrow \frac{1}{s} \quad (1.25)$$

Differentiator:

$$y(t) = \frac{dx(t)}{dt} \Rightarrow Y(s) = sX(s) \Rightarrow \frac{d}{dt} \Leftrightarrow s \quad (1.26)$$

Transfer Function



- Generally, for a filter described the following linear differential equation:

$$\sum_{k=0}^n b_k \frac{d^k v_o(t)}{dt^k} = \sum_{k=0}^m a_k \frac{d^k v_i(t)}{dt^k} \quad (1.27)$$

- The transfer function can be calculated using *Laplace* Transform as:

$$H(s) = \frac{\sum_{k=0}^m a_k s^k}{\sum_{k=0}^n b_k s^k} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0} \quad (1.28)$$

S-Domain Impedance of Components



- By Laplace Transform, we have:

Resistor:

$$v(t) = Ri(t) \Rightarrow V(s) = RI(s) \Rightarrow$$

$$Z_R = R$$

Capacitor:

$$\frac{dv(t)}{dt} = \frac{I(t)}{C} \Rightarrow V(s) = \frac{1}{sC} I(s) \Rightarrow$$

$$Z_C = \frac{1}{sC} \quad (1.29)$$


Inductor:

$$v(t) = L \frac{di(t)}{dt} \Rightarrow V(s) = sLI(s) \Rightarrow$$

$$Z_L = sL$$

Calculation of Transfer Function

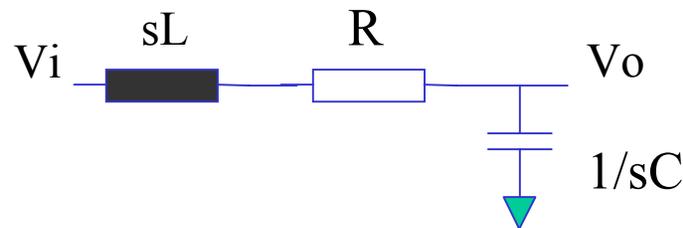- The transfer function of a linear circuit can be calculated by using s-domain impedance through *Kirchhoff's* law:



$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{Z_C}{Z_L + Z_R + Z_C} = \frac{1/sC}{sL + R + 1/sC} \\ &= \frac{1}{s^2 LC + sRC + 1} \end{aligned} \quad (1.30)$$

System Model of CT Filters



- Linear Systems

$$K(a_1x_1(t) + a_2x_2(t)) = a_1K(x_1(t)) + a_2K(x_2(t))$$

Diagram illustrating the linearity property. Two magenta arrows point from the word "constant" above to the coefficients a_1 and a_2 in the equation.

- Time- (shift-) Invariant Systems

$$\text{if } y(t) = K(x(t))$$

$$\text{Then } y(t - t_o) = K(x(t - t_o))$$

S-Domain Representation of Linear Time-Invariant (LTI) Systems



$$\begin{aligned} L\{y(t)\} &= L\{K(x(t))\} = L\left\{K\left(\int_{-\infty}^{\infty} x(\zeta)\delta(t-\zeta)d\zeta\right)\right\} \\ &= L\left\{\int_{-\infty}^{\infty} x(\zeta)K(\delta(t-\zeta))d\zeta\right\} = L\{x(t)\} \cdot L\{K(\delta(t))\} \end{aligned}$$

$$Y(s) \equiv L\{y(t)\}$$

Let:

$$X(s) \equiv L\{x(t)\}$$

Then:

$$h(t) \equiv K(\delta(t))$$

$$H(s) \equiv L\{h(t)\}$$

Impulse response of system

$$\frac{Y(s)}{X(s)} = H(s)$$

Transfer Function (TF) of system

Remark: Continuous-time LTI System can be completely determined by its impulse response.

Steady State Response of Continuous-Time LTI Systems



$$x(t) = Au(t)e^{j\omega t} \Rightarrow X(s) = A \int_0^{\infty} e^{-(s-j\omega)t} dt = \frac{A}{s-j\omega}$$

$$Y(s) = H(s) \cdot X(s) = \frac{H(s)}{s-j\omega} = \frac{H(j\omega)}{s-j\omega} + \text{Other Terms}$$

$$y(t)\Big|_{t \rightarrow \infty} = Au(t)H(j\omega)e^{j\omega t} + y_h(t) = H(j\omega)x(t)$$

Approach zero for stable system

Steady State Response of the system