

# Spring 2002



## **EEE598D: Analog Filters & Signal Processing Circuits**

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering

Arizona State University

Tuesday, February 19, 2002



Today: Introduction to SI Circuits

- Basic SI Circuits
- Errors of Practical SI Circuits
- Basic SI Building Blocks

# Why SI Technique?




- The switched-current (SI) technique for analog signal processing gained interest because of its ability to adapt to digital VLSI trends.
  - Low supply voltage
  - Poor device linearity
  - Lack of precision analog devices
  - Potentially high-speed
  - Very regular structure
- In SI circuits, signal is represented as **CURRENT**.
  - Imply no **DIRECT** impact of voltage scaling to signal swing

# SI or SC Circuits?



- Switched-current
  - low-voltage supply
  - high-speed
  - non-linear capacitors
  - no operational amps
  - modularity
  - possible to increase DR while keeping speed
  - 0.1% matching
- Switched-capacitor
  - high-accuracy
  - linear capacitors
  - high dynamic range
  - stability problems (opamps)
  - Different loads -> diff. OP architectures
  - 0.01% matching

# Basic CMOS Current Mirror

 


$$\frac{I_{out}}{I_{in}} = \frac{\mu_0 C_{ox} aW/L (V_{in} - V_{T2})^2}{\mu_0 C_{ox} W/L (V_{in} - V_{T1})^2} \frac{1 + \lambda_2 V_{out}}{1 + \lambda_1 V_{in}} \approx \frac{a \cdot I_{in}}{I_{in}} \approx a$$

# SI Circuit Principle



- The current through the transistor can be held using a capacitor storing the gate-source voltage of the transistor.


# The First-Generation Memory Cell

 

# The First-Generation Memory Cell



- Phase 1

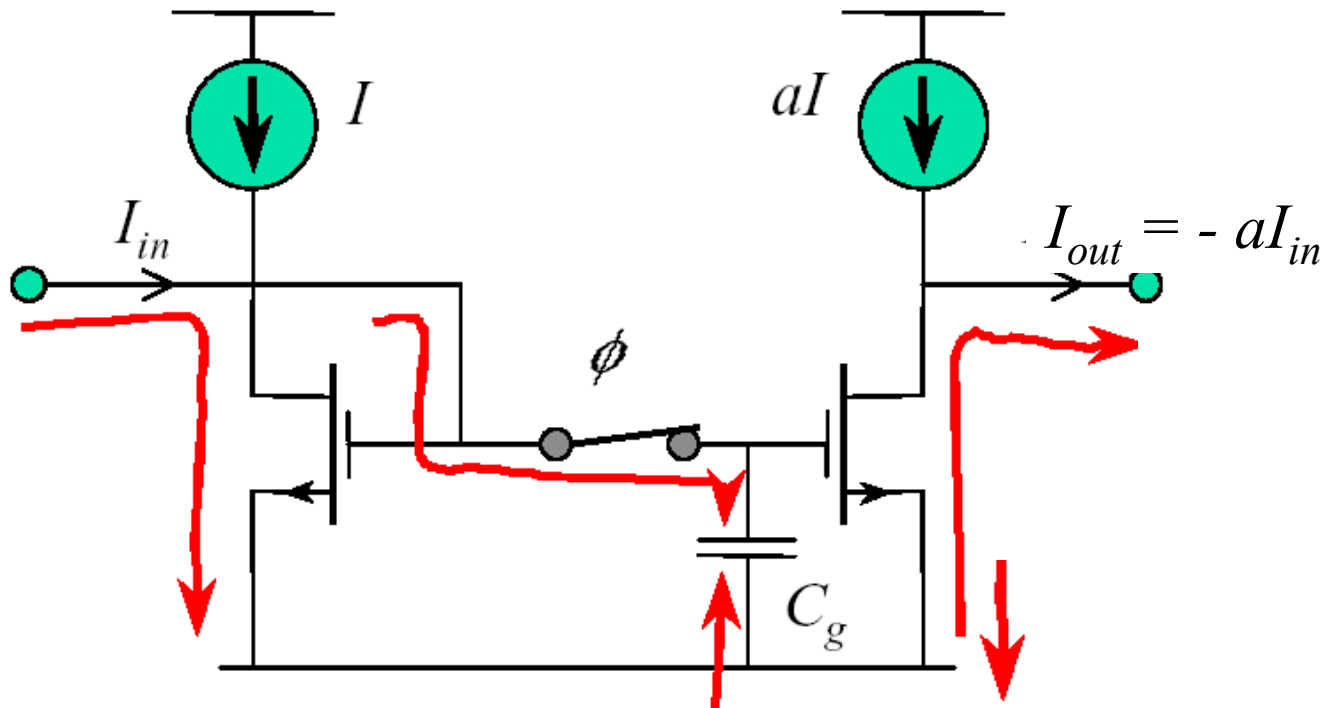





# The First-Generation Memory Cell




- Phase 2

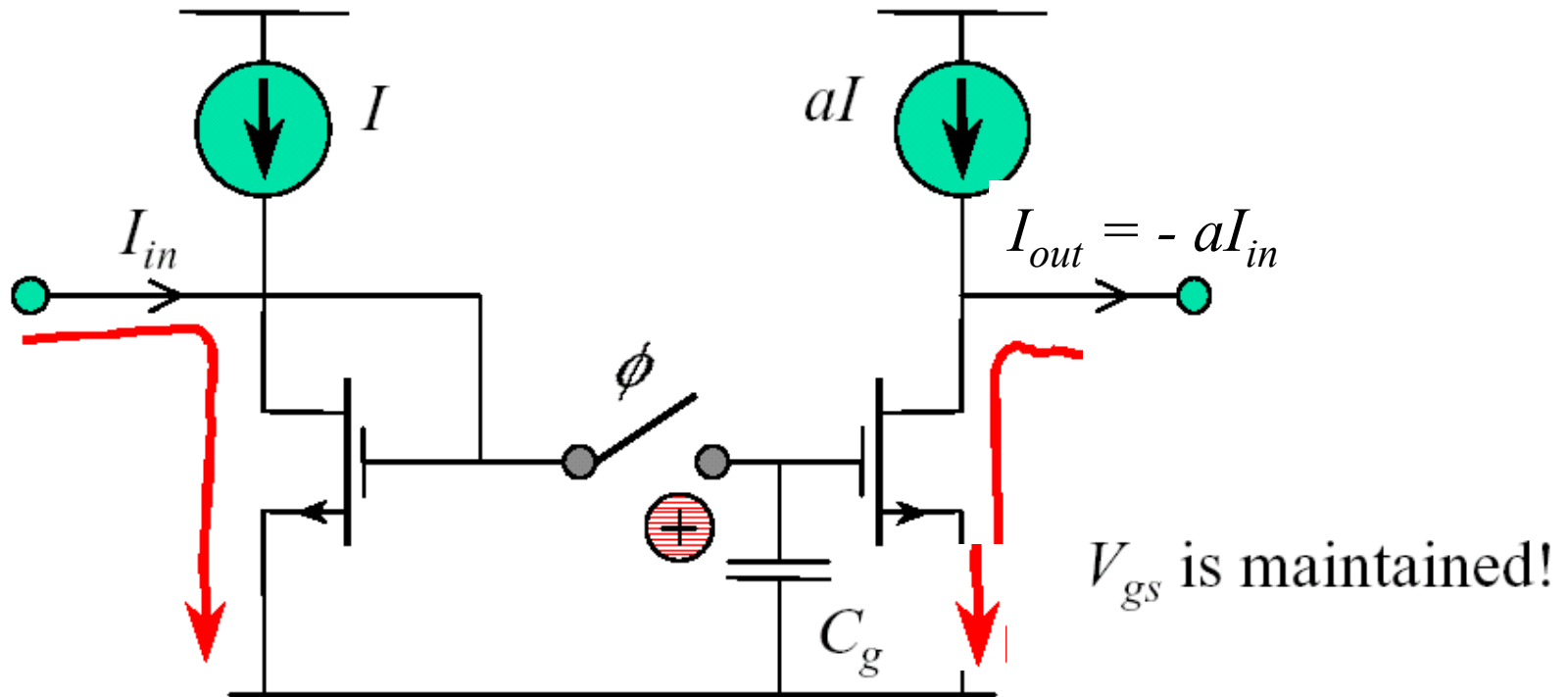

# SI Output Signal Waveform

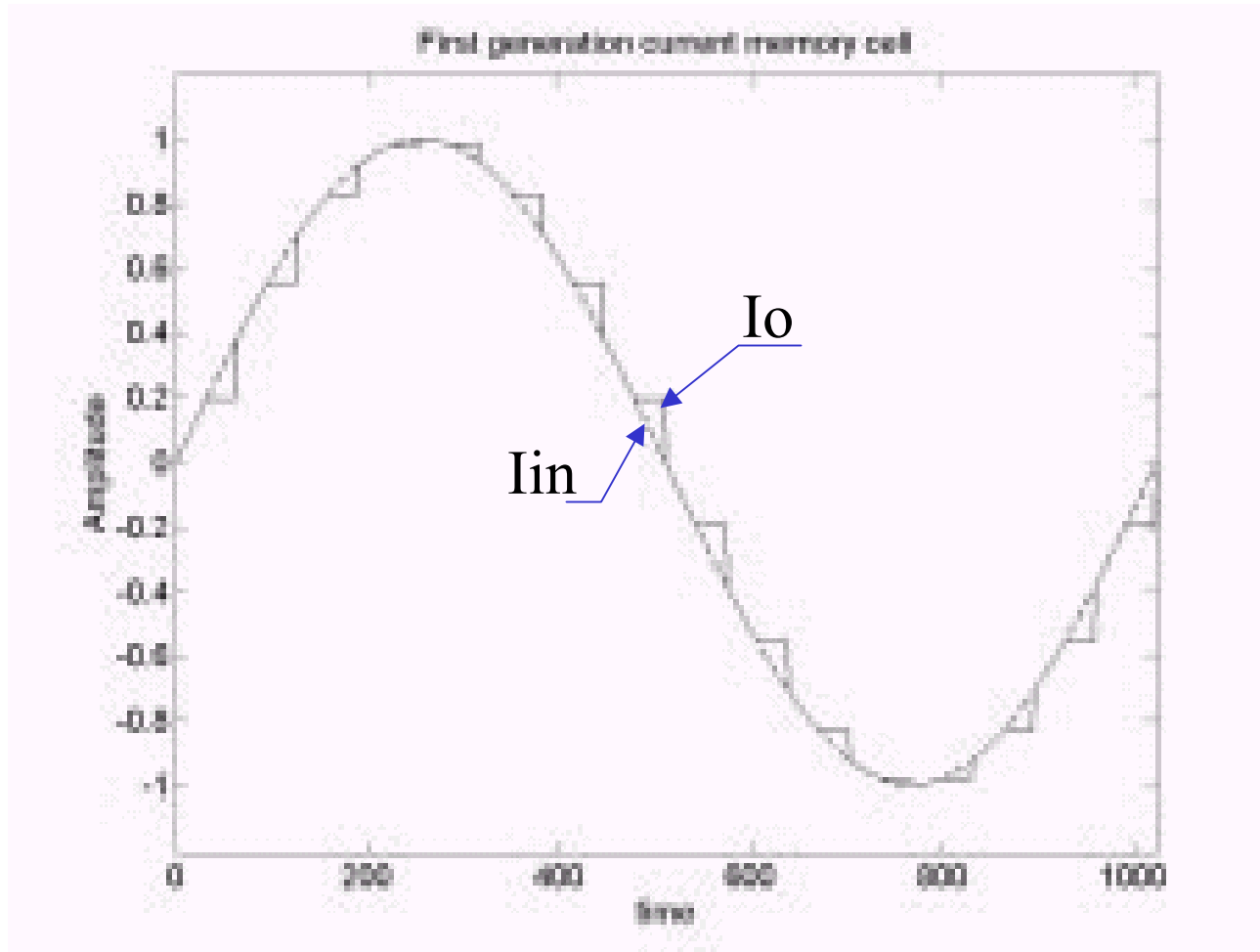


# The Second-Generation Memory Cell

 

# The Second-Generation Memory Cell




- Phase 1

 

# The Second-Generation Memory Cell



- Phase 2

 

$V_{gs}$  is maintained!

# Comparison



- First generation
  - Matching sensitive
  - Simple switching
  - High fan out
- Second generation
  - Matching insensitive
  - Low fan out
  - Less area
  - $1/f$  noise decreased
  - Complex switching

# Non-ideal Effects in Practical SI Circuits




- Device mismatches
- Channel length modulation
- Charge Injection
- Noise
- Settling and Leakage
- Power Line drop and bias mismatch
- Clock Jitter

# Device Mismatches



- MOS transistor mismatch

- Doping concentration
- Oxide thickness
- Finite edge resolution
- Lateral diffusion

$$I_d = k_p \left( \frac{W}{L} \right) (V_{gs} - V_T)^2$$


- Causes linear gain and constant offset errors

$$i_{out} = (1 + \epsilon)i_{in} + \epsilon I$$



# Device Mismatches (Con't)



- Global MOS transistor mismatch
  - Absolute mismatch
  - Overall PVT shift of process run
  - Long distance variation
- Local MOS transistor mismatch
  - Relative mismatch
  - PVT variation of nearby devices

# Device Mismatch Minimization

- Device size/area
- Device separation
- Bias current

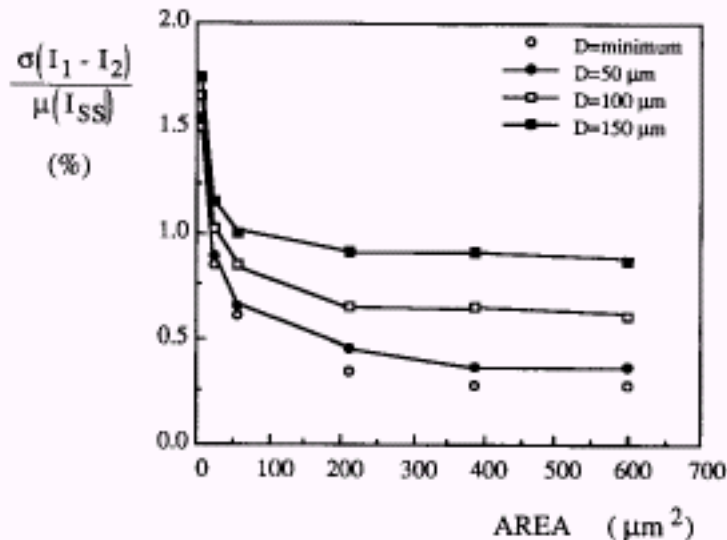


Fig. 13. Simulated device area and separation distance dependence of current mirror circuit. All simulations performed at  $I_{SS} = 50 \mu\text{A}$  and  $W/L = 1.5$ .


 


Fig. 14. Simulated bias dependence of current mirror circuit. All simulations performed for device areas of  $80 \mu\text{m}^2$  and at minimum separation distances.

# Device Mismatch Minimization

- Dynamic Current Mirror

 

 
# Channel Length Modulation



- Output resistance
- Early voltage

$$I_d = k_p \left( \frac{W}{L} \right) (V_{gs} - V_T)^2 (1 + \lambda V_{ds})$$



# Channel Length Modulation Minimization



- Cascade techniques

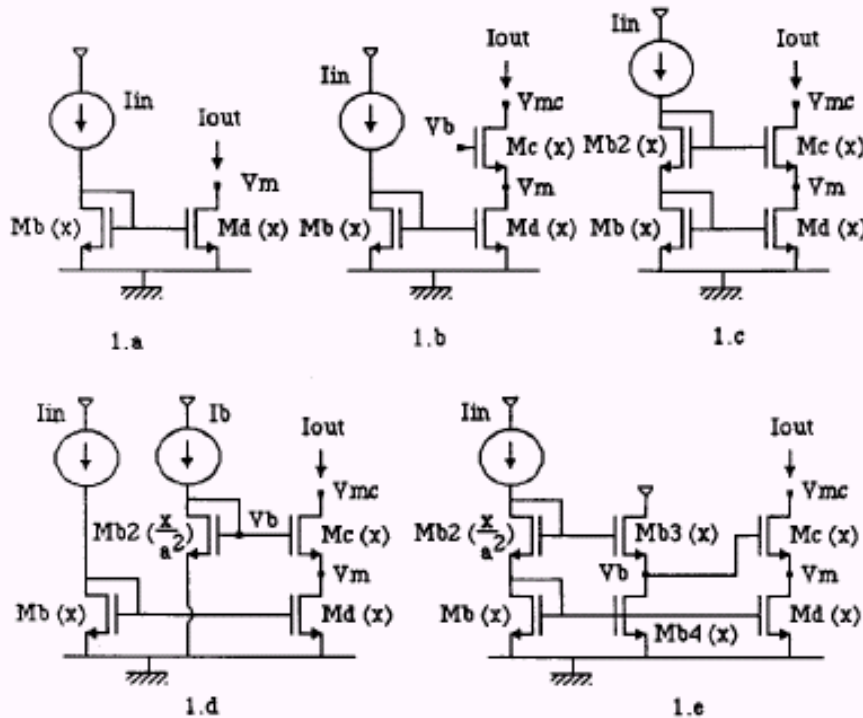


Fig 1. Circuit diagrams of common used current mirror structures ( $I_{in} \leq I_b$ )


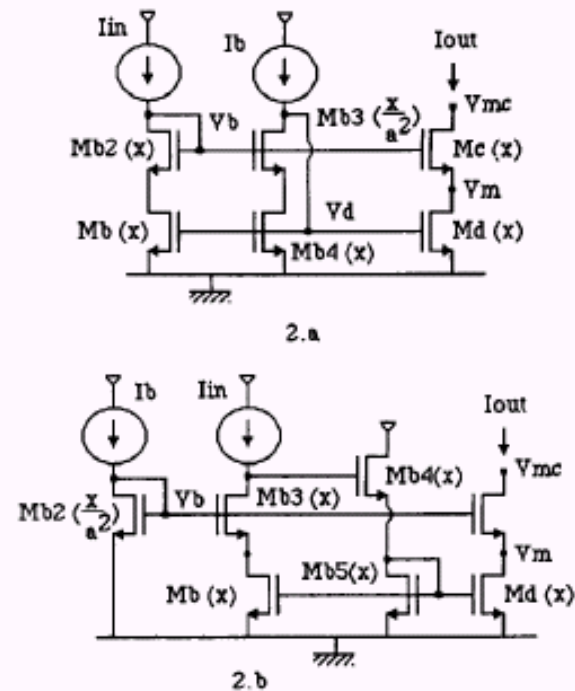


Fig 2. Current mirror structures reducing the channel length modulation


# Clock Feed Through (CFT)

 

- Switch signal coupling to the analog signal through the switches
- Channel-charge injection
- Causes nonlinear gain and constant offset errors



$$V_o = V_{in}$$

 


$$V_o \approx V_{in} - (C_c / C_h) \Delta V$$

# CFT Minimization




- Dummy switch device (I)

 

# CFT Minimization



- Dummy switch device (II)

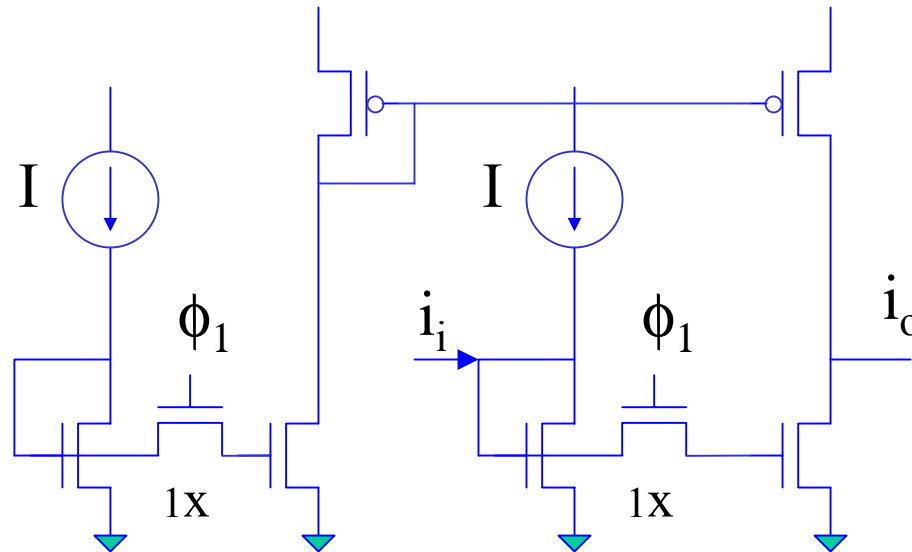





- Continuous-Time Circuit Noise

- Thermal noise
- Flicker noise
- Shot noise

$$S_{thermal} = \frac{8kTg_m}{3}$$

- Switching Noise

- Substrate
- Power line
- Cross-cap



$$S_{flick} = \frac{\alpha}{C_{ox}WL} \frac{1}{f}$$

$$S_{shot} = 2qI_{dj}$$
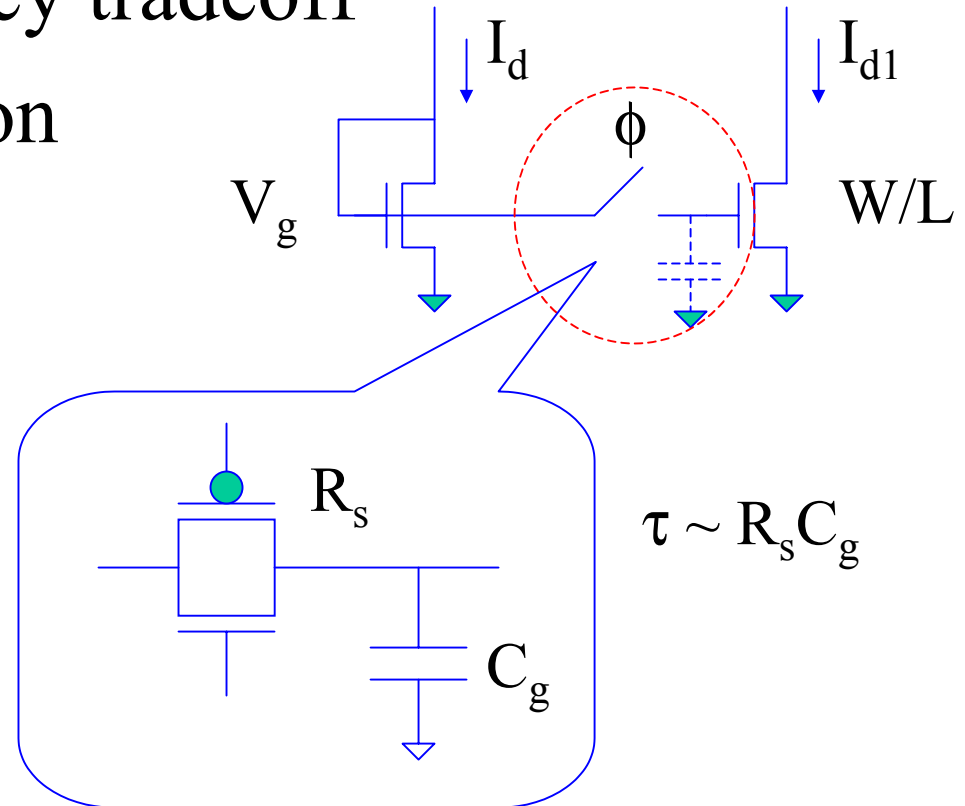 
# Settling





- Speed vs. Accuracy tradeoff
- Low  $V_{cc}$  limitation




# Settling



$$\frac{1}{R_s} \approx \beta_n (V_{cc} - V_{Tn} - V_{signal}) + \beta_p (V_{signal} - |V_{Tp}|)$$

  

A)  $V_{Tn} + |V_{Tp}| < V_{cc}$

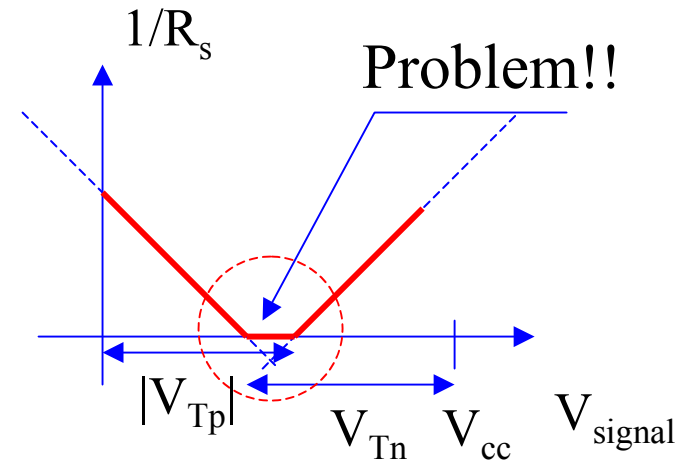


B)  $V_{Tn} + |V_{Tp}| > V_{cc}$
 
# Leakage




- Diode leakage
- Gate leakage
- Low frequency limit


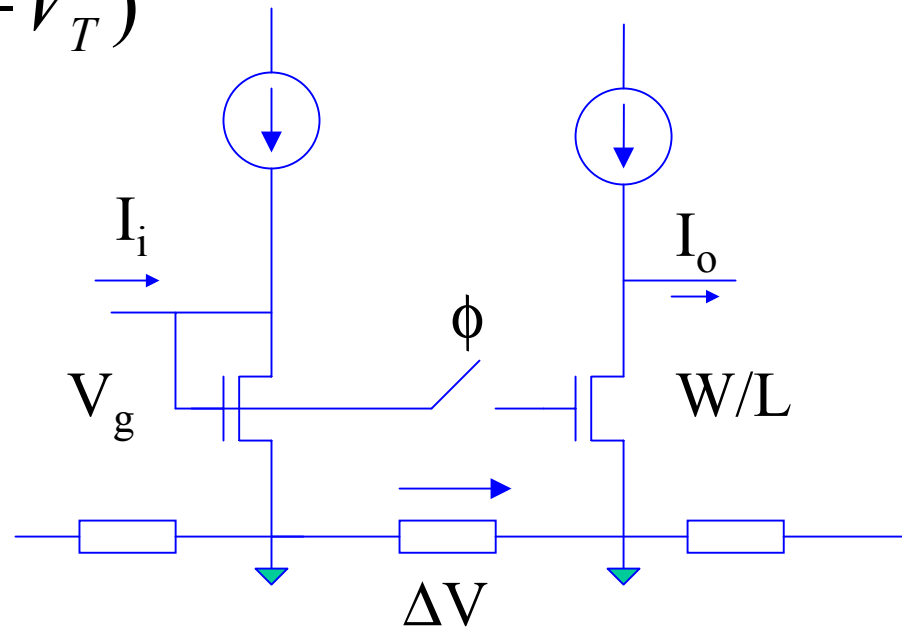
# Power Line IR Drop and Bias Mismatch



$$\frac{\Delta I_d}{I_d} \approx \frac{2\Delta V_{gs}}{(V_{gs} - V_T)}$$






# Basic SI Filter Building Blocks



- SI Delay Elements
- SI Adder
- SI Scalar
- SI Integrator

# SI Delay Element

 
 
 


$$i_o(nT) = i_i((n-1)T)$$

or

$$I_o(z) = z^{-1} I_i(z)$$

# SI Adder

  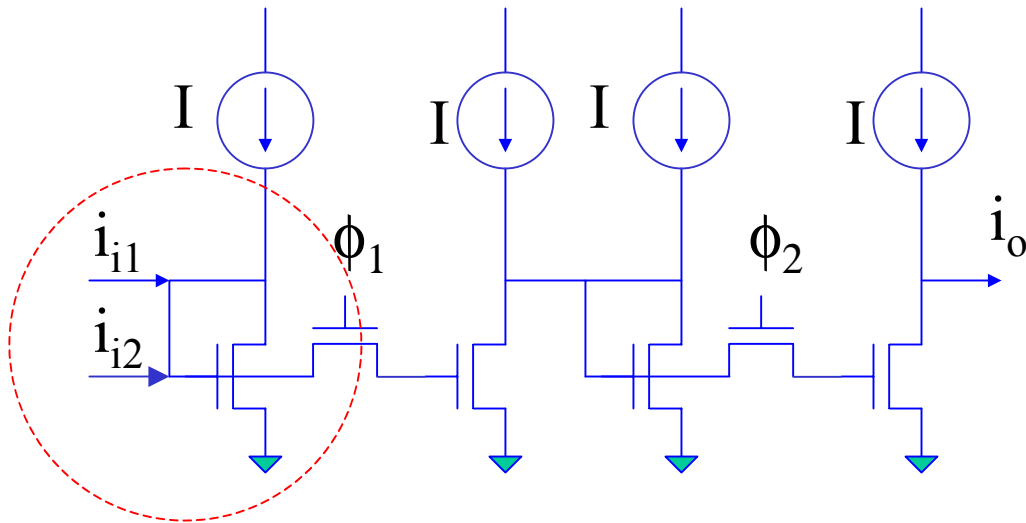


$$i_o(nT) = i_{i1}(nT) + i_{i2}(nT)$$

$$I_o(z) = I_{i1}(z) + I_{i2}(z)$$



# SI Scalar

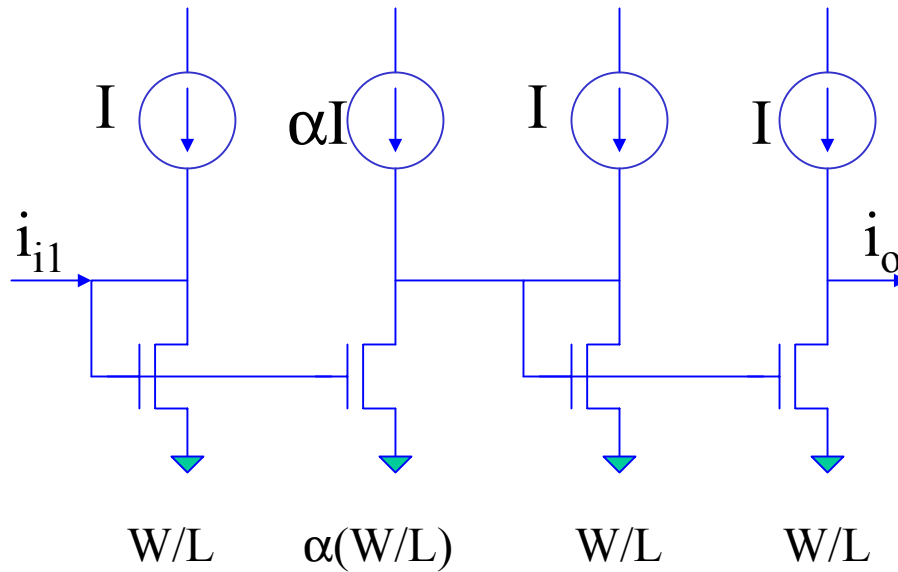

W/L

$\alpha(W/L)$


W/L

W/L


$$i_o(nT) = \alpha i_i(nT)$$

or

$$I_o(z) = \alpha I_i(z)$$

 


# SI Inverter

 


$$i_o(nT) = -i_i(nT)$$

*or*

$$I_o(z) = -I_i(z)$$

 

# SI Integrator

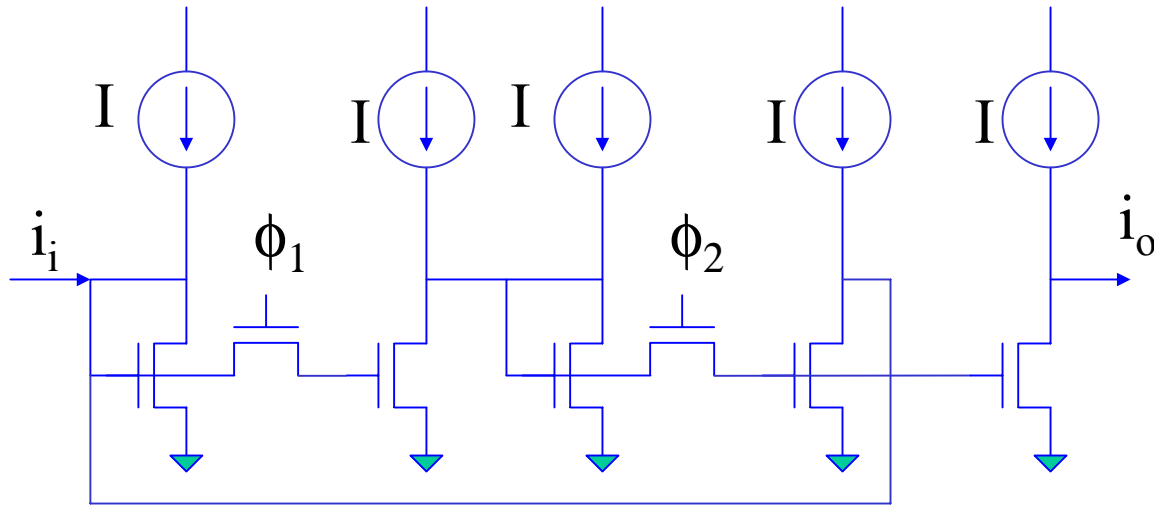

$$i_o(nT) = i_o((n-1)T) + i_i((n-1)T)$$

or

$$\frac{I_o(z)}{I_i(z)} = \frac{z^{-1}}{1 - z^{-1}}$$

