

Spring 2002



EEE598D: Analog Filter & Signal Processing Circuits

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering
Arizona State University

Thursday February 28, 2002



Today:


Frequency Scaling and Transformation

- Lowpass Prototype Filter
- Frequency Scaling
- Frequency Transformation

Lowpass Prototype Filter



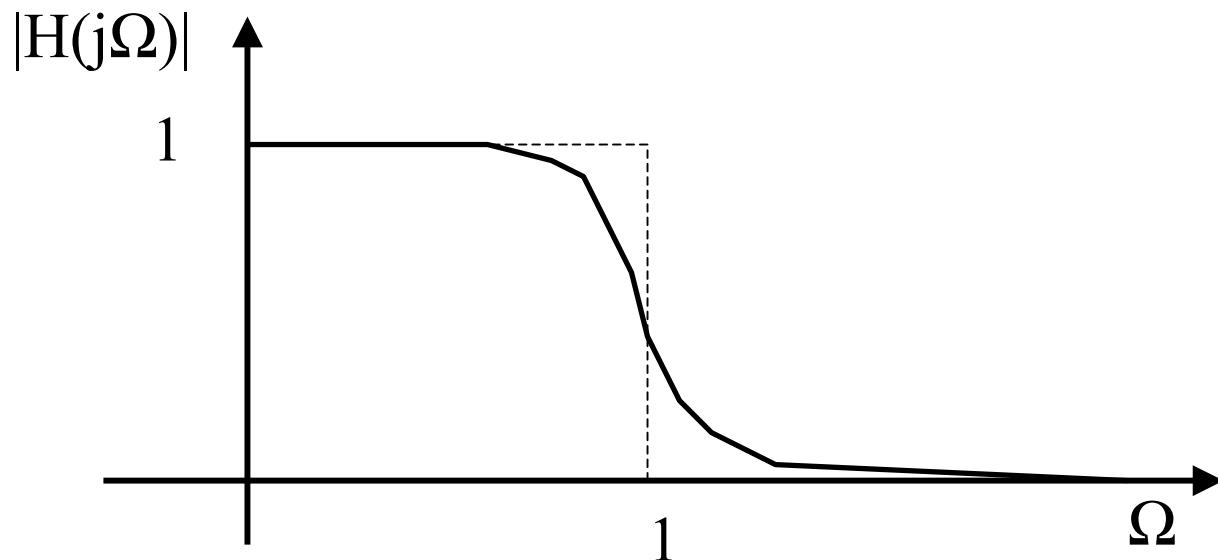
- It is a normalized filter.
- Passband $0 < \Omega < 1$
- Stopband $1 < \Omega$



Frequency Scaling



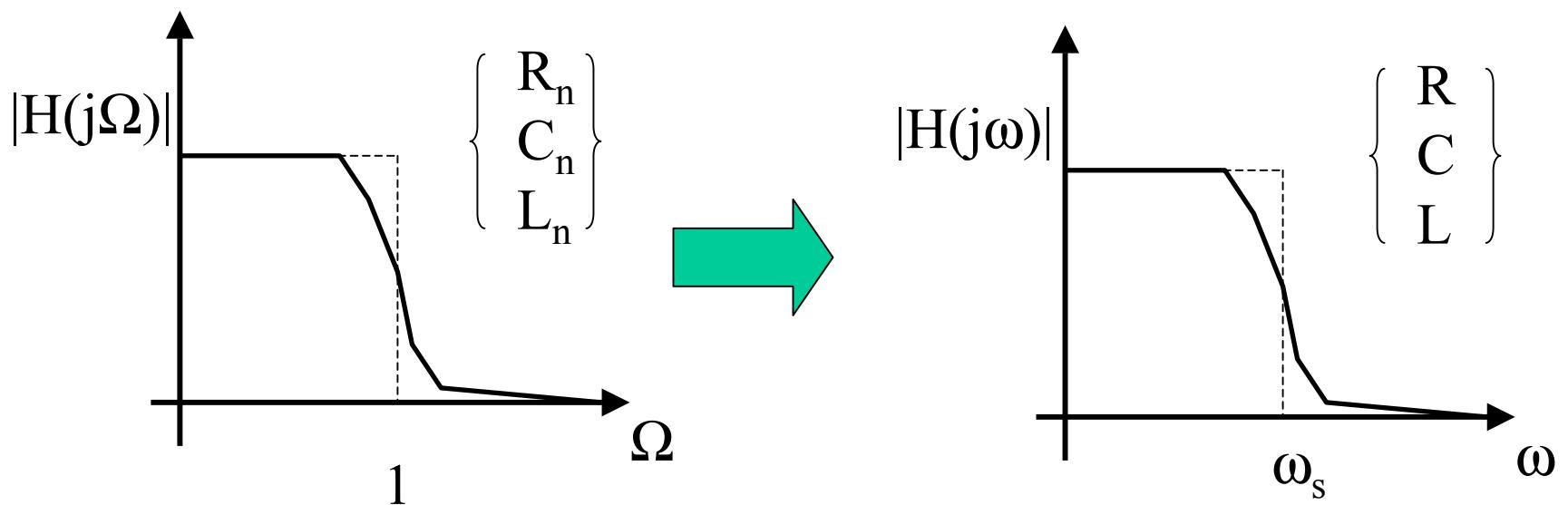- A lowpass filter with cutoff frequency ω_s can be built from the prototype lowpass filter



Frequency Scaling



by scaling the values of RLC with respect to the RLC of normalize (prototype) filter in the following way:

$$R = R_s R_n$$

$$C = \frac{C_n}{\omega_s R_s}$$

Arbitrary resistor scaling factor

$$L = \frac{R_s}{\omega_s} L_n$$

Frequency scaling factor


Frequency Scaling




Location of pole and zero of the transfer function:

$$p \Rightarrow \omega_s p$$


$$z \Rightarrow \omega_s z$$

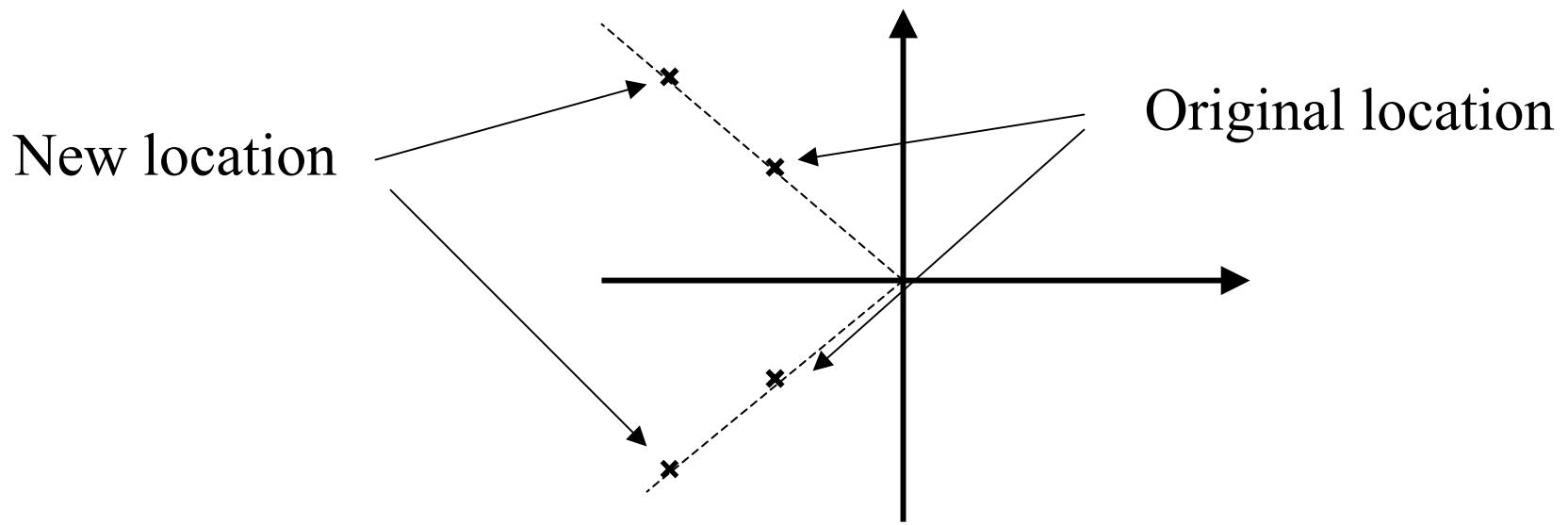

Example: Frequency Scaling

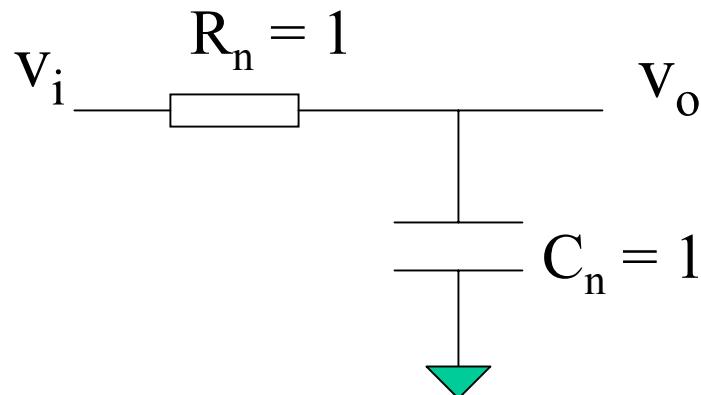

$$H_n(S) = \frac{1}{1 + S}$$

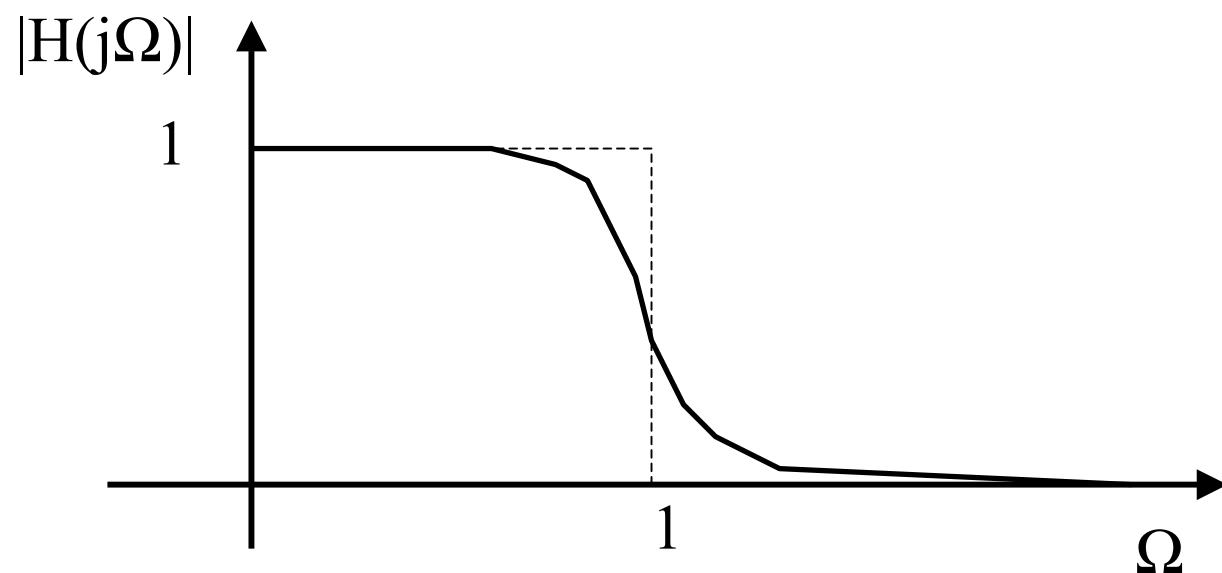


Example: Frequency Scaling (I)



Let $R_s = 1k$, $\omega_s/2\pi = 10\text{kHz}$, we have

$$R = R_s R_n = 1k\Omega$$
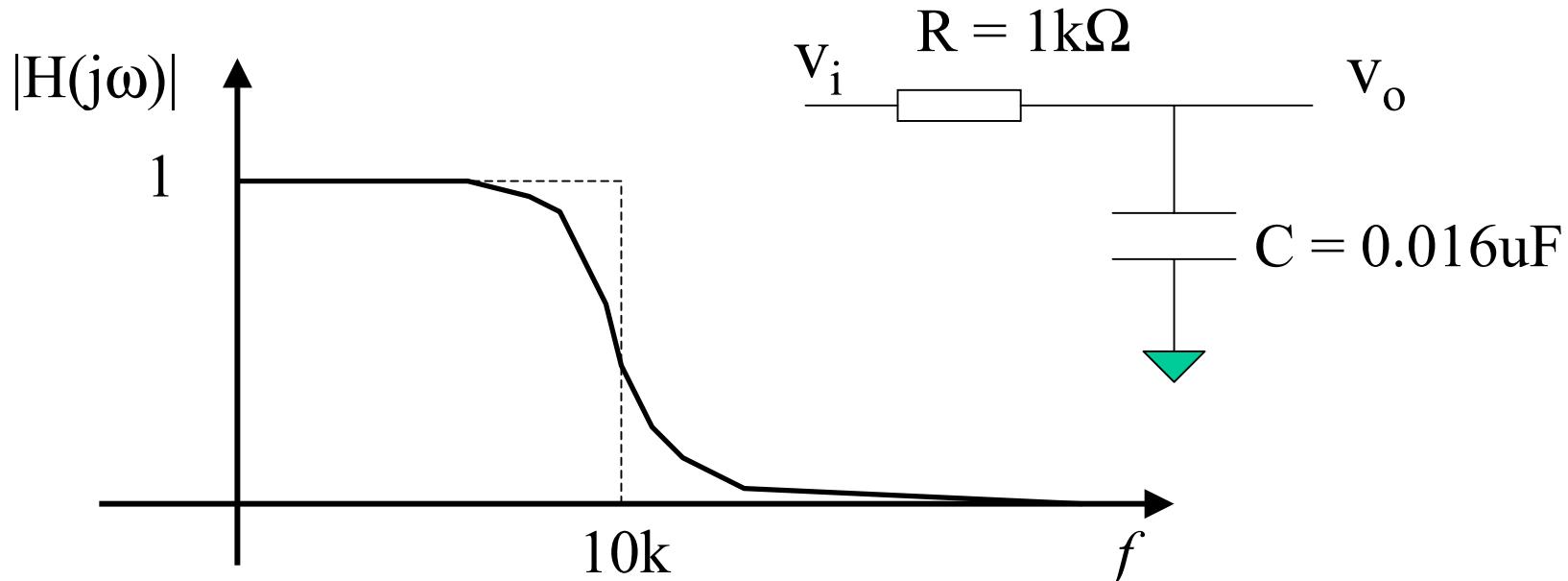
$$C = \frac{C_n}{\omega_s R_s n} = 0.016\mu F$$




Example: Frequency Scaling (II)



If let $R_s = 10k$, $\omega_s/2\pi = 10\text{kHz}$, we have

$$R = R_s R_n = 10k\Omega$$
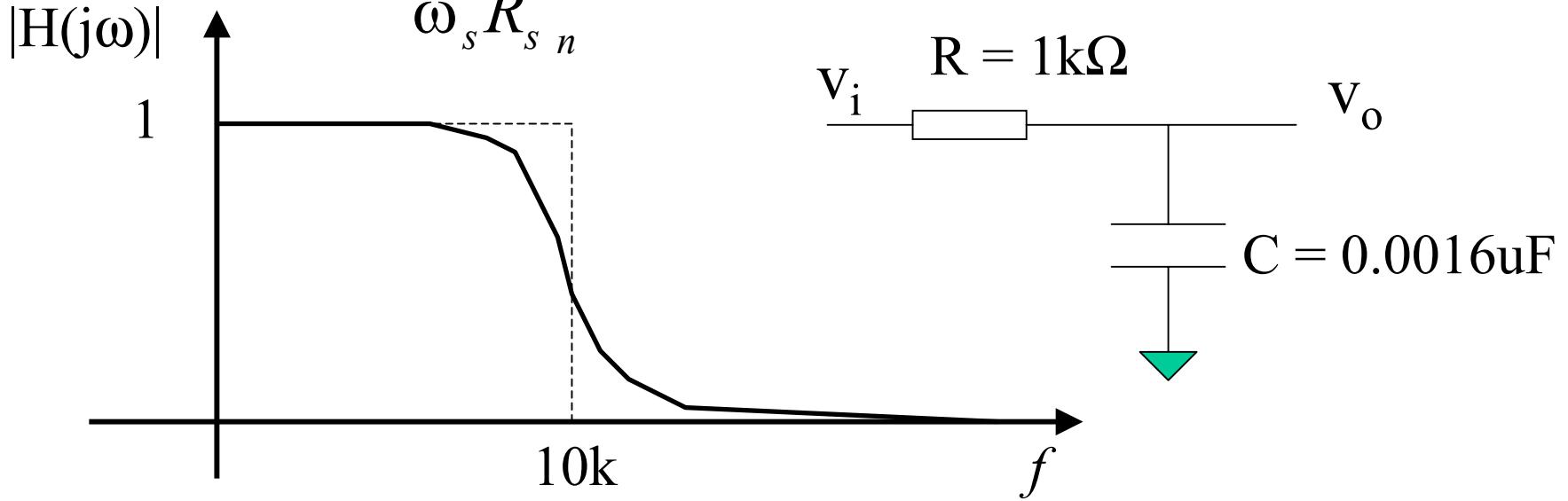
$$C = \frac{C_n}{\omega_s R_s n} = 0.0016\mu F$$



The solution is not unique!!

Typical Component Values in IC



Tolerances: $10 \sim 40\%$ absolute

$0.1 \sim 1\%$ for ratio

Resistor: $50 \sim 100k\Omega$

Capacitor: $0.5 \sim 50\text{pf}$

Inductor: $<10\text{nH}$ (lossy)

Frequency Transformation




- Lowpass-to-highpass transformation
- Lowpass-to-bandpass transformation
- Lowpass-to-bandstop transformation
- Lowpass-to-multi-bandpass transformation


Lowpass-To-Highpass Transformation


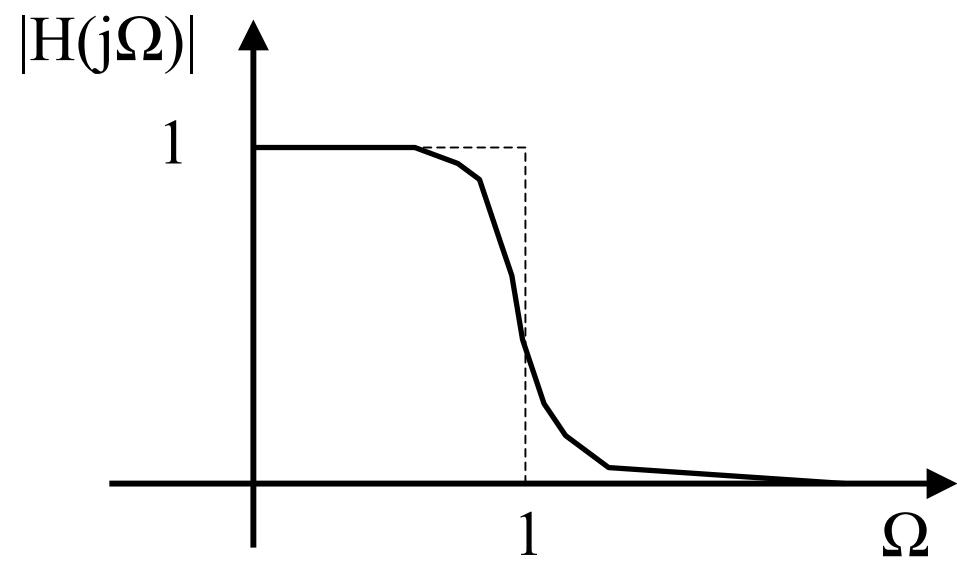
$$\Omega = -\frac{\omega_o}{\omega} \quad \text{or} \quad S = \frac{\omega_o}{s}$$



A) Lowpass prototype

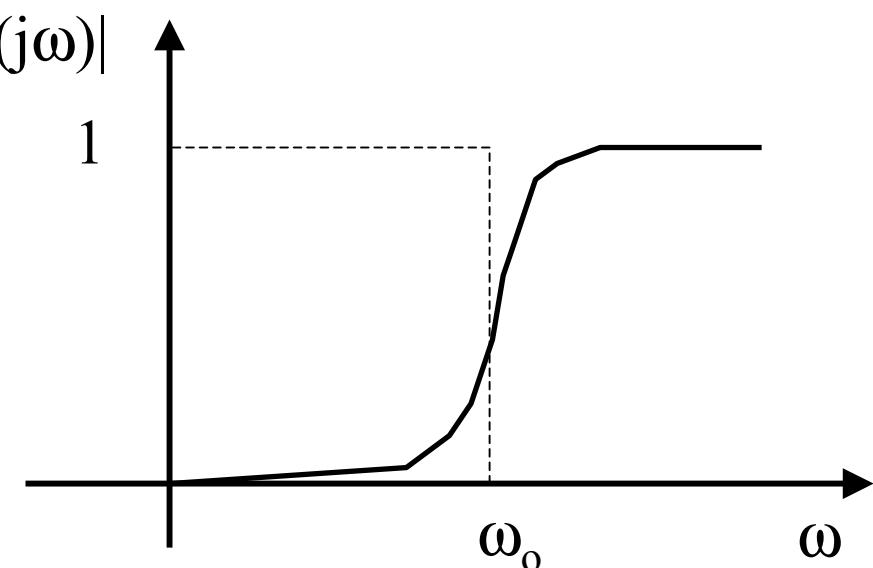


B) Highpass normalized

Lowpass-To-Highpass Transformation



- Location of poles of the transfer function

$$p_{LP} \Rightarrow \frac{p_{HP}}{\omega_o} = \frac{1}{p_{LP}} = \left| \frac{1}{p_{LP}} \right| e^{-\theta_{PL}}$$

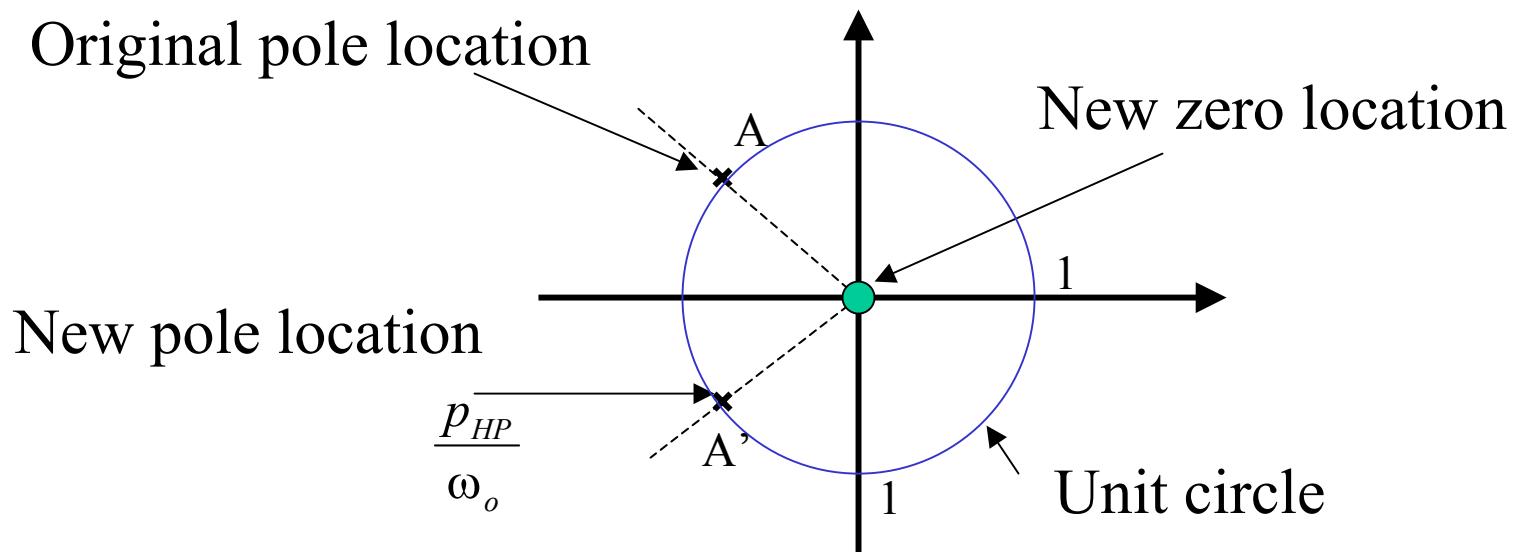

Example: LP-to-HP Transformation



- LP filter:

$$H_L(s) = \frac{1}{1+s}$$


- Transformation

$$s \Rightarrow \frac{1}{s}$$


- LP filter

$$H_H(s) = H_L(\Omega) |_{\Omega=1/s} = \frac{1}{1+1/s} = \frac{s}{1+s}$$

Example: LP-to-HP Transformation

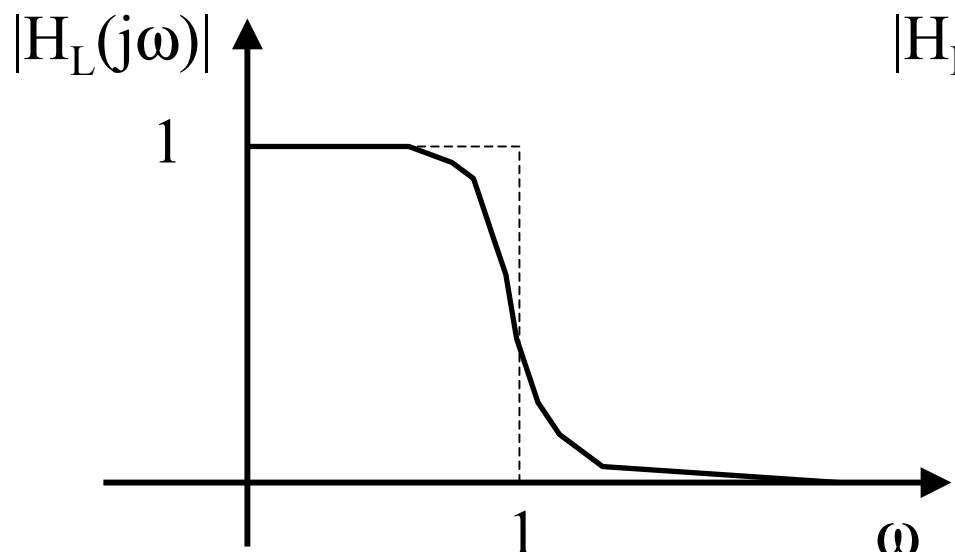

A) Lowpass filter

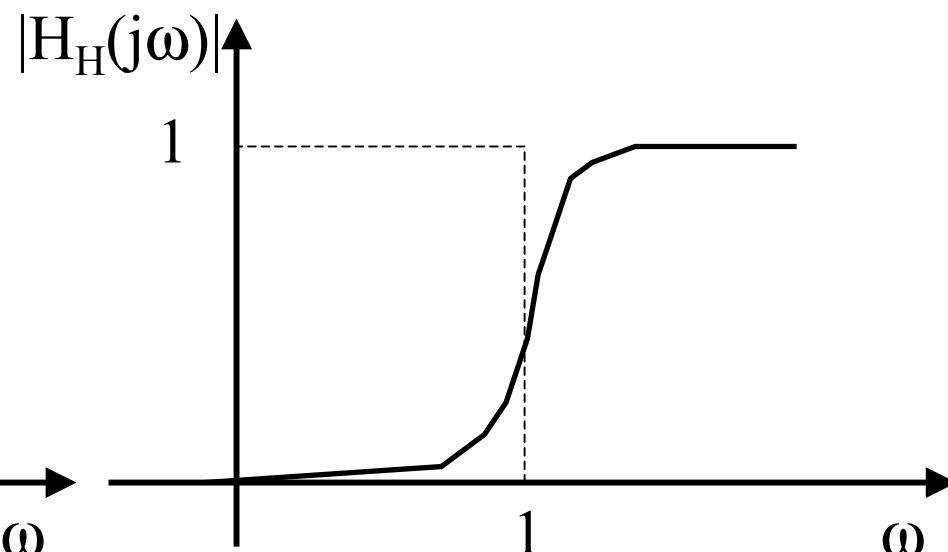


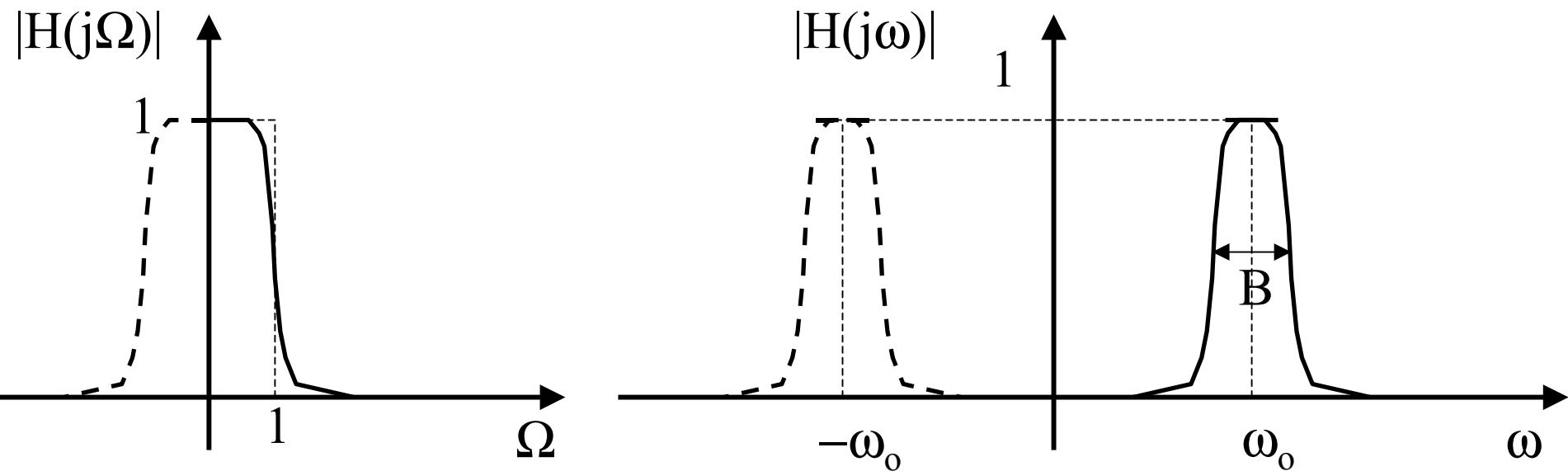B) Highpass filter

Lowpass-To-Bandpass Transformation



$$\Omega = \frac{1}{B} \frac{\omega^2 - \omega_o^2}{\omega} \quad \text{or} \quad S = Q \left(\frac{s}{\omega_o} + \frac{\omega_o}{s} \right)$$



$$Q = \frac{\omega_o}{B}$$

Pole Locations




- For the first-order lowpass prototype:

$$s - p_{Lp} = 0 \Rightarrow Q\left(\frac{s}{\omega_o} + \frac{\omega_o}{s}\right) - p_{Lp} = 0$$

$$\Rightarrow \left(\frac{s}{\omega_o}\right)^2 - \frac{p_{Lp}}{Q} \left(\frac{s}{\omega_o}\right) + 1 = 0$$

$$\frac{p_{BP}}{\omega_o} = \left(\frac{p_{LP}}{2Q} \pm j \sqrt{1 - \left(\frac{p_{LP}}{2Q}\right)^2} \right)$$

Pole Locations

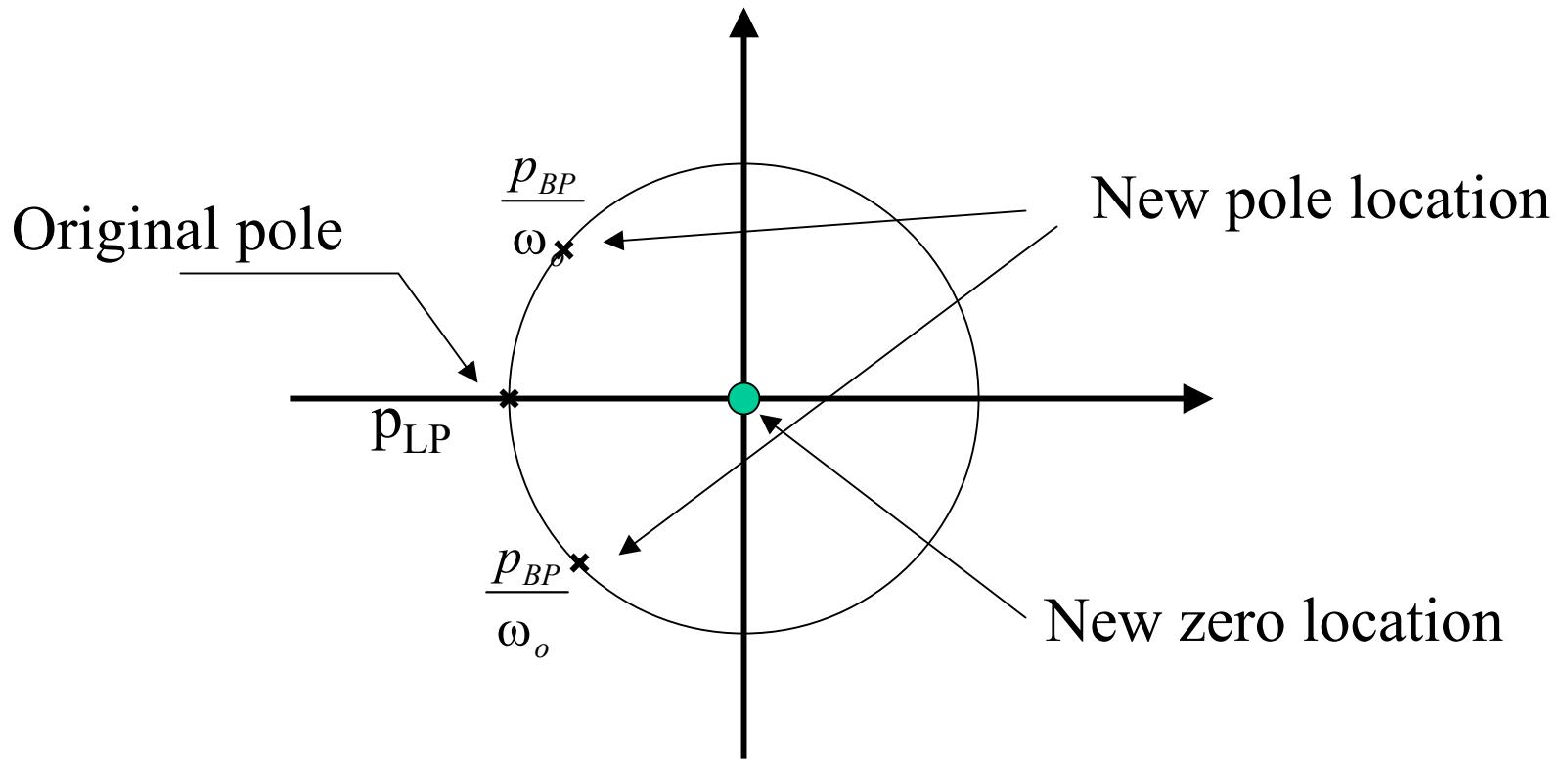

Pole Locations



- For the second-order lowpass prototype:


$$s^2 + \frac{s}{Q_{LP}} + 1 = (s - p_{LP1})(s - p_{LP2}) = 0$$

$$\Rightarrow \left(Q\left(\frac{s}{\omega_o} + \frac{\omega_o}{s} \right) - p_{LP1} \right) \left(Q\left(\frac{s}{\omega_o} + \frac{\omega_o}{s} \right) - p_{LP2} \right) = 0$$

$$\Rightarrow \begin{cases} \frac{p_{BP1}}{\omega_o} = \frac{p_{LP1}}{2Q} \pm \sqrt{\left(\frac{p_{LP1}}{2Q}\right)^2 - 1} \\ \frac{p_{BP2}}{\omega_o} = \frac{p_{LP2}}{2Q} \pm \sqrt{\left(\frac{p_{LP2}}{2Q}\right)^2 - 1} \end{cases}$$

o

Pole Locations:

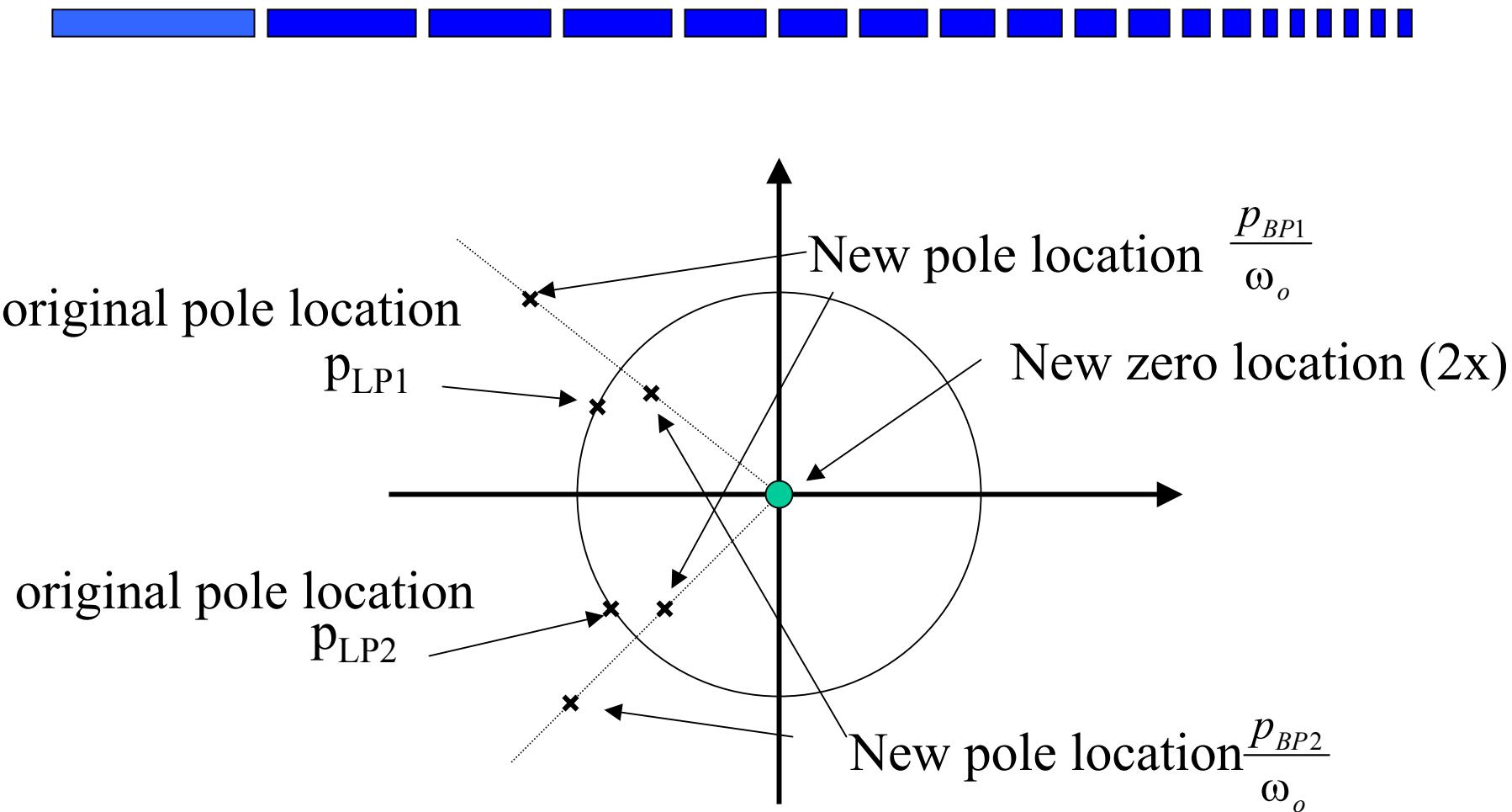



Lowpass-To-Bandstop Transformation



$$\Omega = -B \frac{\omega}{\omega^2 - \omega_o^2}$$

or
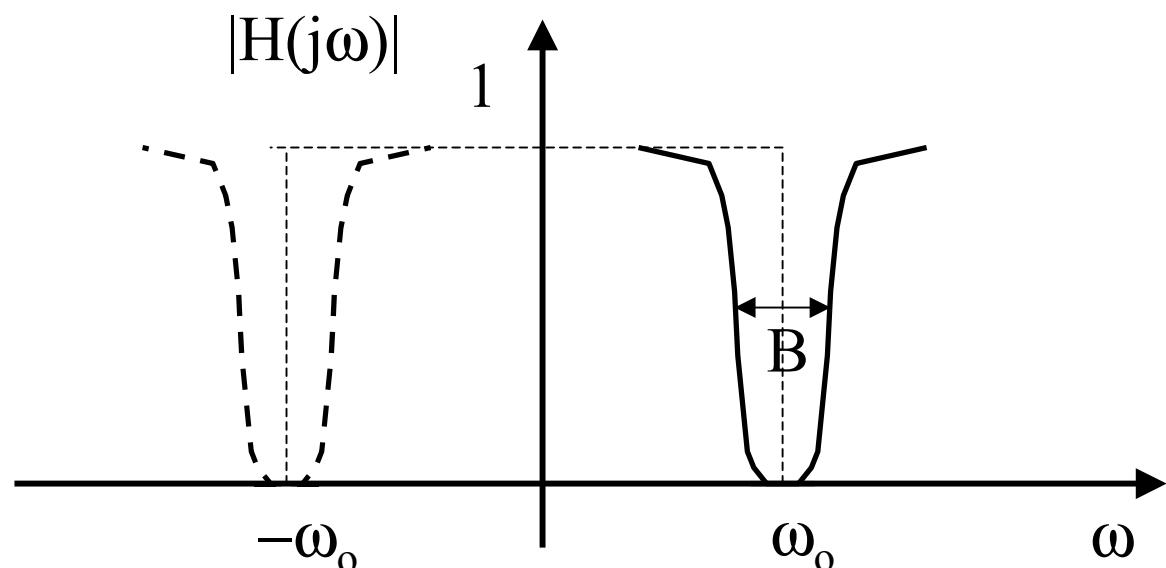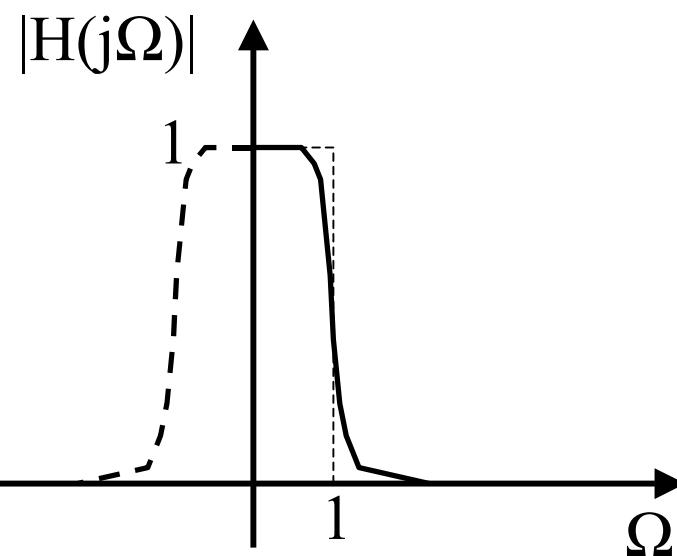
$$S = \frac{1}{Q} \frac{1}{\left(\frac{s}{\omega_o} + \frac{\omega_o}{s} \right)}$$



$$Q = \frac{\omega_o}{B}$$

Pole Location




- For first-order lowpass prototype

$$s - p_{Lp} = 0 \Rightarrow \frac{1}{Q\left(\frac{s}{\omega_o} + \frac{\omega_o}{s}\right)} - p_{Lp} = 0$$

$$\Rightarrow \left(\frac{s}{\omega_o}\right)^2 - \frac{1}{Qp_{Lp}} \left(\frac{s}{\omega_o}\right) + 1 = 0$$

$$\frac{p_{BP}}{\omega_o} = \left(\frac{1}{2Qp_{LP}} \pm j \sqrt{1 - \left(\frac{1}{2Qp_{LP}}\right)^2} \right)$$

Pole Location

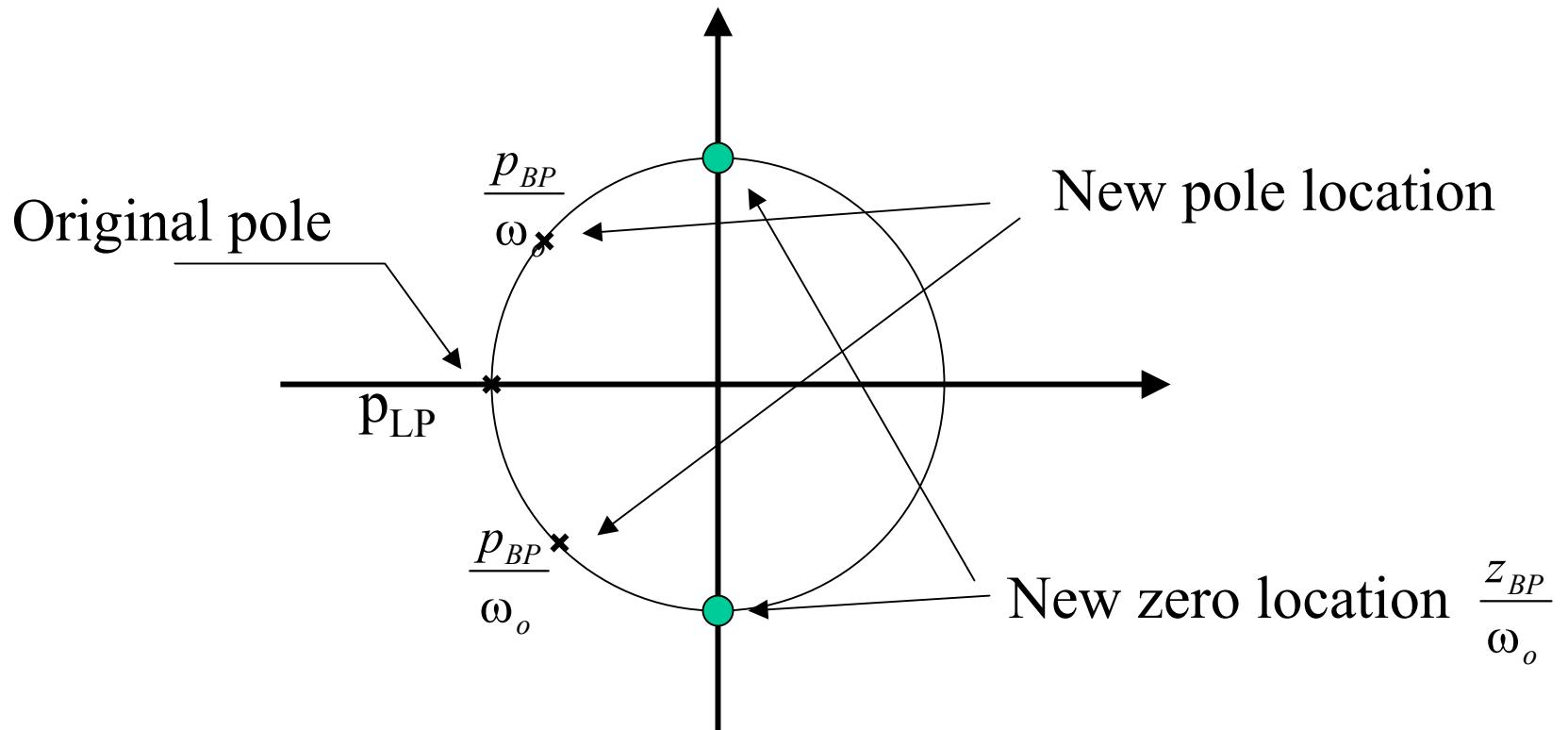

Pole Locations



- For the second-order lowpass prototype:


$$s^2 + \frac{s}{Q_{LP}} + 1 = (s - p_{LP1})(s - p_{LP2}) = 0$$

$$\Rightarrow \left(\frac{1}{Q\left(\frac{s}{\omega_o} + \frac{\omega_o}{s}\right)} - p_{LP1} \right) \left(\frac{1}{Q\left(\frac{s}{\omega_o} + \frac{\omega_o}{s}\right)} - p_{LP2} \right) = 0$$

$$\Rightarrow \begin{cases} \frac{p_{BP1}}{\omega_o} = \frac{1}{2Qp_{LP1}} \pm \sqrt{\left(\frac{1}{2Qp_{LP1}}\right)^2 - 1} \\ \frac{p_{BP2}}{\omega_o} = \frac{1}{2Qp_{LP2}} \pm \sqrt{\left(\frac{1}{2Qp_{LP2}}\right)^2 - 1} \end{cases}$$

o

Pole Locations:

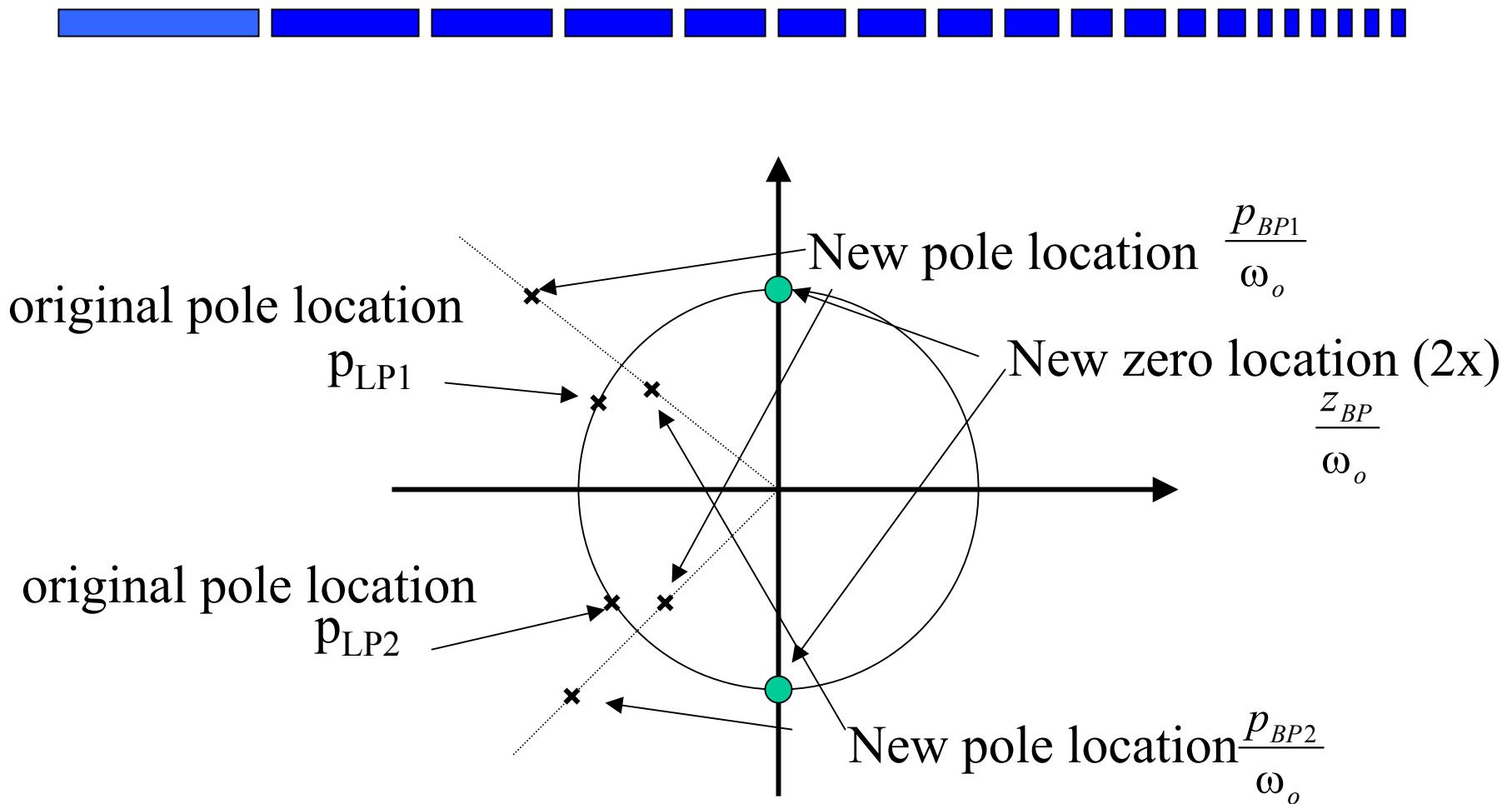

Lowpass-To-Multi-Passband Transformation



$$\Omega = \frac{K}{\omega} \prod_{k=1}^n \frac{(\omega^2 - \omega_{0(2k-1)}^2)}{(\omega^2 - \omega_{0(2k)}^2)}$$

$$S = \frac{K}{s} \prod_{k=1}^n \frac{(s^2 + \omega_{0(2k-1)}^2)}{(s^2 + \omega_{0(2k)}^2)}$$