

Spring 2002



EEE598D: Analog Filters & Signal Processing Circuits

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering

Arizona State University

EEE598D, Thursday March 7, 2001



Today: Gm-C Filter Design



- Basic building blocks
- First-order Gm-C filters
- Second-order Gm-C filters
- High order Gm-C filters

Gm-C filters





- Basic building blocks:
 - Transconductor
 - Capacitor
- Driving application: disk drive read-channel filters
- Now used in many other applications:
 - Telecommunication,
 - Wireless communication
 - Anti-aliasing. etc

Transconductor

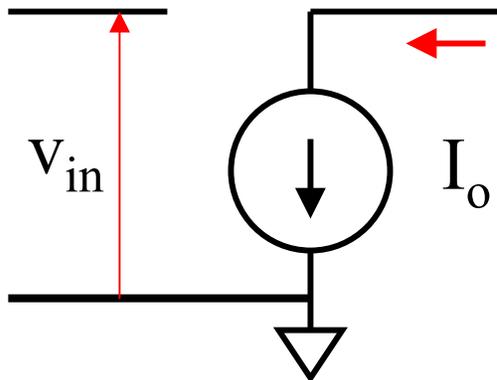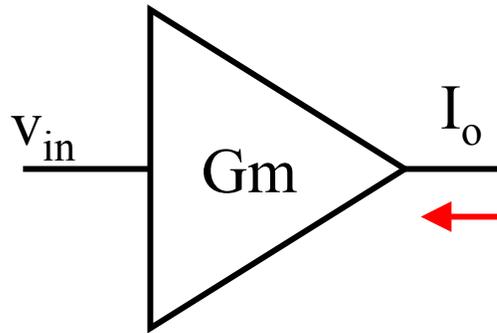


$$i_o = g_m v_{in}$$

Transconductor

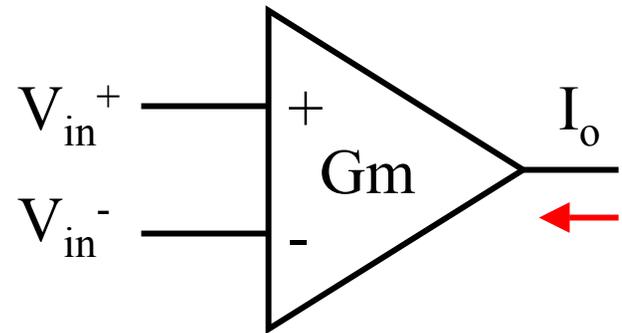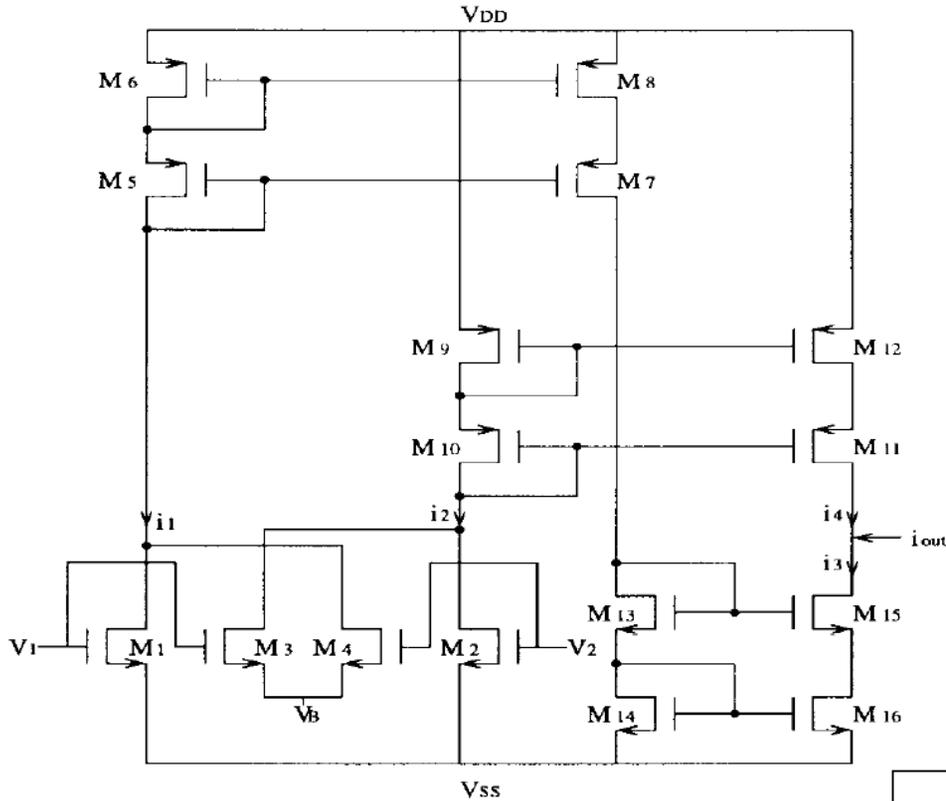


$$i_o = g_m (v_{in}^+ - v_{in}^-)$$

Transconductor

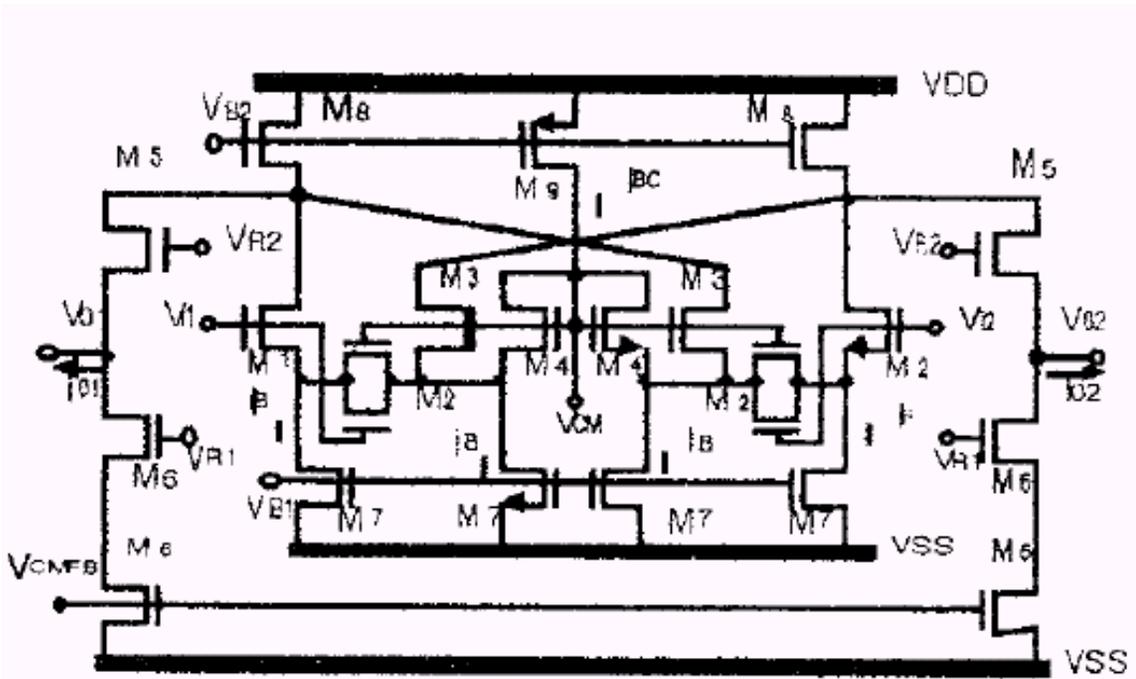

. Fully differential low distortion OTA.

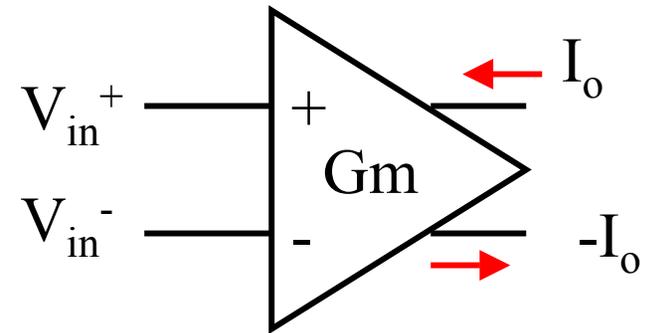


$$i_o = g_m (v_{in}^+ - v_{in}^-)$$

Gm-C Integrator Structures



- Single-ended

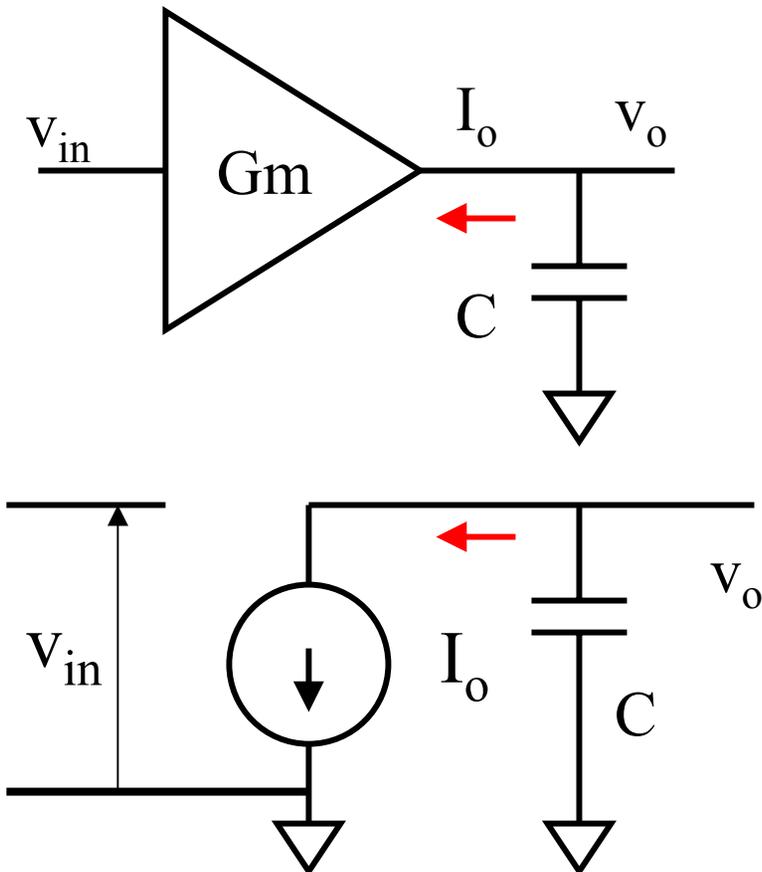


$$H(s) = \frac{V_o(s)}{V_{in}(s)} = -\frac{g_m}{Cs}$$

Gm-C Integrator Structures



- Differential inputs

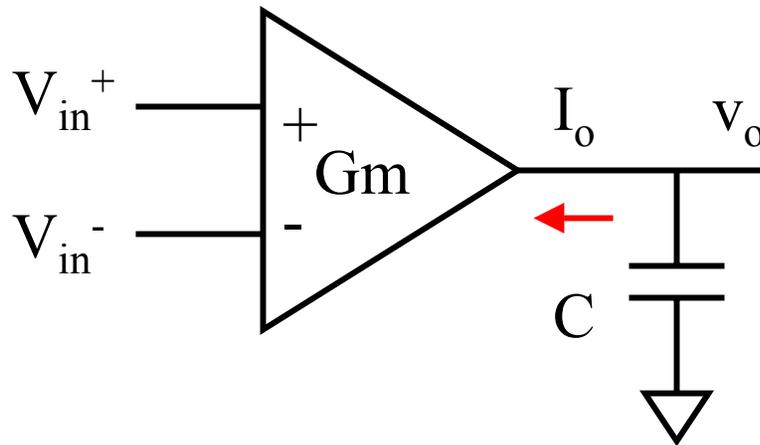


$$H(s) = \frac{V_o(s)}{V_{in}^+(s) - V_{in}^-(s)} = -\frac{g_m}{Cs}$$

Gm-C Integrator Structures



- Fully Differential

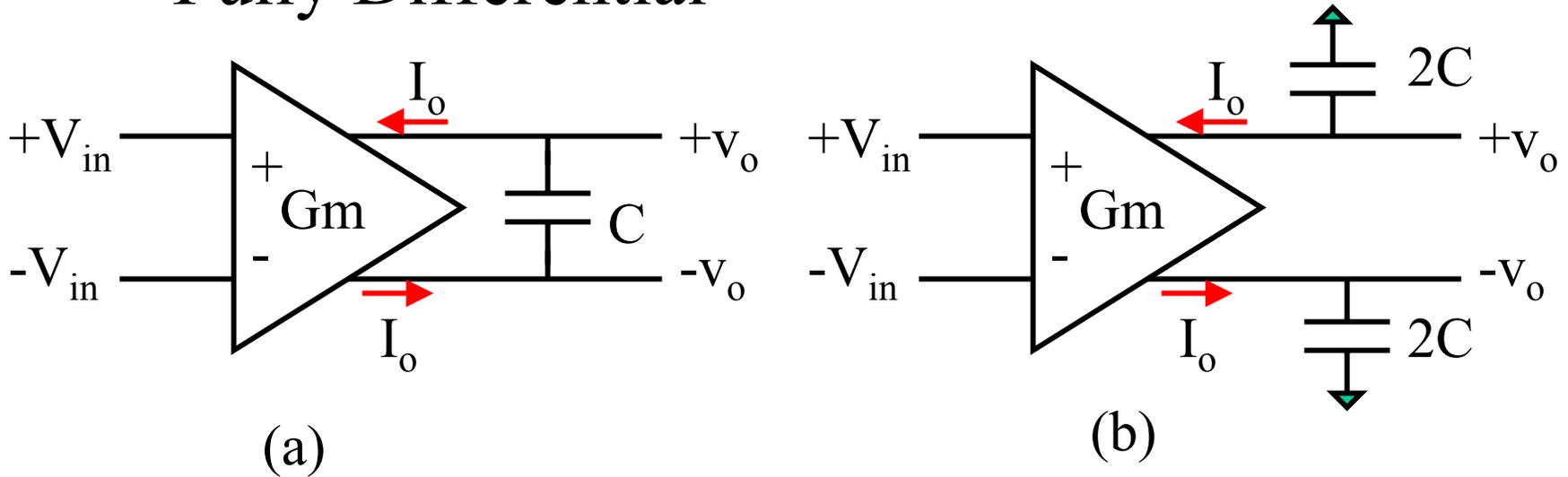


$$H(s) = \frac{V_o(s)}{V_{in}(s)} = -\frac{g_m}{Cs}$$

Gm-C Adder Structures



- Single-ended inputs

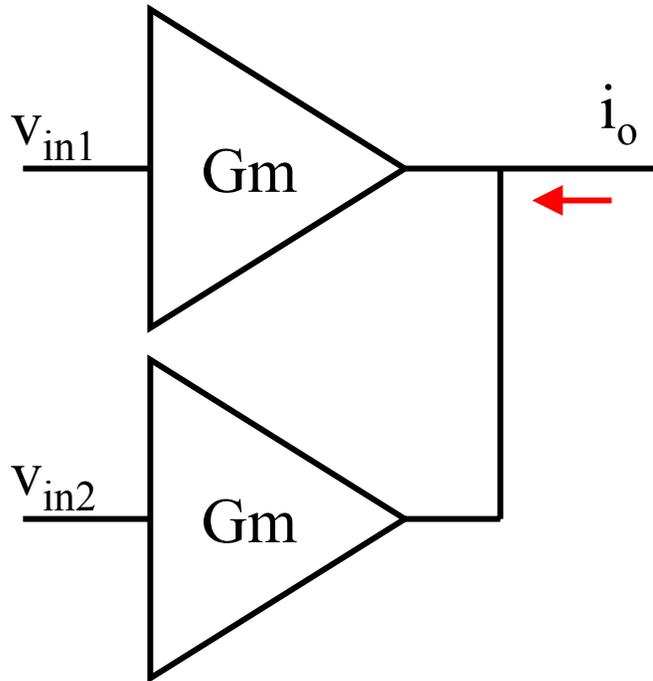


$$i_o = g_m (v_{in1} + v_{in2})$$

Gm-C Adder Structures



- Differential inputs

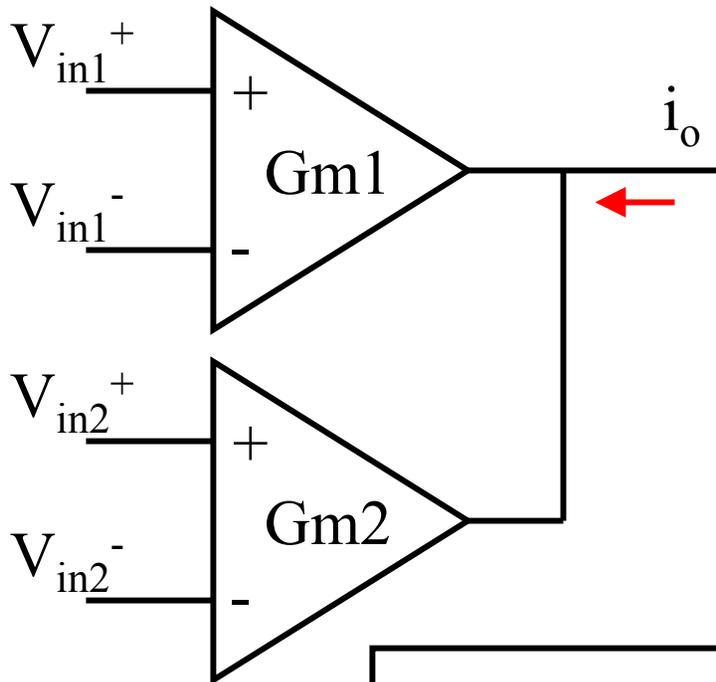


$$i_o = g_{m1} (v_{in1}^+ - v_{in1}^-) + g_{m2} (v_{in2}^+ - v_{in2}^-)$$

Gm-C Adder Structures



- Fully Differential

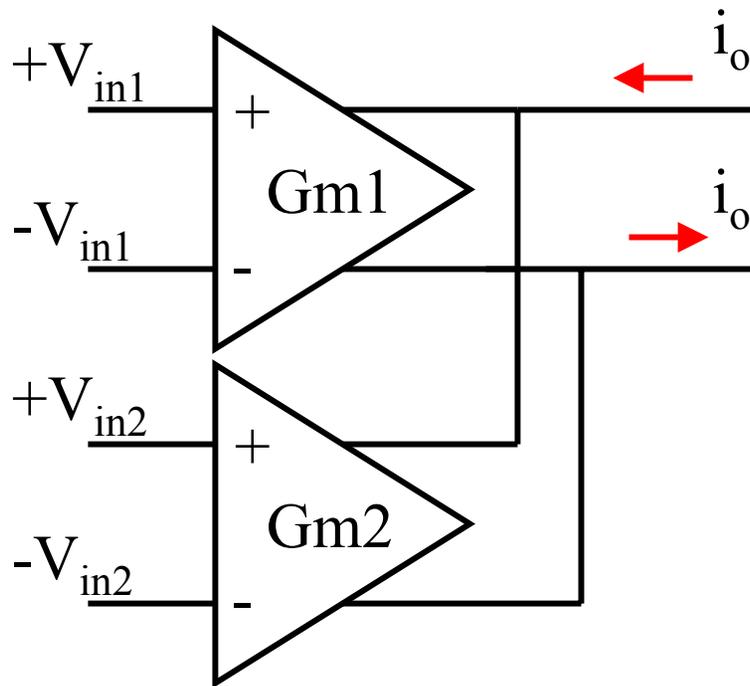


$$i_o = g_{m1}v_{in1} + g_{m2}v_{in2}$$

Gm-C Scaler Structures




- Single-ended

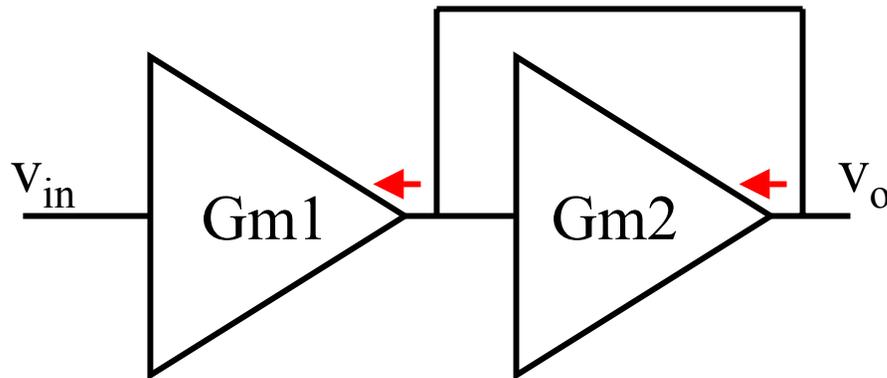

$$v_o = -\frac{g_{m1}}{g_{m2}} v_{in}$$

Gm-C Scaler Structures

- Fully Differential



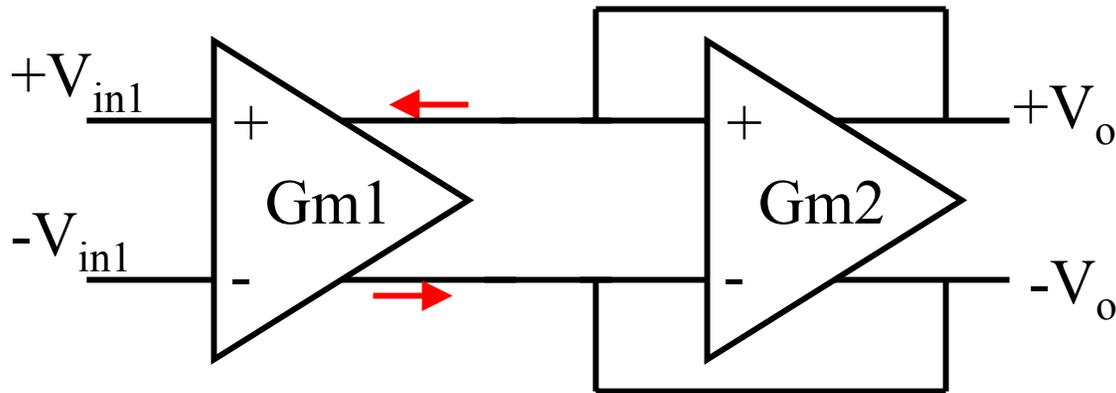


$$v_o = -\frac{g_{m1}}{g_{m2}} v_{in}$$




Gm-C Simulation of Resistors



- Grounded resistor

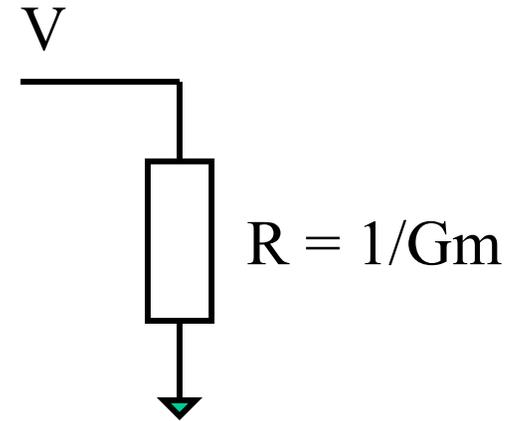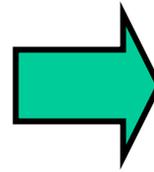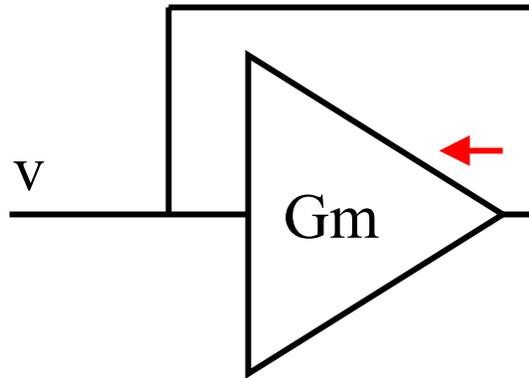


- Floating resistor

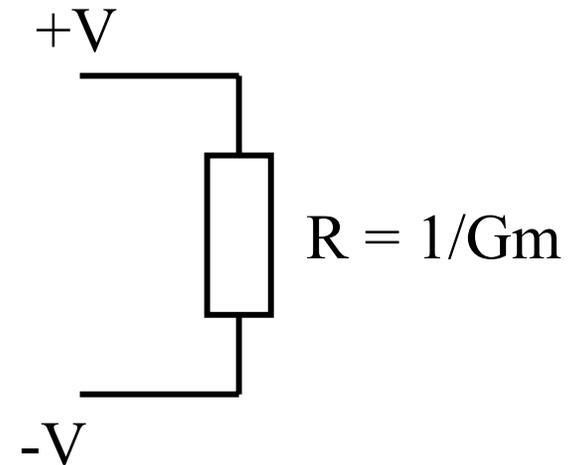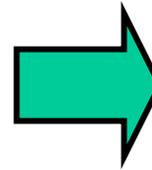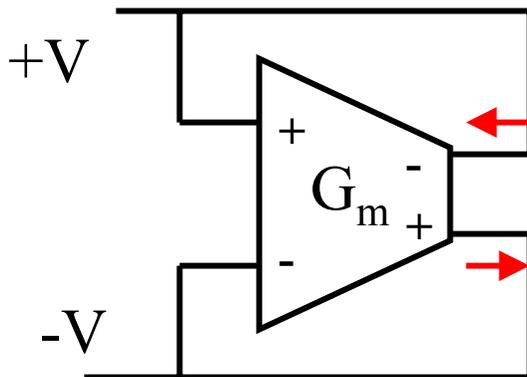

Gm-C Simulation of GIC



- General Impedance Converter (GIC)

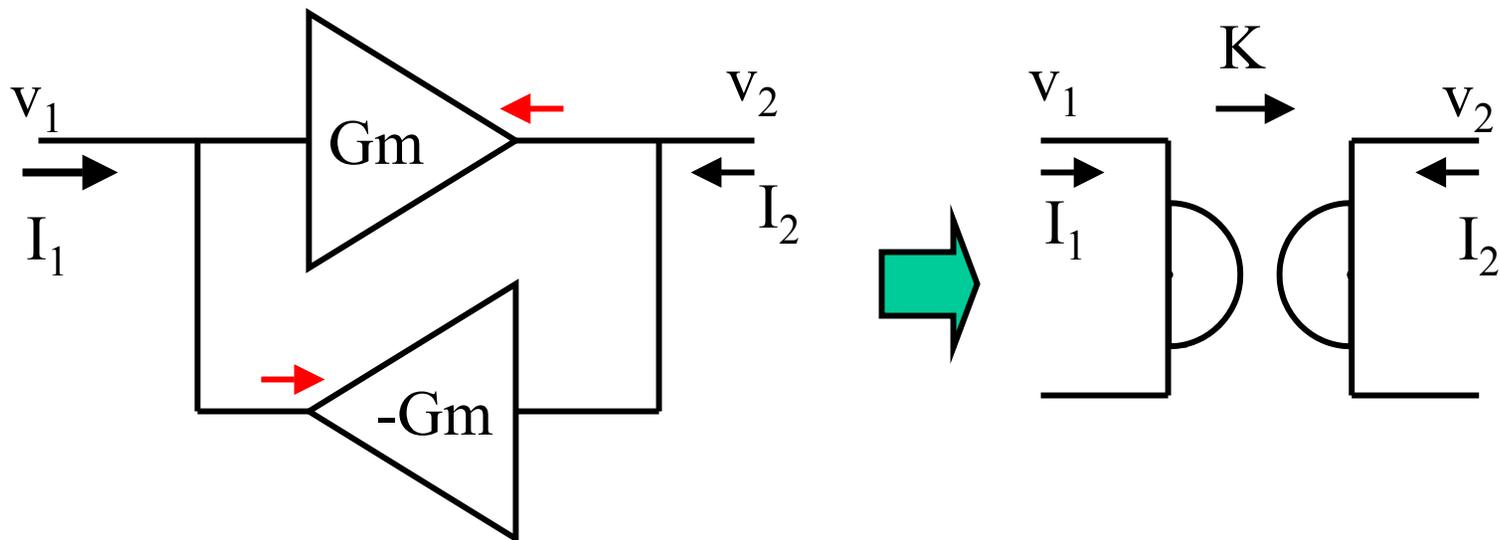


$$\begin{aligned} V_1 &= K I_2 \\ V_2 &= -K I_1 \end{aligned}$$

Gm-C Simulation of Inductors



- Grounded Inductor

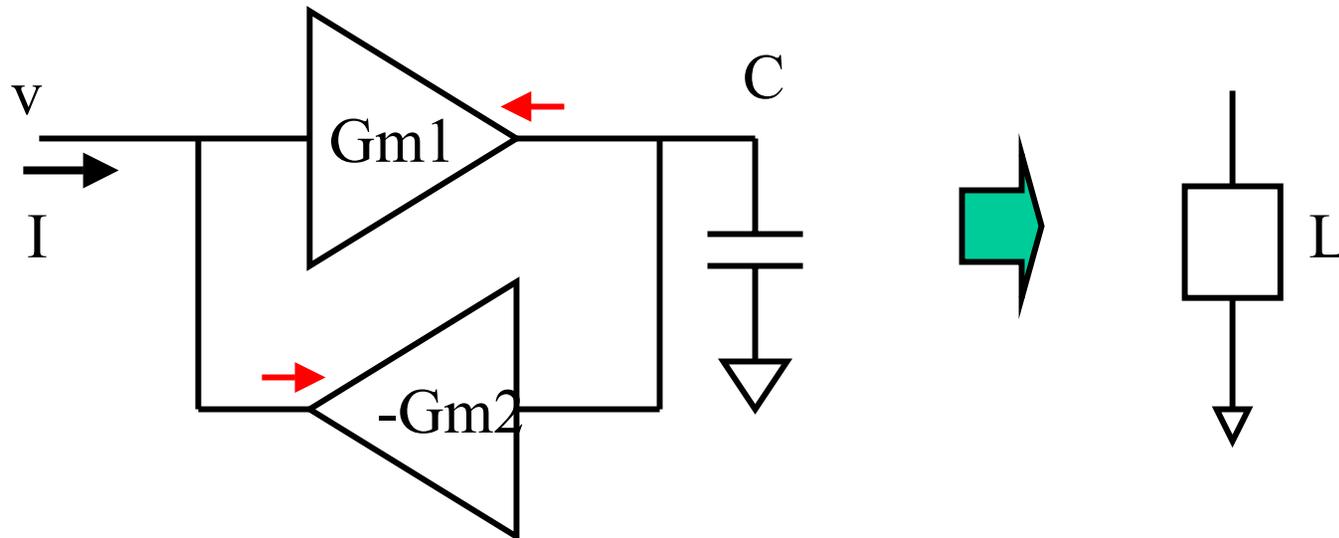


$$L = \frac{C}{g_{m2}g_{m1}}$$

Gm-C Simulation of Inductors



- Floating inductor


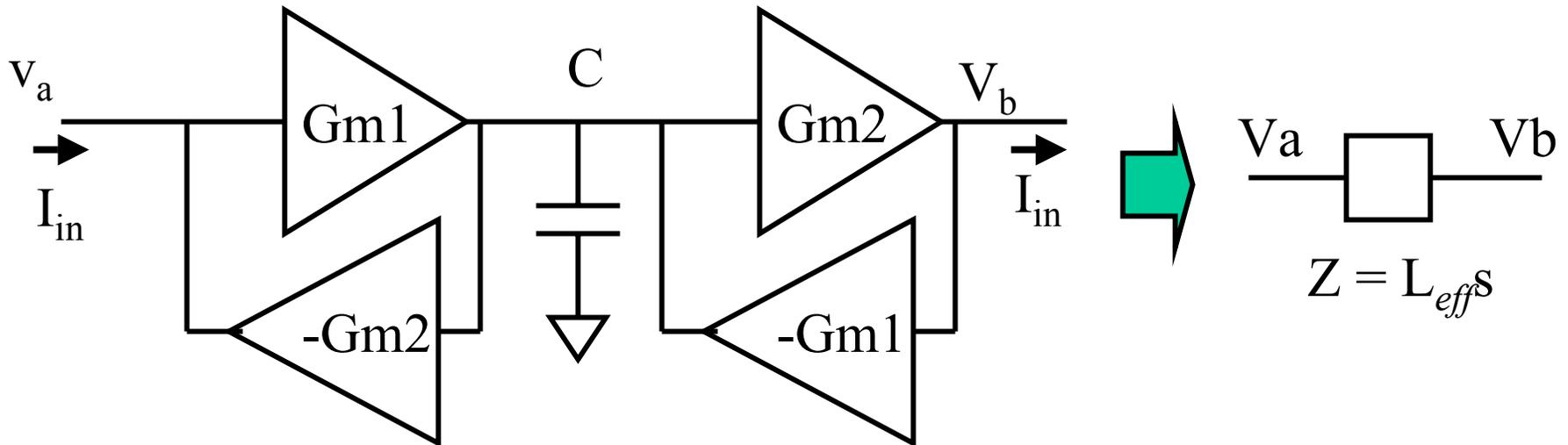


$$L = \frac{C}{g_{m2} g_{m1}}$$

Gm-C Simulation of Inductors



- Fully Differential Inductor (Gyrator)

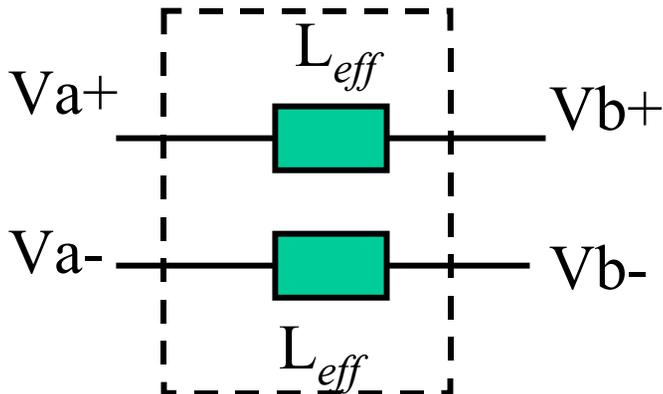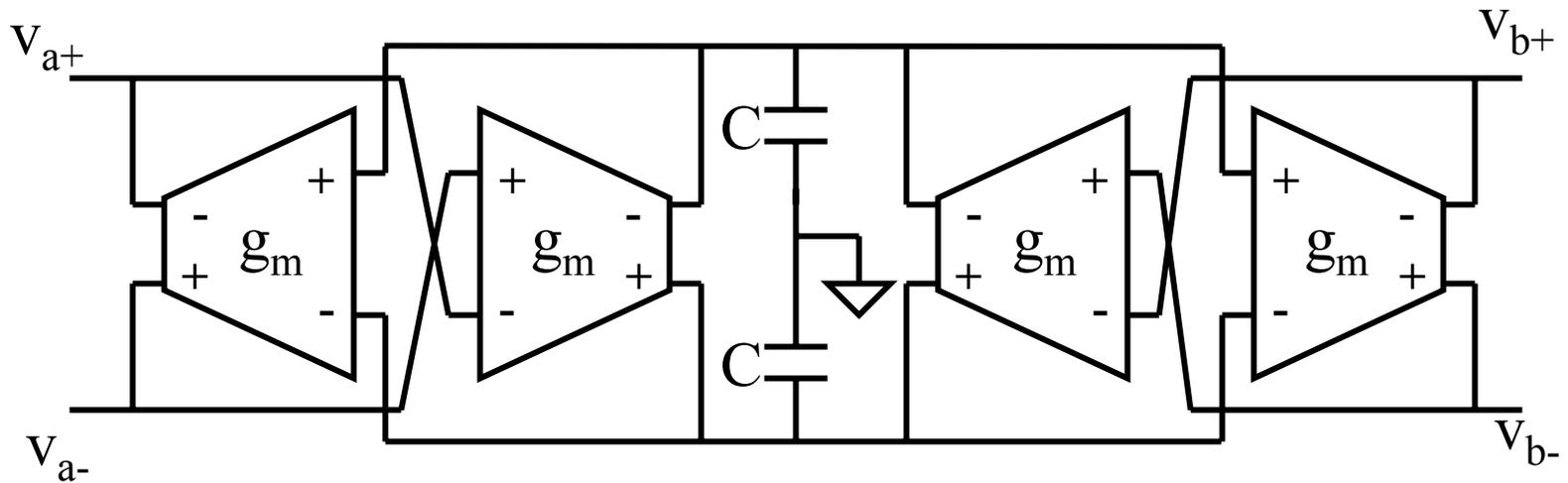


$$L_{eff} = \frac{C}{g_m^2}$$

First Order Gm-C Filters



- Single-ended

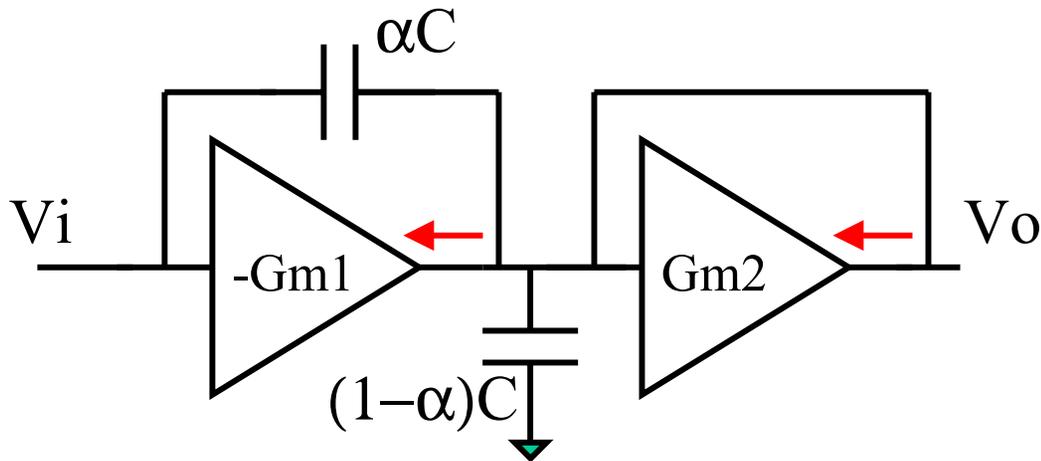


$$H(s) = \frac{V_o(s)}{V_i(s)} = \alpha \frac{s + \frac{g_{m1}}{\alpha C}}{s + \frac{g_{m2}}{C}}$$

First Order Gm-C Filters

- Fully Differential
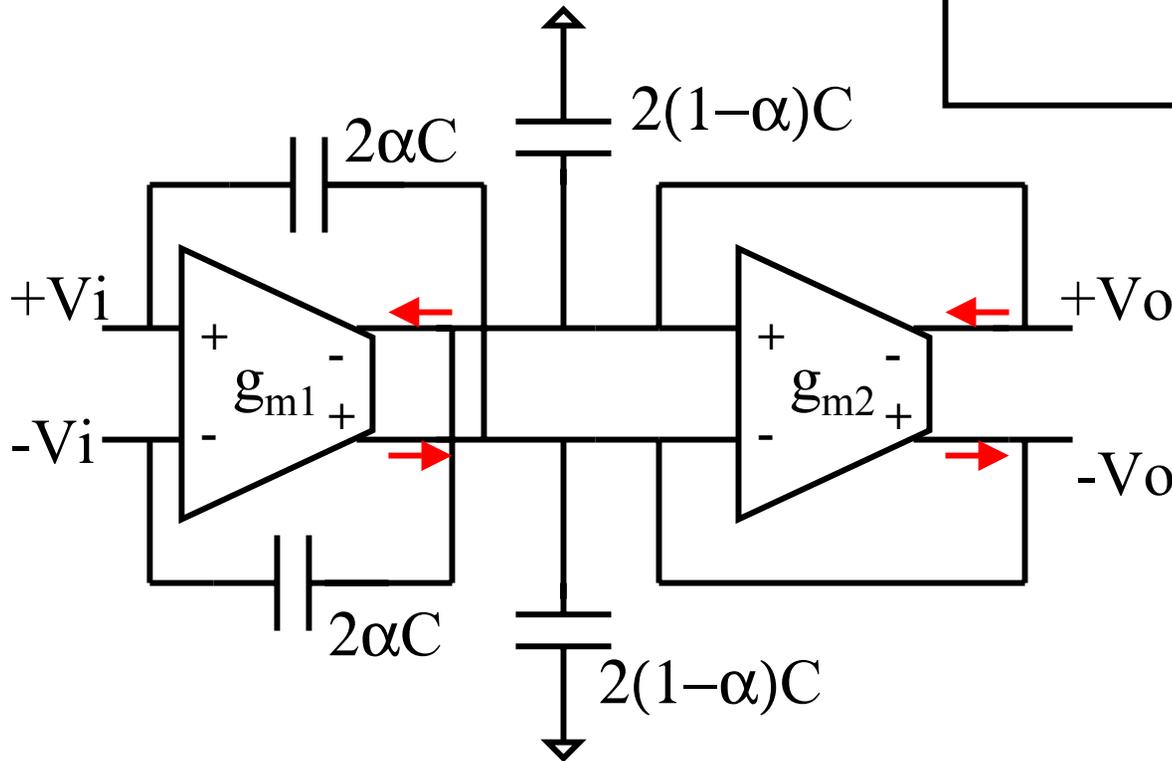
$$H(s) = \frac{V_o(s)}{V_i(s)} = \alpha \frac{s + \frac{g_{m1}}{\alpha C}}{s + \frac{g_{m2}}{C}}$$




Second Order Gm-C Filters



- LP

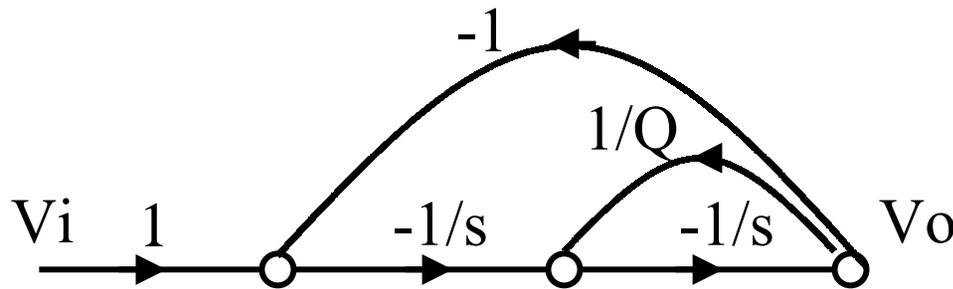
$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 + \frac{1}{Q}s + 1}$$



Second Order Gm-C Filters



- LP

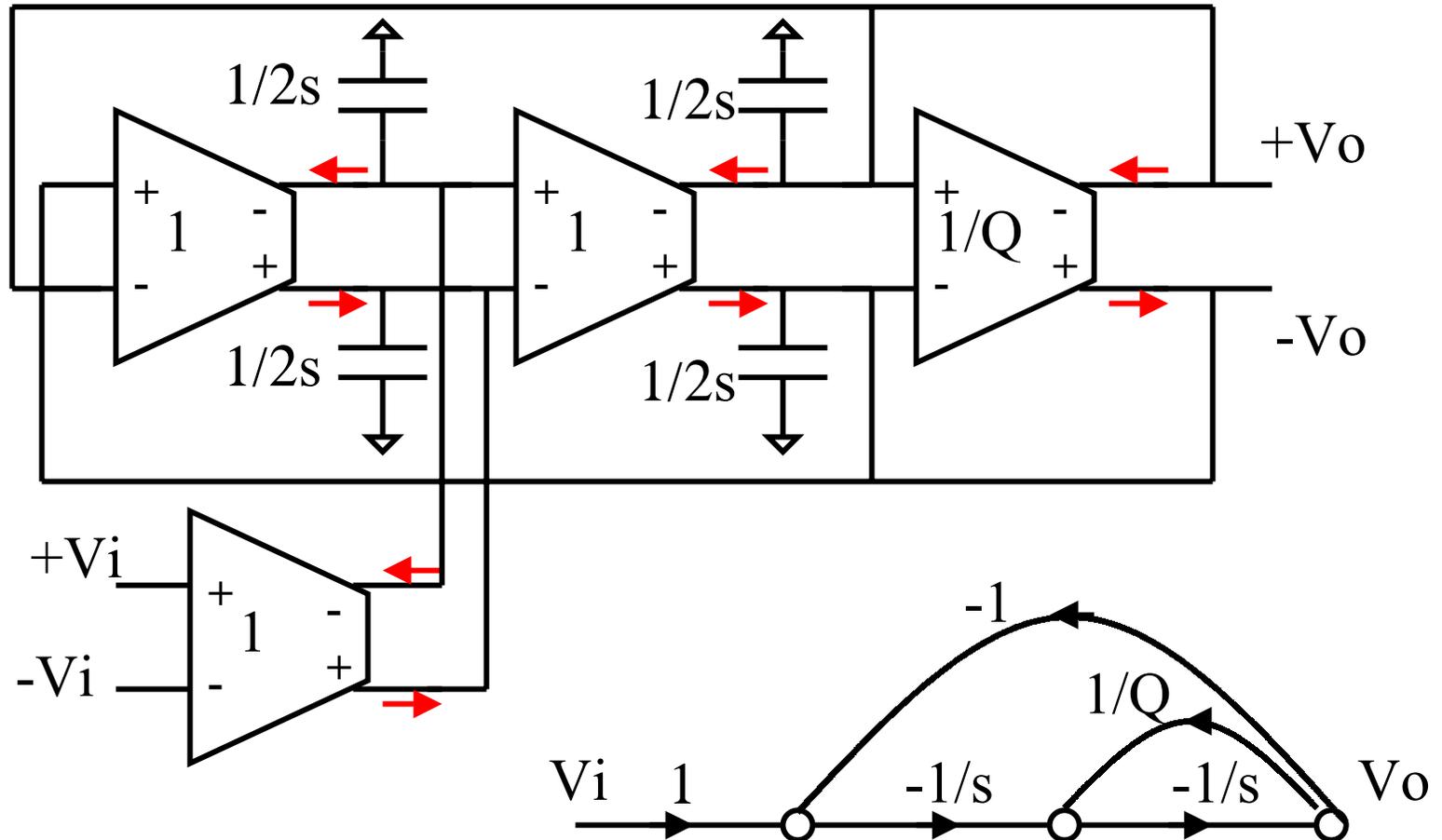


Second Order Gm-C Filters




- BP
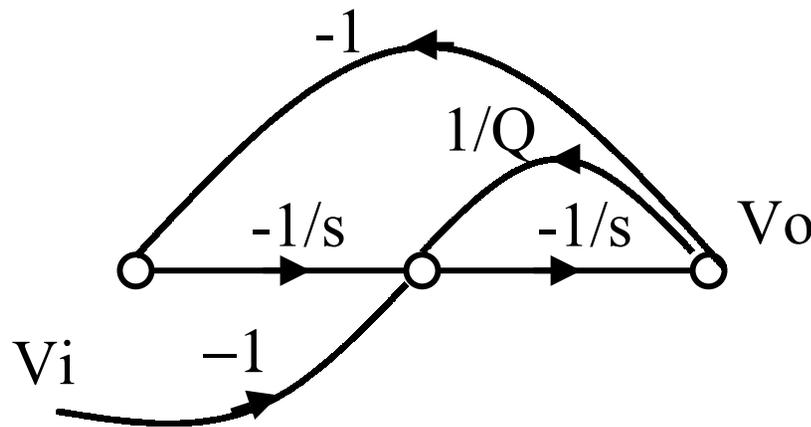
$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{s}{s^2 + \frac{1}{Q}s + 1}$$




Second Order Gm-C Filters

- BP

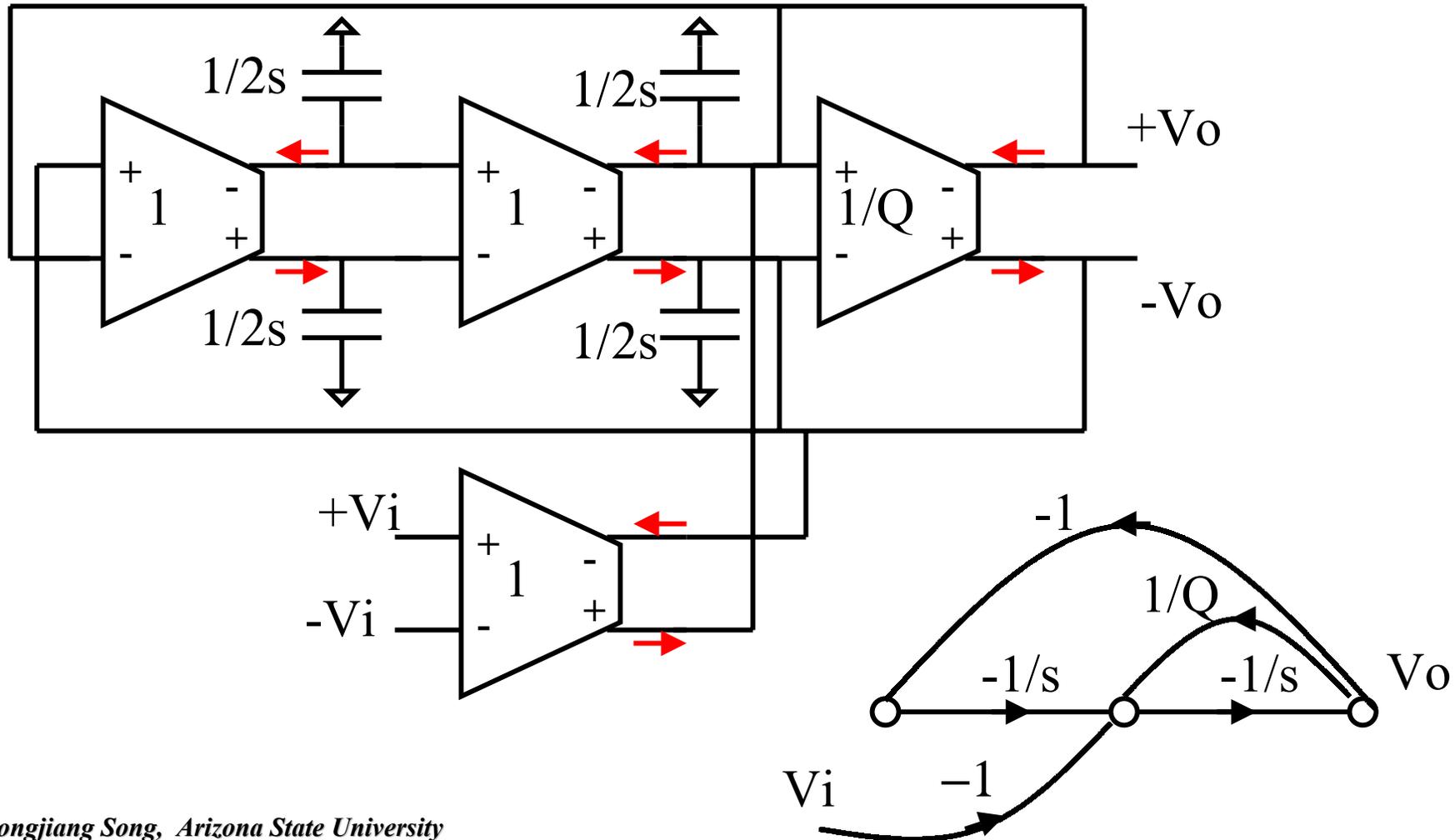

Second Order Gm-C Filter Structures


- LP, HP, and BS

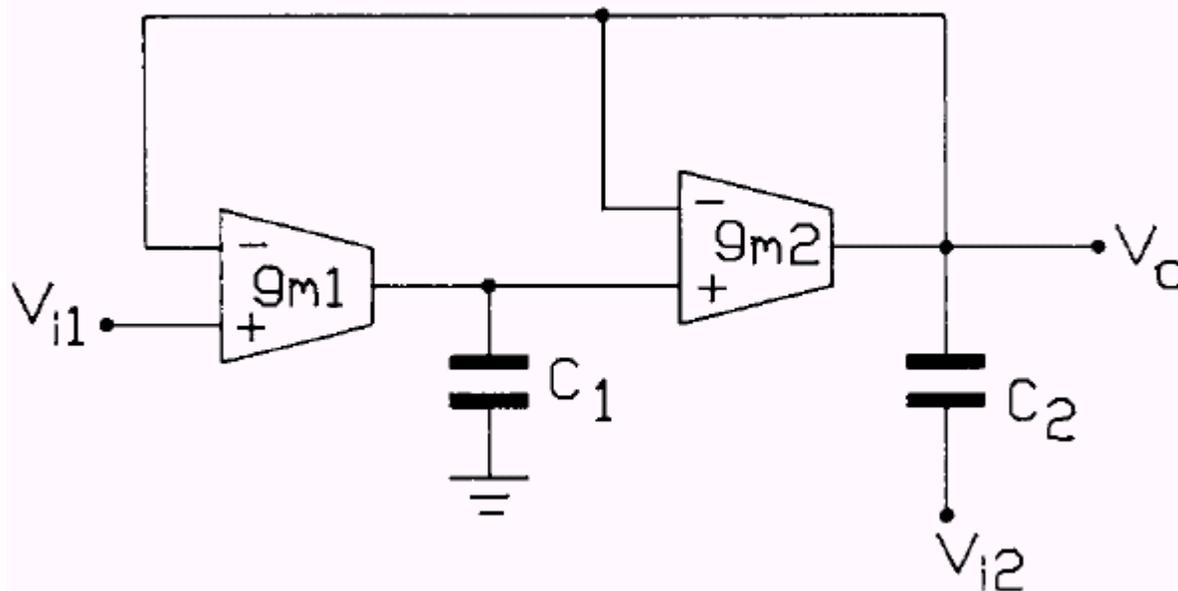


$$V_o = \frac{s^2 V_{i2} + \omega_o V_{i1}}{s^2 + \frac{\omega_o}{Q_o} s + \omega_o^2}$$

$$\omega_o = \sqrt{\frac{g_{m1} g_{m2}}{C_1 C_2}} \quad \text{and} \quad Q_o = \sqrt{\frac{g_{m1} C_2}{g_{m2} C_1}}$$


Second Order Gm-C Filter Structures

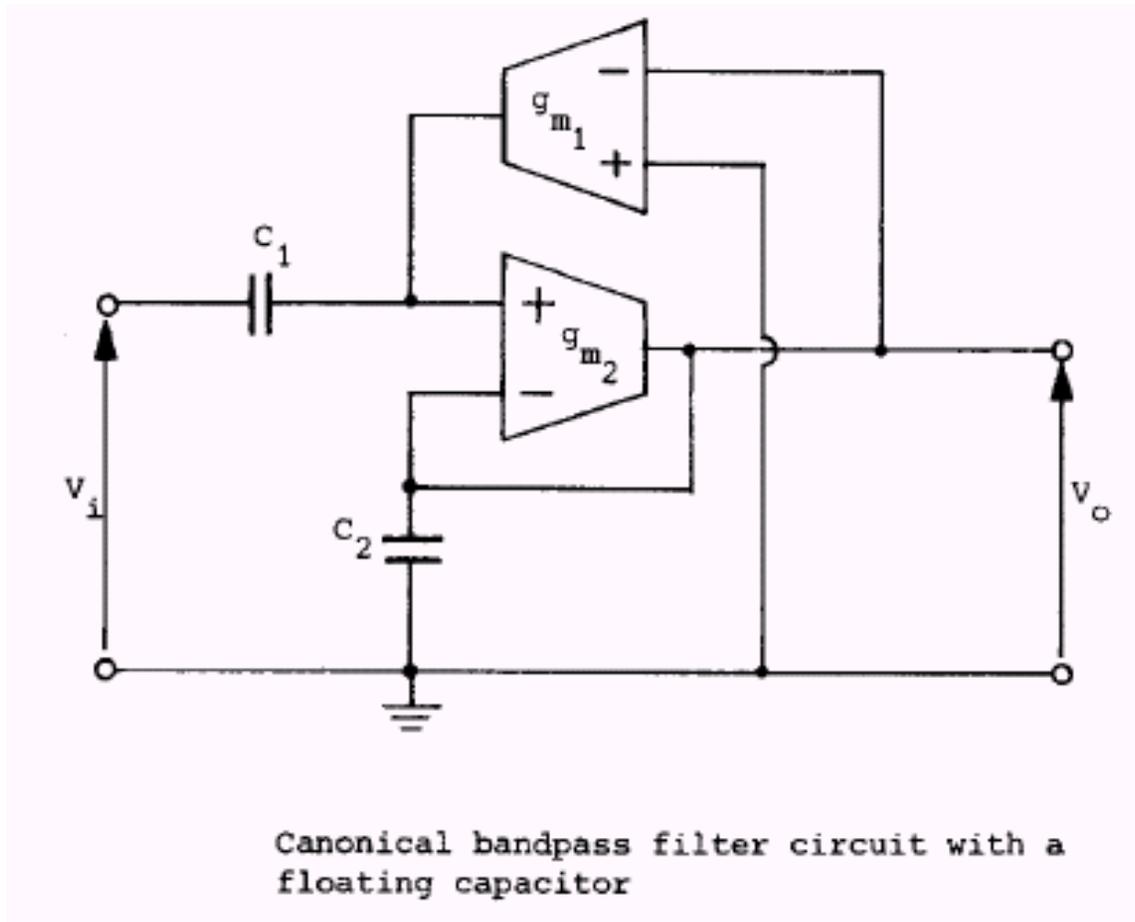


Second Order Gm-C Filter Structures

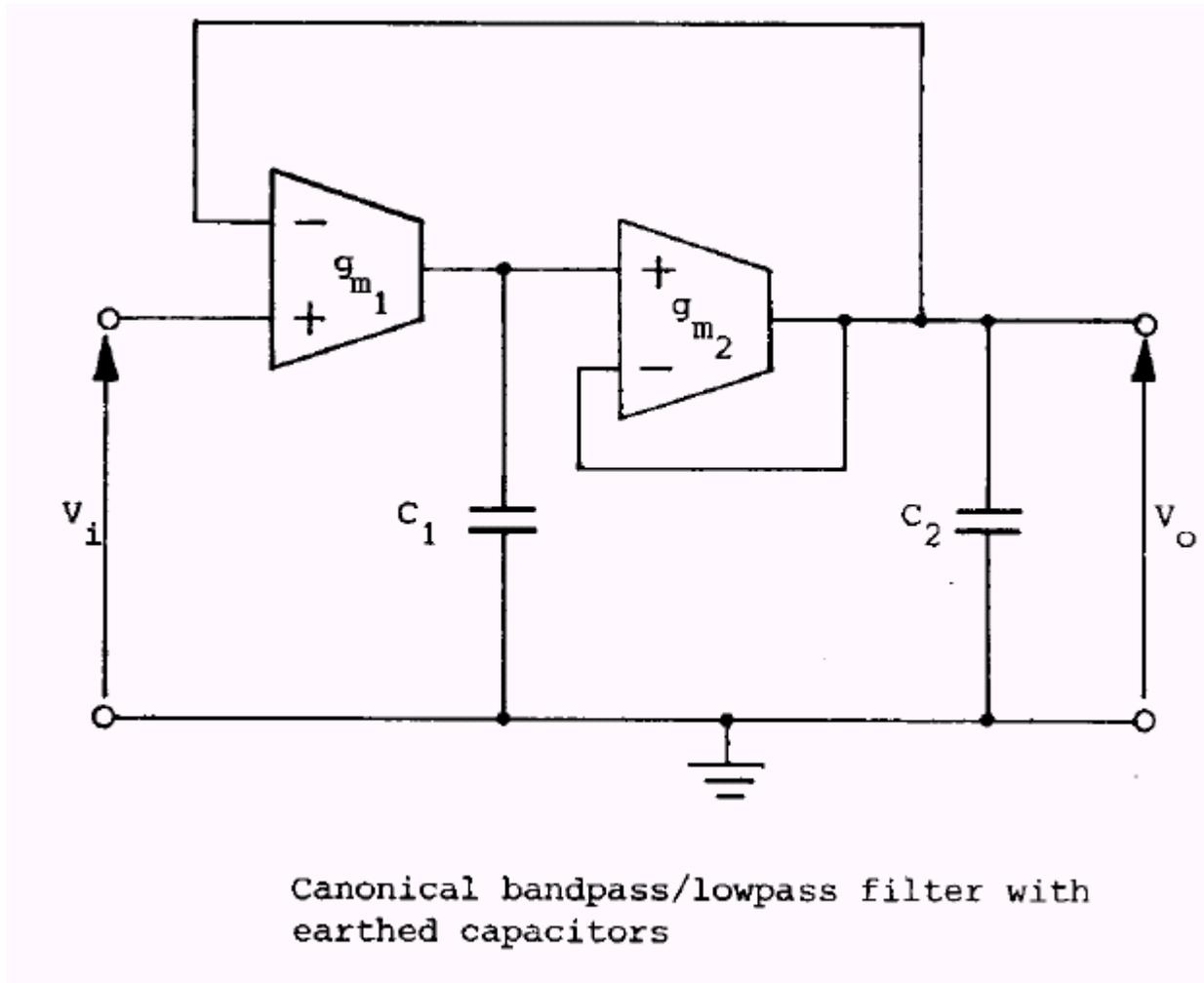

Second Order Gm-C Filter Structures


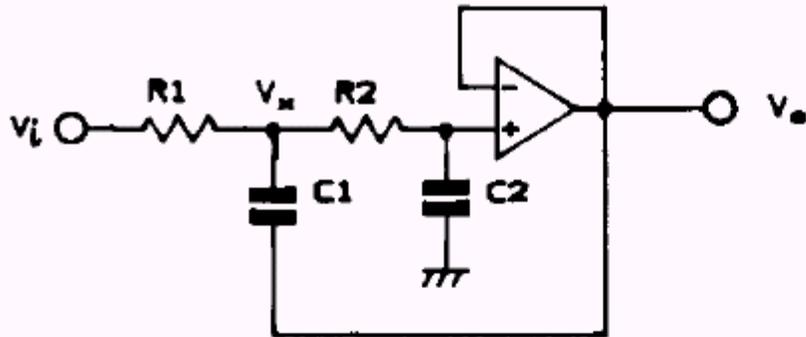


(a)

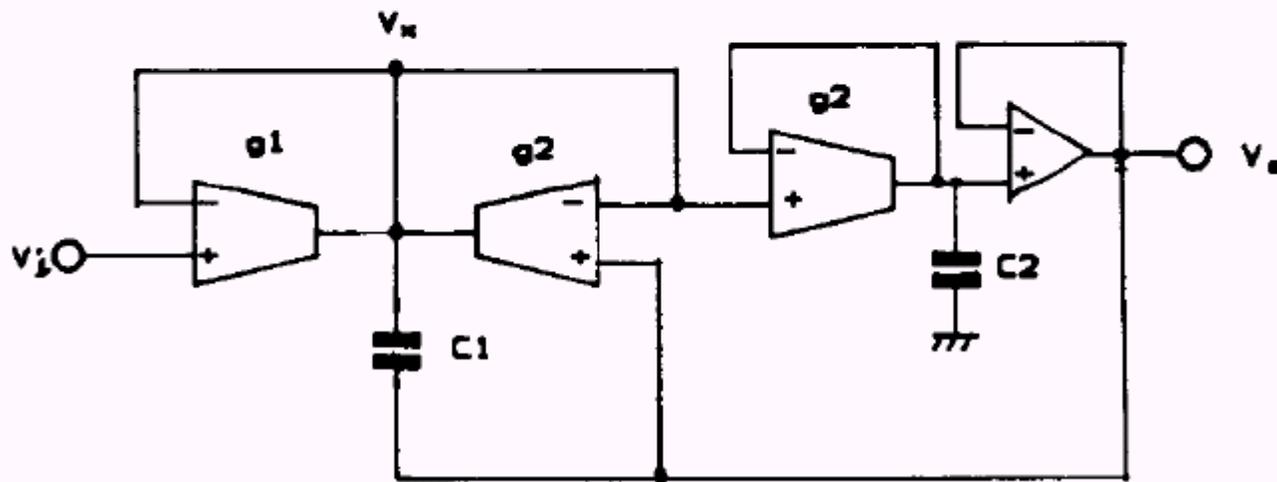

(b)

Second Order Gm-C Filter Structures

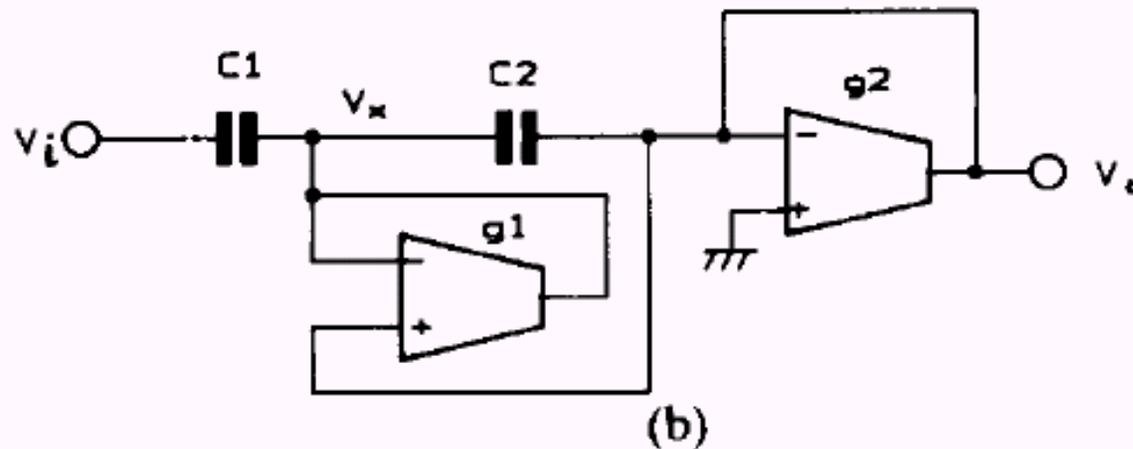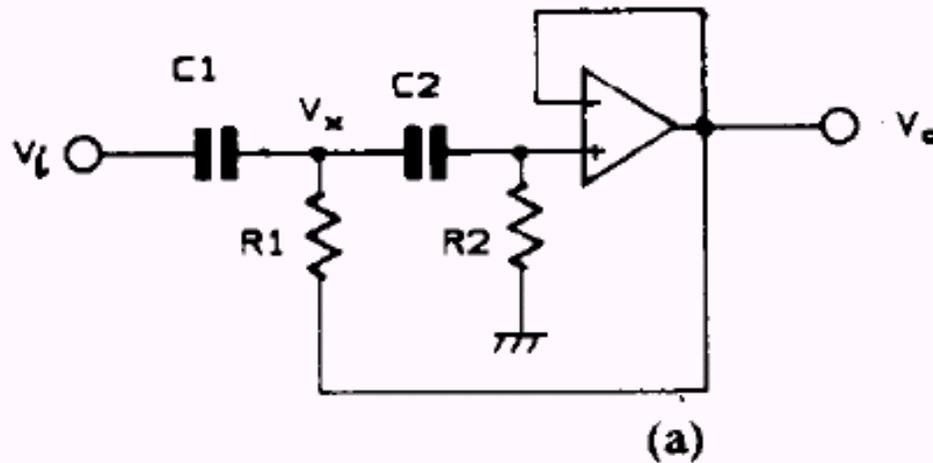

Cascade Design of High Order Filters



- In general, a high order filter can be implemented by cascading of the first- and second-order filters:

$$H(s) = \frac{\sum_{i=0}^m b_i s^i}{\sum_{i=0}^n b_i s^i} = \left(\prod_{i=1}^l \frac{\alpha_{2i} s^2 + \alpha_{1i} s + \alpha_{0i}}{s^2 + s \frac{\omega_{oi}}{Q_i} + \omega_{oi}^2} \right) \left(\frac{as + b}{s - p} \right)$$
$$= \prod_{i=1}^{l+1} H_i(s)$$