

# Spring 2002



## EEE598D: Analog Filters & Signal Processing Circuits

Instructor:  
Dr. Hongjiang Song

Department of Electrical Engineering  
Arizona State University

# EEE598D, Tuesday March 19, 2002




Today: Current-Mode CT Filter Realization

- Current-Mode Active RC Filters
- Current-Mode Gm-C Filters

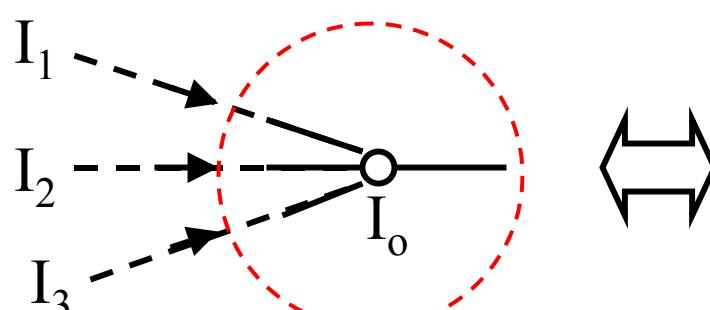
# Current-Mode Active RC Circuits



- Addition
  - It is straightforward to realize addition in current





A) SFG

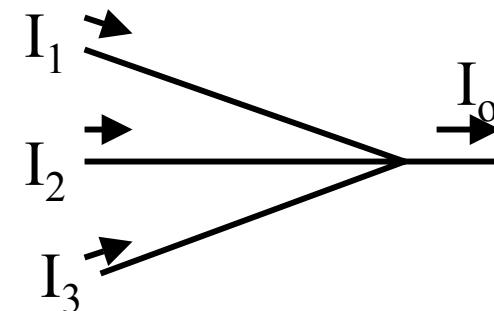

B) Circuit
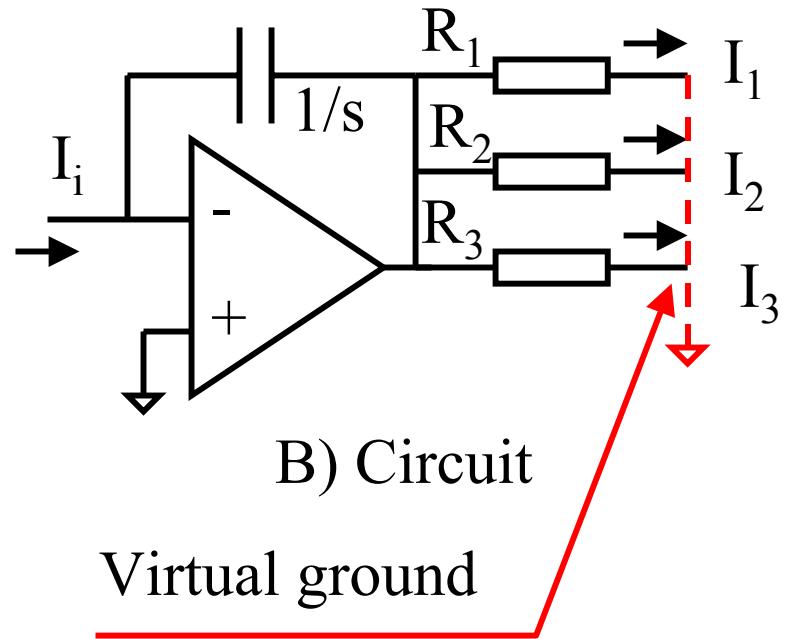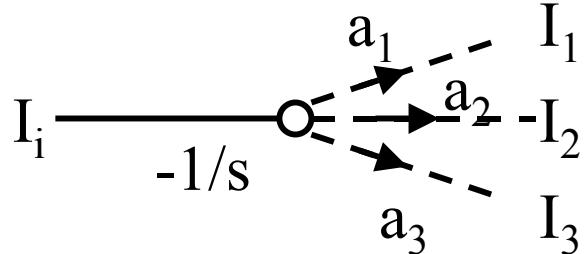
# Current-Mode Active RC Circuits

- Integration with weighted current output



$$R_i = 1/a_i \quad \{i = 1, 2, 3\}$$


# Current-Mode Active RC Circuits



- Scaling

$$I_i \xrightarrow{-a} I_o$$

A) SFG


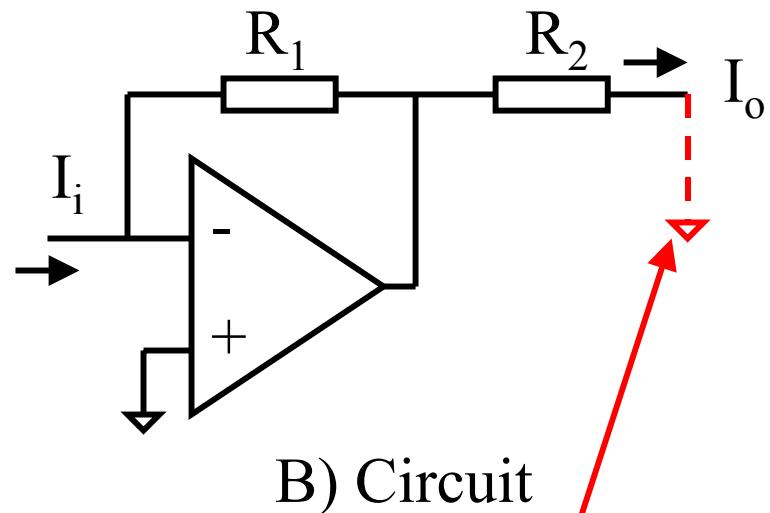


Virtual ground

$$a = R_1/R_2$$

# Current-Mode Active RC Circuits

- V/I and I/V conversion

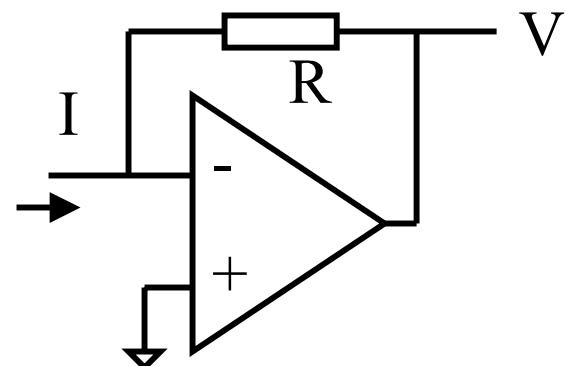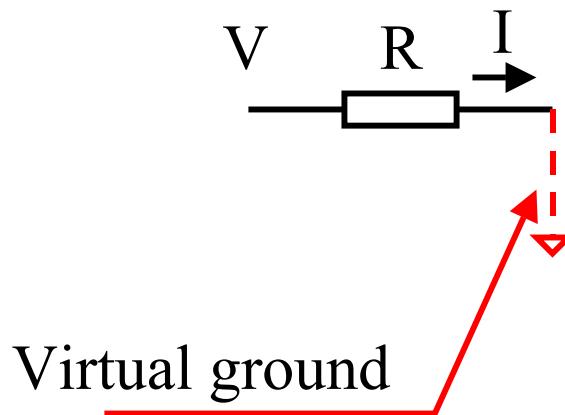



$$I = V/R$$

$$V = - RI$$

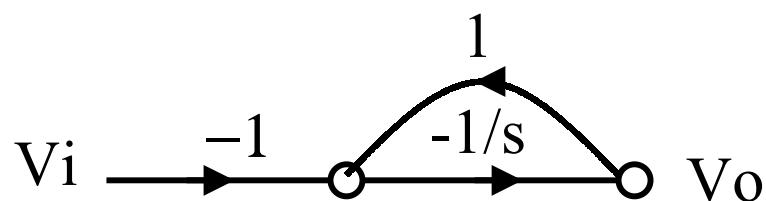
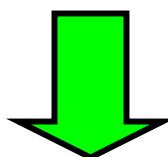
# Example: 1st-Order Filter Realization




$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s + 1}$$




# Example: 1st-Order Filter Realization

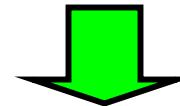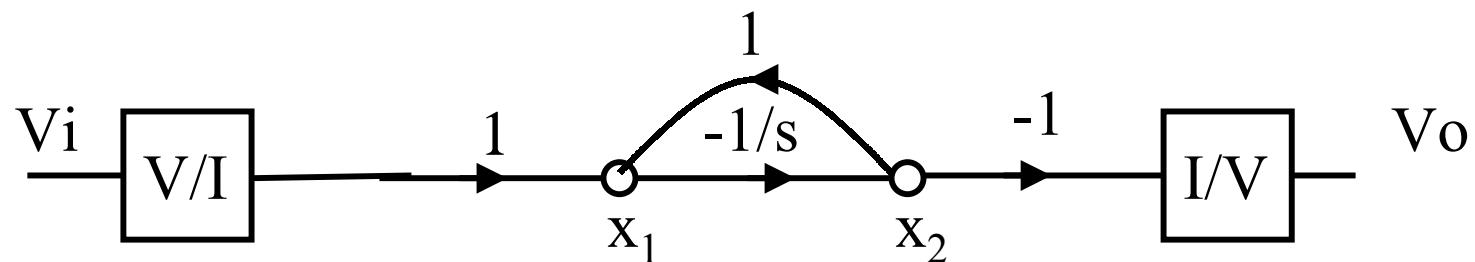


Mapping

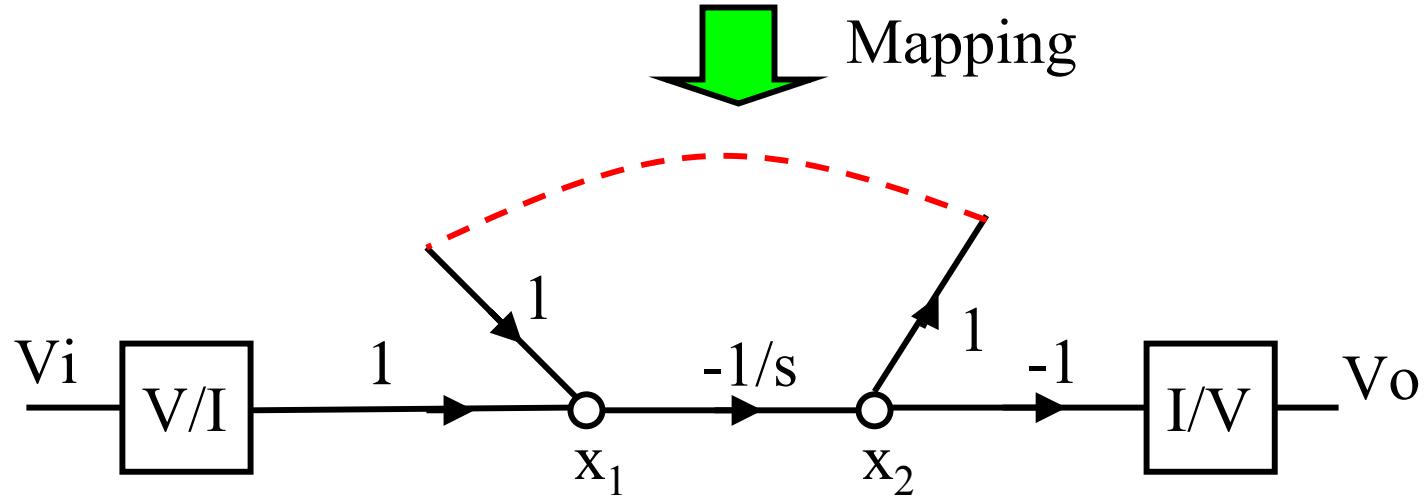


# Example: 1st-Order Filter Realization

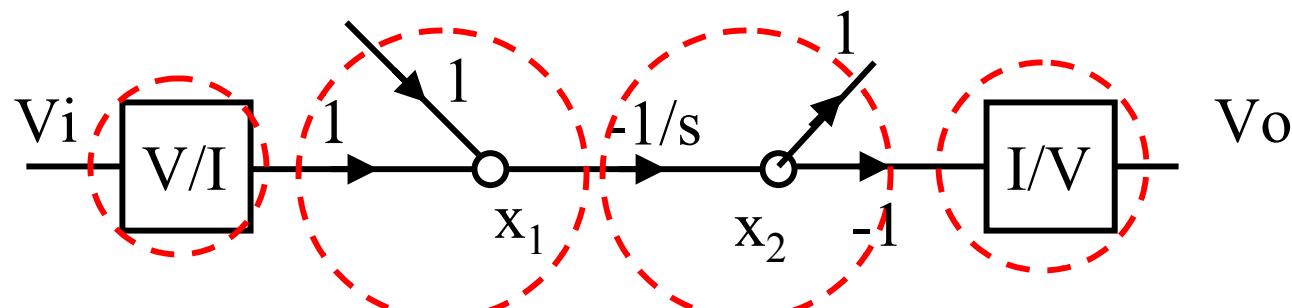

Mapping

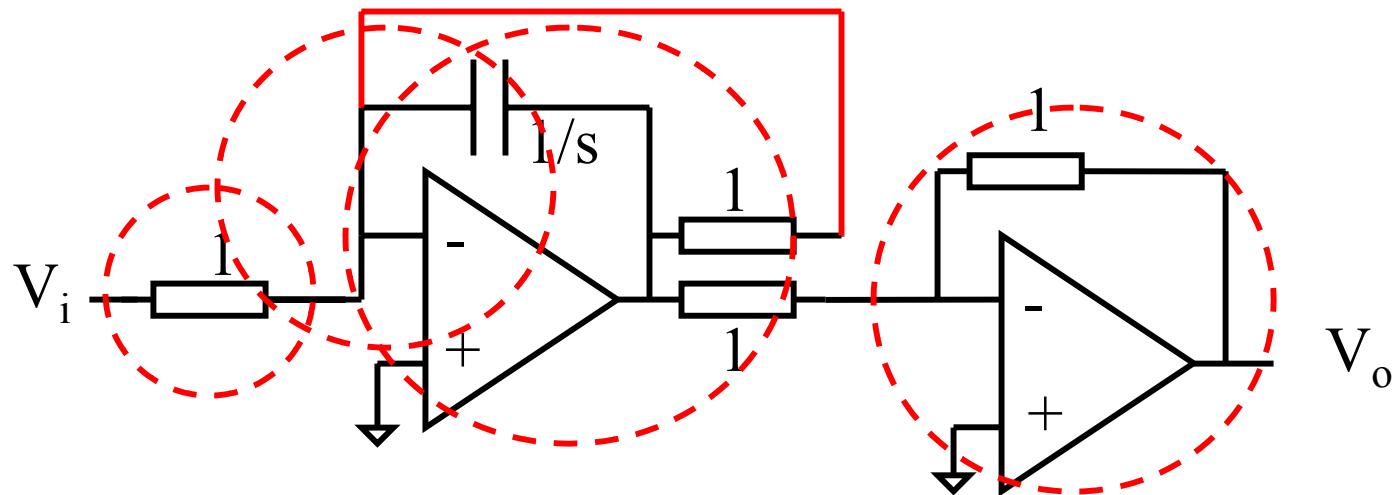



# Example: 1st-Order Filter Realization

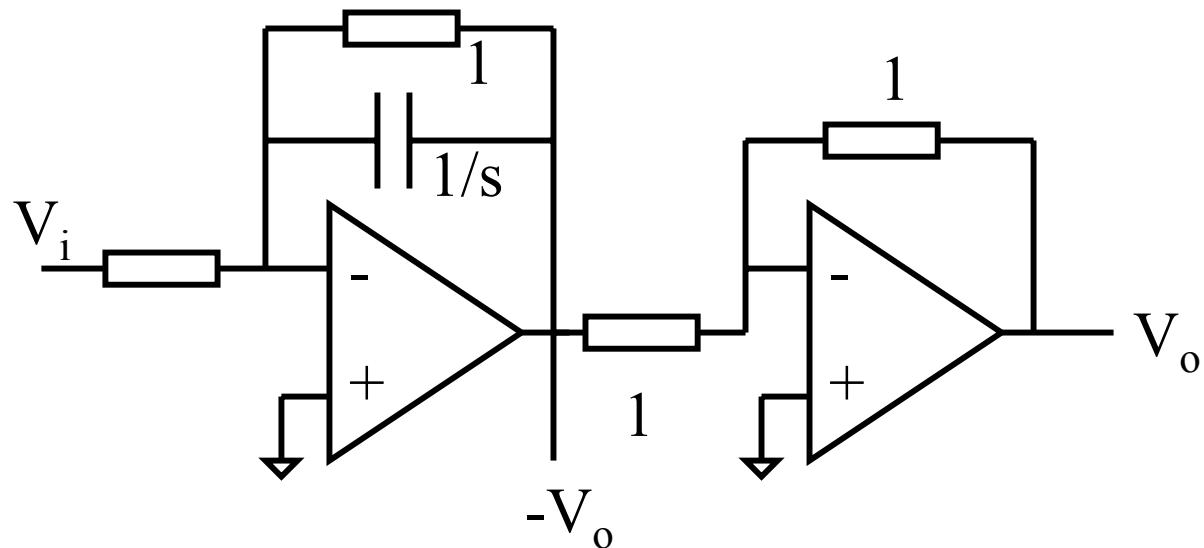

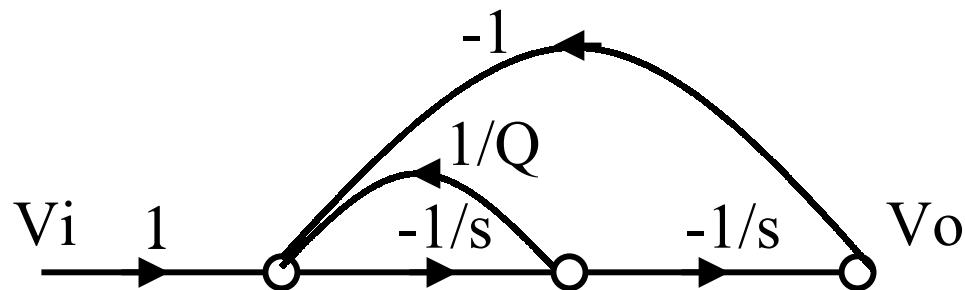
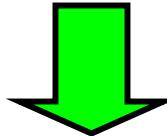
# Example: 2nd-Order Filter Realization





$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 + \frac{1}{Q}s + 1}$$



# Example: 2nd-Order Filter Realization

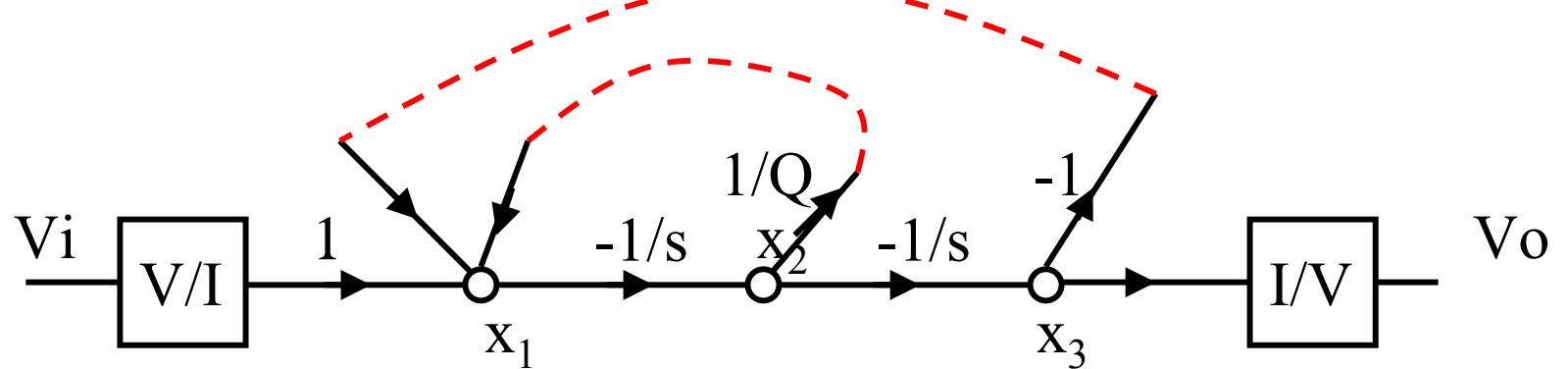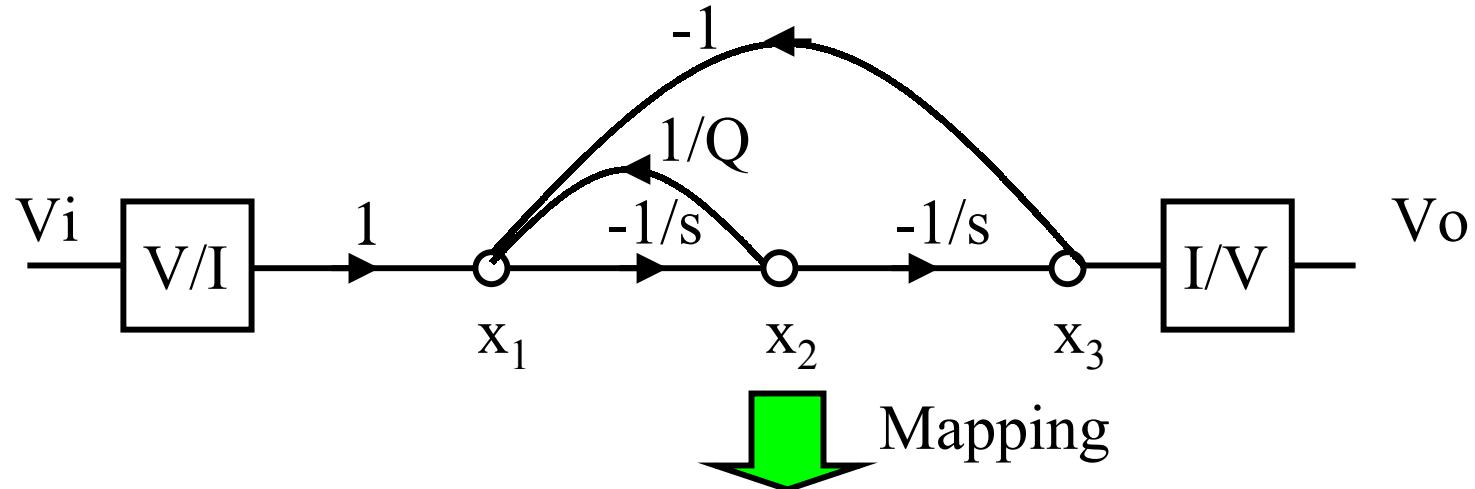


# Example: 2nd-Order Filter Realization

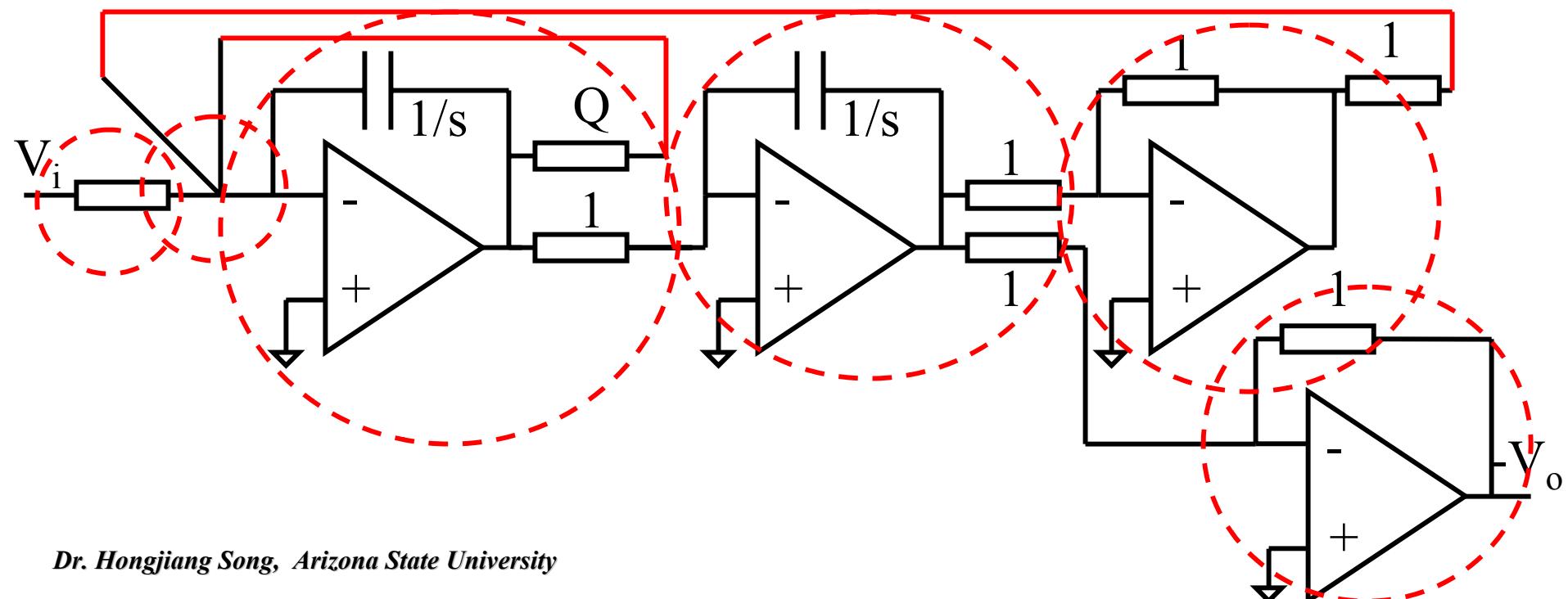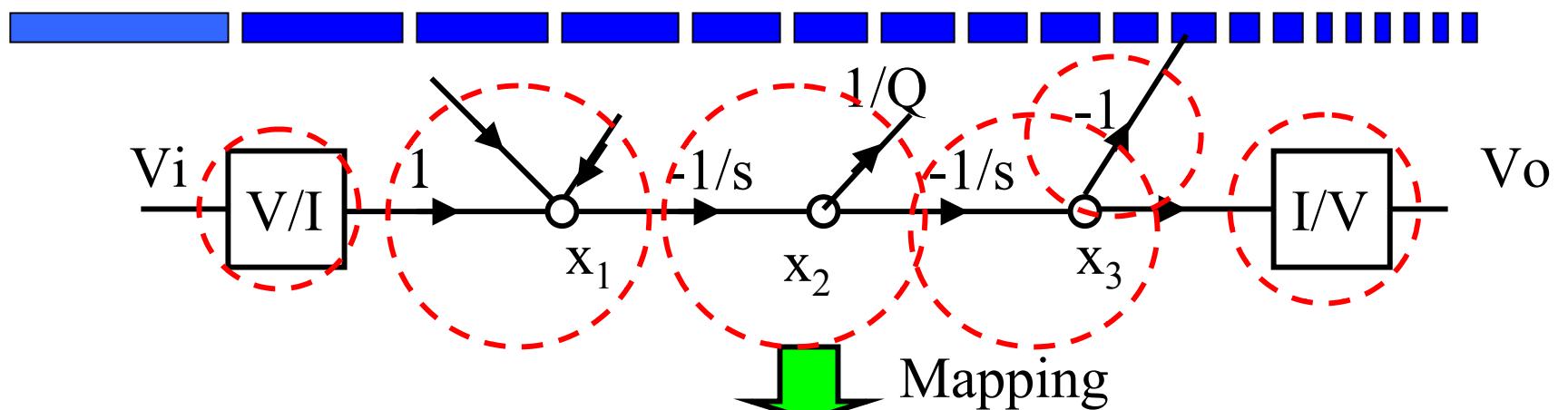


# Example: 2nd-Order Filter Realization



Merge

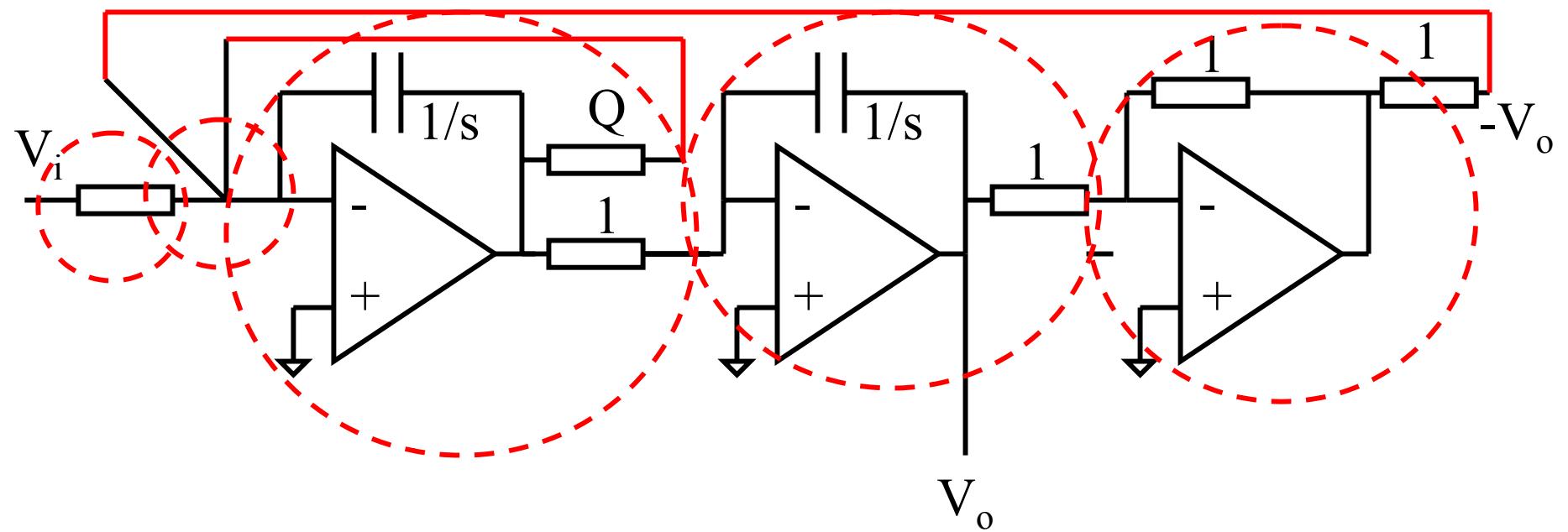


# Example: 2nd-Order Filter Realization

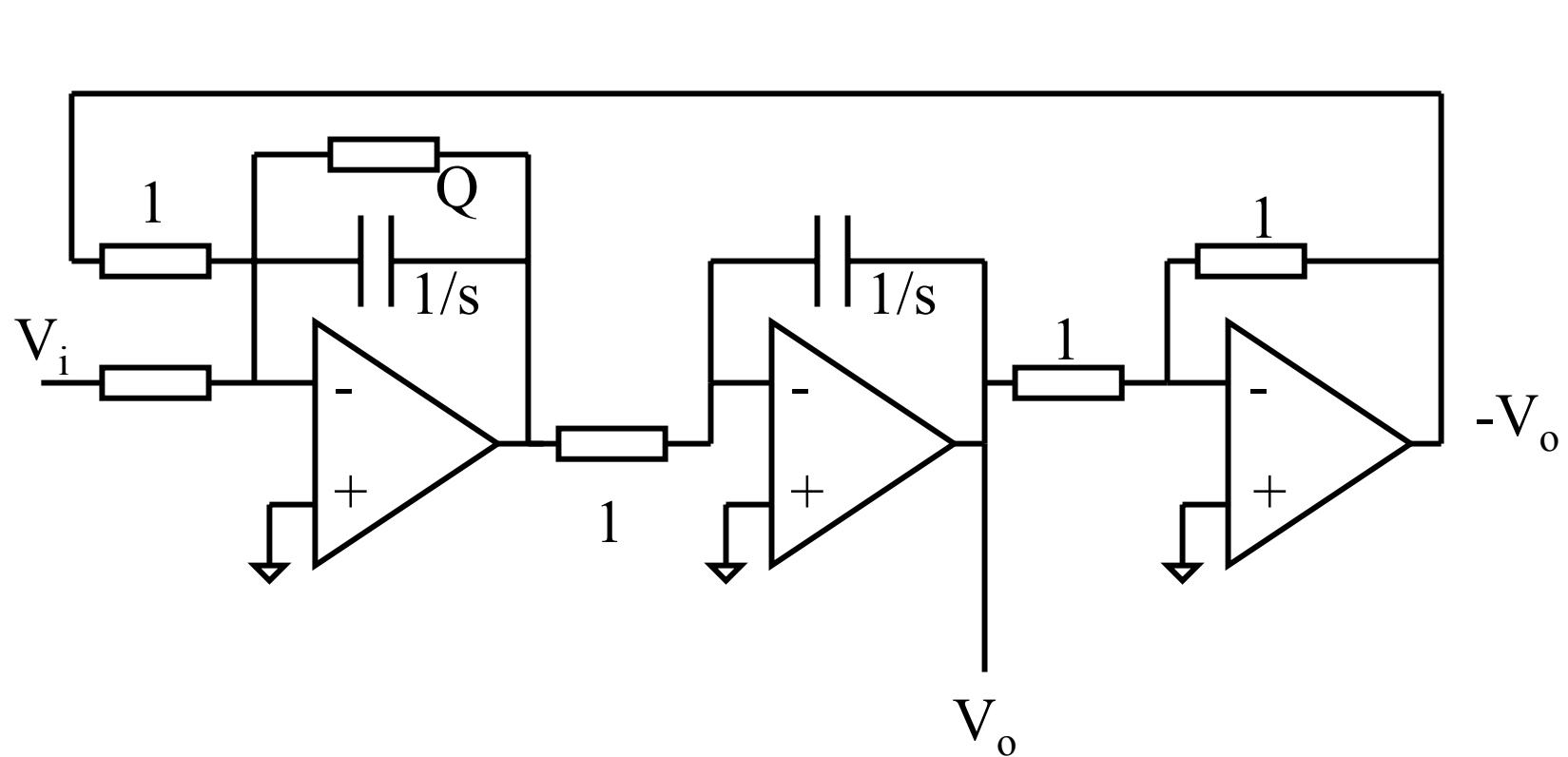

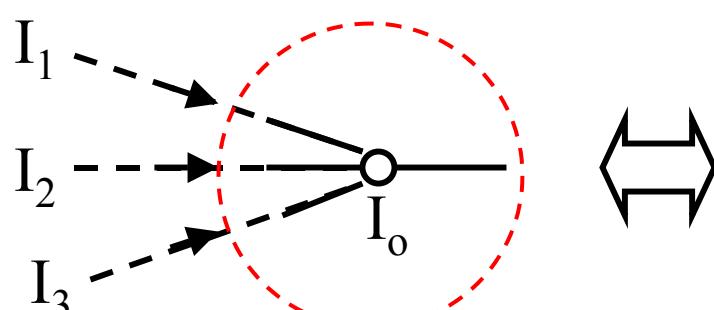
# Current-Mode Gm-C Circuits



- Addition
  - It is straightforward to realize addition in current





A) SFG

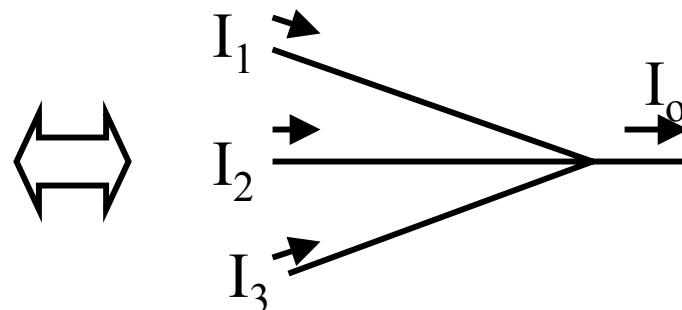

B) Circuit
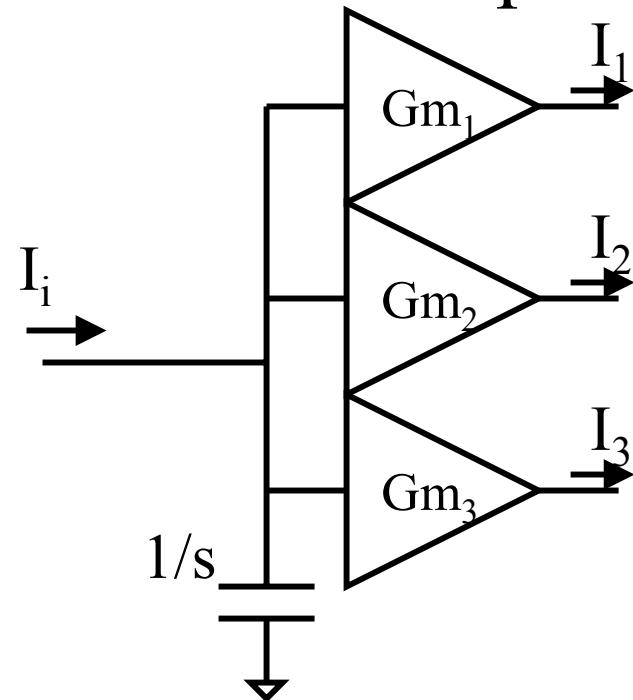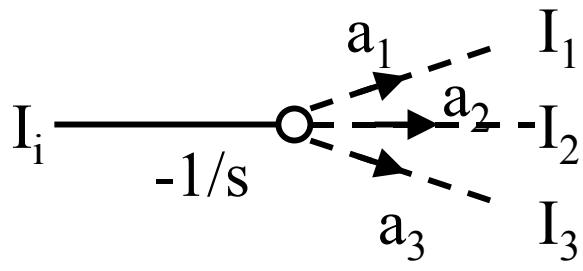
# Current-Mode Gm-C Circuits

- Integration with weighted current output




$$Gm_i = a_i \quad \{i = 1, 2, 3\}$$

# Current-Mode Gm-C Circuits



- Scaling

$$I_i \rightarrow -a \rightarrow I_o$$

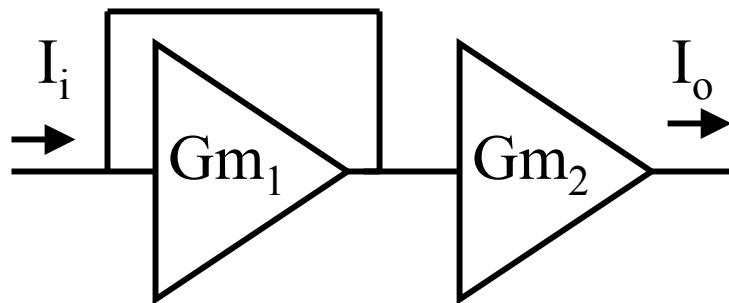

A) SFG



B) Circuit

$$a = Gm_2/Gm_1$$

# Current-Mode Gm-C Circuits



- V/I and I/V conversion

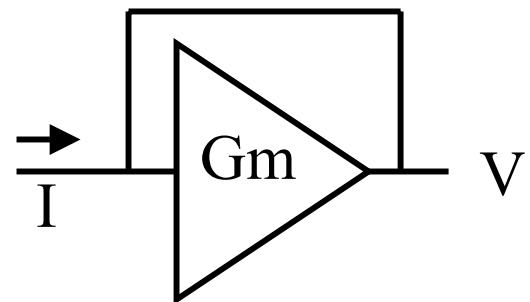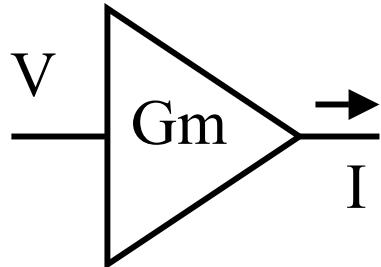



$$I = -GmV$$

$$V = I/Gm$$

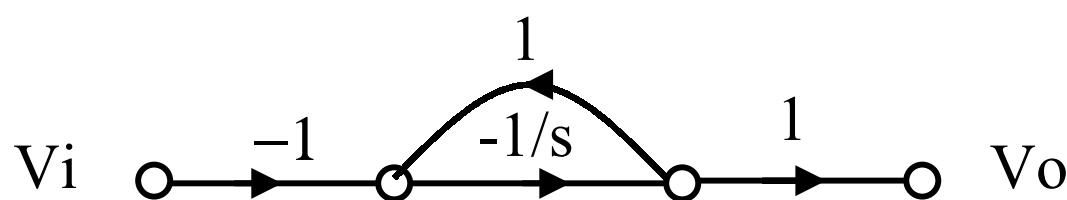
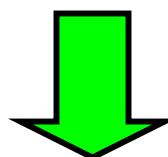
# Example: 1st-Order Filter Realization




$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s + 1}$$




# Example: 1st-Order Filter Realization

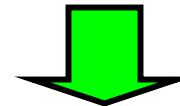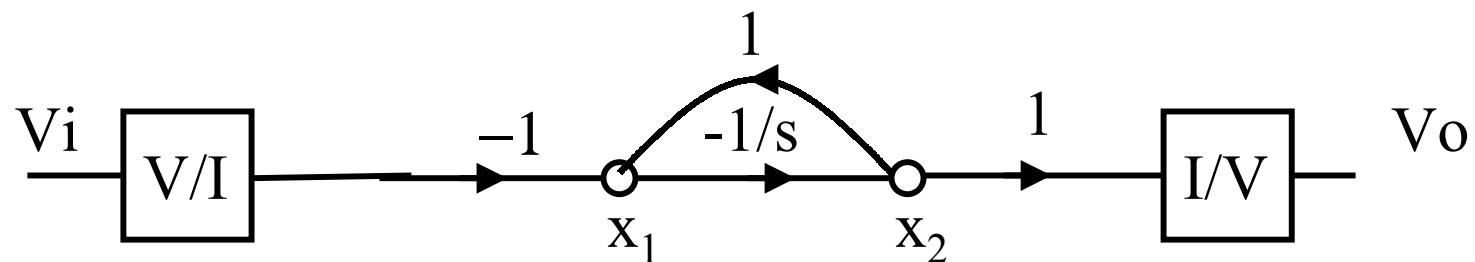


Mapping

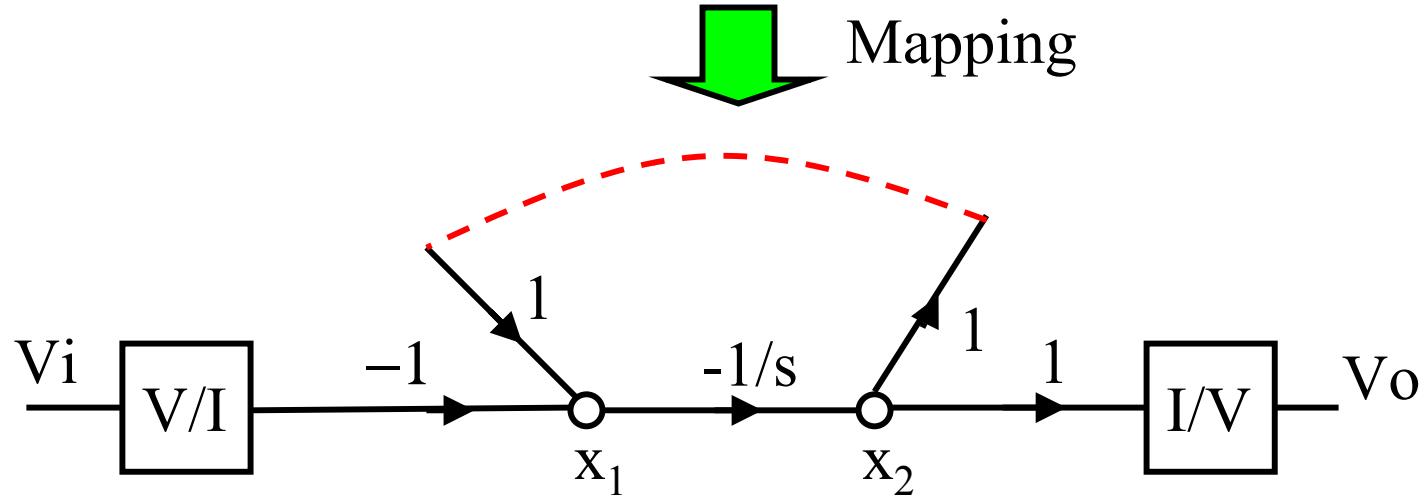


# Example: 1st-Order Filter Realization

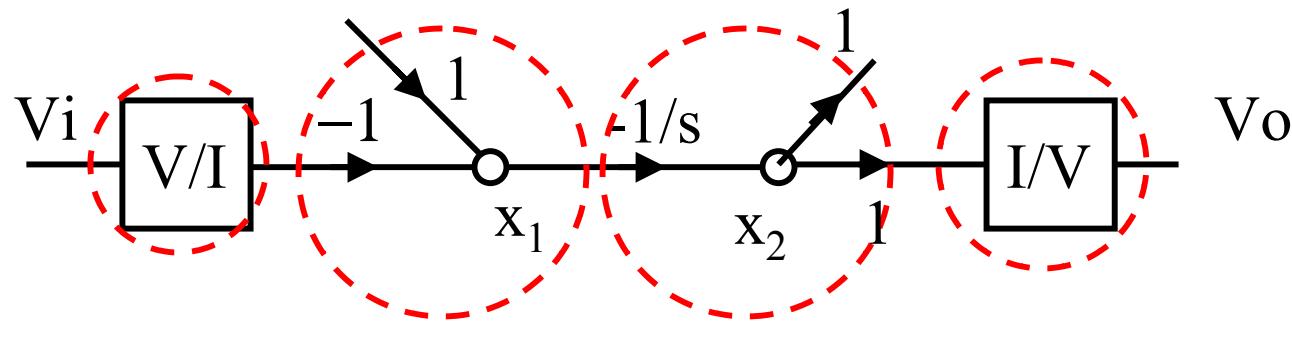

Mapping

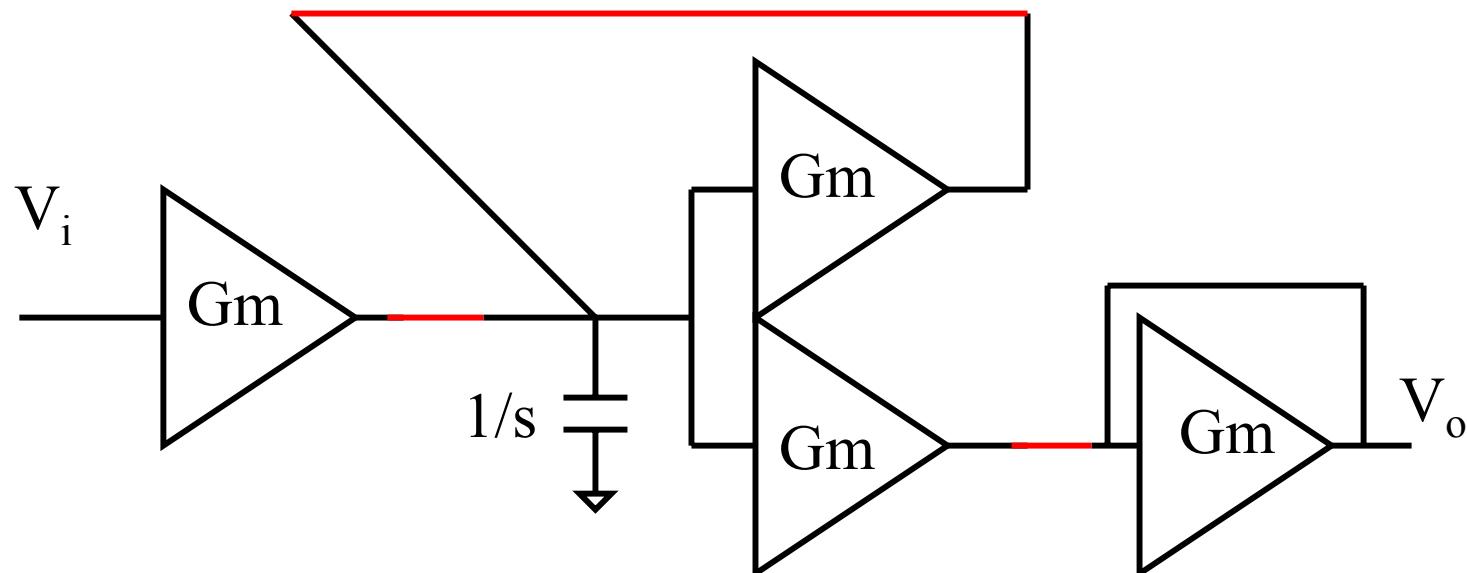


# Example: 1st-Order Filter Realization

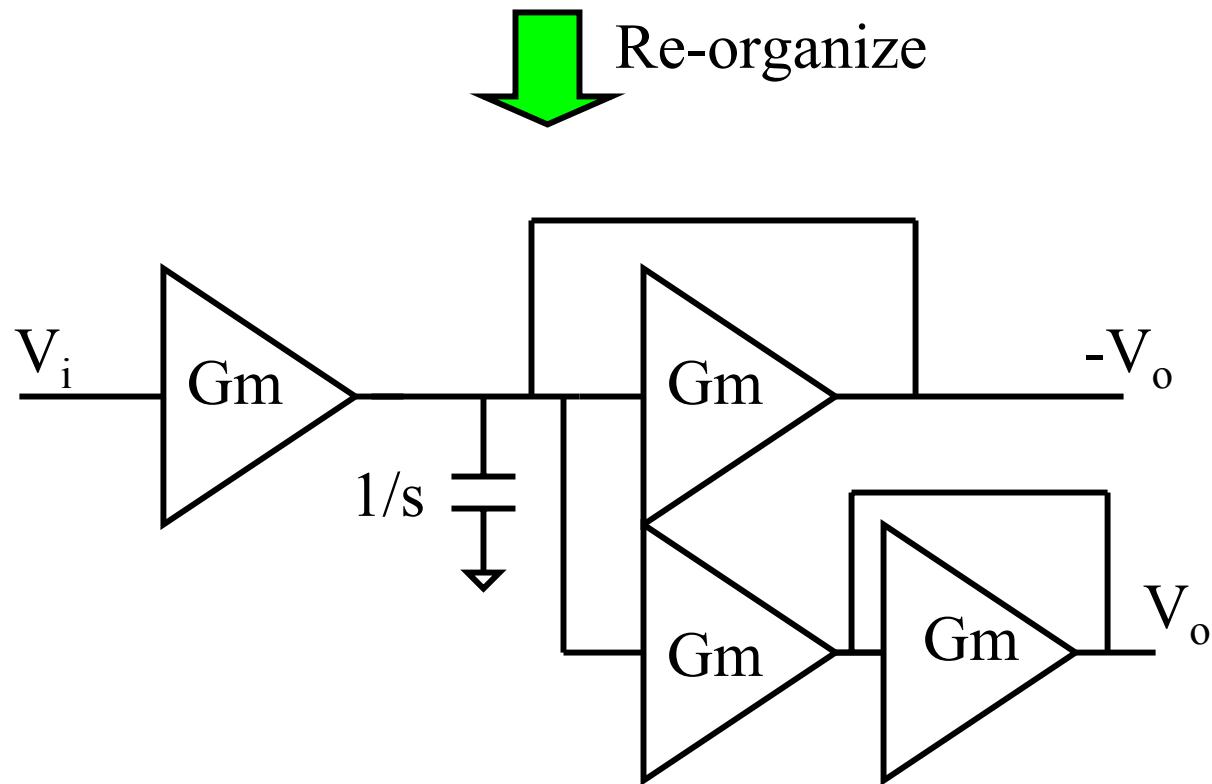

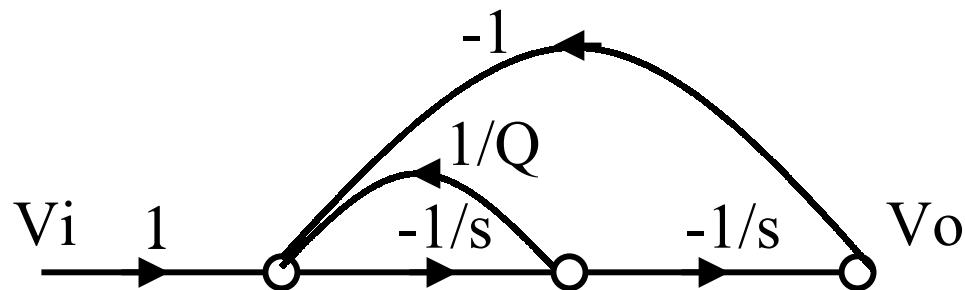
# Example: 2nd-Order Filter Realization





$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 + \frac{1}{Q}s + 1}$$




# Example: 2nd-Order Filter Realization

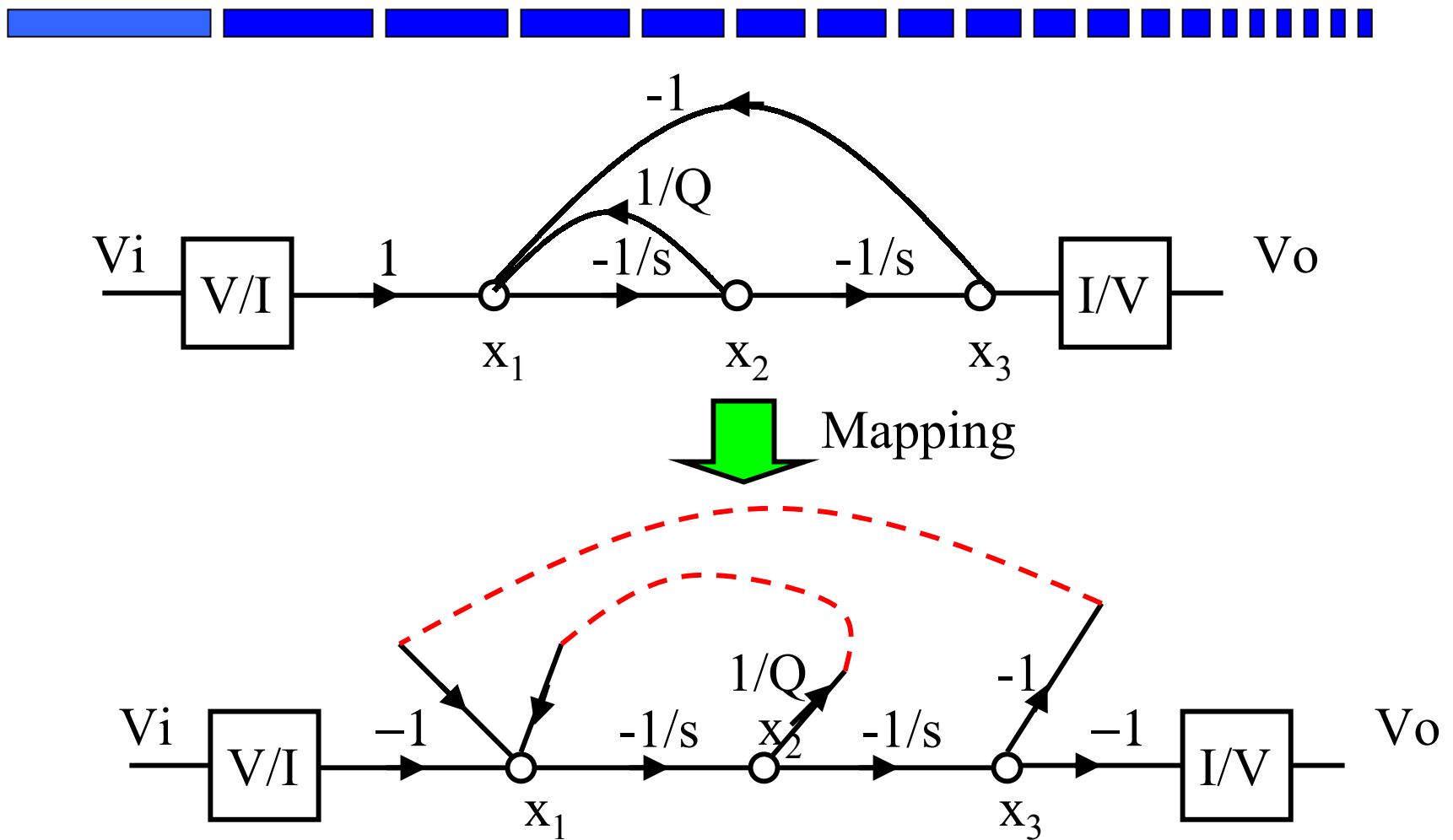

# Example: 2nd-Order Filter Realization

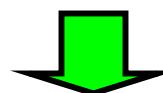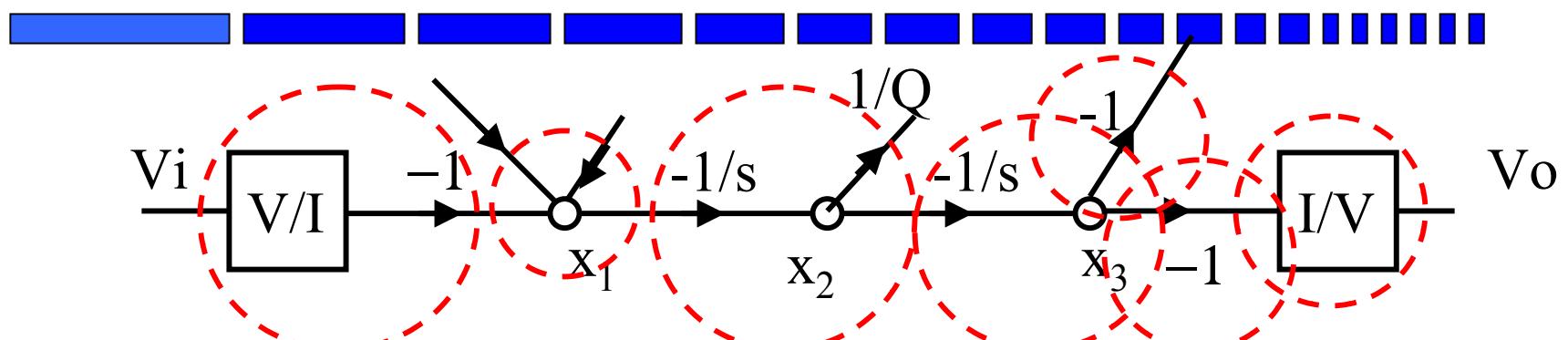


Mapping

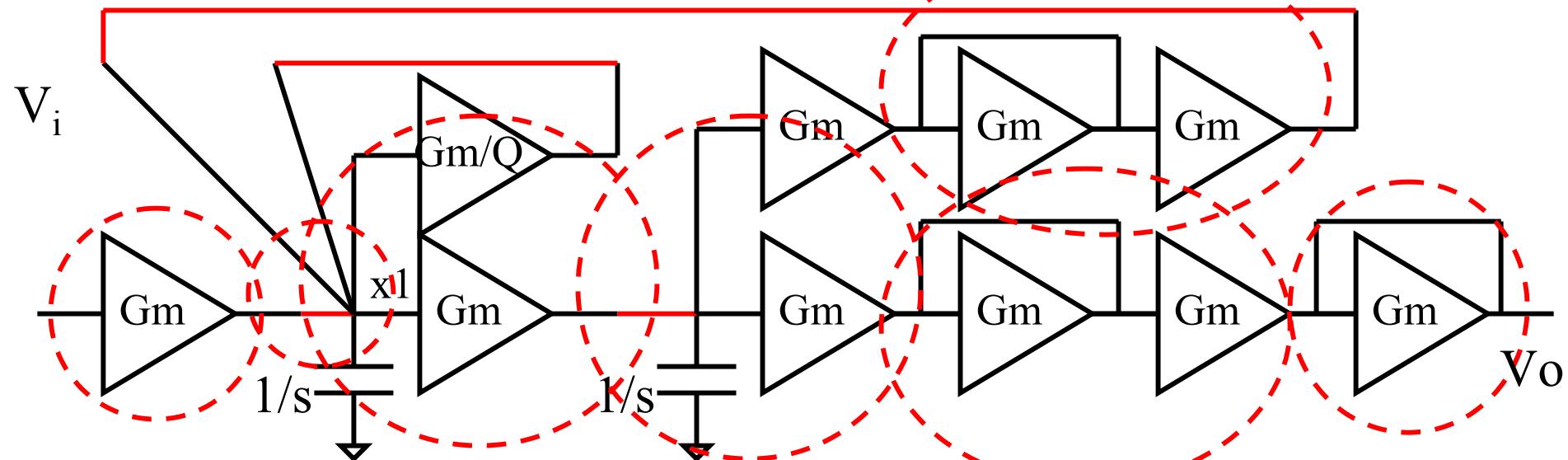


# Example: 2nd-Order Filter Realization



Merge

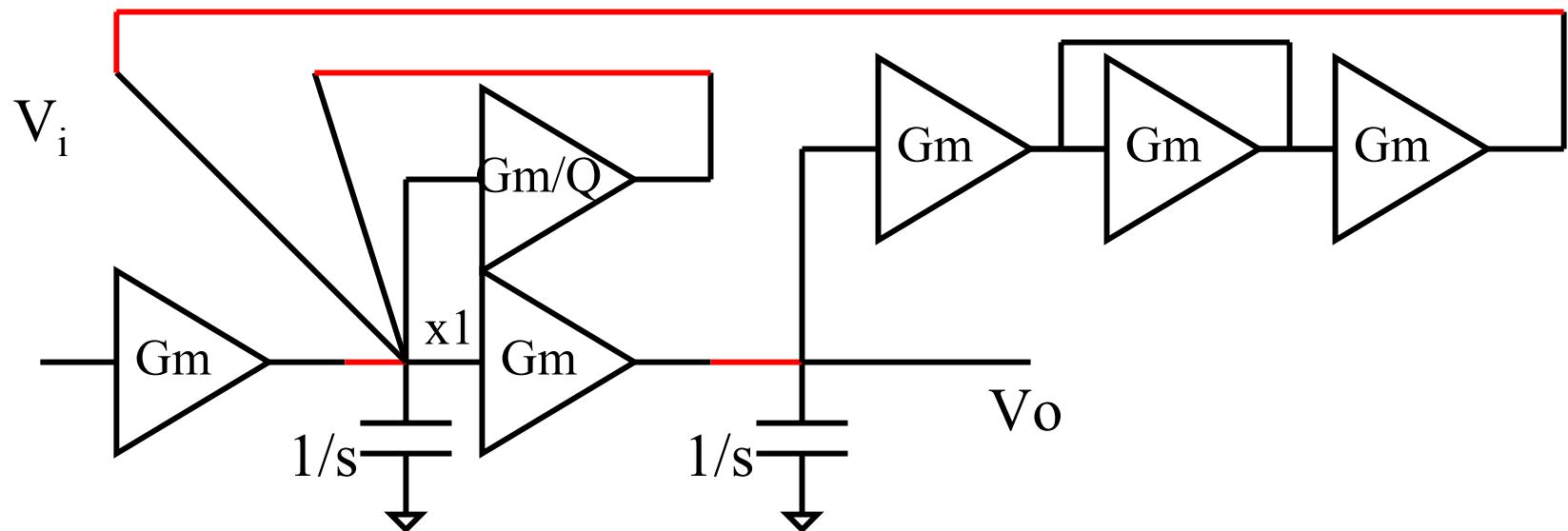

# Example: 2nd-Order Filter Realization

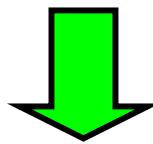

Re-organize

