

Spring 2002



EEE598D: Analog Filter & Signal Processing Circuits

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering

Arizona State University

Tuesday January 22, 2002



Today: Continuous-Time Filter Fundamental

- Pole & Zero of Transfer Function
- Bode Plots
- SFG & Block Diagram
- Classification of Filter Response

Pole & Zero of the TF



- Transfer function of a general CT filter can be expressed as

$$H(s) = \frac{a_m \prod_{k=1}^m (s - z_k)}{b_n \prod_{k=1}^n (s - p_k)} = \frac{a_m (s - z_m)(s - z_{m-1}) \dots (s - z_1)}{b_n (s - p_n)(s - p_{n-1}) \dots (s - p_1)} \quad (2.1)$$

where $\{z_k\}$ and $\{p_k\}$ are s-domain zeros and poles of the transfer function


Example: Pole and Zero of the TF



- For the given example:

$$\left\{ \begin{aligned} H(s) &= \frac{1}{s^2 LC + sRC + 1} = \frac{1}{LC} \frac{1}{(s - p_1)(s - p_2)} \\ p_1 &= -\frac{R}{2L} + j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \\ p_2 &= -\frac{R}{2L} - j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \end{aligned} \right. \quad (2.2)$$

- It has two poles.

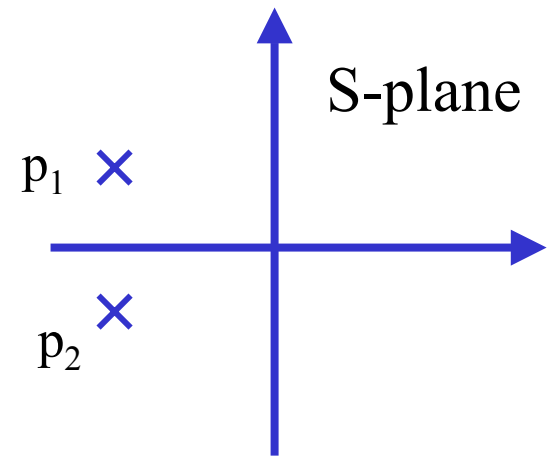


Stability of the Filter



- For stable filters, ALL poles of the transfer function have to be on the left side of the s-plane
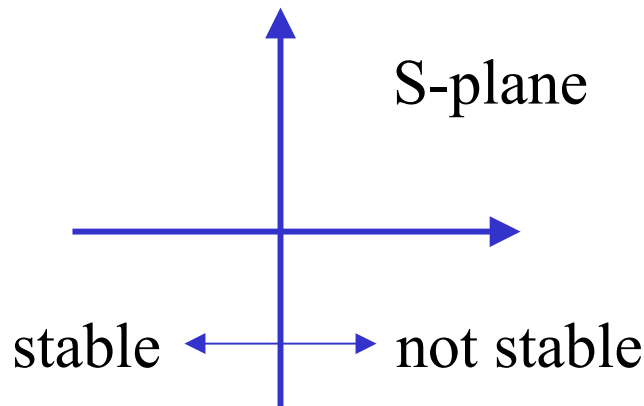
$$H(s) = \frac{a_m (s - z_m)(s - z_{m-1}) \dots (s - z_1)}{b_n (s - p_n)(s - p_{n-1}) \dots (s - p_1)} \quad (2.3)$$



Example: Stability of the Filter System




- For the given example:


$$p_1 = -\frac{R}{2L} + j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \quad (2.3)$$

$$p_2 = -\frac{R}{2L} - j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$


always stable!

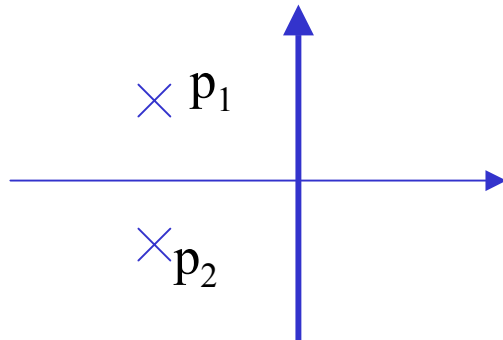
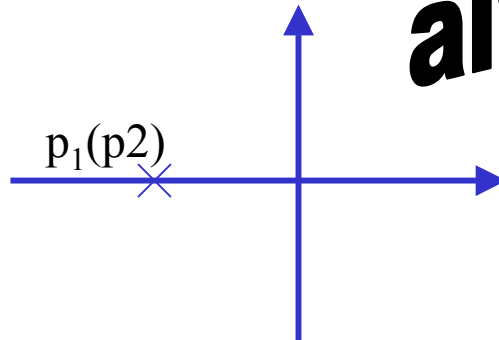
$$\frac{1}{LC} - \left(\frac{R}{2L}\right)^2 > 0$$



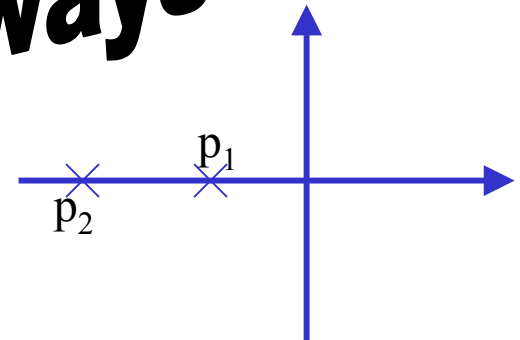
$$\frac{1}{LC} - \left(\frac{R}{2L}\right)^2 = 0$$



$$\frac{1}{LC} - \left(\frac{R}{2L}\right)^2 < 0$$

Bode Plots

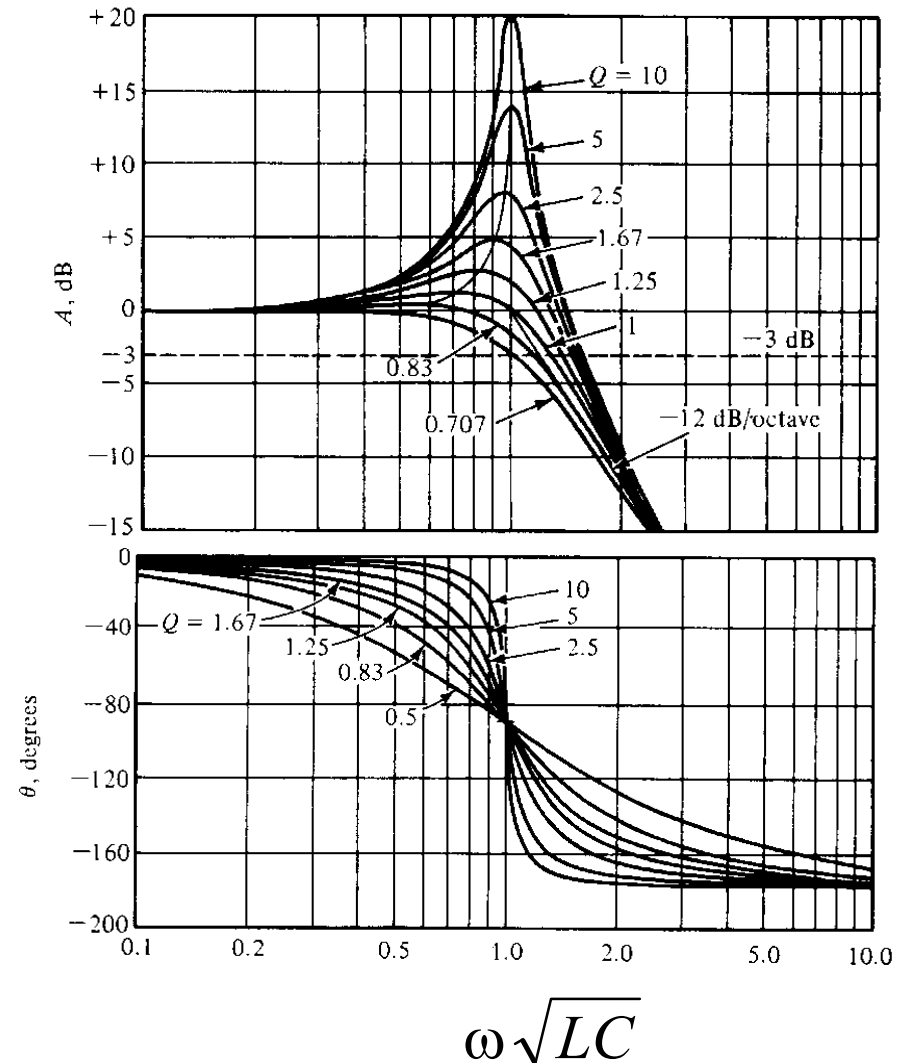- The plots of the gain and phase responses of the system vs. frequency




Bode Plots - the First-Order Systems




- For the first order system, we have
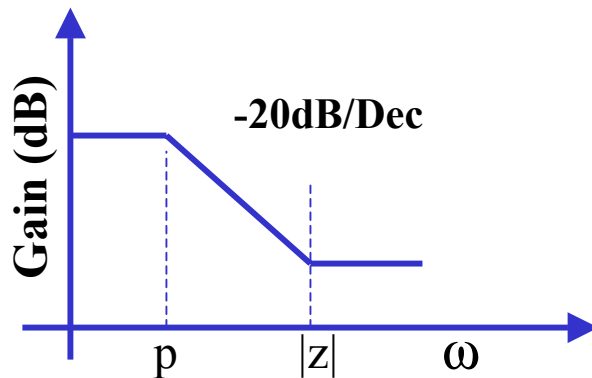
$$H(s) = K \frac{(s - z)}{(s - p)} \quad (2.4)$$



A) $|z| > p$

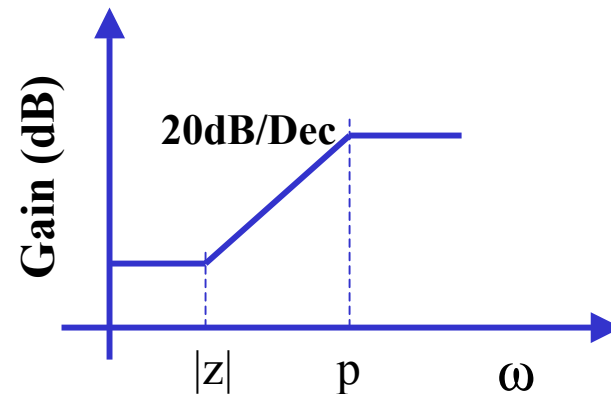


B) $|z| < p$

Bode Plots - the First-Order Systems

- For the first order system, we have (assume $K > 0$)
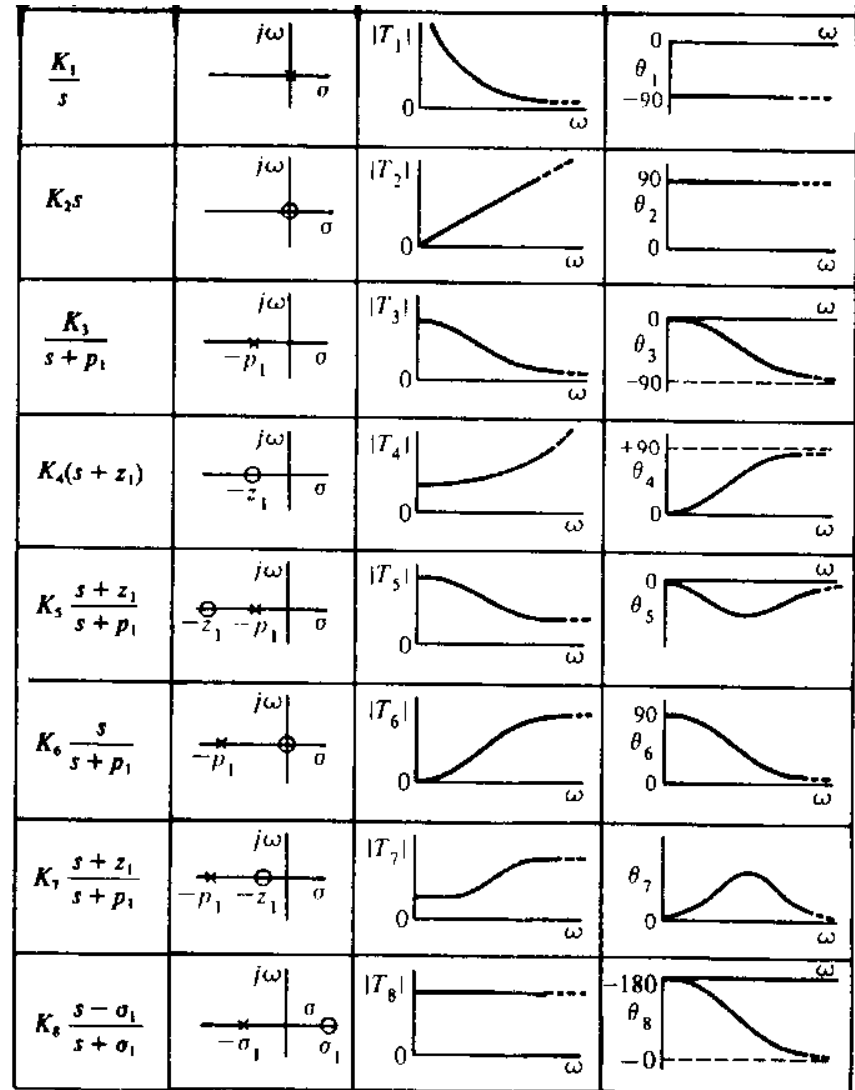
$$H(s)(= T(s)) = K \frac{(s - z)}{(s - p)}$$



* All K_i are assumed positive.

Bode Plots - Important Features



- Both frequency and magnitude are plotted on logarithm scales.
- Logarithm measure of the magnitude make it possible to add and subtract rather than multiply or divide.
- The slope of all lines for bilinear function is $\pm 6\text{dB/Oct}$ or $\pm 20\text{dB/dec}$. In general case all asymptotic lines are integer multiples these two numbers.

Bode Plots - Important Features(Con't)




- In many applications we deal only with asymptotic plots without “filling the corner” to obtain the actual plots.
- The phase angle plots are added and subtracted to obtain total angle response.

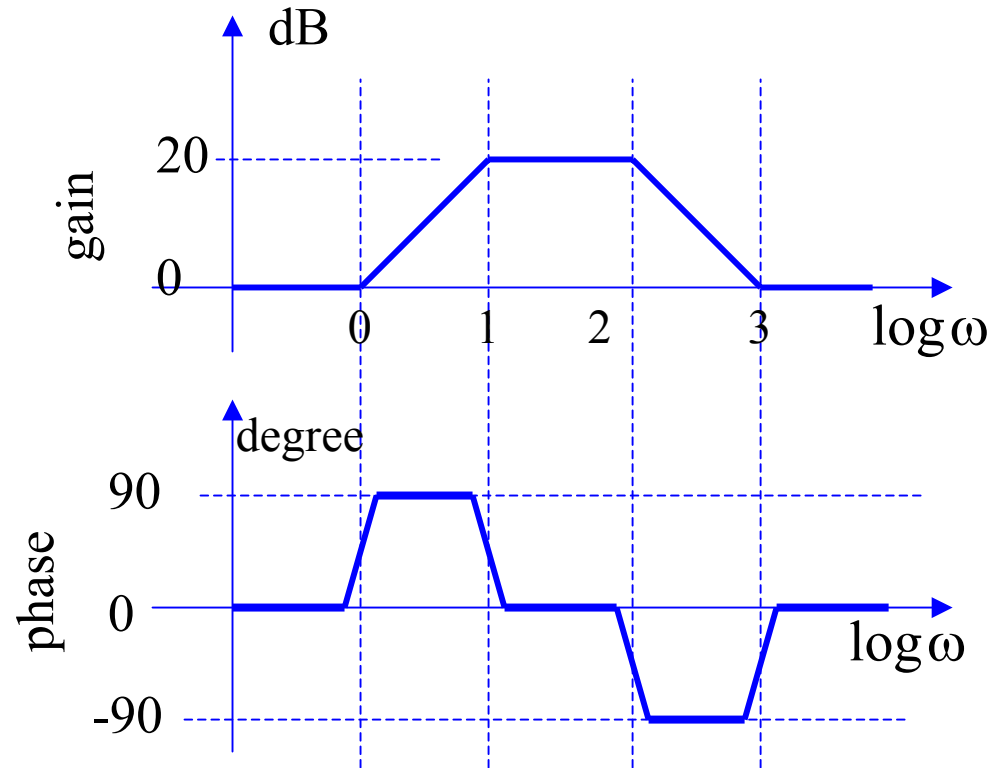Example: Bode Plots



$$H(s) = \frac{(s + 1)(s + 1000)}{(s + 10)(s + 100)}$$



SFG & Block Diagram





- We have seen that a CT filter can be represented by its
 - Schematic
 - Differential Equations
 - Transfer Function
- It can be also expressed as
 - Signal-Flow Graph (SFG), or
 - Block Diagram

SFG & Block Diagram





- Basic elements of CT filter





$$y(t) = x(t - t_0)$$

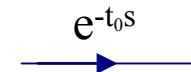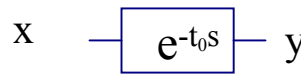

$$y(t) = ax(t)$$

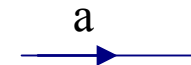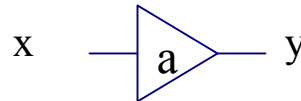


$$y(t) = x_1(t) + x_2(t)$$

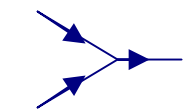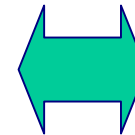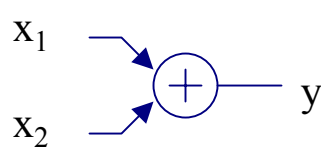
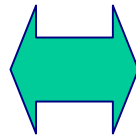


(2.5)












$$y(t) = \frac{dx(t)}{dt}$$

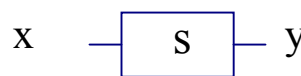

$$y(t) = y(0) + \int_0^t x(t_1) dt_1$$

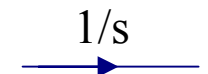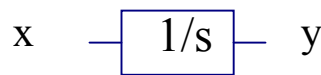


Rules for SFG Reduction

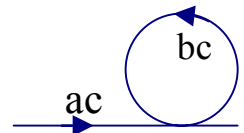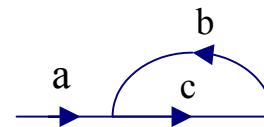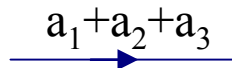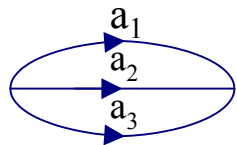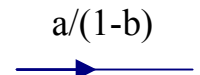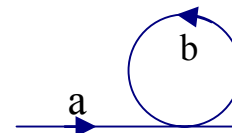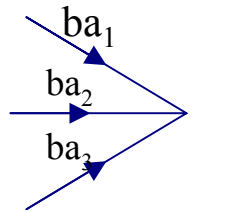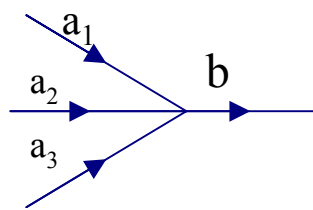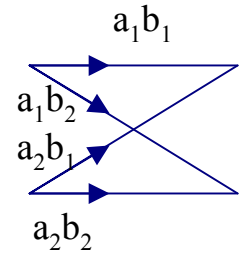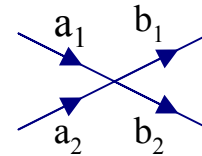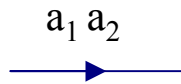


Example: SFG and Block Diagram

- For the filter described below

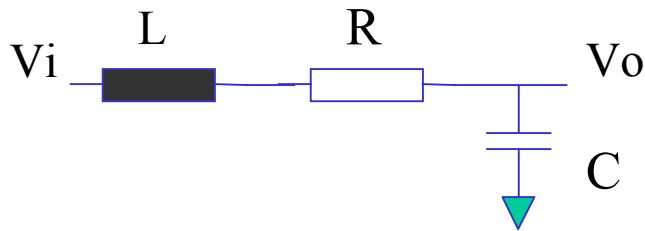


$$v_o(t) = v_i(t) - LC \frac{d^2 v_o(t)}{dt^2} - RC \frac{dv_o(t)}{dt} \quad (2.6)$$

- We have real-space block diagram:

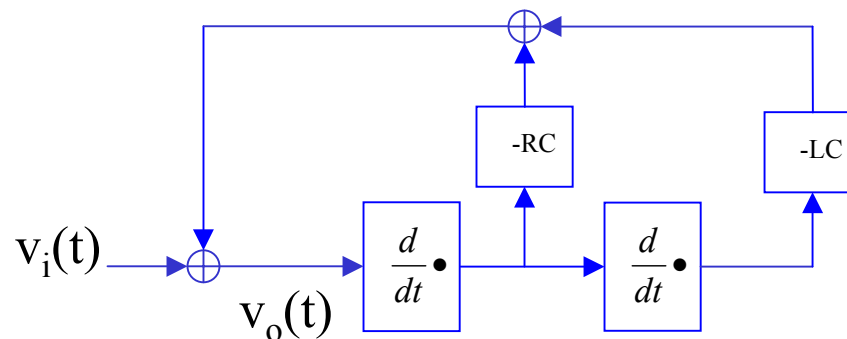


Example: SFG and Block Diagram

- S-domain block diagram:

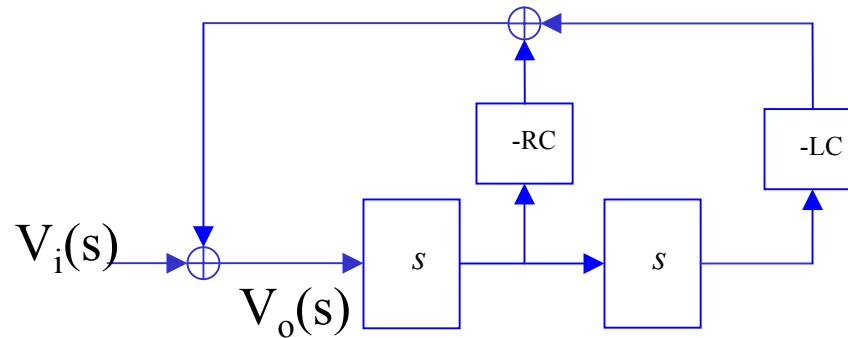


- SFG:

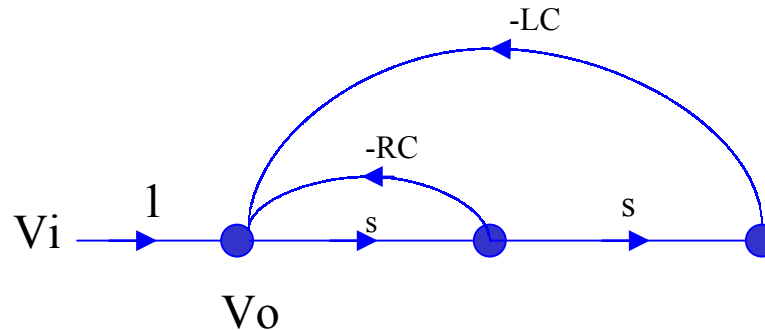

Alternative SFG and Block Diagram



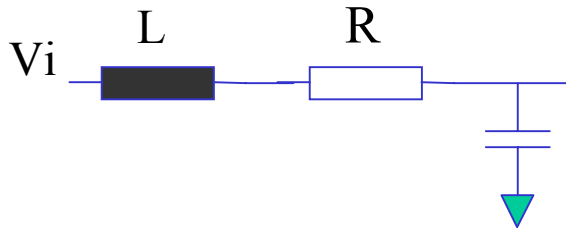- In practical cases, differentiator tends to amplify the noise. Therefore integrator is preferred in the filter design.
- For the filter discussed in the example, we may have alternative equation




$$\begin{aligned} LC \frac{d^2 v_o(t)}{dt^2} + RC \frac{dv_o(t)}{dt} + V_o(t) &= v_i(t) \\ \Rightarrow (LCs^2 + RCs + 1)V_o(s) &= V_i(s) \\ \Rightarrow V_o(s) &= \frac{1}{s^2} \frac{V_i(s)}{LC} - \frac{1}{s^2} \frac{V_o(s)}{LC} - \frac{1}{s} \frac{R}{L} V_o(s) \end{aligned} \quad (2.7)$$


Alternative Block Diagram and SFG



- System built using integrators:

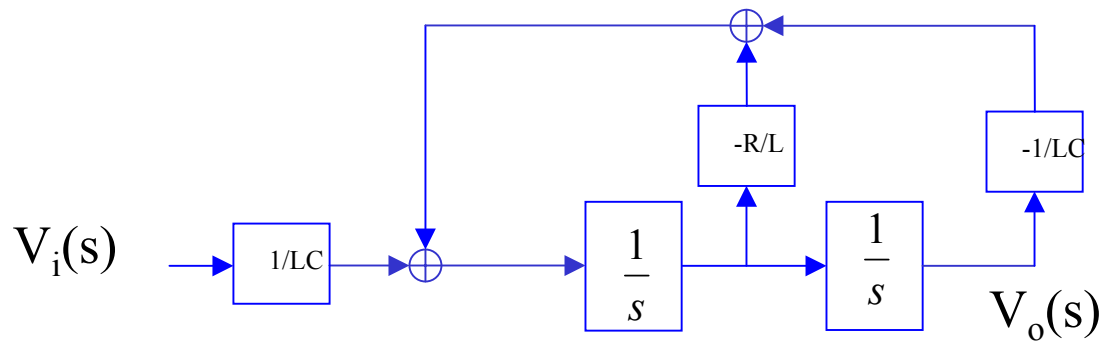

- With the alternative SFG:

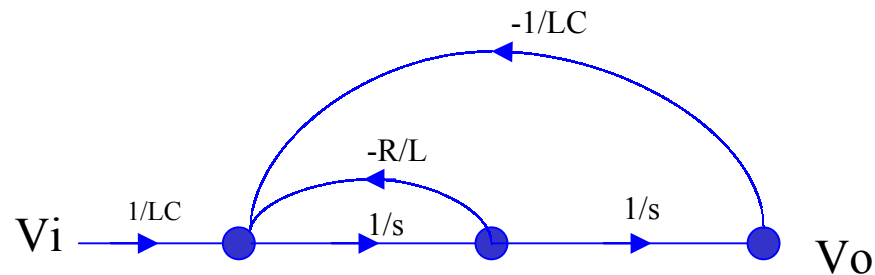

Classification of Filters Response




- Filters are classified according to the function they are to perform.
- In ideal case, a passband is the range of frequency of the filter where $|H(j\omega)|=1$.
- In a idea stopband $|H(j\omega)|=0$.

Classification of Filters Response




- The pattern of passbands and stopbands that give rise to the most common filters are defined as:
 - Lowpass (LP) filters
 - Highpass (HP) filters
 - Bandpass (BP) filters
 - Bandstop (BS) filters


Ideal Filters Response

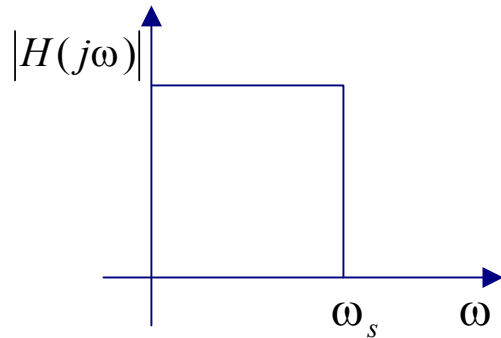


A) Lowpass Filter

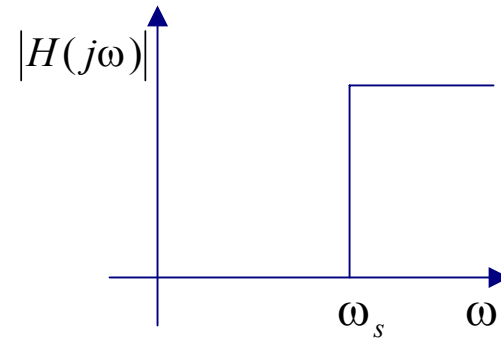

B) Highpass Filter

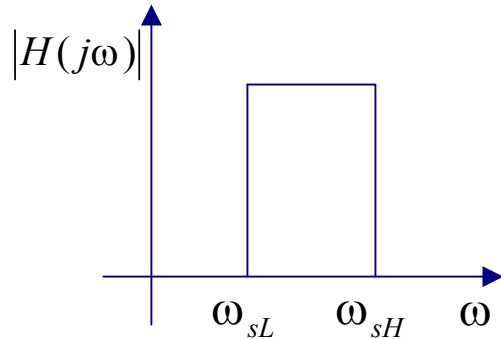

C) Bandpass Filter

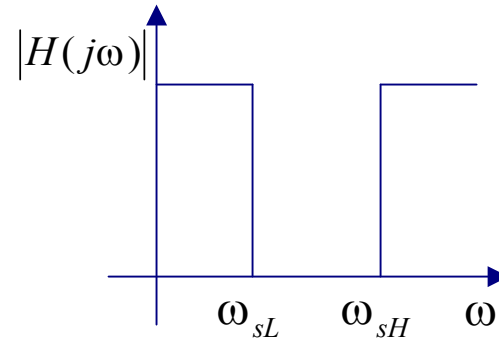

D) Bandstop Filter

Specification of Realistic Filter



- In practice, it is not possible to realize the ideal transfer function with realistic filter consisting of a finite number of elements.
- A realistic filter is always described by real rational function of the complex frequency given as:


$$H(s) = \frac{\sum_{k=0}^m a_k s^k}{\sum_{k=0}^n b_k s^k} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0} \quad (2.4)$$

Specification of Realistic Filter




- Such a transfer function are seen have finite transition region (known as transition bands) between passbands and stopbands.
- Filters may be specified either in
 - Gain of transfer function, or
 - Attenuation of transfer function


Specification of Realistic LP Filter

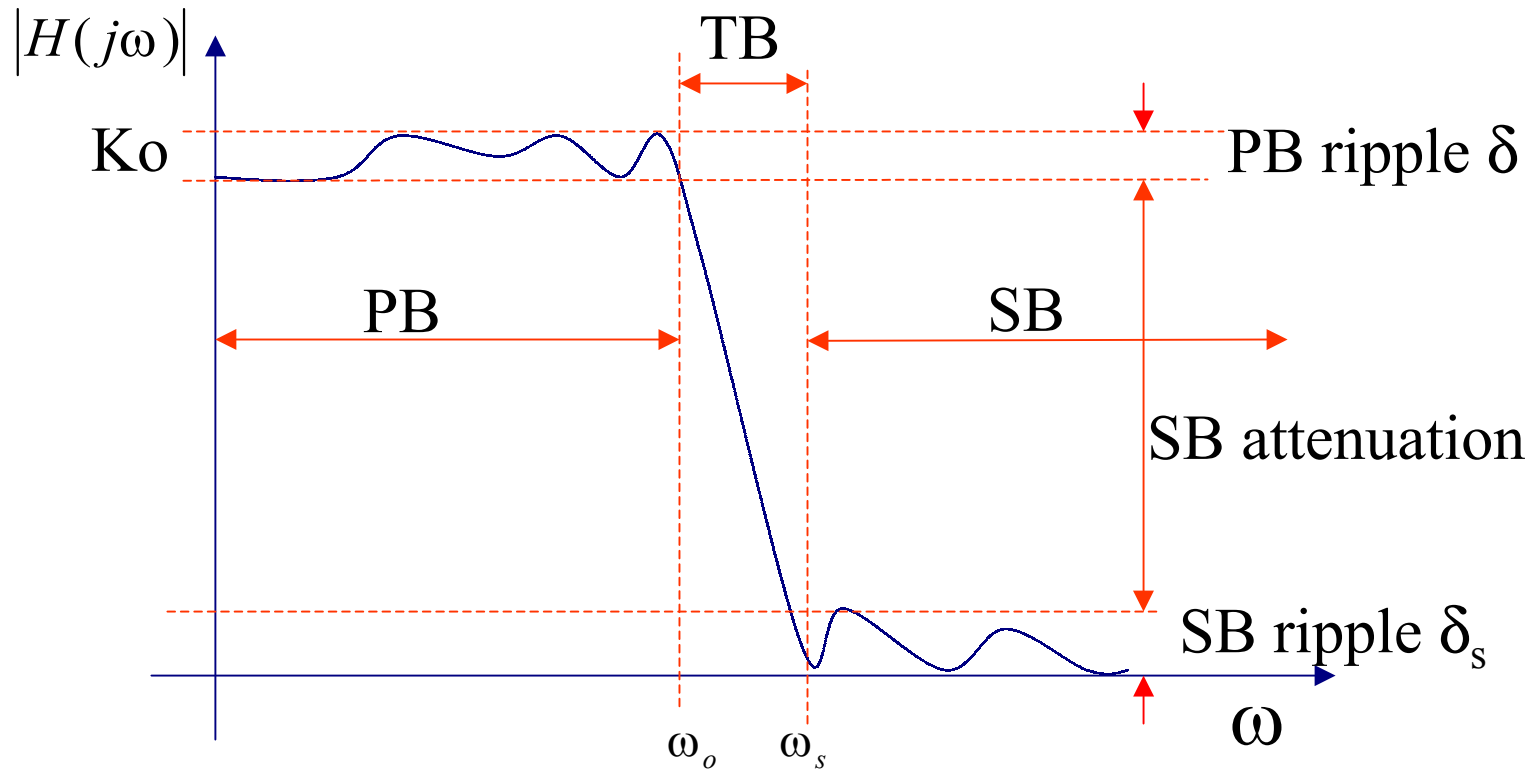

Specification of Realistic HP Filter

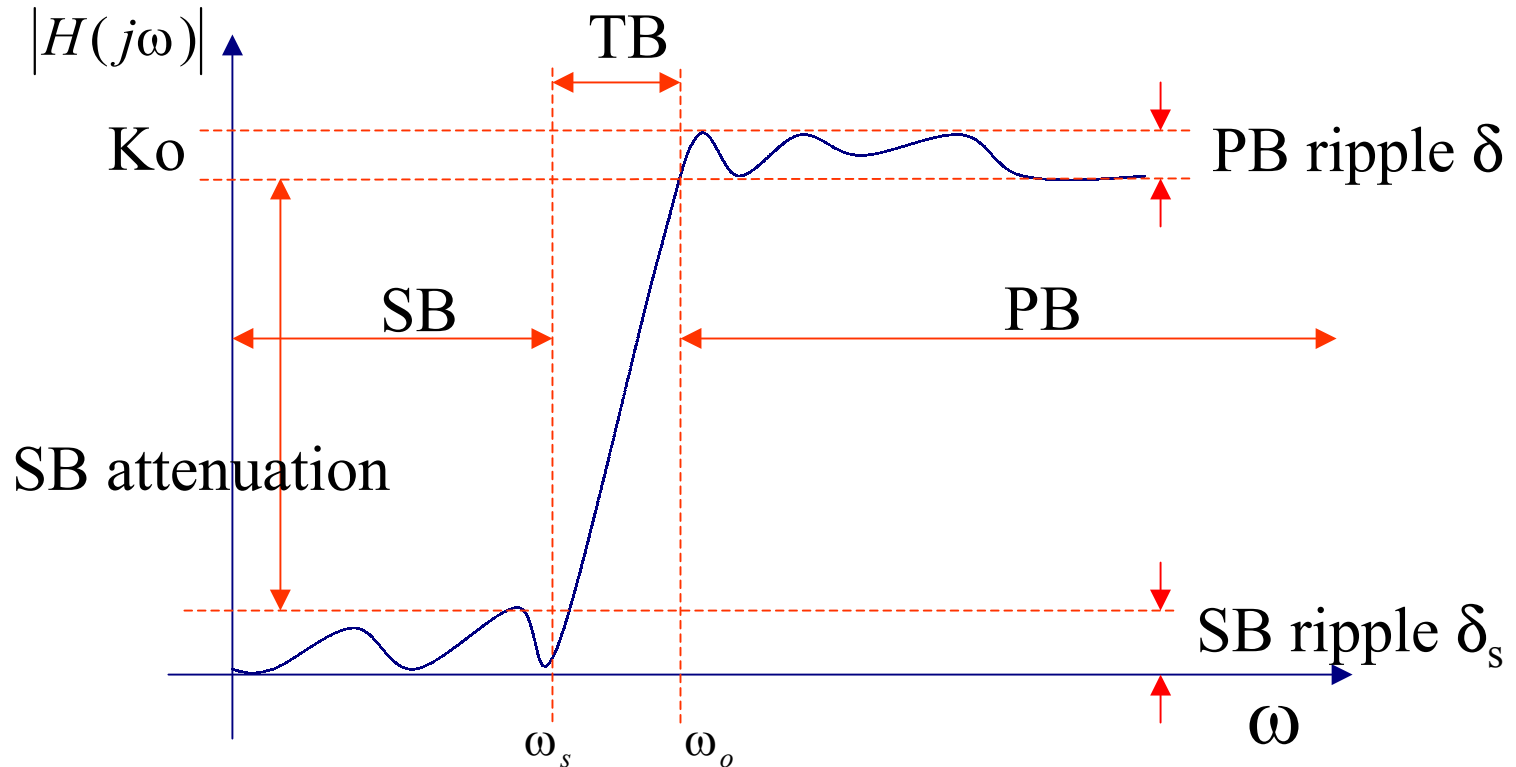

Specification of Realistic BP Filter

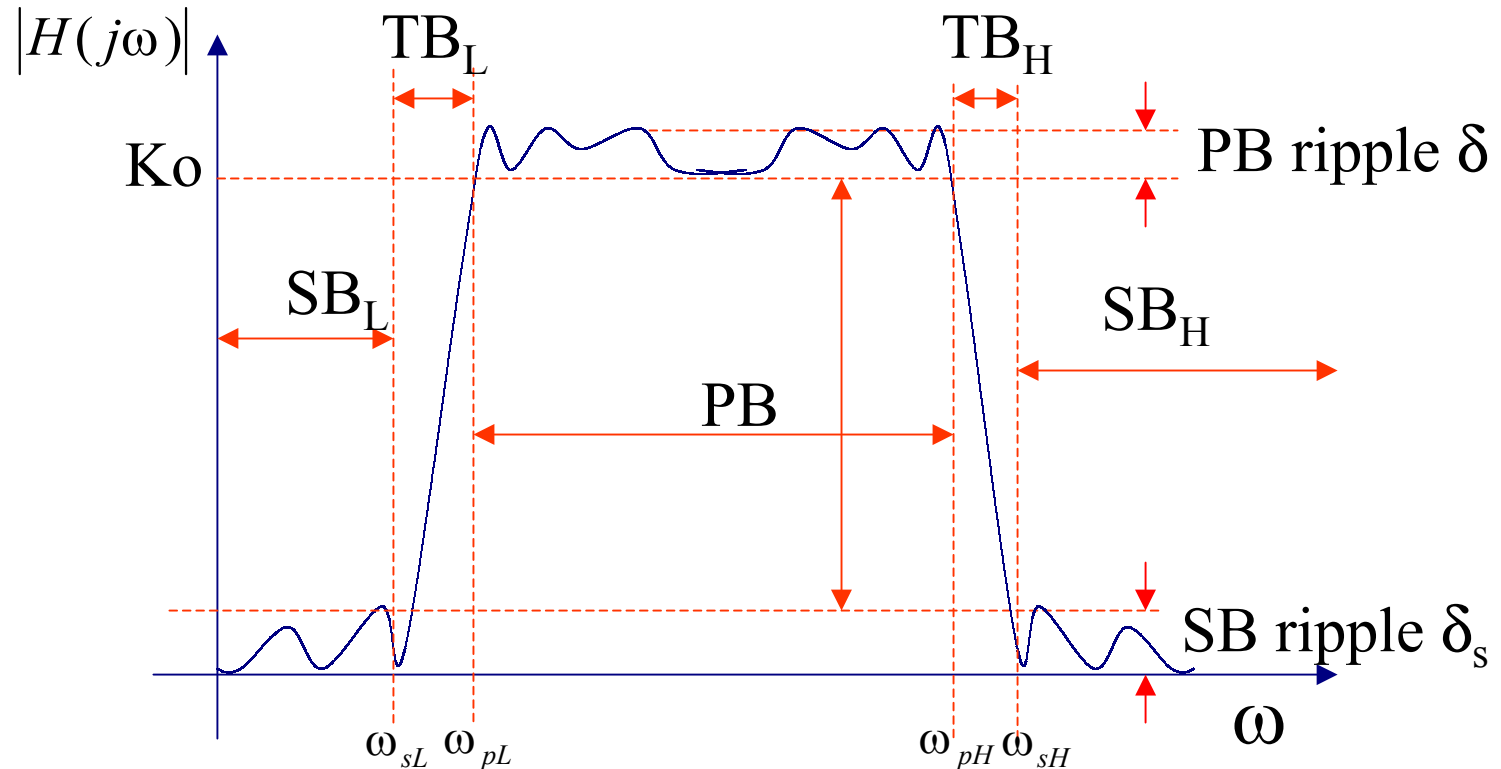

Specification of Realistic BS Filters

