

Spring 2002



EEE598D: Analog Filter & Signal Processing Circuits

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering

Arizona State University

Tuesday February 12, 2002



Today: Introduction to SC Circuits

- SC Circuit Fundamental
- Charge Redistribution Analysis
- Transfer Function

Introduction



- A SC circuit operates as a DT signal processor.
- Most easily analyzed using the z-transform.
- Require anti-aliasing and smoothing filters.
- The technique has become extremely popular due to:
 - Accurate frequency response (determined by capacitance ratios that can be set with an accuracy of 0.1% or better)
 - Good linearity and dynamic range
- Applications:
 - Filters, gain-stages, oscillators and modulators.

Switched-Capacitor Fundamentals



- A switched capacitor simulates a resistor



$$q(t) = C \cdot V_1$$

$$q(t + \tau) = C \cdot V_2$$

$$\Delta q(t) = C \cdot (V_1 - V_2)$$

$$I = \Delta q(t) / T = C \cdot (V_1 - V_2) / T$$


$$R_{eq} = T / C$$

  

First (Poor) SC Integrator



 - Use the active-RC integrator and replace the resistor with a switched capacitor
- Capacitor ratio determines the transfer function
 - Improved matching
 - Low power possible



$$V_2 = -\frac{C_1}{sTC_2}V_1$$

Charge Redistribution Analysis




- Consider the charge transportation
- OP outputs can take/give charge
- OP (CMOS) inputs cannot take/give charge
- Equilibrium will take place after settling
- No charge can disappear from an unconnected capacitor plate
- A capacitor with both plates connected to same potential will lose all of its charge

Charge Redistribution Analysis



 
- Investigate both clock phases and denote the initial conditions in each phase
- Investigate the charge conservation and find the transfer function



Charge Redistribution Analysis



- At $t = t$

 


$$q_1(t) = C_1 \cdot V_1(t)$$
$$q_2(t) = C_2 \cdot V_2(t)$$

Denote references on the capacitors

Charge Redistribution Analysis



- At $t = t + T/2$

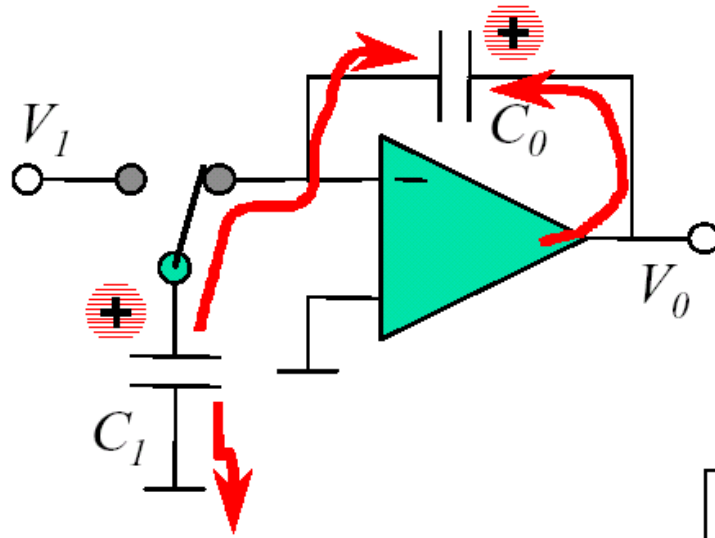

$$q_1(t + \frac{T}{2}) = 0$$

$$q_2(t + \frac{T}{2}) = C_2 \cdot V_2(t + \frac{T}{2})$$


$$q_2(t + \frac{T}{2}) = -q_1(t) + q_2(t)$$

- CI loses its charge to ground and C0

Charge Redistribution Analysis



- At $t = t+T$

 

$$q_1(t+T) = C_1 \cdot V_1(t+T)$$
$$q_2(t+T) = C_2 \cdot V_2(t+T)$$

$$q_2(t+T) = q_2\left(t + \frac{T}{2}\right)$$

- Charge conservation.

Transfer Function



$$q_2(t+T) = q_2(t + \frac{T}{2}) = -q_1(t) + q_2(t)$$

$$C_2 \cdot V_2(t+T) = C_2 \cdot V_2(t) - C_1 \cdot V_1(t)$$

$$C_2 \cdot V_2(z) \cdot z = C_2 \cdot V_2(z) - C_1 \cdot V_1(z) \Rightarrow$$



$$C_2 \cdot V_2(z) \cdot (z-1) = -C_1 \cdot V_1(z) \Rightarrow$$

$$H(z) = \frac{V_2(z)}{V_1(z)} = -\frac{C_1}{C_2} \cdot \frac{1}{z-1} = -\frac{C_1}{C_2} \cdot \frac{z^{-1}}{1-z^{-1}}$$

Inverting Discrete-time Integrator

Influence of Parasitic Capacitors

  - Parasitic from fringing capacitors and bottom-plate to substrate




$$C_{p2} \sim 20\% C_1 !!$$

Parasitic Capacitance



 - Include parasitic to all capacitors, switches, etc.
- Remove those who do not effect the transfer function



Transfer Function



$$q_2(t+T) = q_2(t + \frac{T}{2}) = -q_1(t) + q_2(t)$$

$$C_2 \cdot V_2(t+T) = -C_2 \cdot V_2(t) + (C_1 + C_P) \cdot V_1(t)$$

$$C_2 \cdot V_2(z) \cdot z = C_2 \cdot V_2(z) - (C_1 + C_P) \cdot V_1(z) \Rightarrow$$

$$C_2 \cdot V_2(z) \cdot (z - 1) = -(C_1 + C_P) \cdot V_1(z) \Rightarrow$$

$$H(z) = \frac{V_2(z)}{V_1(z)} = -\frac{C_1 + C_P}{C_2} \cdot \frac{1}{z - 1} = -\frac{C_1 + C_P}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}}$$

- Gain is affected by the parasitic.


Parasitic Capacitors - Conclusions



Parasitic insensitive vs. sensitive


- To minimize the influence of parasitic:
 - Switch the capacitor between a voltage source and ground
 - Switch the capacitor between ground and virtual ground

Parasitic Insensitive SC Circuits

 

Parasitic Insensitive SC Circuits

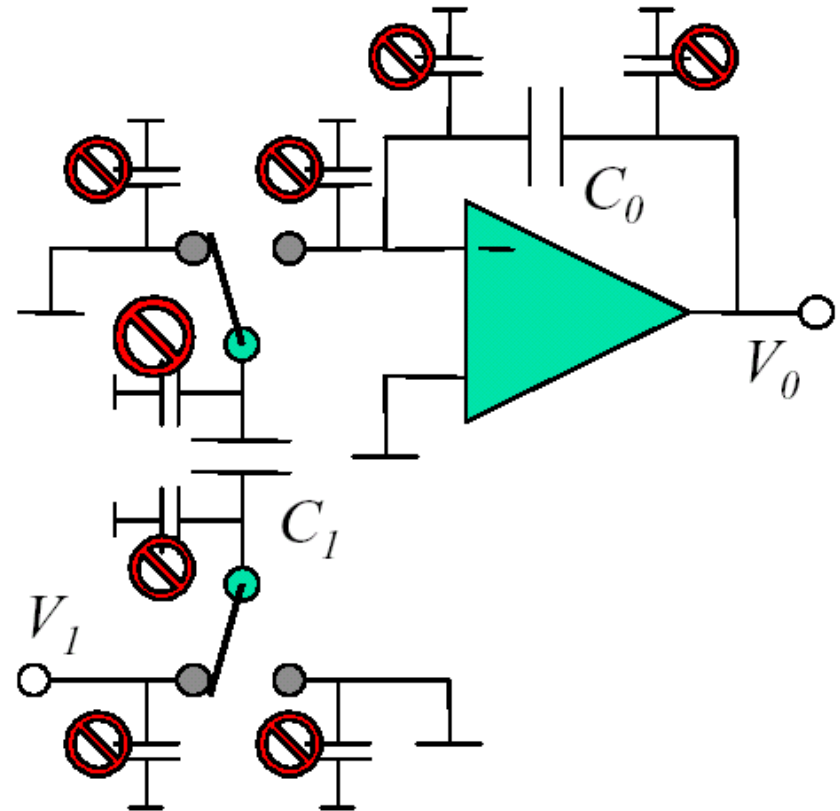
- Include parasitic to all capacitors, switches, etc.
- Remove those who do not effect the transfer function.



Charge Redistribution Analysis



- At $t = t$

 


$$q_1(t) = C_1 \cdot V_1(t)$$
$$q_2(t) = C_2 \cdot V_2(t)$$

Charge Redistribution Analysis



- At $t = t + T/2$

 

$$q_1(t + \frac{T}{2}) = 0$$

$$q_2(t + \frac{T}{2}) = C_2 \cdot V_2(t + \frac{T}{2})$$


$$q_2(t + \frac{T}{2}) = q_1(t) + q_2(t)$$

C_1 loses its charge to ground and C_2 .

Charge Redistribution Analysis



- At $t = t + T$

 

$$q_1(t + T) = C_1 \cdot V_1(t + T)$$
$$q_2(t + T) = C_2 \cdot V_2(t + T)$$

$$q_2(t + T) = q_2(t + \frac{T}{2})$$

Charge conservation

Transfer Function



$$q_2(t+T) = q_2(t + \frac{T}{2}) = q_1(t) + q_2(t)$$

$$C_2 \cdot V_2(t+T) = C_2 \cdot V_2(t) + C_1 \cdot V_1(t)$$

$$C_2 \cdot V_2(z) \cdot z = C_2 \cdot V_2(z) + C_1 \cdot V_1(z) \Rightarrow$$

$$C_2 \cdot V_2(z) \cdot (z-1) = C_1 \cdot V_1(z) \Rightarrow$$

$$H(z) = \frac{V_2(z)}{V_1(z)} = \frac{C_1}{C_2} \cdot \frac{1}{z-1} = \frac{C_1}{C_2} \cdot \frac{z^{-1}}{1-z^{-1}}$$

Discrete-time Integrator

Parasitic Capacitors Impact On Speed



- Both clock phases have to be investigated!
- Parasitic may influence the speed although the transfer function is not effected.
- Consider the feedback factor in each phase.

(Feedback factor, β , is the amount of output signal fed back to the input, typically voltage divider).

Parasitic Capacitors Impact On Speed




Phase 1

- The parasitic affect the load capacitance

$$\beta = \frac{C_0}{C_0 + C_{P1}}$$

$$\omega_{-3dB} = \beta \cdot \omega_u = \frac{C_0 \cdot \omega_u}{C_0 + C_{P1}}$$

$$\tau = 1 / \omega_{-3dB}$$

 

Parasitic Capacitors Impact On Speed




Phase 2

- Phase 2 is slower!

$$\beta = \frac{C_0}{C_0 + (C_{P2} + C_1)}$$
 
$$\omega_{-3dB} = \frac{C_0 \cdot \omega_u}{C_0 + (C_{P2} + C_1)}$$





Switches in SC Circuits



- Realized with NMOS transistors

 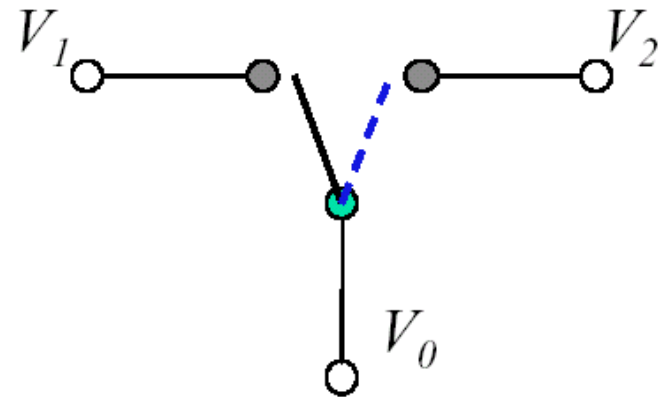
- To increase speed
- To reduce size
- RC-timing!



Switches In SC Circuits



 - Non-overlapping clock-phases
 - Guarantee that the two NMOS transistors, cannot conduct at the same time
 - Reduces charge leakage



Switches In SC Circuits




- Clock Feedthrough (CFT)
 - CFT affects the transfer function
 - Use small MOS switches
 - CFT Cancellation Techniques
 - Channel charge injection

Influence of Non-Ideal OP



 - Finite gain.
 - Assume the OP has a finite gain, A , (as in the real world)



Influence of Finite Gain OP



$$\begin{cases} q_1(t) = C_1 \cdot V_1(t) \\ q_2(t) = C_2 \cdot (V_2(t) - (-V_2(t) \cdot \frac{1}{A})) \end{cases}$$

$$\begin{cases} q_1(t + \frac{T}{2}) = -C_1 \cdot (-V_2(t + \frac{T}{2}) \cdot \frac{1}{A}) \\ q_2(t + \frac{T}{2}) = C_2 \cdot V_2(t + \frac{T}{2}) \cdot (1 + \frac{1}{A}) \end{cases}$$

$$q_2(t + \frac{T}{2}) + q_1(t + \frac{T}{2}) = q_1(t) + q_2(t)$$

$$q_2(t + T) = q_2(t + \frac{T}{2}) \Rightarrow V_2(t + \frac{T}{2}) = V_2(t)$$

$$C_2 \cdot V_2(t + T) \cdot (1 + \frac{1}{A}) = C_1 \cdot V_1(t) + C_2 \cdot V_2(t) \cdot (1 + \frac{1}{A}) - C_1 \cdot V_2(t + T) \cdot \frac{1}{A}$$

Influence of Finite Gain OP



$$C_2 \cdot V_2(z) \cdot z \cdot \left(1 + \frac{1}{A}\right) = C_1 \cdot V_1(z) + C_2 \cdot V_2(z) \cdot \left(1 + \frac{1}{A}\right) - C_1 \cdot V_2(z) \cdot z \cdot \frac{1}{A}$$

$$V_2(z) \cdot \left(C_2 \cdot z \cdot \left(1 + \frac{1}{A}\right) - C_2 \cdot \left(1 + \frac{1}{A}\right) - C_1 \cdot z \cdot \frac{1}{A}\right) = C_1 \cdot V_1(z)$$

$$H(z) = \frac{V_2(z)}{V_1(z)} = \frac{C_1}{C_2} \cdot \frac{1}{z \cdot \frac{1}{1 + \frac{C_1/C_2}{1+A}}} \cdot \frac{1}{1 + \left(1 + \frac{C_1}{C_2}\right) \cdot \frac{1}{A}}$$

The pole is moved


The gain is changed

- Lossy Integrator!

Influence of OP Offset Voltage



 - Input offset voltage.
 - Matching errors can be modeled as a voltage source, V_{off} , at the input of the OP.



Influence of OP Offset Voltage



$$\begin{cases} q_1(t) = C_1 \cdot V_1(t) \\ q_2(t) = C_2 \cdot (V_2(t) - V_{off}) \end{cases}$$

$$\begin{cases} q_1(t + \frac{T}{2}) = -C_1 \cdot V_{off} \\ q_2(t + \frac{T}{2}) = C_2 \cdot (V_2(t + \frac{T}{2}) - V_{off}) \end{cases}$$

$$q_2(t + \frac{T}{2}) + q_1(t + \frac{T}{2}) = q_1(t) + q_2(t)$$

$$q_2(t + T) = q_2(t + \frac{T}{2}) \Rightarrow V_2(t + \frac{T}{2}) = V_2(t)$$

$$C_2 \cdot (V_2(t + T) - V_{off}) = C_1 \cdot V_1(t) + C_2 \cdot (V_2(t) - V_{off}) + C_1 \cdot V_{off}$$

$$C_2 \cdot V_2(t + T) = C_1 \cdot V_1(t) + C_2 \cdot V_2(t) + C_1 \cdot V_{off}$$

Influence of OP Offset Voltage



$$C_2 \cdot V_2(z) \cdot z = C_1 \cdot V_1(z) + C_2 \cdot V_2(z) + C_1 \cdot V_{off}$$

$$V_2(z) = \frac{C_1}{C_2} \cdot \frac{1}{z-1} \cdot V_1(z) + \frac{C_1}{C_2} \cdot \frac{1}{z-1} \cdot V_{off}$$

Offset voltage is accumulated

- We need an SC circuit with offset compensation technique. That circuit must have a so called auto-zeroing phase.