

Spring 2002



EEE598D: Analog Filter & Signal Processing Circuits

Instructor:

Dr. Hongjiang Song

Department of Electrical Engineering

Arizona State University

Thursday February 14, 2002





Today: Basic SC Circuit Building Blocks

- SC S/H Circuits
- SC Delay Circuits
- SC Gain Stage Circuits
- SC Integrator Circuits

Sample-and-Hold Circuits

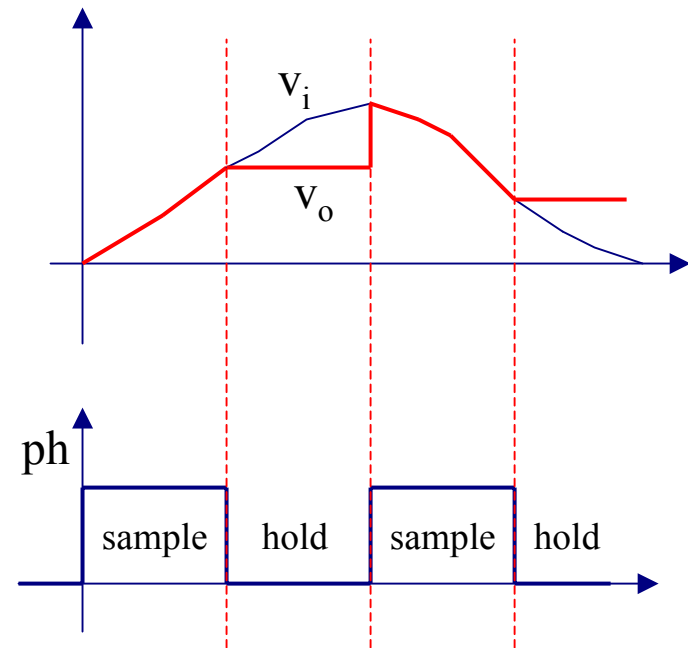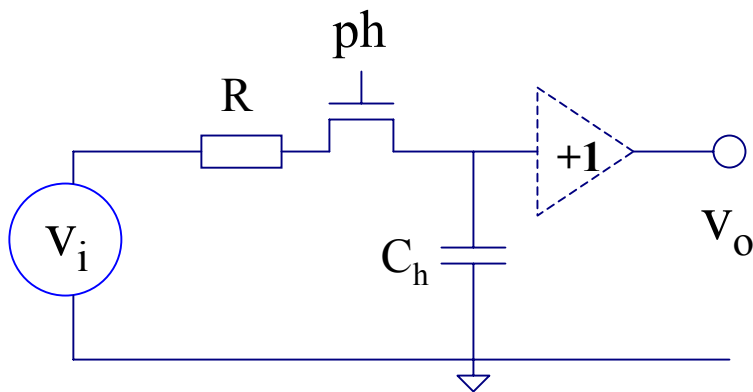- S/H circuits are used to avoid continuous signal feed through which causes frequency response distortion.





Sample-and-Hold Circuits



- Practical S/H Circuits

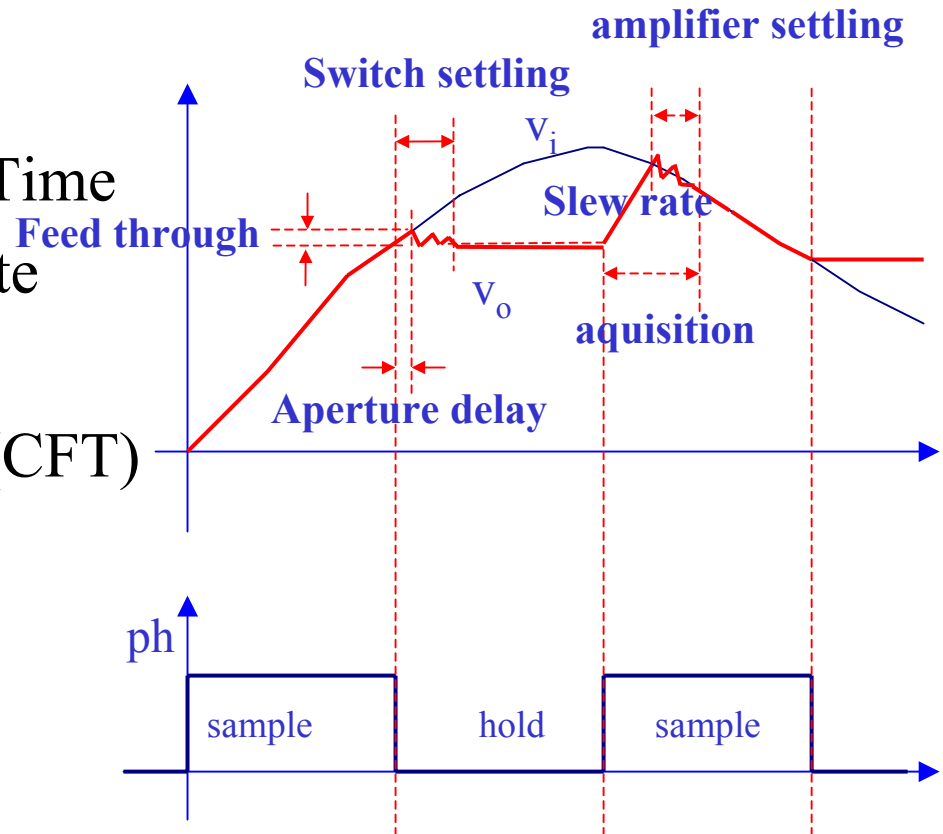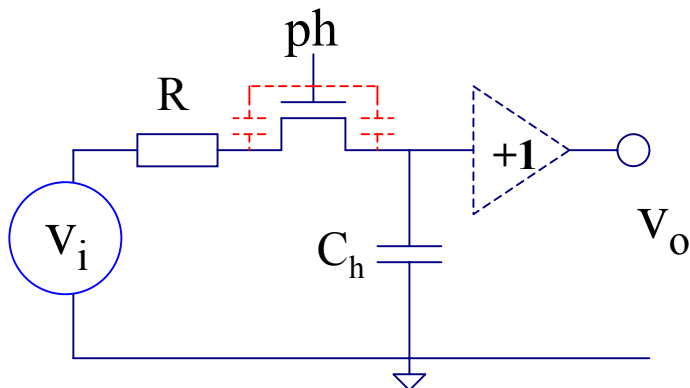
- Acquisition Time
- Slew Rate
- Aperture uncertainty Time
- Hold-mode Droop Rate
- Offset
- Clock Feed Through (CFT)



Sample-and-Hold Circuits




- CFT minimization technique

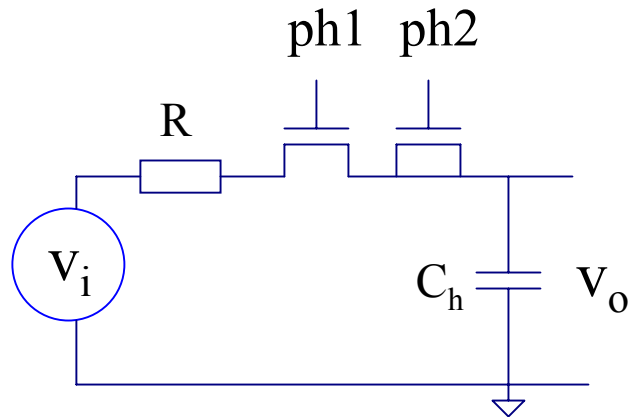

(a)

Dummy switch

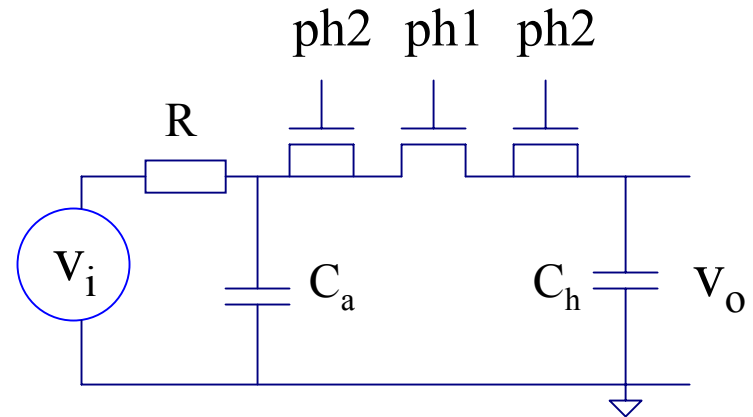


(b)

Balanced dummy switch

S/H Amplifier Structures




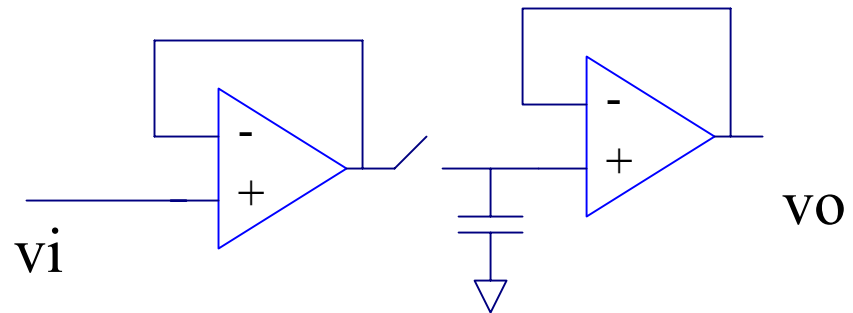- Buffered S/H
 - Better drive capability
 - Better Isolation
 - Sensitive to offset




Improved S/H Circuit

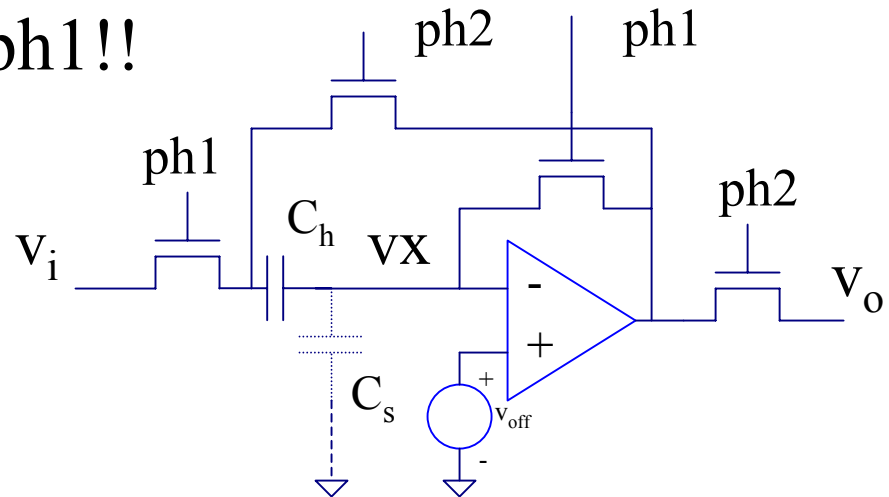- Offset minimization
- $1/f$ noise minimization
- PSSR improvement
- V_o unavailable at ph1!!



CDS S/H Circuit

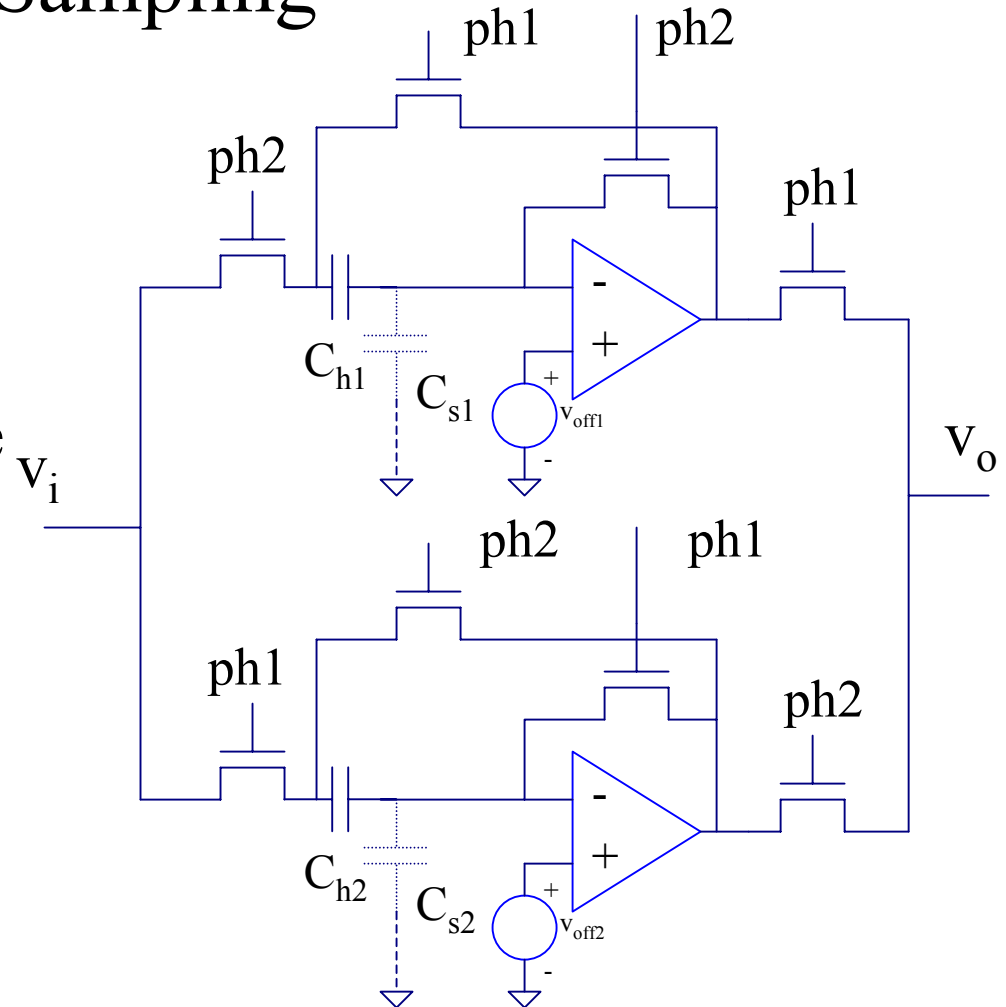
- Correlated Double Sampling
- CDS Minimizes:
 - Offset
 - 1/f Noise
 - Power supply noise



Offset & Parasitic Free S/H Circuit



- Alternative Approach

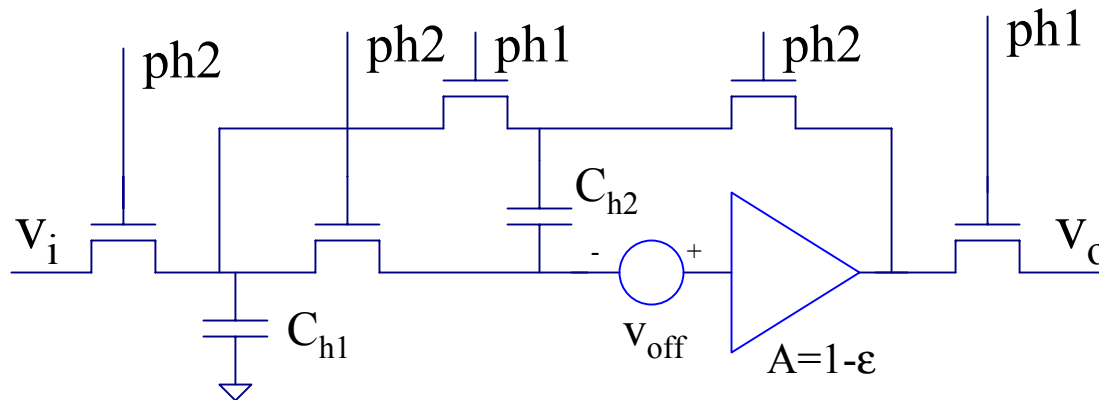


$$v_o = (1 - \epsilon^2)v_i + \epsilon(1 - \epsilon)v_{off}$$


Fully Differential S/H Circuit



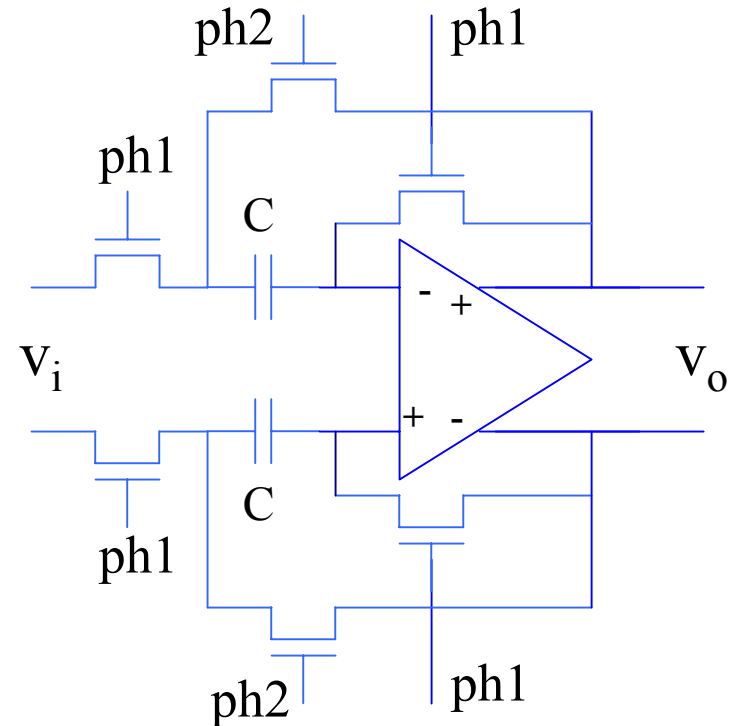- Cancellation of
 - Charge injection
 - Power supply noise
 - Common Mode Signal




SC Delay Stage

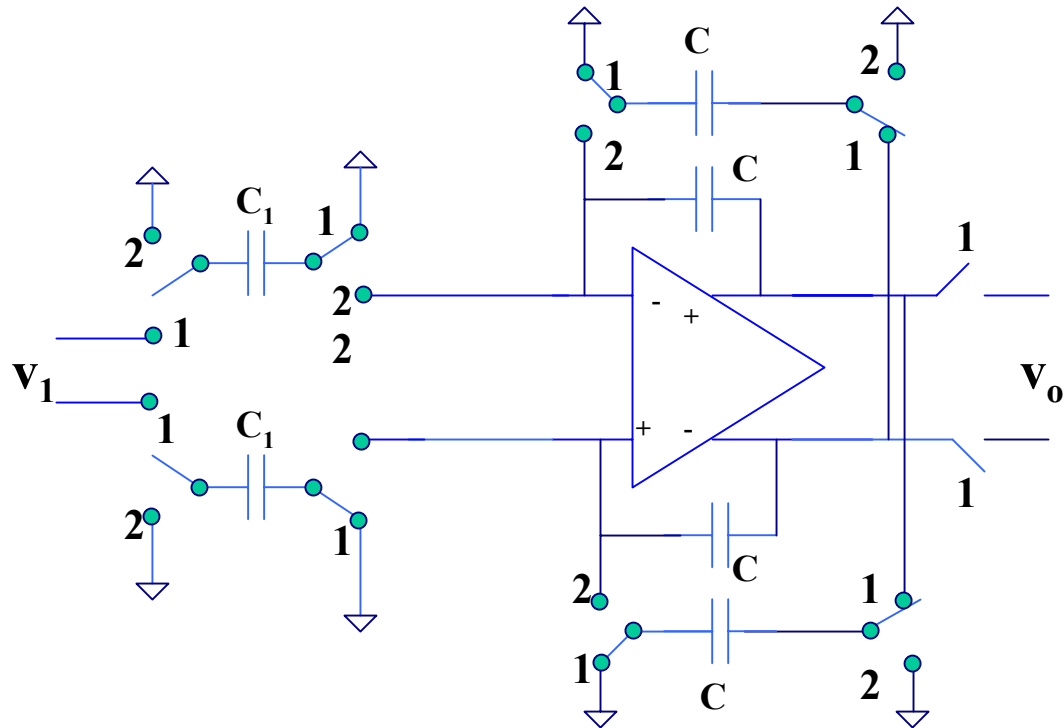

1 = ph1
2 = ph2

$$\frac{V_o(z)}{V_i(z)} = \frac{C_1}{C} z^{-1}$$


Delay Stage with Weighted Addition

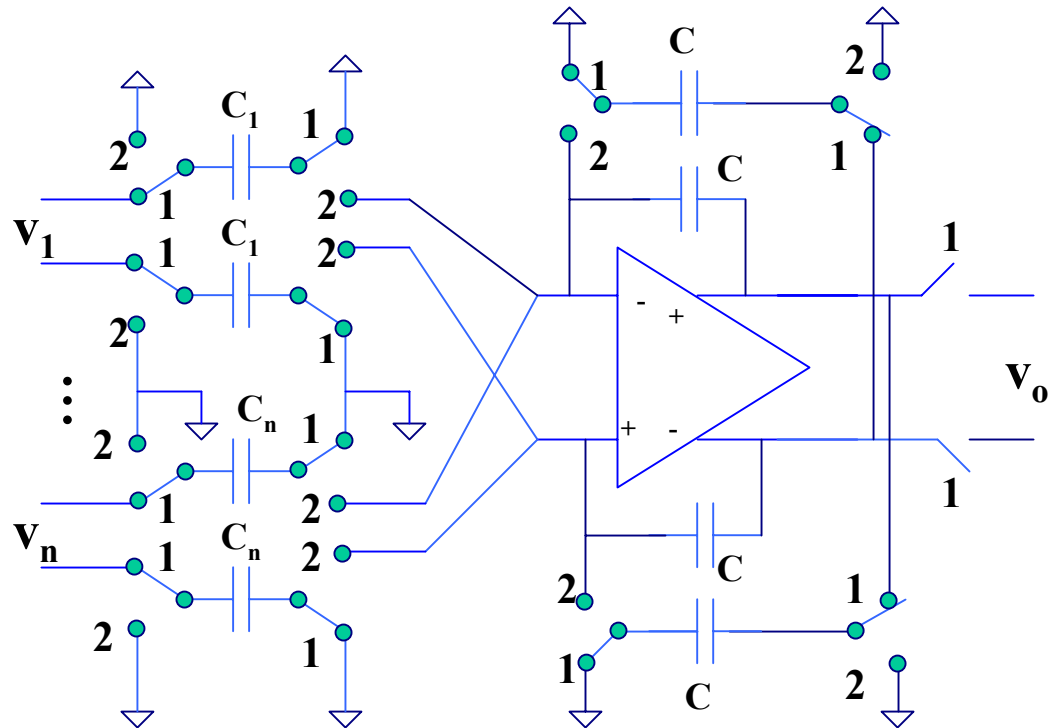


1 = ph1
2 = ph2

$$v_o(z) = \frac{z^{-1}}{C} \sum_{k=1}^n C_k v_k(z)$$

Basic SC Amplifier Structures

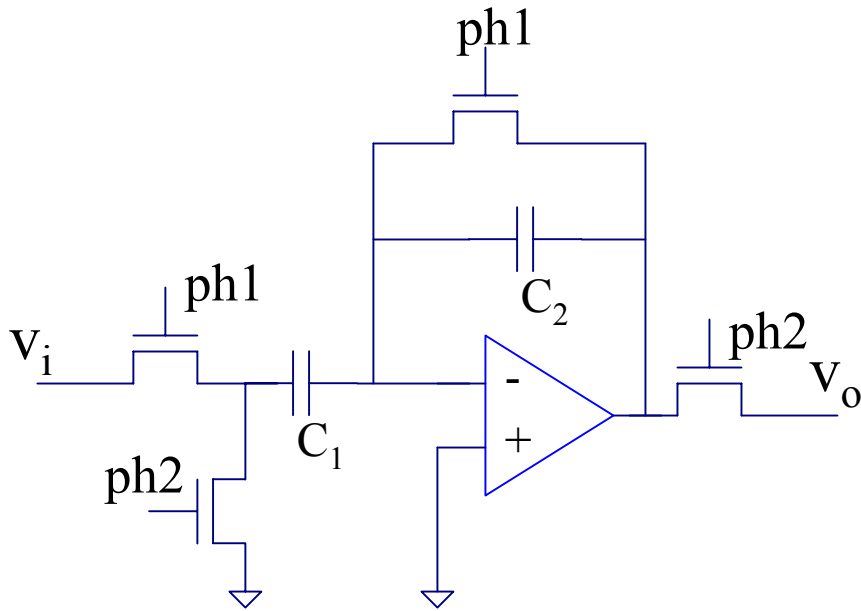


$$V_o = \frac{C_1}{C_2} V_i$$

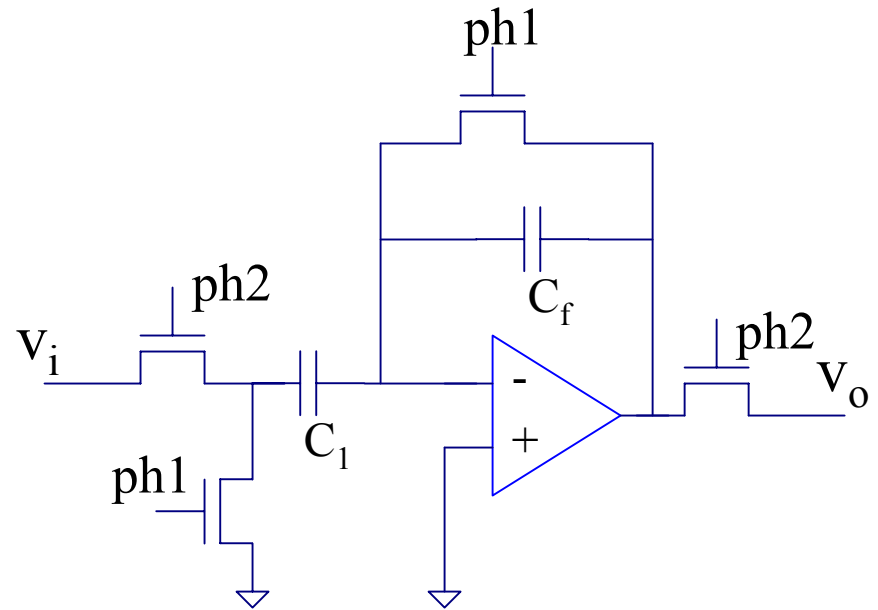


$$V_o = -\frac{C_1}{C_2} V_i$$

CFT Reduced Technique

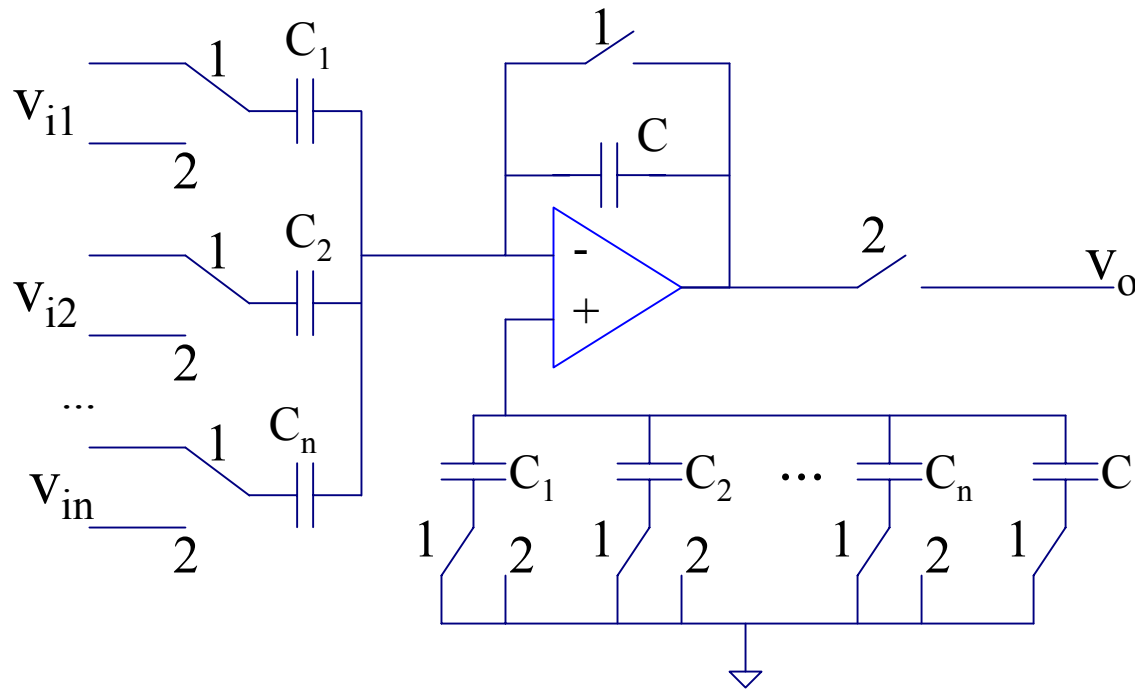

$$V_o(z) = \frac{z^{-1}}{C} \sum_{k=1}^n C_k V_k(z)$$


SC Integrator Structure

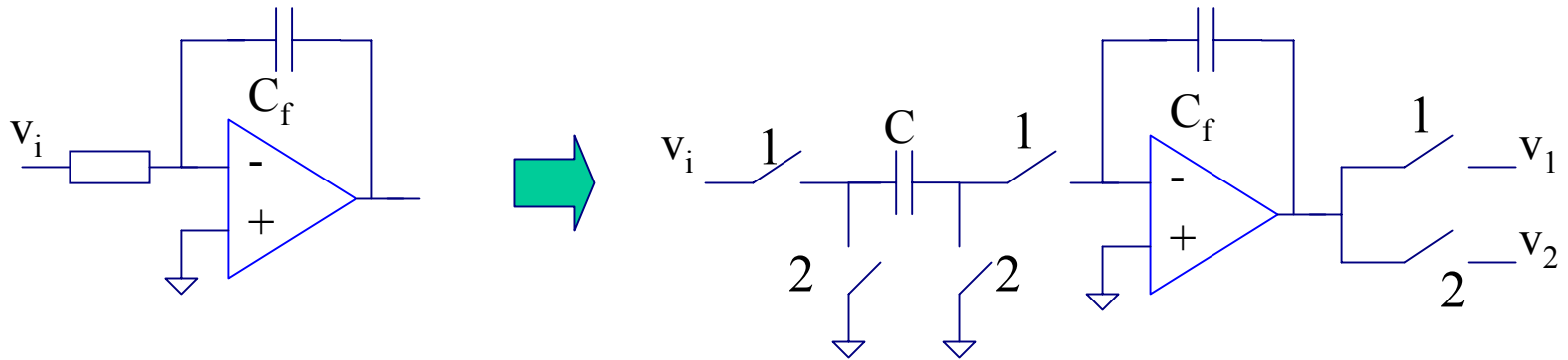

$$\frac{V_1(z)}{V_i(z)} = -\frac{C_1}{C_f} \frac{1}{1-z^{-1}}$$

$$\frac{V_2(z)}{V_i(z)} = -\frac{C_1}{C_f} \frac{z^{-1/2}}{1-z^{-1}}$$

Lossy (Damped) SC Integrator Structure

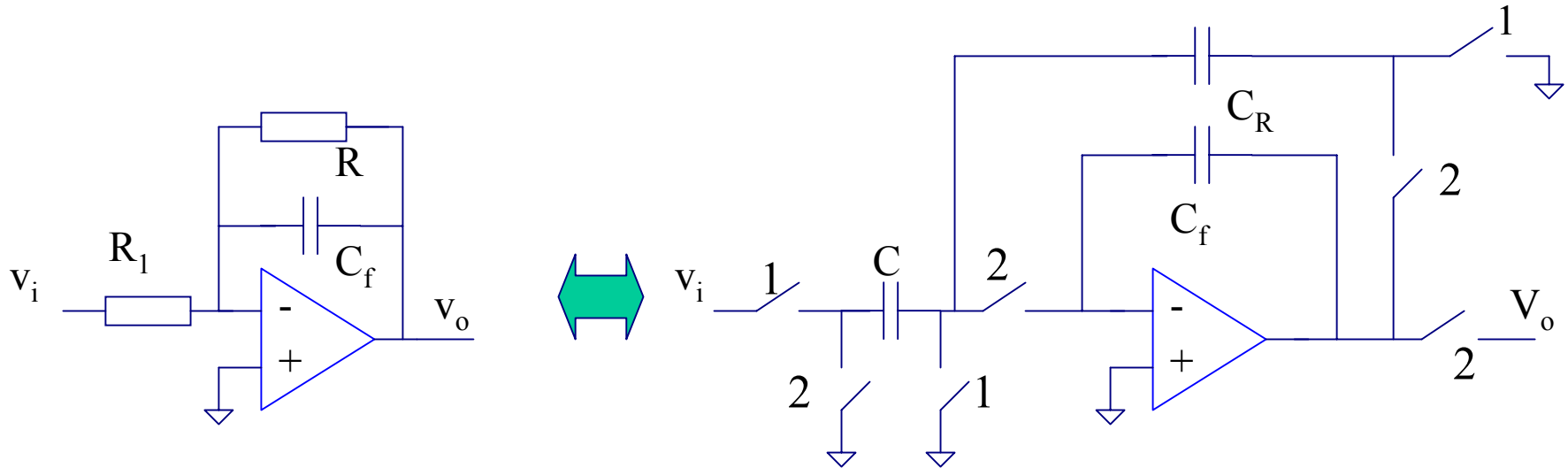


$$\frac{V_o(z)}{V_i(z)} = \frac{C_1}{(C_f + C_R)} \frac{z^{-1/2}}{\left(1 - z^{-1} \frac{C_f}{C_R + C_f}\right)}$$

Lossy (Damped) SC Integrator Structure



- Alternative (Positive Damped)

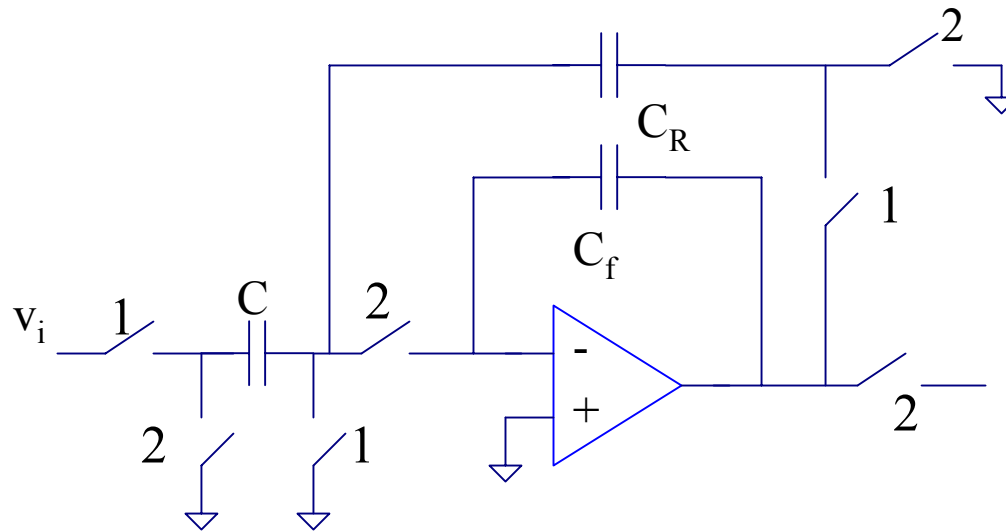


$$\frac{V_o(z)}{V_i(z)} = \frac{C_1}{C_f} \frac{z^{-1/2}}{(1 - z^{-1} \frac{C_R}{C_f})}$$

Multiple Inputs SC Integrator Structure




- Ideal Case

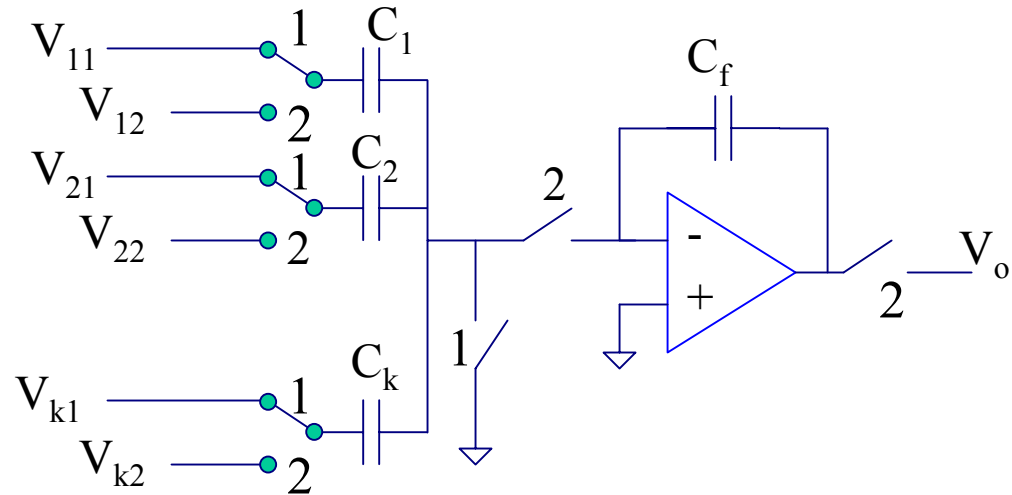


$$\frac{V_o(z)}{V_i(z)} = \sum_{i=1}^k \frac{C_i}{C_f} \frac{z^{-1/2} V_{i1}(z) - V_{i2}(z)}{(1 - z^{-1})}$$

Bilinear SC Integrator Structure

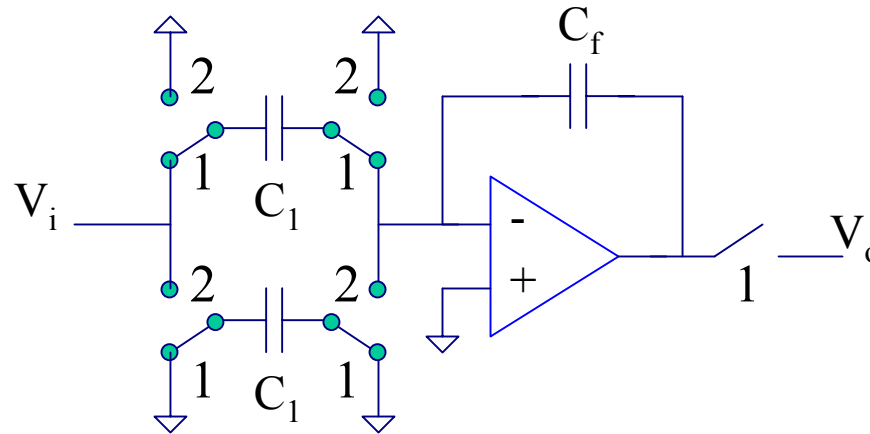

$$\frac{V_o(z)}{V_i(z)} = -\frac{C_1(1+z^{-1})}{C_f(1-z^{-1})}$$

2-Step SC Integrator Structure

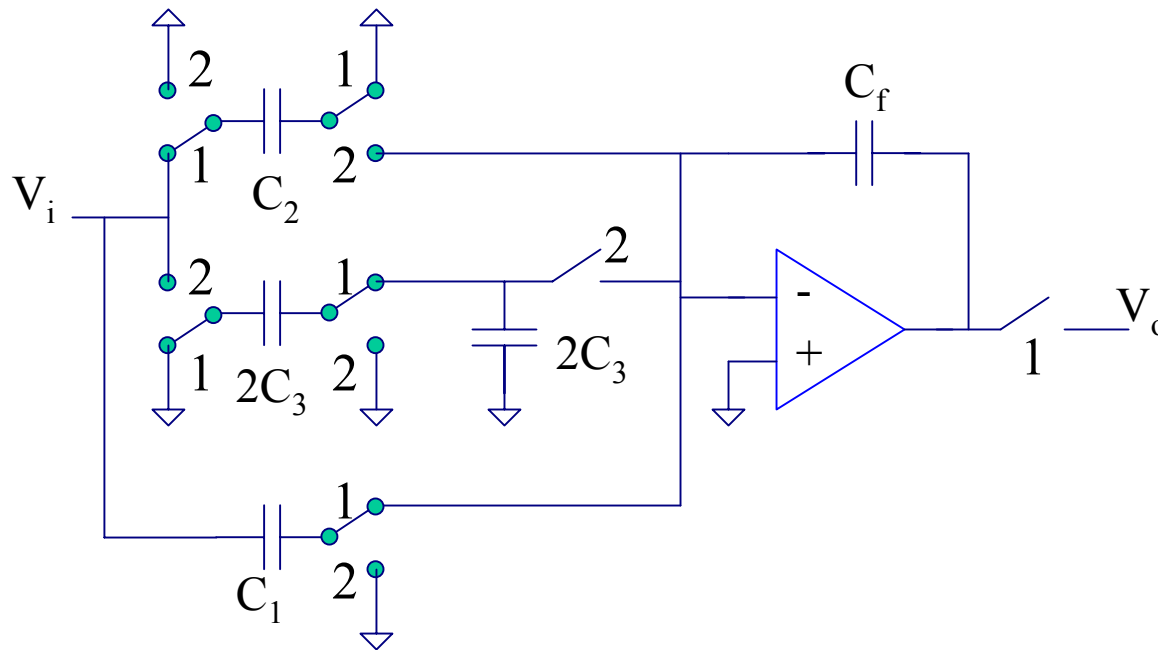

$$\frac{V_o(z)}{V_i(z)} = \left(\frac{C_1}{C_f} z^{-1/2} \right) \frac{1 + \frac{C_2}{C_1} z^{-1/2} + \frac{C_3}{C_1} z^{-1}}{(1 - z^{-1})}$$

2-Step SC Integrator Structure



$$\frac{V_o(z)}{V_i(z)} = \left(\frac{C_1}{C_f} z^{-1/2}\right) \frac{1 + \frac{C_2}{C_1} z^{-1/2} + \frac{C_3}{C_1} z^{-1}}{(1 - z^{-1})}$$

$C_2 / C_1 = 4 \quad C_3 / C_1 = 1 \Rightarrow$ *Simpson Integrator*

$C_2 / C_1 = 8/5 \quad C_3 / C_1 = 1 \Rightarrow$ *Gauss Integrator*

$C_1 / C_f = C_3 / C_f = 0.3584 \quad C_2 / C_f = 1.2832 \Rightarrow$ *Tick's Integrator*

$C_2 / C_1 = 2 \quad C_3 / C_1 = 1 \Rightarrow$ *Bilinear Integrator*


...

Full Differential SC Integrator



- Charge Injection
- Power Supply Rejection
- High Speed
- Common Mode Rejection

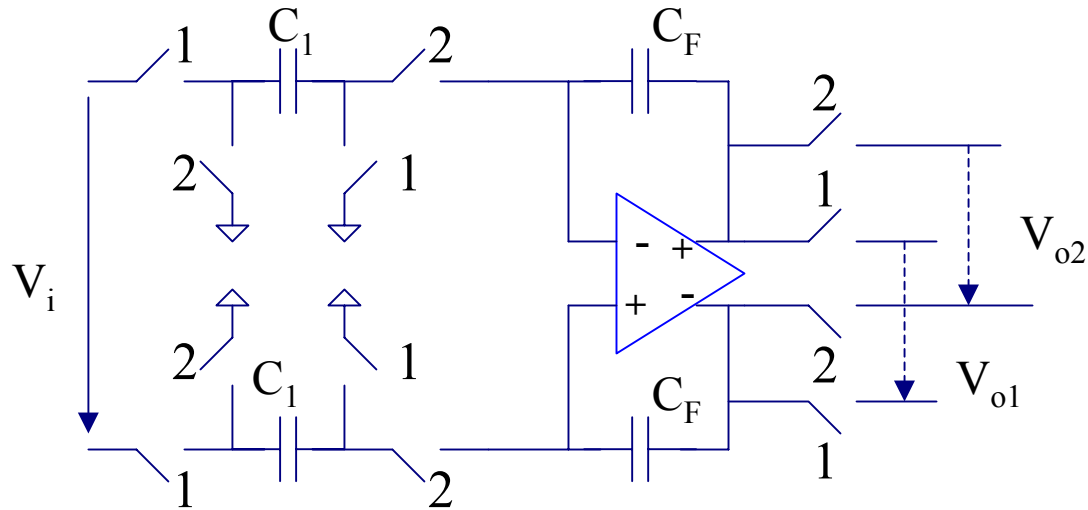
Full Differential SC Integrator Structure(I)



$$\frac{V_{o1}(z)}{V_i(z)} = \frac{C_1}{C_F} \frac{z^{-1/2}}{1 - z^{-1}}$$

$$\frac{V_{o2}(z)}{V_i(z)} = \frac{C_1}{C_F} \frac{1}{1 - z^{-1}}$$

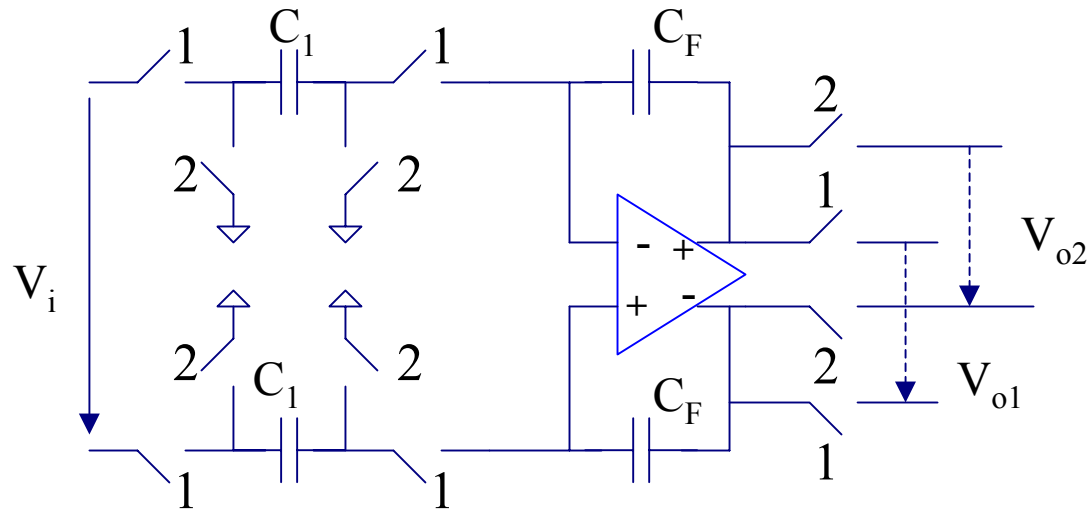
Full Differential SC Integrator Structure (II)



$$\frac{V_{o1}(z)}{V_i(z)} = \frac{C_1}{C_F} \frac{1}{1 - z^{-1}}$$


$$\frac{V_{o2}(z)}{V_i(z)} = \frac{C_1}{C_F} \frac{z^{-1/2}}{1 - z^{-1}}$$

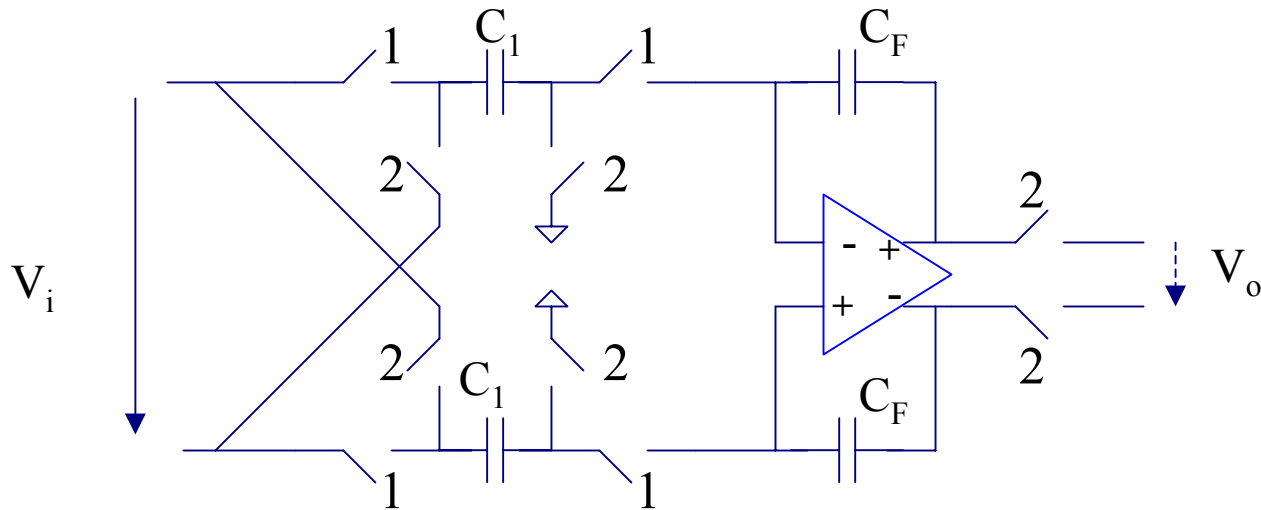Full Differential SC Integrator Structure (III)



$$\frac{V_o(z)}{V_i(z)} = \frac{C_1}{C_F} \frac{1+z^{-1}}{1-z^{-1}}$$

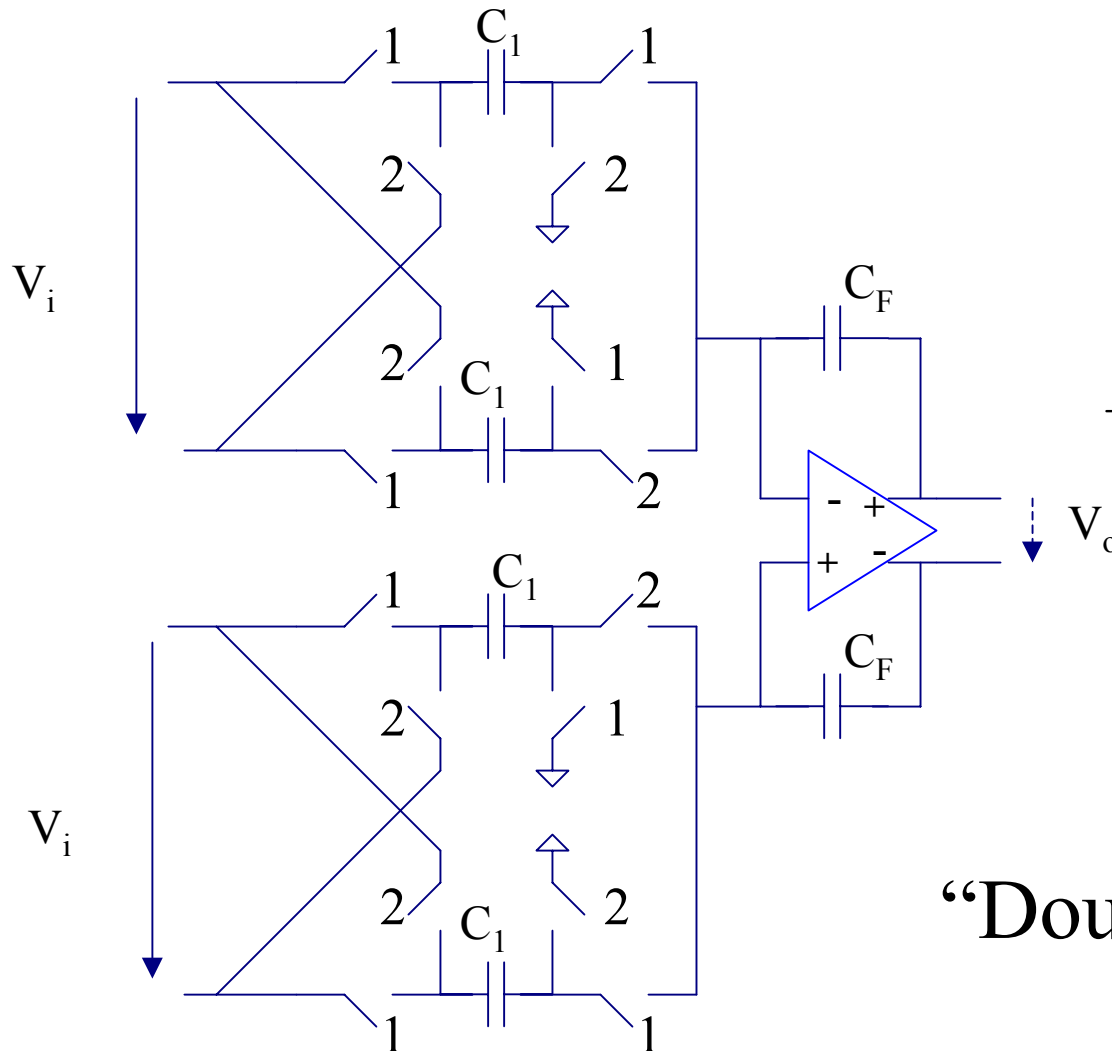
Full Differential SC Integrator Structure (IV)



$$\frac{V_o(z)}{V_i(z)} = \frac{C_1}{C_F} \frac{1+z^{-1/2}}{1-z^{-1/2}}$$

“Double-Pump”

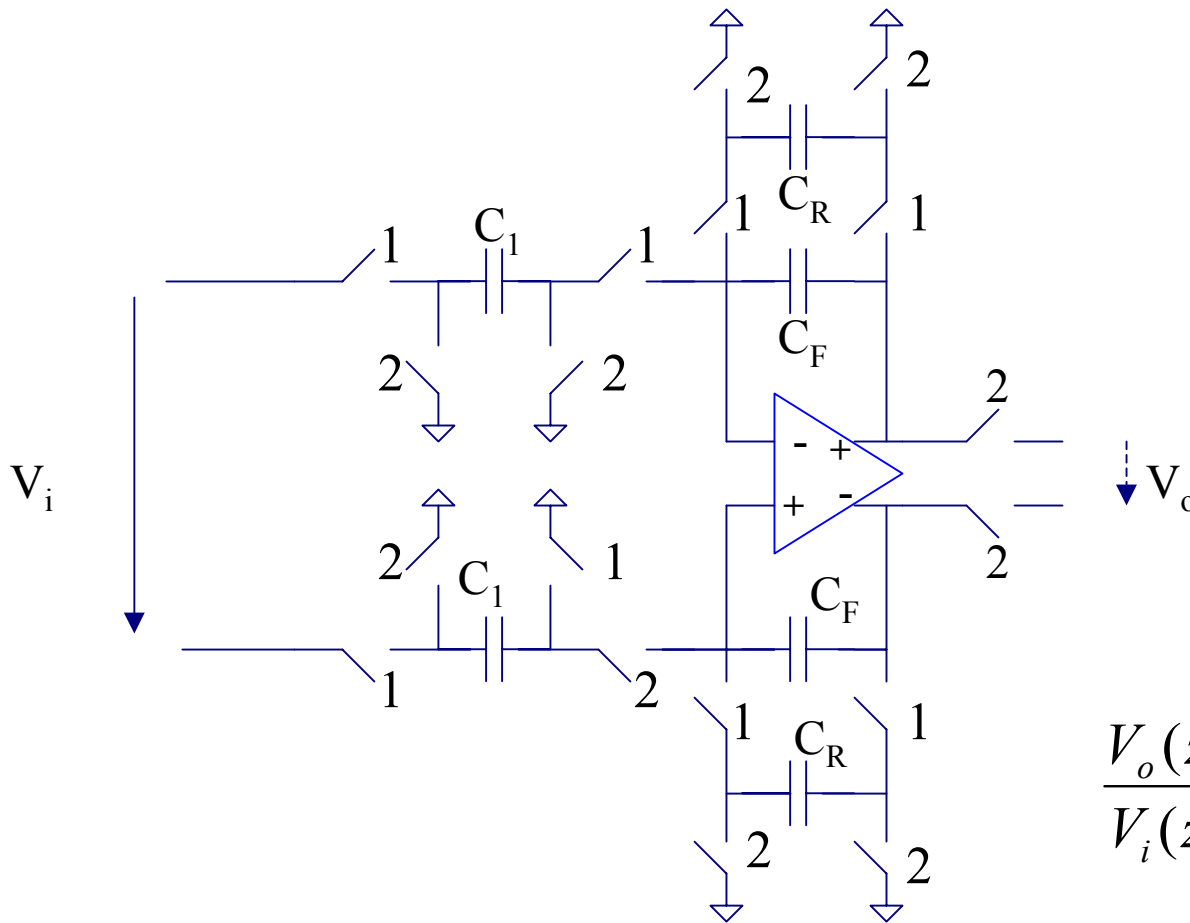Full Differential SC Integrator Structure (V)



$$\frac{V_o(z)}{V_i(z)} = \frac{C_1 z^{-1/2}}{C_F(1 - z^{-1}) + C_R}$$

