


# Operational Transconductance – C (OTA-C) and Current-Mode Filter Structures

- OTA-C Filter Topologies
- What is current-mode and how is related to Transconductance mode ?
- Current-Mode Filters
- How to use a conventional OTA as a filter by adding capacitances at the internal nodes.




Edgar Sánchez-Sinencio


## Controlled Impedance Elements

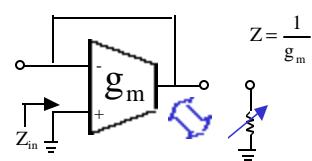

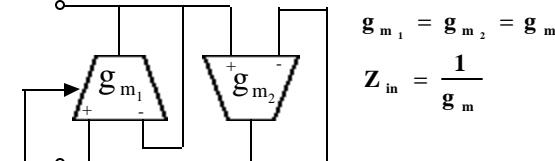
(a) Single-ended voltage variable resistor (VVR).





(b) Floating VVR


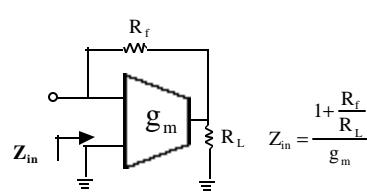


(c) Scaled VVR

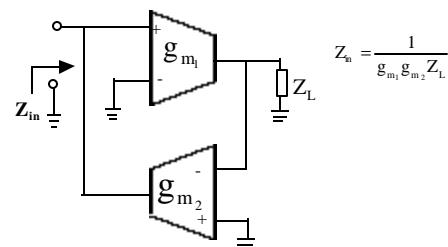


(d) Voltage variable impedance inverter

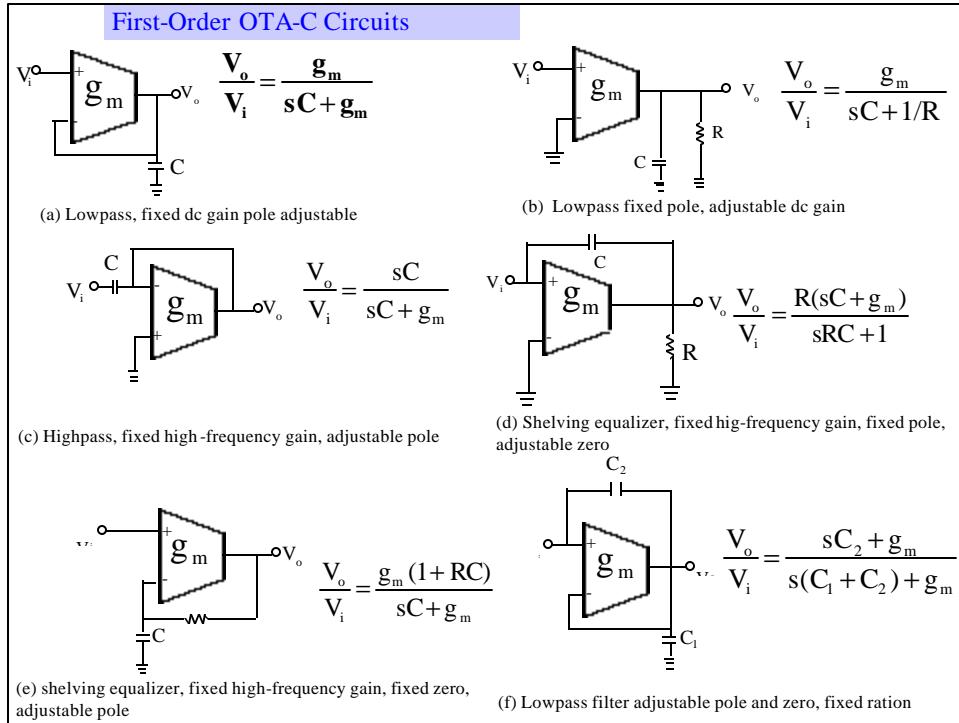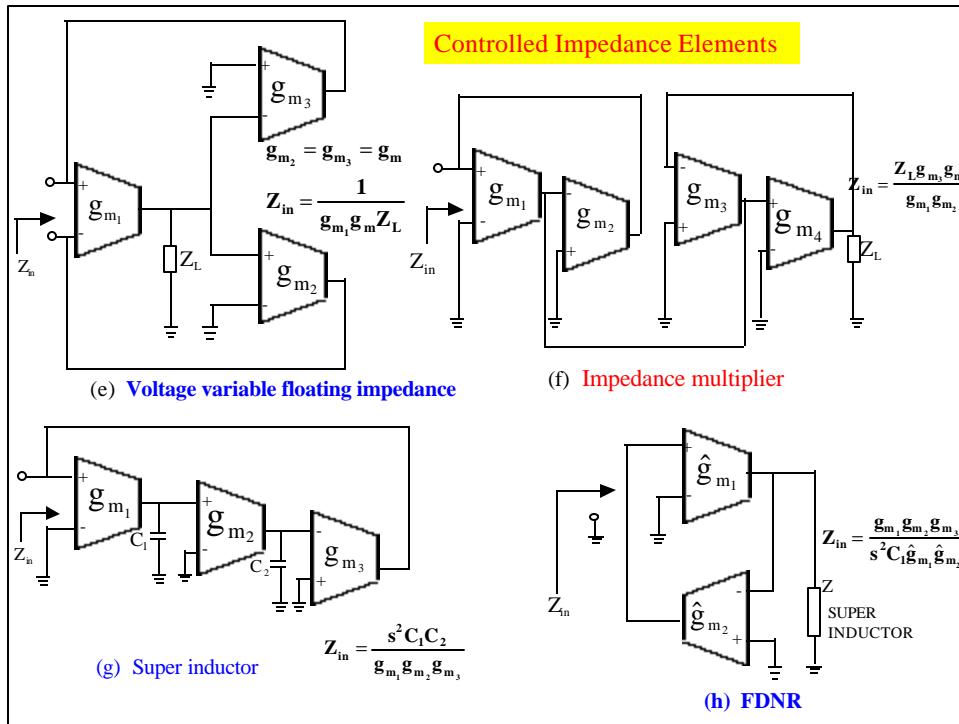

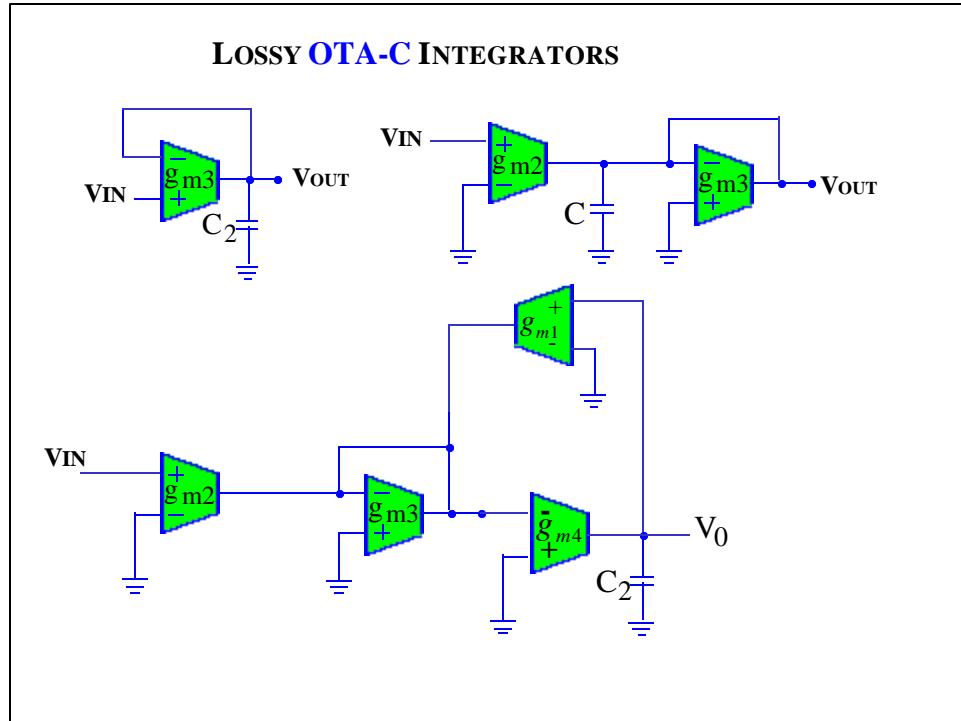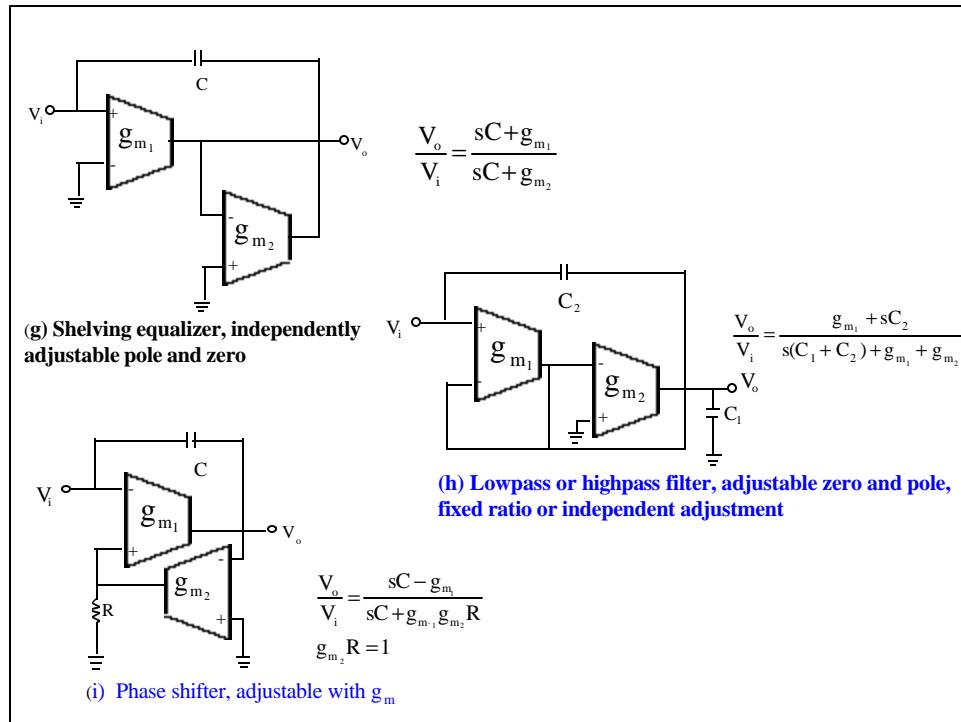

### TWO-INTEGRATOR LOOP OTA-C

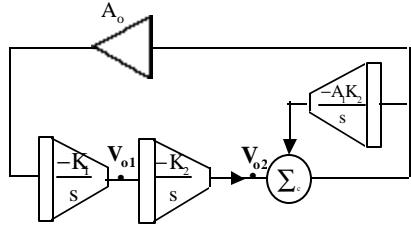

(a) Cascade of one lossless and one lossy integrators


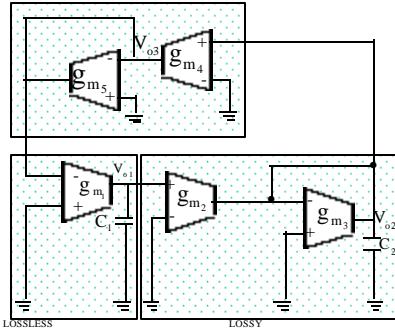


Fig. 7. Circuit implementation of Fig. 6(a)

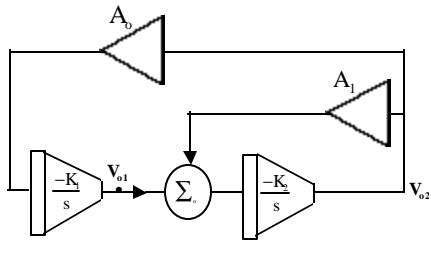

(b) Cascade of two lossless integrators


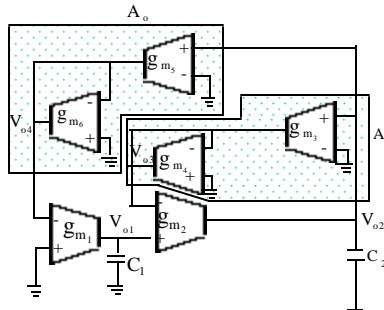
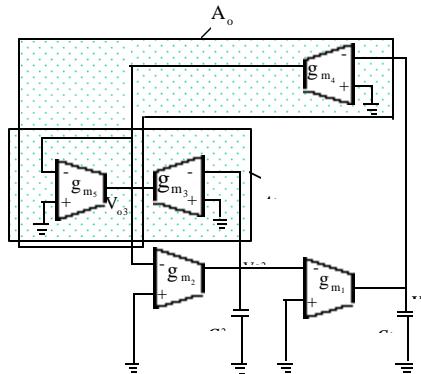




Fig. 8. Circuit implementation of Fig. 6(b)
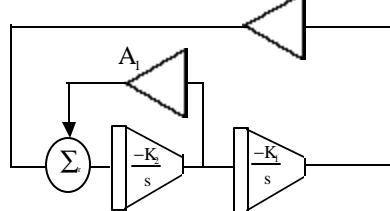
### Two integrator loops with a single feedback summer




### OTA-C Two Integrator Loop Filters

**Two OTAs Filter**

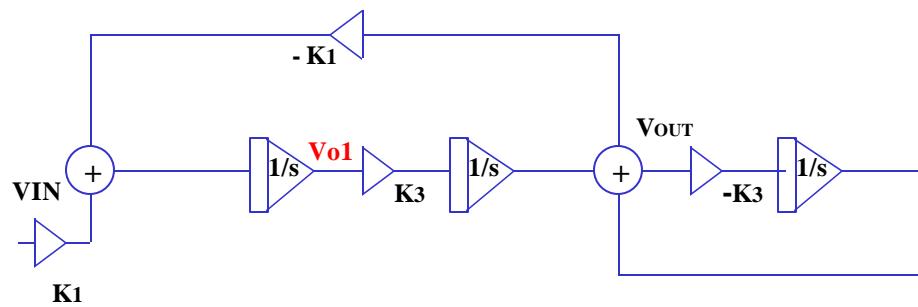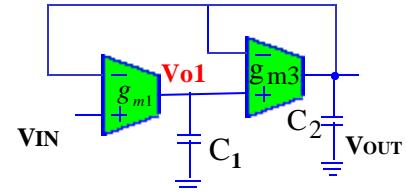


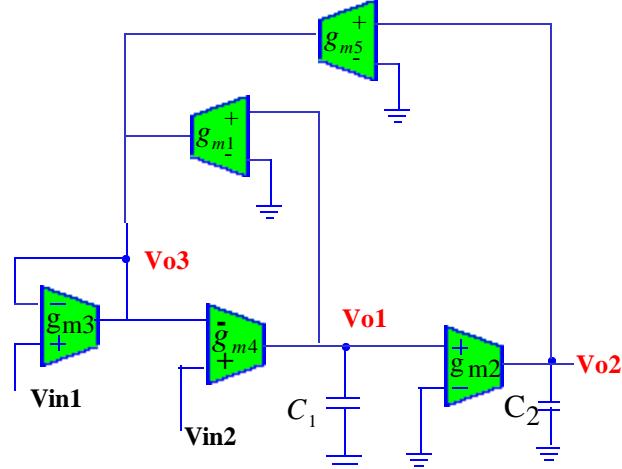**KHN Two-integrator Loop with OTA-C Implementation.**


Where  
 $K_5 = g_{m5}/g_{m3}$   
 $K_1 = g_{m1}/g_{m3}$   
 $K_4 = g_{m4}/C_1$   
 $K_2 = g_{m2}/C_2$


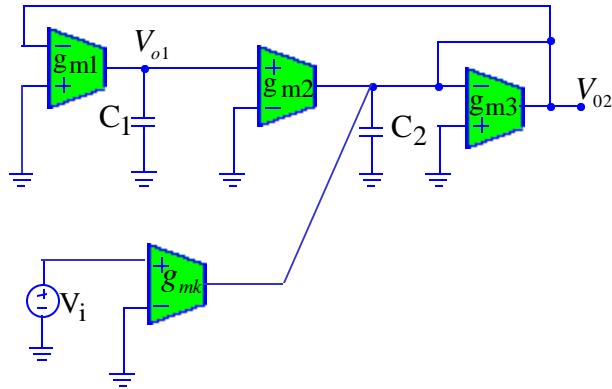
## OTA-C Biquadratic Filter based on a Two-integrator Loop



## INTERNAL VOLTAGE SCALING

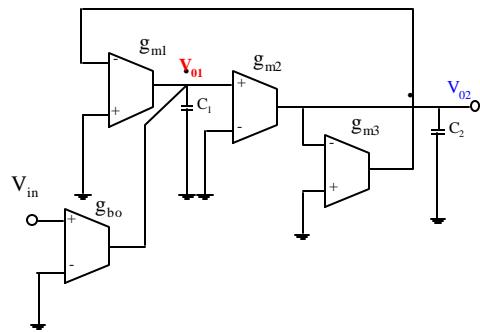


Assume the voltage  $V_{o1}$  needs to be scaled by a factor “ $a$ ” without changing the other node voltages:

1. The impedance at the node under consideration must be increased by “ $a$ ”. In this case  $C_1$  becomes  $C_1/a$ .
2. Multiply all the transconductances leaving that node by the factor “ $a$ ”. In this case  $g_{m2}$  becomes  $a g_{m2}$ ,

## Real example – Low Pass/Low Frequency Filter

FILTER TOPOLOGY    with  $g_m = 11.8\text{nA/V}$

DESIGN EQNS

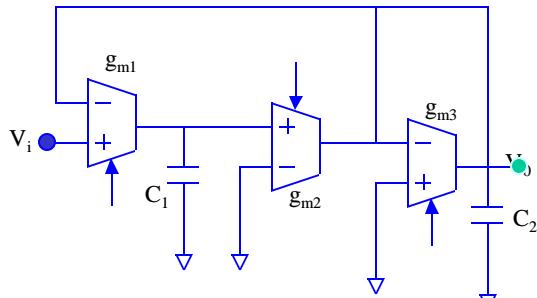

- Bulk driven OTAs used due to higher input range
- $V_i$  can be applied to the input of OTA 1 because the input parasitic capacitance does not affect the performance.

$$\left( \frac{V_o}{V_i} \right) = \frac{w_0^2}{s^2 + \frac{w_0}{Q}s + w_0^2}$$

$$w_0 = \sqrt{\frac{g_{m1}g_{m2}}{C_1C_2}} = \frac{g_m}{C}$$

$$Q = \frac{1}{g_{m3}} \sqrt{g_{m1}g_{m2} \frac{C_2}{C_1}}$$


$$Q = \frac{g_m}{g_{m3}}$$

$$g_{m1} = g_{m2} = g_m$$

$$C_1 = C_2 = C$$


Reference.- A. Veeravalli, E. Sanchez-Sinencio and J. Silva-Martinez, "Transconductance Amplifiers with Very Small Transconductance: A Comparative Design Approach" to appear in J. of Solid-State Circuits

Bulk-Driven OTA used in the filter

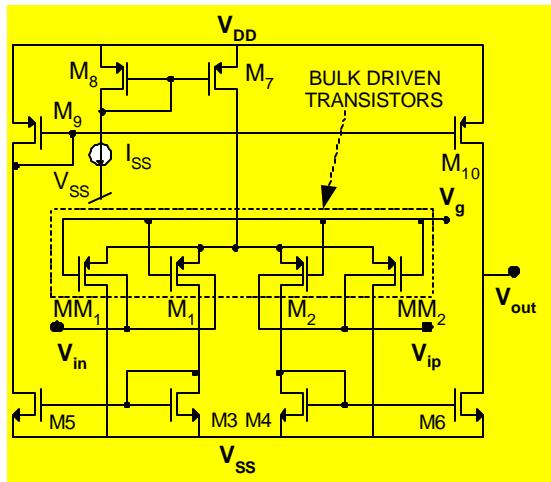


$$SNR = 20 \log \left( \frac{V_{in\_rms}}{V_{n\_rms}} \right) = 20 \log \left[ \left( \frac{\frac{G_m}{K_p} \sqrt{32HD_3}}{\sqrt{\frac{2K_F}{C_{ox}^2} \ln \left( \frac{f_2}{f_1} \right)}} \right) \left( \frac{L^{1.5}W^{0.5}}{\alpha} \right) \right]$$

## MEASURED RESULTS

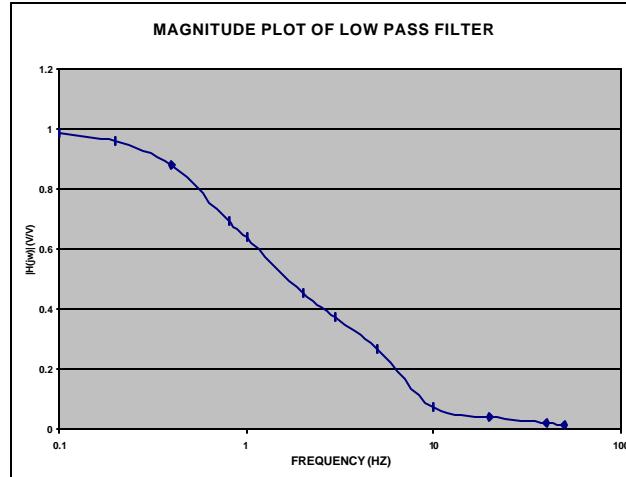

- $f_{3dB} \sim 0.7$  Hz with  $C_L = 2.7\text{nF}$
- $gm = 2\pi C_L f_{3dB} \sim 11.8\text{nA/V}$

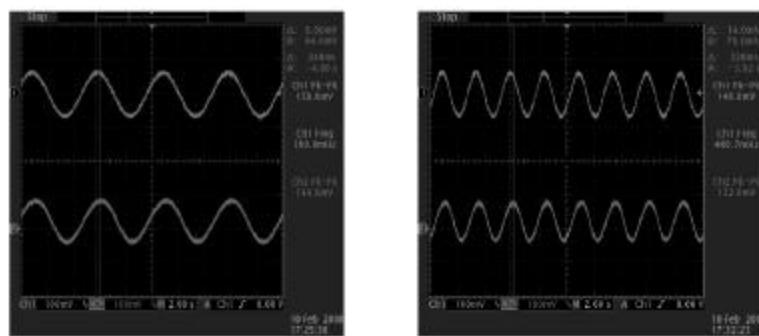
## EXPERIMENTAL RESULTS 1.2 micron technology




Input Ch1 150mVpp @ 0.2 Hz  
Output Ch2 144mVpp

Input Ch1 150mVpp @ 0.4 Hz  
Output Ch2 132mVpp

## WAVEFORMS...

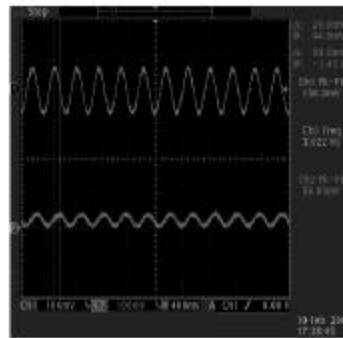

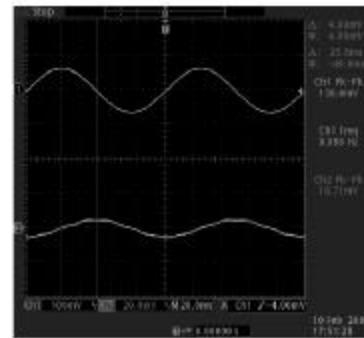Input Ch1 150mVpp @ 3 Hz  
Output Ch2 56mVpp



Input Ch1 150mVpp @ 10 Hz  
Output Ch2 11mVpp

## Summary of Experimental results

PARAMETER	VALUE
Filter order	2
-3dB Bandwidth (Hz)	0.3
$HD_3 @ V_{in}=150\text{mVpp}$ (dB)	-45
Total input noise ( $\mu\text{Vrms}$ )	15.6
SNR (dB)@ $HD_3 = -45\text{dB}$	70.5
Power consumption ( $\mu\text{W}$ )	8.18
Power supply (V)	$\pm 1.35$
Total filter area ( $\text{mm}^2$ )	0.06

- HD2 ~ -33dBm ~ 2.2 %

- **FULLY CURRENT-MODE**

**Input Signal:** Current

**Output Signal:** Current

**Basic Building Blocks are:**

Inverting Integrators



Inverting (Current Amplifiers)

**Primitive Circuit Implementations:**



Single Transistor Inverting Amplifier

Simple Current Mirror


Capacitor

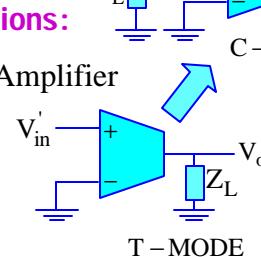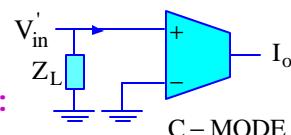

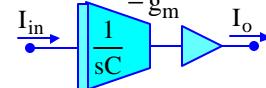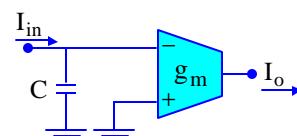
### Current-Mode Implementation using OTA's



Integrator

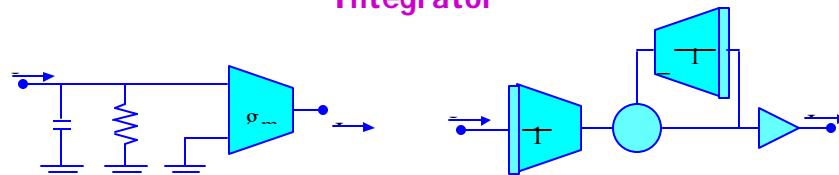


Self Loop Integrator

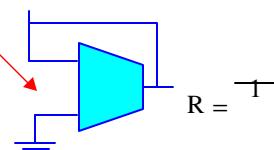


In order to fully obtain the benefits of current-mode techniques simpler circuits with reduced parasitics are desireable.


### Primitive CM Circuits

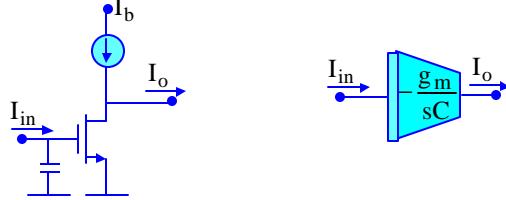

Inverting Integrator

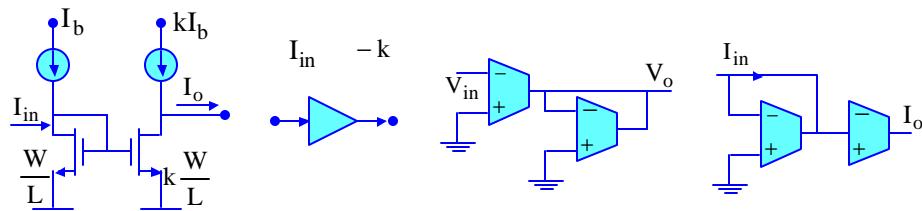


Amplifier (Multiplier by a constant)


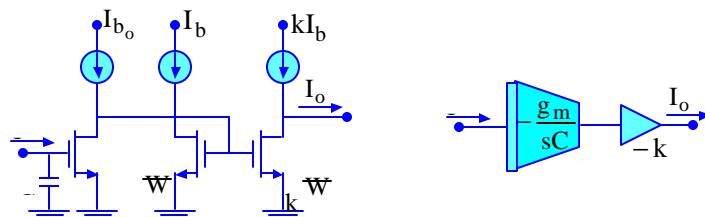


Non-Inverting Integrator

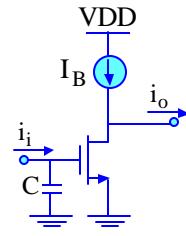3.3V Power supply  
 High frequency  
 Low area  
 Suitable for digital process  
 Good PSR  
 Poor linearity, efficiency ( $1\% \text{ THD} \Rightarrow \eta < 4\%$ )  
 Poor voltage gain



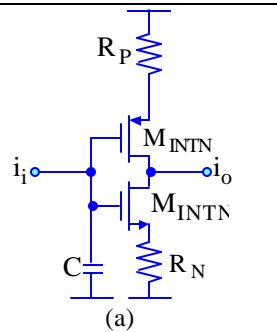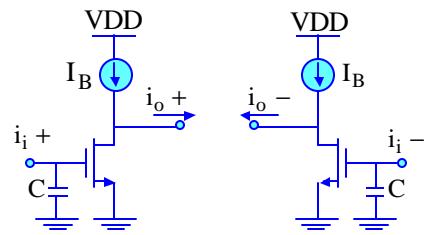Low power supply (3.3V)  
 High frequency  
 Low area  
 Suitable for digital process  
 Very good PSR  
 Good Linearity (differential)  
 Excellent efficiency ( $\approx 100\%$ )  
 Poor common mode rejection



(a) Tunable CMOS class AB integrator (b) Transistor Implementation with Mrn and Mrp operating in triode region (c) Bias implementation (diffusion or poly resistors).

Linearity sufficient

Very high efficiency ( $> 100\%$ )  $\Rightarrow$  AB, low power



Very high frequency

Small area


Low Power Supply

Linearity dep. on process variations

PSR poor

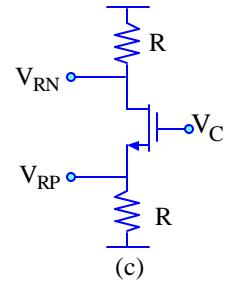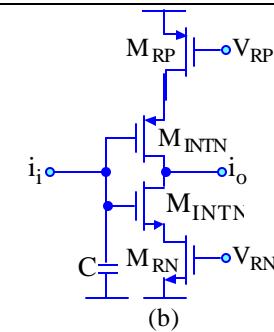

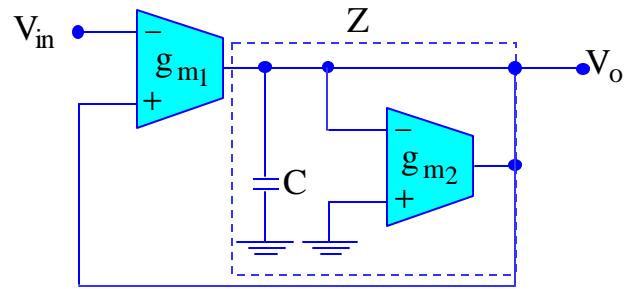
### Lossy Integrator With Positive Feedback






$$\frac{V_o}{V_{in}} = \frac{-g_{m1}Z}{1-g_{m1}Z} = -\frac{g_{m1}}{sC_2 + (g_{m2} - g_{m1})}$$


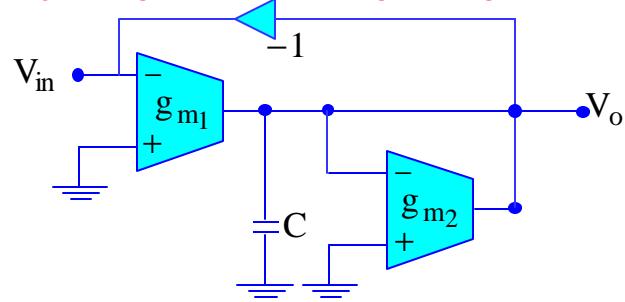
### OTA-C Lossy Integrator With Single (Negative) Input OTA's





Current-Mode Version

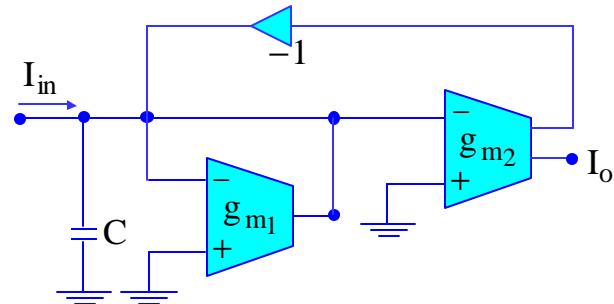

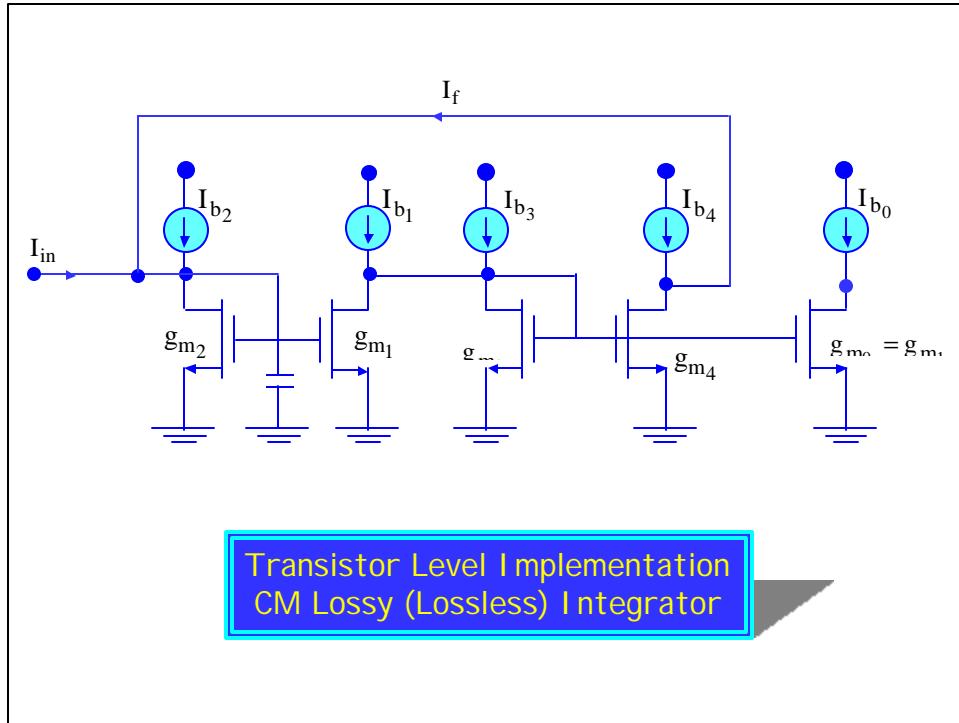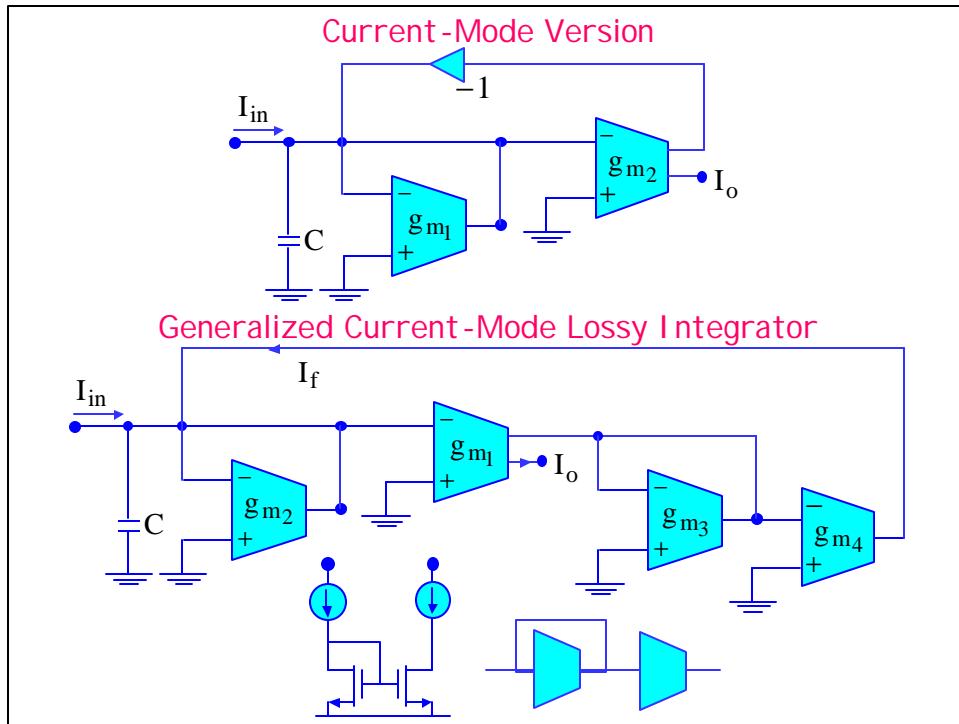

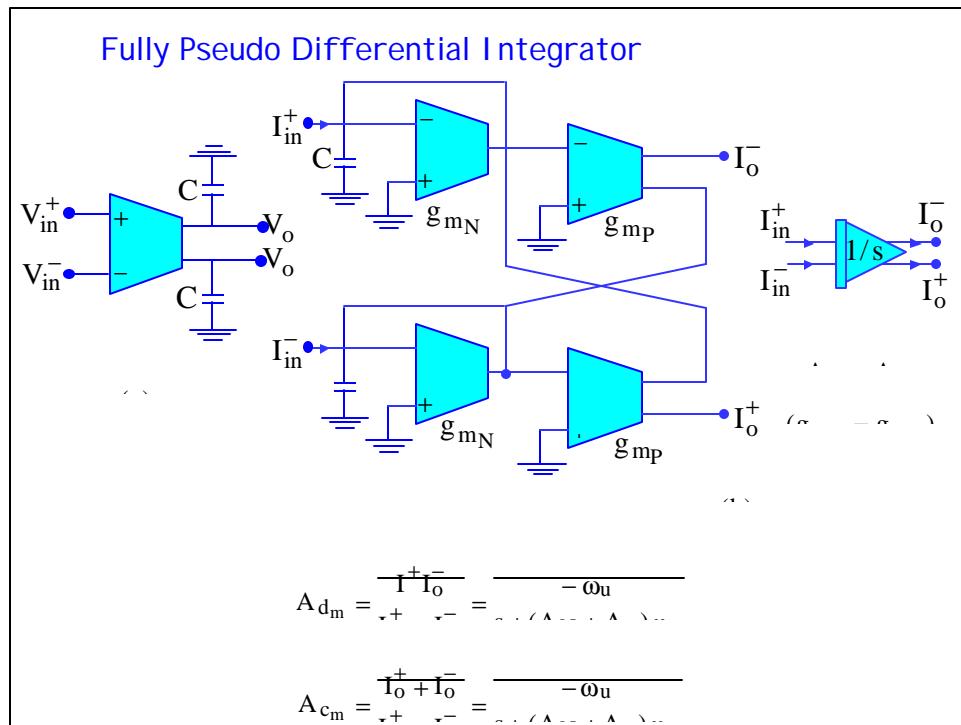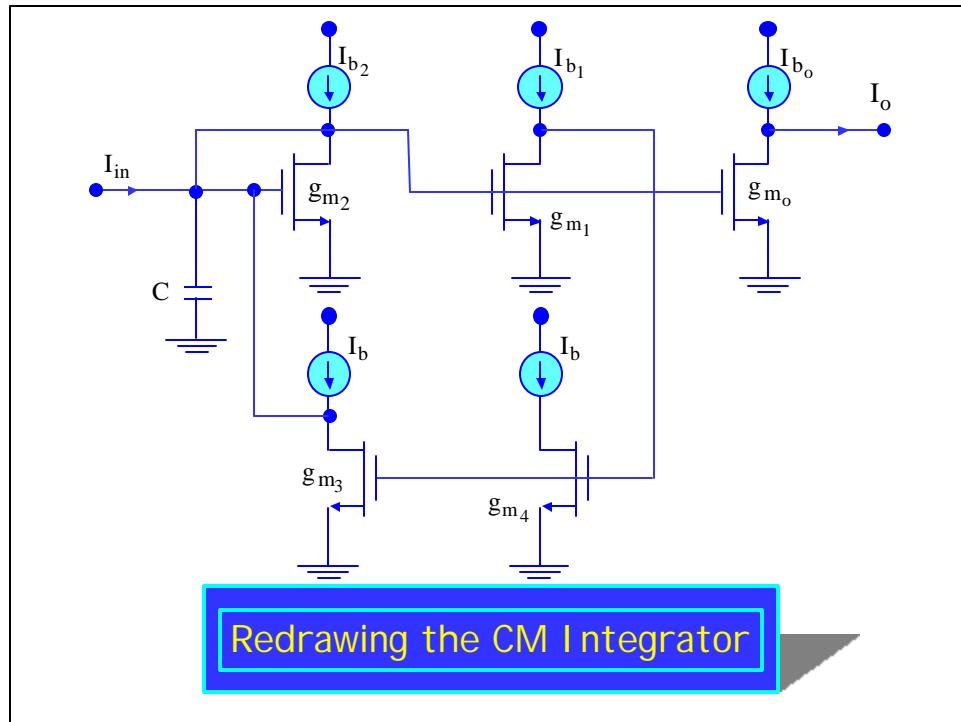

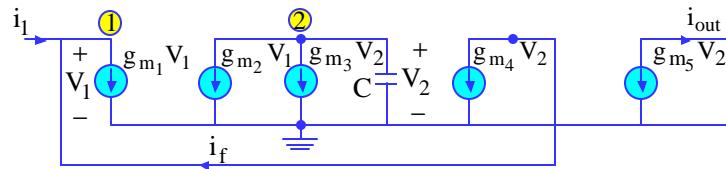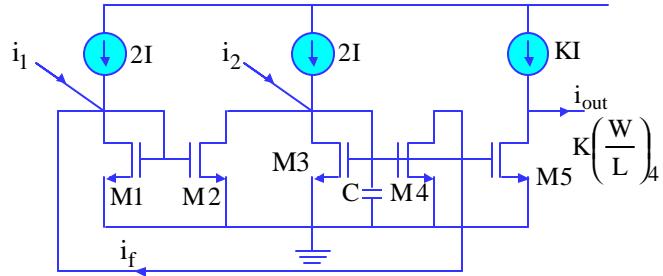**Continuous - Time Current-Mode Integrator  
Based On Current-Mirrors.**



$$i_f = \frac{i_1 \frac{g_{m_2}}{g_{m_1}} - i_2}{g_{m_1}(g_{m_3} + sC) - g_{m_2}g_{m_4}} \bullet g_{m_1}g_{m_4}$$

$$i_f = g_{m_1}g_{m_4} \frac{i_1 \frac{g_{m_2}}{g_{m_1}} - i_2}{g_{m_1}g_{m_3} - g_{m_2}g_{m_4} + g_{m_1}sC}$$

a) Lossless Integrator

$$\alpha_s = \alpha_r \quad \text{and} \quad \alpha_s = \alpha_r$$

$$i_f = \frac{\overline{g_{m_4}}}{\overline{g_{m_1}}} (i_1 - i_2)$$

$$i_{out} = K \frac{\overline{g_{m_4}}}{\overline{g_{m_1}}} (i_1 - i_2)$$

b) Lossy Integrator

$$g_{m_1}g_{m_3} > g_{m_2}g_{m_4}, \quad g_{m_1} = kg_{m_2}, \quad g_{m_3} = kg_{m_4}$$

$$i_f = \frac{k}{k^2 - 1} \frac{\frac{ki_1 - i_2}{sC}}{1 + \frac{g_{m_4}}{g_{m_4}} \frac{k^2 - 1}{k}}, \quad k > 1$$

i.e.  $k = 2$

$$i_f = \frac{2}{3} \frac{2i_1 - i_2}{1 + \frac{sC}{g_{m_4}} \frac{3}{2}}$$

If the parasitic capacitances and the output conductances are considered, then

$$i_f = \frac{-k_1(s - z_1)i_1}{(s + p_1)(s + p_2)} - \frac{k_2(s + z_2)}{(s + p_1)(s + p_2)}$$

Where

$$k_1 = g_o / C_1, \quad k_2 = g_m / C_2$$

$$p_1 = 4g_o / C_2, \quad p_2 = g_m / C_1$$

$$z_1 = \frac{g_m}{C_2} \frac{g_o}{g_o}, \quad z_2 = \frac{g_m + g_o}{C_1}$$


All transistors are equal, and  $C_1$  and  $C_2$  are the lumped nodal capacitances associated with nodes 1 and 2. Note that  $p_1$  moves from the origin to

$$p_1 \rightarrow \overline{\omega_o} = \frac{\overline{C_2}}{\alpha} = \frac{\overline{g_{m_3}} \overline{4g_o}}{g_m C_2}$$

And

$$Q = -\frac{\overline{g_{m_1}} \overline{C_2}}{\alpha C_1}$$

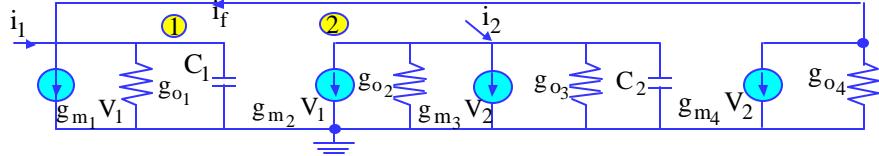Let's consider the input and output impedance,



$$z_{in} = \frac{V_1}{i_1} \Big|_{i_2=0} = \frac{g_{m_3} + g_{o_2} + g_{o_3} + sC_2}{-g_{m_4}g_{m_2} + (g_{m_1} + g_{o_1} + g_{o_4} + sC_1)(g_{m_3} + g_{o_2} + g_{o_3} + sC_2)}$$

$$z_{in} = \frac{V_1}{i_1} \Big|_{i_2=0} \approx \frac{g_{m_3}(1 + sC_2/g_{m_3})}{-g_{m_4}g_{m_2} + g_{m_1}g_{m_3} + s(C_2g_{m_1} + C_1g_{m_3}) + s^2C_1C_2}$$

a) Lossless Integrator

$$z_{in}(0) \approx \frac{g_{m_3}}{-g_{m_4}g_{m_2} + g_{m_1}g_{m_3}} \Bigg| \begin{array}{l} g_{m_1}=g_{m_2} \\ g_{m_3}=g_{m_4} \end{array} \rightarrow \infty$$

b) Lossy Integrator


$$z_{in}(0) \approx \frac{\frac{k^2}{2}}{1 - \frac{1}{\omega}} , \quad k > 0$$

$$z_o(0) \approx \frac{1}{\omega}$$

### Current-Mode: Single and Double-Ended


FullyDiff.ppt

**Basic Cell**

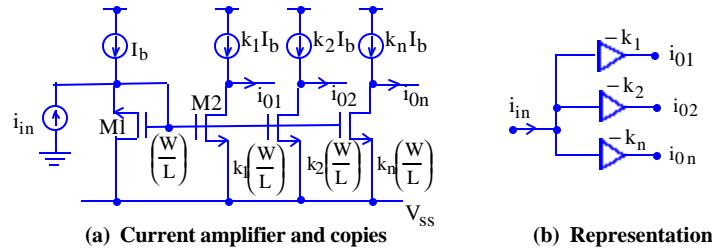

(a) Current amplifier and copies


(b) Representation

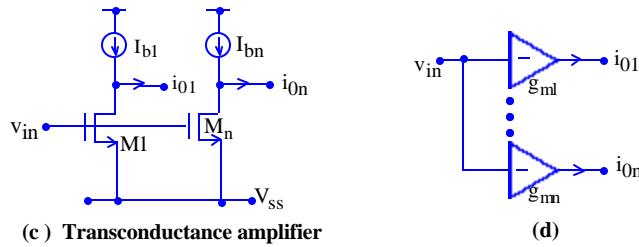


(c) Transconductance amplifier

(d)


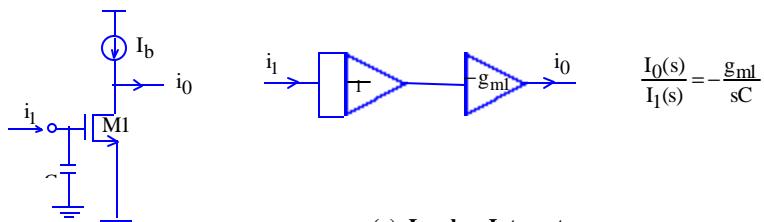
### Current-Mode Integrators Single-Ended



(a) Lossless Integrator

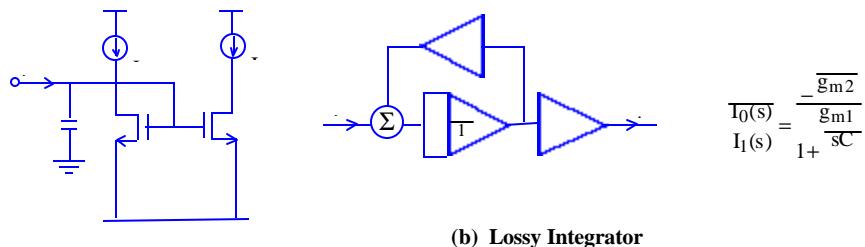


(b) Lossy Integrator

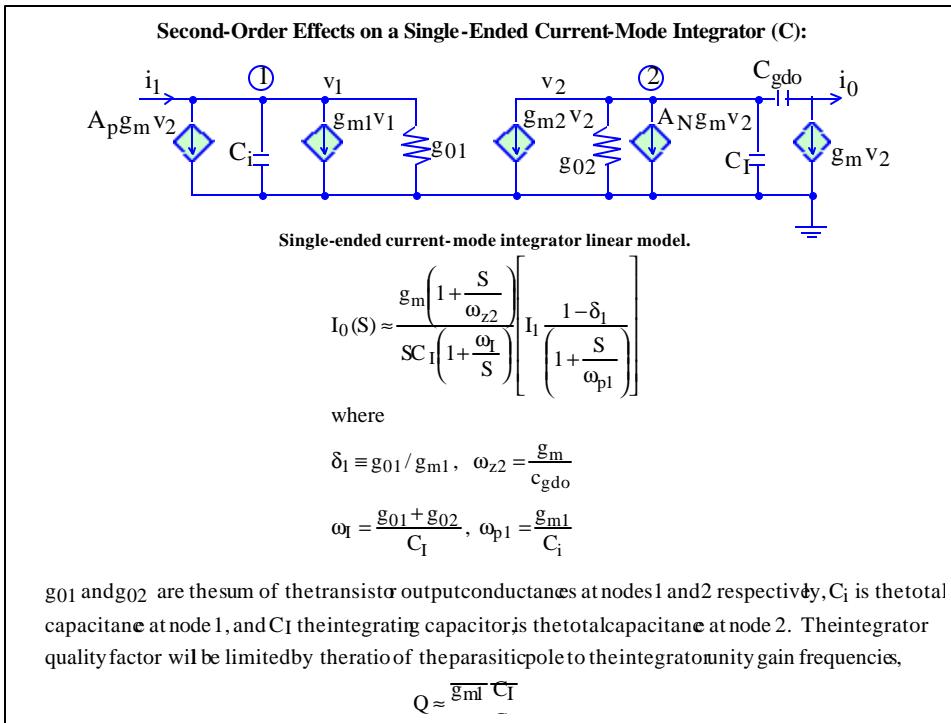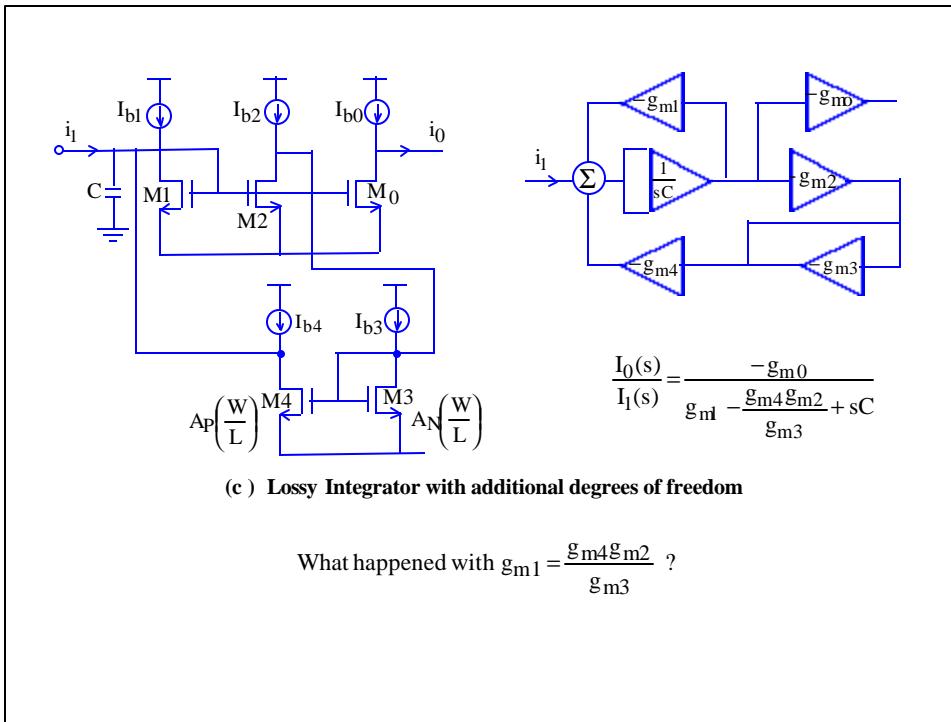

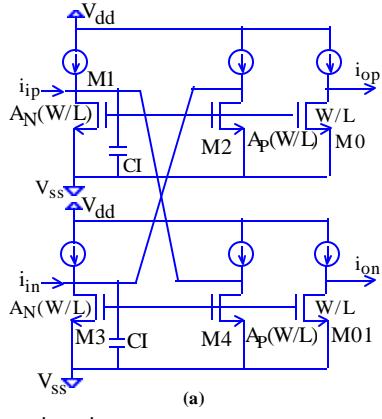
## Improved Balanced Integrators (Double-Ended)

Using the previous single-ended integrator, a double-ended integrator is obtained:  
**Version 1**



(a)

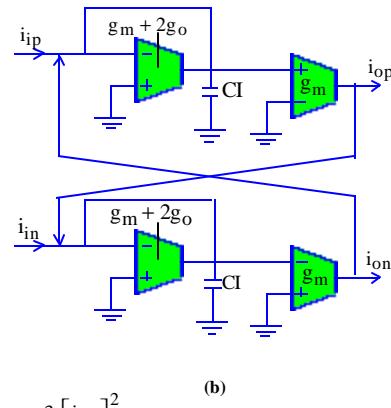

(b)

$$A_{cm1} = \frac{i_{op} + i_{on}}{i_{ip} + i_{in}} = \frac{-g_m}{sC_I + (A_N + A_P)(g_m + 2g_0)}$$


$$A_{dml} = \frac{i_{op} - i_{on}}{i_{ip} - i_{in}} = \frac{g_m}{sC_I + (A_N - A_P)(g_m + 2g_0)}$$

$$IM_3 \approx \frac{3}{32} \left[ \frac{i_{0d}}{2I_b} \right]^2$$

and that the harmonic distortion can be approximated by

$$THD_3 \approx \frac{1}{32} \left[ \frac{i_{0d}}{2I_b} \right]^2$$


## Frequency Compensation

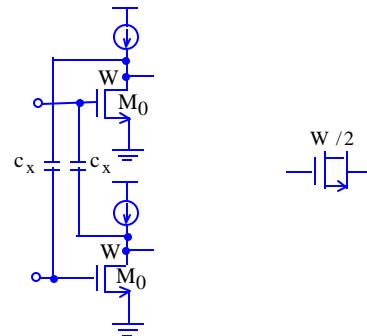


(a)

(b)

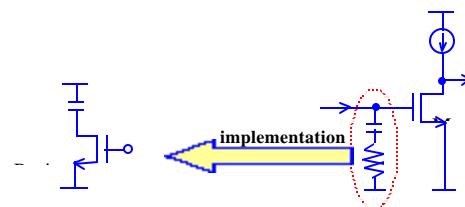Gate-drain capacitance cancellation. (a) circuit. (b) capacitor implementation.



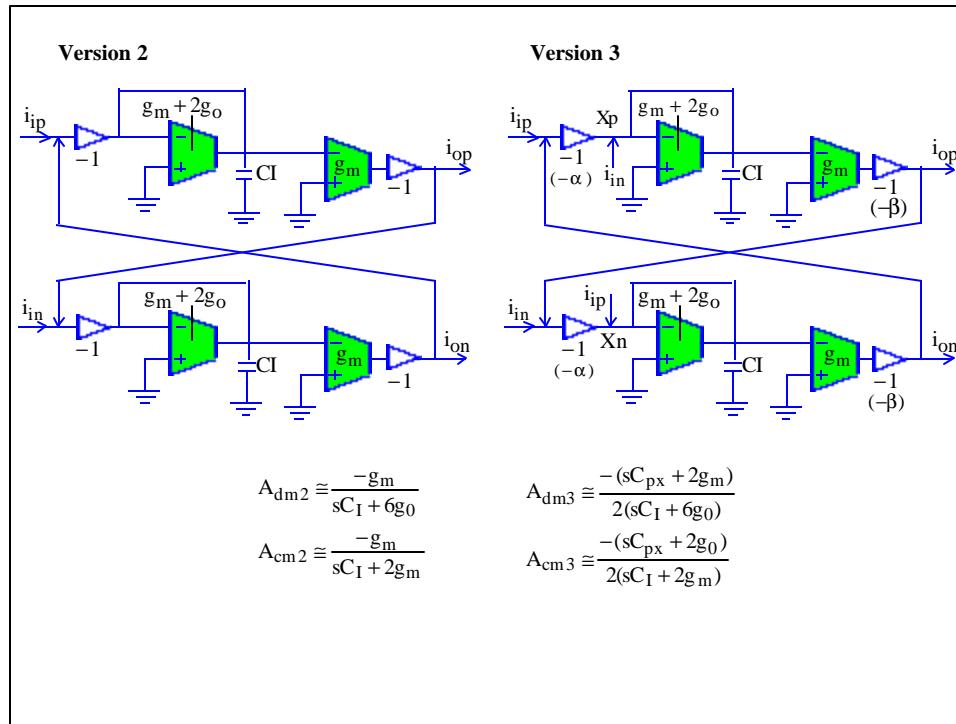Passive phase compensation of current integrators.



**A Comparative Table**

	Case 1	Case 2	Case 3
$A_{dm}(0)$	$\frac{g_m}{2g_o}$	$\frac{g_m}{6g_o}$	$\frac{g_m}{6g_o}$
$A_{cm}(0)$	$\frac{1}{2}$	$\frac{1}{2}$	$\frac{g_o}{2g_m}$
$CMRR(0)$	$\frac{g_m}{g_o}$	$\frac{g_m}{3g_o}$	$\frac{g_m^2}{g_o^2}$
$CMRR(\infty)$			

### Improved Sensitivity

$$A_{dm} \equiv \frac{-(sC_{px} + (\alpha\beta + \beta)g_m)}{sC_1 + 6g_0 + (1 - \varepsilon - \alpha\beta)g_m}$$
$$A_{dm}(0) = \frac{\alpha\beta + \beta}{6g_0 / g_m + (1 - \varepsilon - \alpha\beta)}$$

What are the values of  $\alpha$  and  $\beta$ ?

$$\alpha\beta < 1$$

say  $\beta = 9$  and  $\alpha = 0.1$

**Can you suggest a better common-mode circuit?**

Reference:

X. Quan, S. Embabi and E. Sánchez-Sinencio, "Improved Fully Balanced Current-Mirror Integrator", Electronic Letters, vol. 34, No. 1, pp. 1-3, January 1998.

Analog and Mixed-Signal Center, TAMU


**How can you use a conventional OTA  
as a filter?**

How high can the  $\omega_o$  or the  $\omega_o Q$  of  
a second-order filter be obtained?

Can we reach the limits of the  
technology?

How can we use OTA multiple  
outputs?

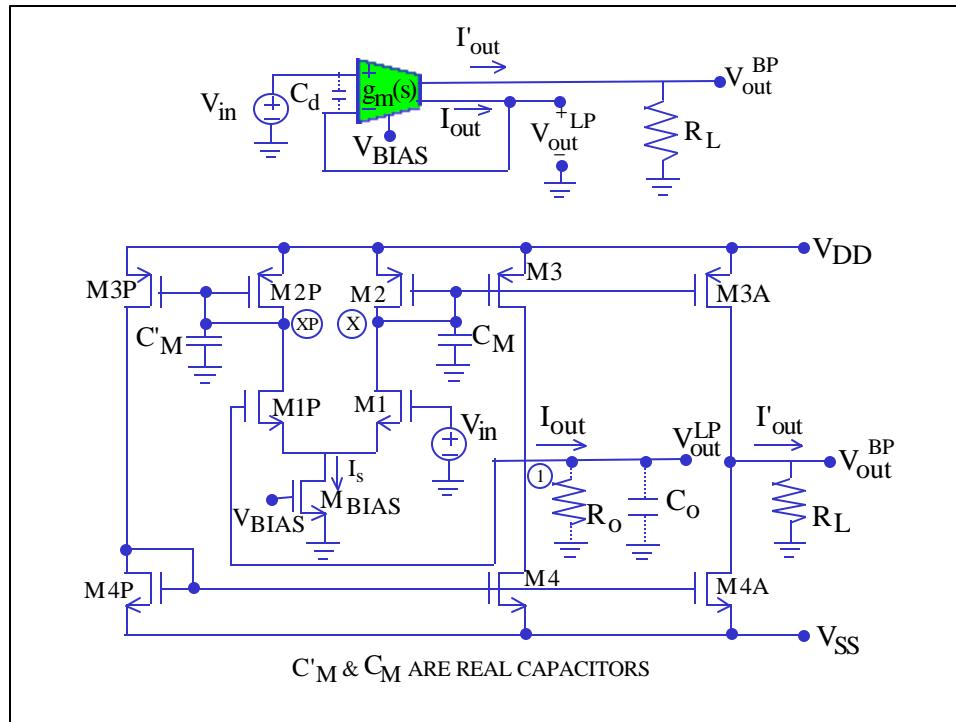Reference: J. Ramírez-Angulo, E. Sánchez-Sinencio and M. Howe, "Large foQ Second-Order Filters Using  
Multiple Outputs OTAs", Trans. Circuits and Systems II, vol. 41, No. 9, pp. 587-592, September 1994.



The corresponding transfer functions are:

$$H_{LP}(s) = \frac{V_{out}^{LP}(s)}{V_{in}(s)} = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$H_{BP}(s) = \frac{V_{out}^{BP}(s)}{V_{in}(s)} = \frac{K_{BP} \frac{\omega_0}{Q}s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

Where

$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{C_0 C_m}} \quad Q = \sqrt{\frac{C_m g_{m1}}{C_0 g_{m2}}}$$

And

For  $\omega / \omega_p \ll 1$  and  $g_m(s) \approx g_m^0 e^{-s/\omega_p}$

$$\omega_p = \frac{g_m^0}{C_m}$$

$$GB = A_{vo}BW = g_m R_0 \frac{1}{R_0 C_0} = \frac{g_m}{C_0}$$

Where  $R_0 = 1/(g_{03} + g_{04})$


$$\omega_0 = \sqrt{\frac{g_m^0 \omega_p}{C_0}} = \sqrt{GB \omega_p}$$

$$Q = \sqrt{\frac{g_m^0}{C_0 \omega_p}} = \sqrt{\frac{GB}{\omega_p}}$$

$$K_{BP} = g_m^0 R_L$$

$$f_0 Q = GB / 2\pi$$

Analog and Mixed -Signal Center, TAMU

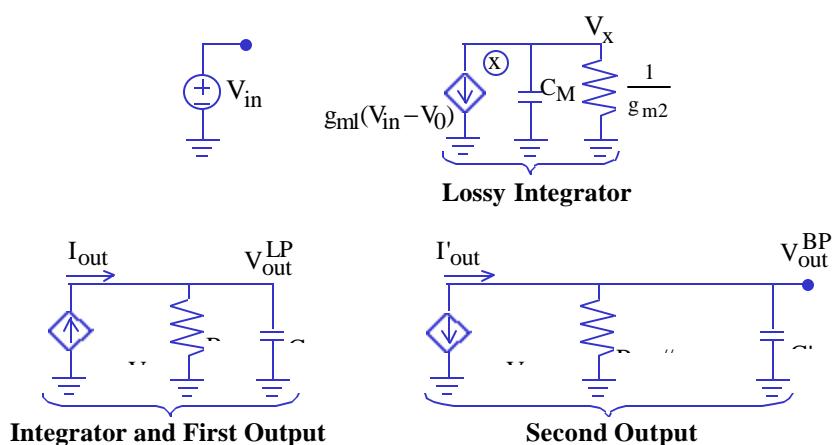


$$GB = \frac{g_{m1}}{C_{PAR}} = \frac{\mu_n C_{ox} \frac{W}{L_1} (V_{GS1} - V_T)}{2 C_{ov} (W L_1)} \approx \frac{\mu_n (V_{GS1} - V_T)}{L_1^2} \frac{3}{2}$$

i.e., 2μm technology  $f_0 Q \sim 2\text{GHz}$

Analog and Mixed -Signal Center, TAMU

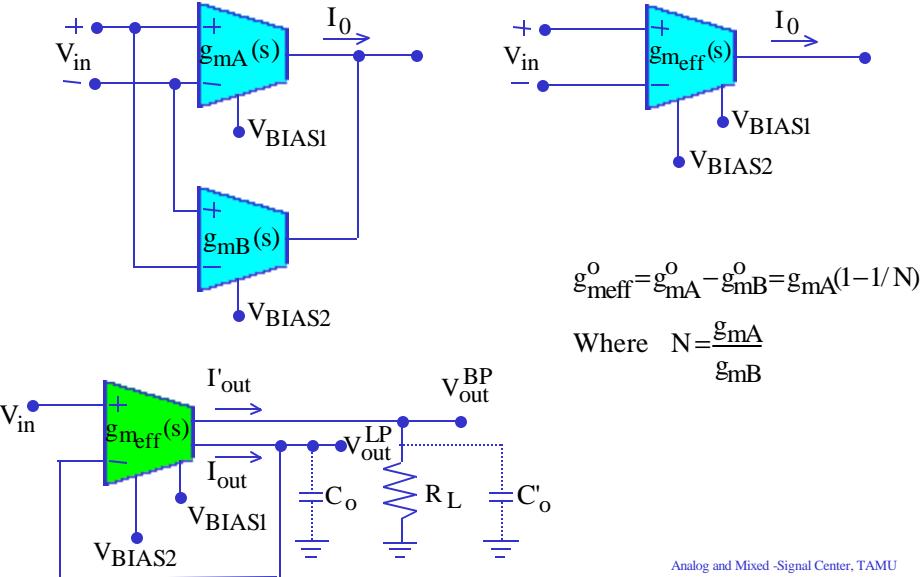How can we obtain  $Q$  and  $f_0$  independently tuned?  
A possible solution is shown next.



### Summary of the Results

$$\omega_0 = \sqrt{\frac{g_{\text{mA}}}{C_0}} \omega_{p_A} \sqrt{1 - \frac{1}{N^2}}$$

$$Q = \frac{1}{\frac{\omega_{p_A}}{\omega_0} \left[ 1 + \frac{1}{N} - \frac{1}{N+1} \right] - \frac{\omega_0}{2\omega_{p_H}} \left[ 1 - \frac{1}{N} \right]}$$

DEPENDENCE OF Q AND  $\omega_0$  WITH N.

N	$\omega_0 / \text{MHz}$	Q
$\infty$	16.45	56.66
15	16.41	40.90
7.0	16.28	27.72
3.0	15.50	13.83


$$C_m = 20 \text{ pF}, \quad C_0 = 1 \text{ pF}, \quad g_{\text{mA}} = 850 \mu\text{A/V}, \quad f_{pH} = 75 \text{ MHz} \quad \text{and} \quad f_{pA} = 2 \text{ MHz}$$

Where  $\omega_{pH}$  is the high frequency pole of mirror M4, M4P.



Implementations of  $g_{\text{meff}}$  :

- Two equal OTAs with different bias to satisfy the  $N = g_{mA} / g_{mB}$  or different (W/L)s.
- One OTA: To inject a current  $I_X$  to the drains of the differential pair. This yields different currents through the load transistor M2 and M2P. Consequently, we can have independent Q tuning.

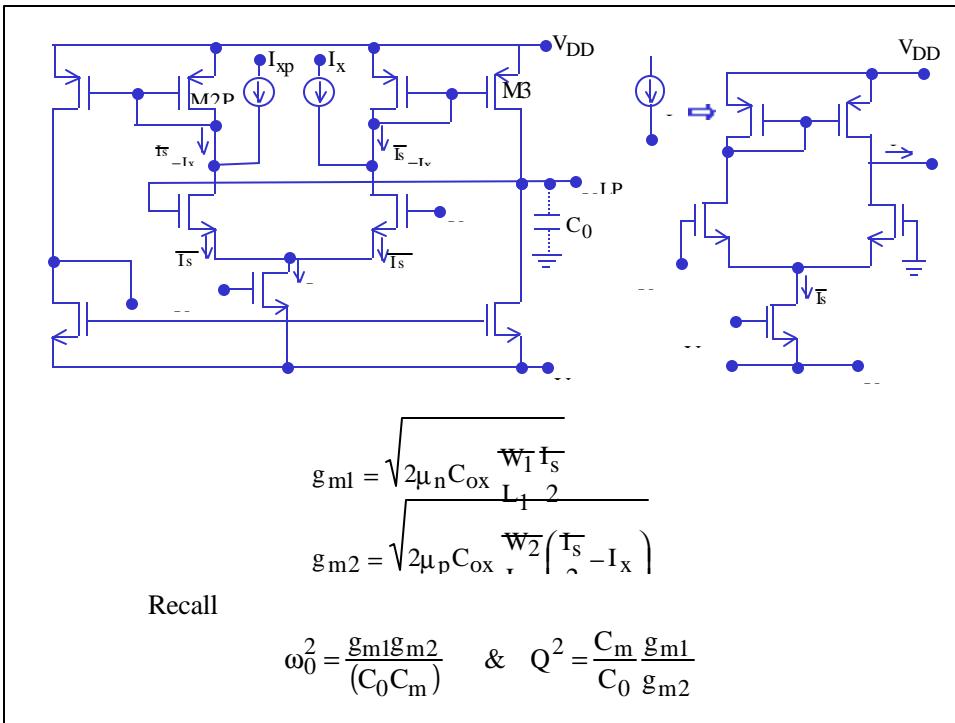The actual implementation is discussed next.



### Experimental Results

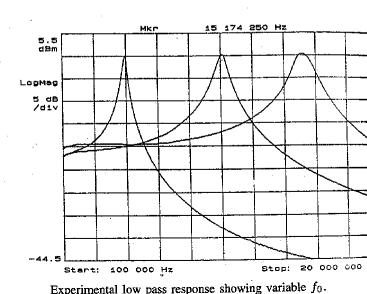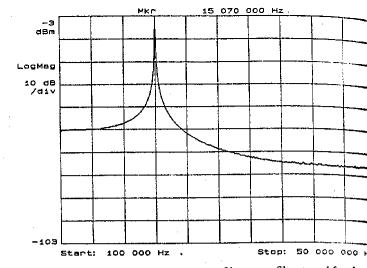

### Appendix: Derivation of Expressions

$$N = \frac{g_{m_A}^0}{g_{m_B}^0} = \frac{\omega_{p_A}}{\omega_{p_B}}$$

$$\omega_0 = \sqrt{\frac{g_{m_A}}{C_0} \omega_{p_A}} \sqrt{\left(1 - \frac{1}{N^2}\right)}$$

$$\tan^{-1} x = \frac{\pi}{2} - \tan^{-1} \frac{1}{x}$$

$$\tan^{-1} x = x - \frac{x^3}{3} + \frac{x^5}{5} - \frac{x^7}{7} + \dots$$

$$\Phi(\omega) = \frac{\omega_{p_A}}{\omega} \left[ 1 + \frac{1}{N} - \frac{1}{N+1} \right] - \frac{\omega}{2\omega_{pH}} \left[ 1 - \frac{1}{N} \right]$$

$$Q = \frac{1}{\frac{\omega_{p_A}}{\omega_0} \left[ 1 + \frac{1}{N} - \frac{1}{N+1} \right] - \frac{\omega_0}{2\omega_{pH}} \left[ 1 - \frac{1}{N} \right]}$$

$$Q(N \rightarrow \infty) = \frac{1}{\frac{\omega_{p_A}}{\omega_0} - \frac{\omega_0}{2\omega_{pH}}}$$

## References

1. GEIGER, R.L. and SÁNCHEZ-SINENCIO, E., "Active filter design using operational transconductance amplifiers: a tutorial," *IEEE Circuits and Devices Magazine*, Vol. 2, No. 1, January 1985, pp. 20-32.
2. WILSON, R.S. and WITTINGE, H.A., "OTA obsoletes OP, AMP," *P. Nat. Econ. Conf. I*, 1969, pp. 152-157.
3. TAN, K.S. and GRAY, P., "Fully-integrated analog filters using bipolar JFET technology," *IEEE J. of Solid-State Circuits*, Vol. SC-13, No. 6, December 1980, pp. 814-821.
4. Moulding, K.W., Quarterly, J.R., Rankin, P.J., Thompson, R.S. and Wilson, G.A., "Gyrorator video filter IC with automatic tuning," *IEEE J. of Solid-State Circuits*, Vol. SC-15, No. 6, Dec. 1980, pp. 963-968.
5. Fukahori, K., "A bipolar voltage-controlled tunable filter," *IEEE J. of Solid-State Circuits*, Vol. SC-16, No. 6, December 1981, pp. 729-737.
6. Khorrami, H., Gray, P.R., "High-frequency CMOS continuous-time filters," *IEEE J. Solid-State Circuits*, Vol. SC-19, December 1984, pp. 939-948.
7. Johns, D.A. and Martin, K., "Analog Integrated Circuit Design," John Wiley & Sons, New York, 1997.
8. Deliyannis, T., Sun, Y., and Fidler, J.K., "Continuous-Time Active Filter Design," Boca Raton, CRC Press 1999.
9. Kardoukhchik, J.E., "Introduction to the design of transconductor-capacitor filters," Boston, Kluwer Academic Publishers, 1992.
10. Park, C.S. and Schuman, N., "Design of a 4 MHz analog integrated CMOS transconductance-C bandpass filter," *IEEE J. of Solid-State Circuits*, Vol. SC-23, No. 4, August 1988, pp. 987-996.
11. Park, C.S., "CMOS triode transconductor for continuous-time active integrated filters," *Electronics Letters*, Vol. 21, Aug. 1985, pp. 817-818.
12. Ganti, U., Maloberti, F., and Torodili, G., "CMOS triode-transistor transconductor for high-frequency continuous-time filters," *Proc. IEE Circuits, Devices and Systems*, Vol. 141, No. 6, Dec. 1994, pp. 462-468.
13. Ramírez-Angulo, J. and Sánchez-Sinencio, E., "Programmable BiCMOS transconductor for capacitor-transconductance filters," *Electronics Letters*, Vol. 28, June 1992, pp. 1185-1187.
14. Wysynski, A., "Low-Voltage CMOS and BiCMOS triode transconductors and integrators with gain enhanced linearity and output impedance," *IEE Electronics Letters*, Vol. 30, 3, Feb. 1994, pp. 211-212.
15. Itakura, T., Ueno, T., Tanimoto, H., and Arai, T., "A 2 Vpp linear input range fully balanced CMOS transconductor and its application to 2.5V 2.5 MHz Gm-C LPF," *Proc. IEEE CICC*, 1999, pp. 509-512.
16. DUQUE-CARRILLO, J.F., "Control of the common-mode component in CMOS continuous-time fully differential signal processing," *Analog Integrated Circuits and Signal Processing*, Kluwer Academic Publishers, 1993, pp. 131-140.
17. RODRIGUEZ, F., BASCHIROTTO, A., AND CASTELLO, R., "A 3 V 12.5-MHz BiCMOS pseudo-differential continuous-time filter," *IEEE Trans. Circuits and Systems, I*, Vol. 42, November 1995, pp. 896-903.
18. SMITH, S.L., SÁNCHEZ-SINENCIO, E., "Low voltage integrators for high-frequency CMOS filters using current mode techniques," *IEEE Trans. Circuits and Systems, II*, Vol. 43, 1996, pp. 39-48.
19. Gazinski, A., Bialko, M., and Matheau, J.C., "Body-driven differential amplifier for application in continuous-time active-C filter," *Proc. ECCT*, Vol. 1, September 1987, pp. 313-320.
20. Panekiewicz, B., Szczepanski, S., "Body-biased CMOS OTA for continuous-time analog filter applications," *ICECS '96*, Proc. of the Third IEEE International Conference, Vol. 1, pp. 132-135.
21. dielscher, f., hauptmann, j., reisinger, j., steiner, r.r., and rojer, h., "A software programmable CMOS telephone circuit," *IEEE J. Solid-State Circuits*, Vol. 26, 7, July 1991, pp. 1015-1026.
22. BLALOCK, B.J., ALLEN, P.E., and RHINCON-MORA, G.A., "Designing 1-V Op Amps Using Standard Digital CMOS Technology," *IEEE Trans. Circuits and Systems II*, 45, July 1998, pp. 769-780.
23. Khorrami, H., Gray, P.R., "Characterization of linear MOS active attenuator and amplifier," *Electronics Letters*, Vol. 31, March 1995, pp. 511-513.
24. Han, G., Sánchez-Sinencio, E., "CMOS transconductance multipliers: a tutorial," *IEEE Trans. Circuits Systems II*, Vol. 45, December 1998, pp. 1550-1563.
25. Song, B.S., "CMOS RF circuits for data communications applications," *IEEE J. Solid-State Circuits*, Vol. SC21, April 1986, pp. 310-317.
26. Czarnul, Z., Fang, S.C., and Tsividis, Y., "Improving linearity in MOS fully-integrated continuous-time filters," *IEEE Proc. ISCAS* 86, June 1986, pp. 1169-1172.
27. WANG, Z., "Novel linearisation technique for implementing large-signal MOS tunable transconductor," *IEEE Electronics Letters*, Vol. 26, No. 2, January 1990, pp. 138-139.
- 28.