
 


Switched-Capacitor Circuits

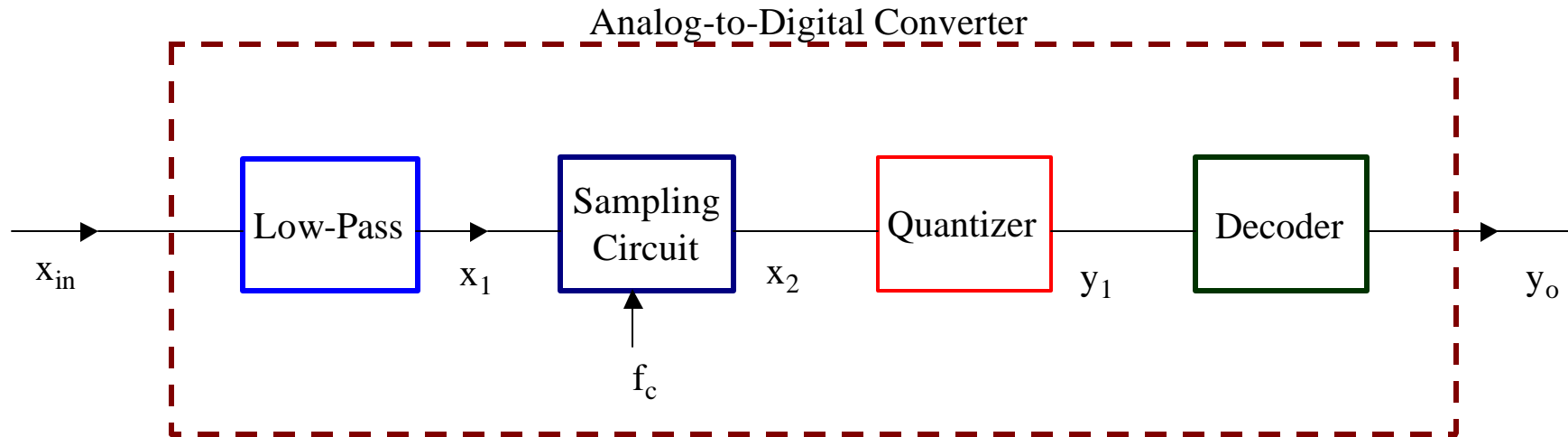- Mathematical Background
- Basic Building Blocks
- SC Filters
- SC Oscillators
- SC PLL



Examples of Analog and Digital Signals



Analog and Digital Signals and Systems Concepts

Types of signals

- Continuous-Time (CT)
 - Continuous values in time
 - Continuous values in magnitude
- Sampled Data (SD)
 - Continuous values in magnitude
 - Discrete values in time
- Digital
 - Discrete values in magnitude
 - Discrete values in time

Mathematical Description

Laplace

Z-Transform


Z-Transform

Examples of Basic Implementations


- First-order Low Pass (Continuous-Time)

$$H(s) = \frac{K}{1 + s/\omega_p} ; \quad \frac{V_o(s)}{V_{in}(s)} = \frac{K\omega_p}{s + \omega_p} ; \quad \frac{dv_o(t)}{dt} + \omega_p v_o(t) = K\omega_p v_{in}(t)$$


Continuous-time

 

s-plane

 


 Stability implies to have poles in the left-half plane (LHP)



$$H(s) \Big|_{s=j\omega} = H(j\omega) = \frac{-K}{1+j\omega/\omega_p} = \frac{K}{[1+(\omega/\omega_p)^2]^{1/2}} \angle -\tan^{-1} \omega/\omega_p$$

Frequency Response

 

$$h(t) = K\omega_p e^{-\omega_p t}$$

Impulse Response

- First-Order Low-Pass (Discrete-Time)
Sampled-Data (i.e., Switched-Capacitor)

$$H(z) = \frac{V_o(z)}{V_{in}(z)} = \frac{K_1}{1 - z^{-1}/\omega_{pl}} = \frac{K_1 \omega_{pl}}{\omega_{pl} - z^{-1}} ;$$

$$[\omega_{pl} - z^{-1}]V_o(z) = K_1 \omega_{pl} V_{in}(z)$$

$$\omega_{pl} V_o(z) - z^{-1} V_o(z) = K_1 \omega_{pl} V_{in}(z)$$

Taking the inverse z-transform

$$\omega_{pl} v_o(nT) - v_o(n-1)T = K_1 \omega_{pl} v_{in}(nT)$$


$$v_o(n-1)T - \omega_p v_o(nT) = -K_1 \omega_{pl} v_{in}(nT)$$

This difference equation represents the first-order low pass in the Z-domain.


Note that

$$Z^{-1}X_o(z) \Rightarrow x_o(n-1)T$$

$$Z^{-b}X_o(z) \Rightarrow x_o(n-b)T$$

 

 
Stability implies poles inside
unity circle



Frequency Response (A periodic transfer function!)

$$H(z) = \frac{K_1 \omega_{p1} Z}{\omega_{p1} Z - 1} \bigg|_{z = e^{j\omega}} = \frac{K_1 \omega_{p1} (\cos \omega T + j \sin \omega T)}{(\omega_{p1} \cos \omega T - 1) + j \sin \omega T}$$
 
$$H(e^{j\omega}) = \frac{K_1 \omega_{p1}}{\{(\omega_{p1} \cos \omega T - 1)^2 + \sin^2 \omega T\}^{1/2}} \left[\overbrace{\omega T - \tan^{-1} \frac{\sin \omega T}{\omega_{p1} \cos \omega T - 1}}^{\text{phase}} \right]$$



where

$$K_1 \omega_{p1} = \frac{C_1}{C}$$

$$\omega_{p1} = 1 + \frac{C_2}{C}$$

What are the relationships between the s-plane and z-plane?

- There are a number of mappings between the two planes
- The most popular and exact is the bilinear mapping.


$$s = \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} = \frac{2}{T} \frac{z - 1}{z + 1} \quad \text{or} \quad z = \frac{1 + (T/2)s}{1 - (T/2)s}$$

- The commonly used for high-sampling rate is:

$$s = \frac{1}{T} \frac{1 - z^{-1}}{z^{-1}} = \frac{1}{T} \frac{z - 1}{1}$$


or

$$z = sT + 1$$

 


Example. Approximate a first-order low-pass continuous-time to a discrete-time low-pass under high-sampling conditions. ($f_s/f \gg 1$)

$$H(s) = \frac{K}{1 + s/\omega_p} = \frac{K\omega_p}{s + \omega_p} \quad \left| \quad s = \frac{1}{T}(z - 1) \right.$$

 
 
$$H(z) = \frac{K\omega_p T}{z - 1 + \omega_p T} = \frac{K\omega_p T}{z - (1 - \omega_p T)}$$



What is the 3dB cut-off frequency in both domains?

$$f_{3dB} = \omega_p \quad \text{CT}$$

For $H(z)$ is more complex than the computation of f_{3dB} .

$$H(e^{j\omega T}) = \frac{K\omega_p T}{\cos \omega T + j\sin \omega T - (1 - \omega_p T)}$$

$$\left| H(e^{j\omega T}) \right| = \left| H(e^{j\omega_{3dB} T}) \right| / \sqrt{2}$$

$\omega = \omega_{3dB}$

$$\omega_{3dB} = \frac{1}{T} \cos^{-1} \frac{2 - 2\omega_p T - (\omega_p T)^2}{2(1 - \omega_p T)}$$

Numerical example. Low-Pass (First Order)

$$\omega_p = 2\pi \times 10^3 \text{ r/s}$$

$$f_c = f_s = 20\text{KHz} \quad ; \quad T = 1/f_s \quad ; \quad \omega_p T = \frac{2\pi \times 10^3}{20 \times 10^3} = 0.1\pi$$

$$K = 2$$

For the continuous-time

$$f_{3\text{dB}} = 1\text{KHz}$$

$$H(j\omega) \Big|_{\omega = \omega_{3\text{dB}}} = \frac{2}{\sqrt{2}} = 1.4142$$

For the sample-data

$$f_{3\text{dB}} = \frac{f_s}{2\pi} \cos^{-1} \frac{2 - 2\omega_p T - (\omega_p T)^2}{2(1 - \omega_p T)}$$

$$f_{3\text{dB}} \cong 1.16\text{KHz}$$

Switched - Capacitor Filters


- Use Z-transform mathematics
- Are described by difference equations
- Time constants are proportional to capacitor ratios
- Best implementation for audio applications
- Originally the basic goal was to replace resistors by switches and capacitors
- This design approach is one of the most popular in the industry

Advantages



- Reduced silicon area
- Good accuracy. Time constants are implemented with capacitor ratios ($\sim 0.1\%$)
- Don't require a low-impedance output stage (OTA's could be used)
- Could be implemented using digital circuit process technology
- Very useful in the audio range

NOTATION

Switches

 


Representation

 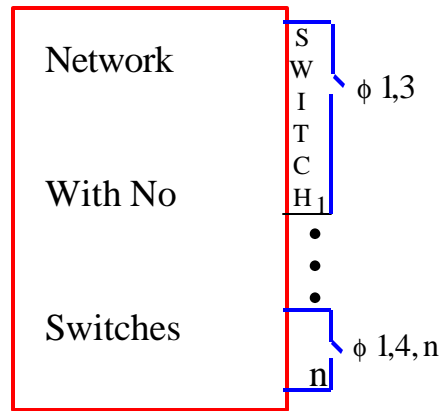


EXAMPLE $n=2$

NON-OVERLAPPING

 

 PHASE PERIODS OF A CONVENTIONAL CLOCK SEQUENCE




S/H and its respective odd and even components

$$y_H(t) = y_H^o(t) + y_H^e(t)$$

or

$$Y_H(Z) = Y_H^o(Z) + Y_H^e(Z)$$

 

$$V_{in}(Z) = V_{in}^e(Z) + V_{in}^o(Z)$$

$$V_o(Z) = V_o^e(Z) + V_o^o(Z)$$

$$H(Z) = \frac{V_o(Z)}{V_{in}(Z)}$$

CONVENTIONAL NOTATION FOR TRANSFER FUNCTION IS:



$$H^{ij}(Z) = \frac{V_o^j(Z)}{V_{in}^i(Z)}$$

i and j can be either “e” or “o”. i.e.,


$$H^{eo}(Z) = \frac{V_o^o(Z)}{V_{in}^e(Z)}$$

TWO-PHASE CLOCK GENERATOR

SINGLE PHASE

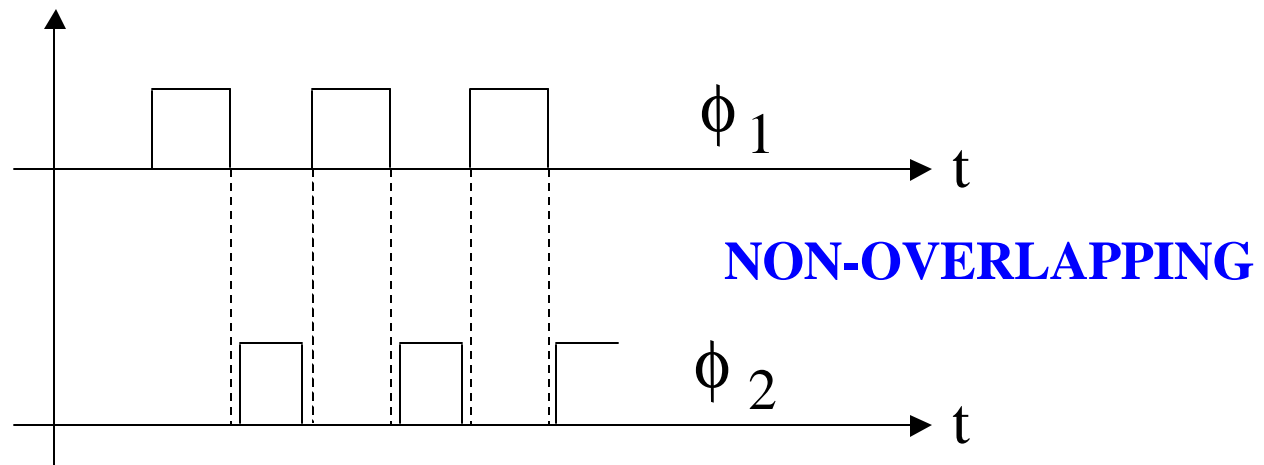 



SWITCHED-CAPACITOR EQUIVALENT RESISTOR

 

Continuous (Conventional) Resistor


$$R = \frac{V_1 - V_2}{I_1} = \frac{V_2 - V_1}{I_2} \Rightarrow I_2 = \frac{V_2 - V_1}{R}$$

V_1 and V_2 are constant voltage sources

  


At time $t = t_0$ we apply the clocks.

At ϕ_1

 

$$Q(t_0 + T/2) = CV_1$$


At ϕ_2

 

$$Q(t_0 + T) = CV_2 - CV_1$$

$$Q(t_0 + T) = C(V_2 - V_1)$$

For the next period, at ϕ_1

 

$$Q(t_0 + \frac{3T}{2}) = C(V_1 - V_2)$$

$$i = \frac{dQ}{dt}$$

$$Q_1 = \int_{t_0 + T}^{t_0 + 3T/2} i_1(t) dt = \int_{t_0 + T/2}^{t_0 + 3T/2} i_1(t) dt$$

The average current I_1 (aver) becomes

$$I_1 \text{ (aver) } = \frac{Q \left(t_o + \frac{3T}{2} \right)}{T}$$

$$I_1 \text{ (aver) } = \frac{1}{T} \int_{t_o + 3T/2}^{t_o + 3T/2} i_1(t) dt$$

$$I_1 \text{ (aver) } = \frac{C (V_1 - V_2)}{T} = \frac{\Delta Q}{\Delta t}$$

or

$$\frac{T}{C} = \frac{V_1 - V_2}{I_1 \text{ (aver)}}$$

Comparing with the continuous time resistor

$$\longrightarrow R_{eq} = \frac{T}{C} = \frac{1}{f_C C} \longleftarrow$$

EXAMPLE. $R = 250K\Omega$, $f_C = 128KHz$

$$\left(\frac{A_R}{A_C} \cong 32 \right) \longleftarrow C = \frac{1}{R_{eq} f_C} = \frac{1}{250 \times 128 \times 10^6} = 31.25pF$$

	Continuous R	“SC-R”	
AREA	5,776	178.57	mils ²

ACCURACY OF TIME CONSTANTS

● CONTINUOUS TIME:

$$\tau = R_1 C_2$$

$$\frac{d\tau}{\tau} = \frac{dR_1}{R_1} + \frac{dC_2}{C_2} \rightarrow \pm 40\% \rightarrow \pm 65\%$$

where $\frac{d\tau}{\tau}$ is interpreted as the accuracy of τ .

TEMPERATURE DEPENDANT!

● DISCRETE TIME:

$$\tau = \frac{1}{f_C C_1} \cdot C_2 = T \left(\frac{C_2}{C_1} \right)$$


$$\frac{d\tau}{\tau} = \frac{dT}{T} + \frac{dC_2}{C_2} - \frac{dC_1}{C_1}$$

$$\frac{d\tau}{\tau} \cong \frac{dC_2}{C_2} - \frac{dC_1}{C_1} \rightarrow 0.1\%$$

KC_HL KIRCHOFF “CHARGE” LAW

$$\sum_{i=1}^n Q_i = 0$$

$$Q_j = C_j V_{C_j}$$

 

at $t = t_2$


$$V_{C_j} = V_x(t_2) - V_y(t_2) - (V_x(t_1) - V_y(t_1))$$

Voltage across the capacitor $V_{C_j} =$ voltage difference (at present time) across the capacitor minus initial condition (at past time).


CHARGE CONSERVATION

ANALYSIS METHOD

$$q_L(n) = q_M(n-1) + \hat{q}_C(n)$$

 

EXAMPLE

 

for ϕ_2

$$C_2[V_2^e(n) - V_2^o(n - \frac{1}{2})] + C_1[V_2^e(n) - V_1^o(n - \frac{1}{2})] = 0$$

for ϕ_1

$$C_2[V_2^o(n - \frac{1}{2}) - V_2^e(n - 1)] = 0 \Rightarrow V_2^o(n - \frac{1}{2}) = V_2^e(n - 1)$$

THEN

$$C_1 v_2^0(n) + C_2 v_2^0(n) = C_2 v_2^0(n-1) + C_1 v_1^0(n-1)$$

$$(C_1 + C_2)V_2^0(Z) - C_2 Z^{-1}V_2^0(Z) = C_1 V_1^0(Z)Z^{-1}$$

$$H^{oo}(Z) = \frac{\frac{C_1}{C_1} Z^{-1}}{\frac{C_1 + C_2}{C_1} - \frac{C_2}{C_1} Z^{-1}} = \frac{Z^{-1}}{1 + \alpha - \alpha Z^{-1}}$$

$$H^{oo}(Z) = \frac{\frac{C_1}{C_1} Z^{-1}}{\frac{C_1 + C_2}{C_1} - \frac{C_2}{C_1} Z^{-1}} = \frac{Z^{-1}}{1 + \alpha - \alpha Z^{-1}}$$

$$H^{oo}(Z) = \frac{V_o^0(Z)}{V_{in}^0(Z)} = \frac{V_o^e(Z)Z^{-1/2}}{V_{in}^o(Z)}$$

$$V_2^e(n) = V_2^e(n + 1/2)$$

$$C_2[V_2^0(n + 1/2) - V_2^0(n - 1/2)] + C_1[V_2^0(n + 1/2) - V_1^0(n - 1/2)]$$

$$C_2[V_2^0(Z)][Z^{1/2} - Z^{-1/2}] + C_1V_2^0(Z)Z^{1/2} = C_1V_1^0(Z)Z^{-1/2}$$

$$C_2(1 - Z^{-1})V_2^0(Z) + C_1V_2^0(Z) = C_1V_1^0(Z)Z^{-1/2}$$

$$\frac{V_2^0(Z)}{V_1^0(Z)} = \frac{C_1Z^{-1}}{C_2(1 - Z^{-1}) + C_1} = \frac{C_1Z^{-1}}{C_2 + C_1 - C_2Z^{-1}}$$

$$\frac{V_2^0(Z)}{V_1^0(Z)} = \frac{C_1}{(C_2 + C_1)Z - C_2} \bigg|_{Z \cong 1 + ST} = \frac{C_1}{(C_2 + C_1) + (C_2 + C_1)ST - C_2}$$

For high-sampling rate $\omega T \ll 1$

$$\frac{V_2^0(Z)}{V_1^0(Z)} \bigg|_{Z \cong 1 + ST} = \frac{C_1}{C_1 + (C_2 + C_1)5T} = \frac{1}{1 + \frac{(C_2 + C_1)5T}{C_1}} = \frac{1}{1 + \frac{5}{\frac{C_1}{(C_2 + C_1)T}}}$$

$$f_{3dB} \cong \frac{1}{2\pi} \cdot \frac{C_1}{(C_2 + C_1)T} = \frac{1}{2\pi} \cdot \frac{f_c}{1 + \frac{C_2}{C_1}}$$

Aside:

$$f_{3dB} \cong \frac{1}{2\pi} \cdot \frac{1}{R_1C_2} \cong \frac{1}{2\pi} \cdot \frac{1}{\frac{TC_2}{C_1}} = \frac{1}{2\pi} \cdot \frac{f_c}{\frac{C_2}{C_1}}$$


Switched-Capacitor techniques advantages

- Reduced silicon area
- Good accuracy. Time constants are implemented with capacitor ratios ($\sim 0.1\%$)
- Don't require a low-impedance output stage (OTAs could be used)
- Could be implemented using digital circuit process technology
- Very useful in the audio range


Switched-Capacitor (SC) Filters

How to design SC Filters ?

- Two basic approaches

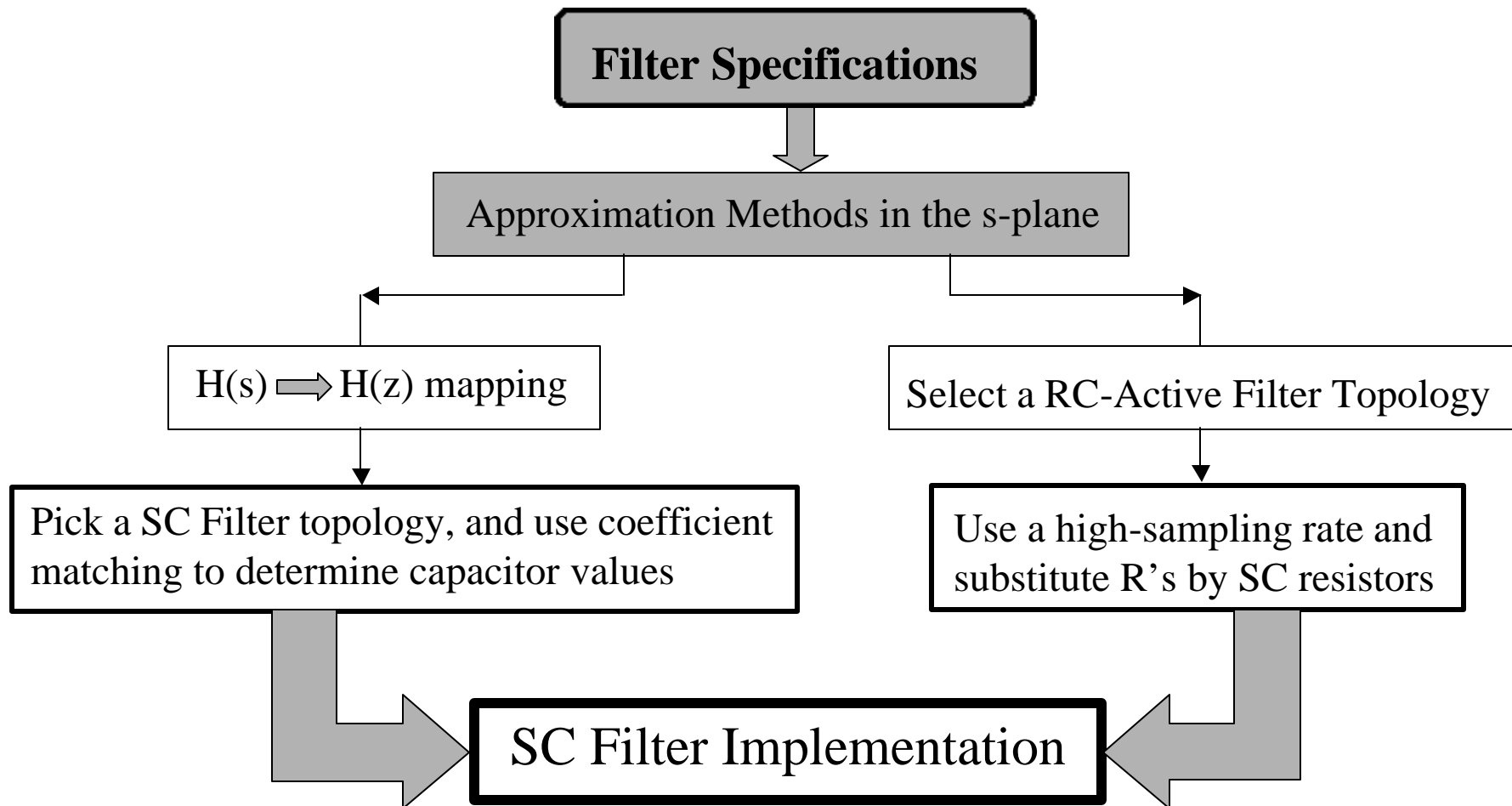

Systematic SC Filter Design

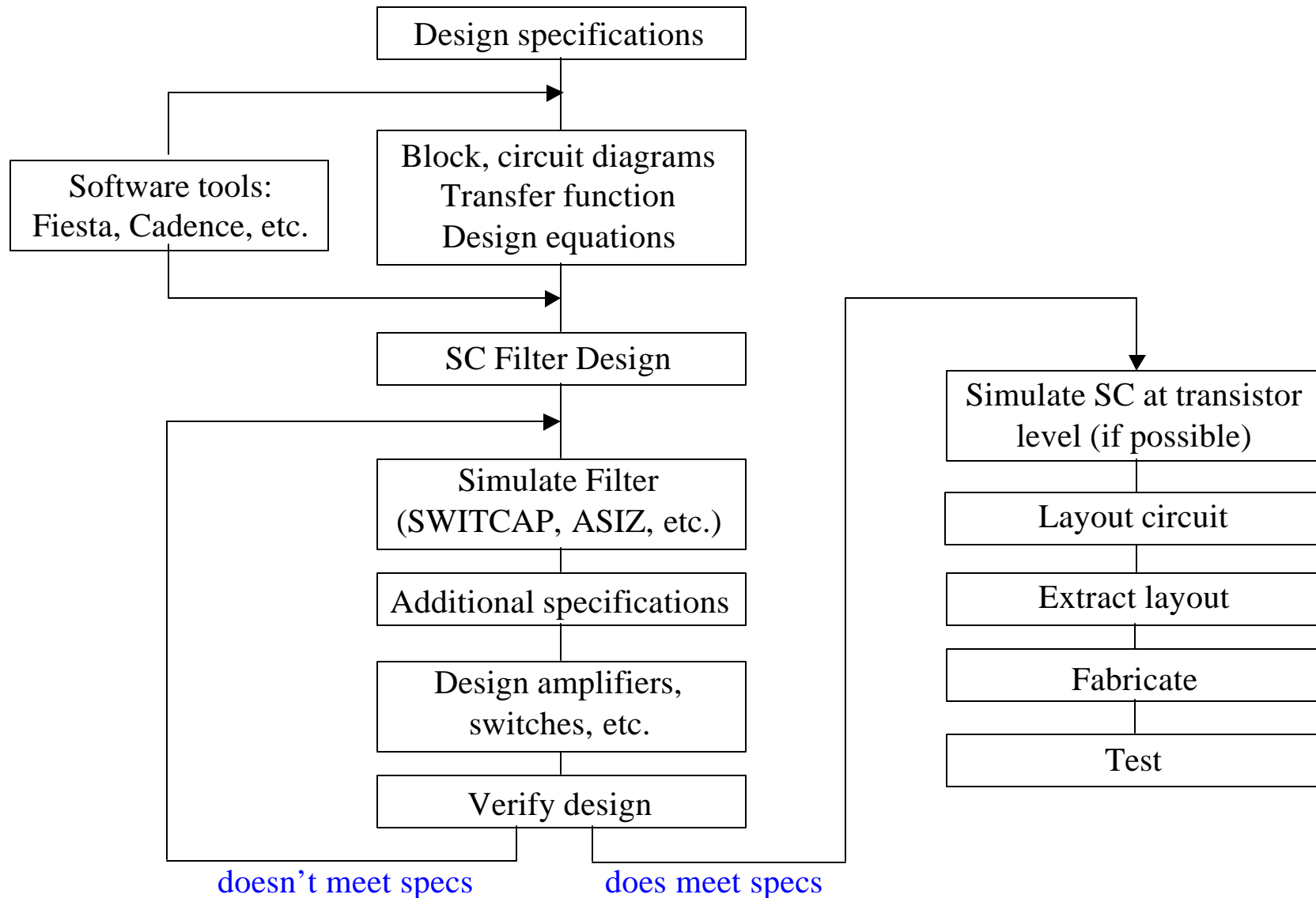

What are the advantages and disadvantages of the two filter design procedures ?

- Mapping Techniques

- + Systematic and well documented (see FIESTA-2)
- + It can use any sampling rate, including the (minimum) Nyquist rate.
- Difficult to implement by hand calculation

- Transforming R to SC resistors

- + It is, conceptually, easier to follow for analog designer
- + Its design is straightforward
- Yields not an optimal design for area, imposed high sampling rate involves larger capacitor ratios.

Switched-Capacitor Filters Components

Basic Elements

Capacitors

- polysilicon
- metal1-metal2
- parasitics, clock-feedthrough


Switches

- N-MOS
- Transmission gates
- Noise and on-resistance

OTAS


- DC-gain
- settling time (GBW, phase margin)
- noise

Non-overlapping clock phases

 


Typical switched-capacitor integrator

Switched-Capacitor Filters: CAPACITORS

 


polysilicon

 

C_{P1} , $C_{P2''}$ are very small (1-5 % of C_1)

$C_{P2'}$ is around 10-30 % of C_1

metal1-metal2

 


SWITCHES

MOS transistors biased in triode region, ~100-100 k Ω

Off resistances ~ G Ω

N-MOS

 


- $V_1, V_2 < V_G - V_T$ ($V_T \sim 1$ V)

- Resistance $R_s \cong \frac{L}{\mu_n C_{ox} W (V_{GS} - V_T)}$

- Small resistance for low voltages but high resistance for large voltages

- Transmission gates

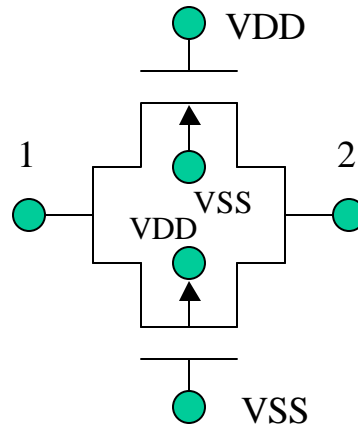

- Rail to rail operation, provided that V_{DD} and $V_{SS} > V_T$



- Smaller resistance (fast response)

- 2 clock phases

- More parasitics

Switched-Capacitor Filters: SWITCHES


Transmission gates

  

$$R_n \cong \frac{L}{\mu_n C_{ox} W (V_{DD} - V_1 - V_T)}$$


For $V_1, V_2=0$, $W/L=1$, $\mu_n C_{ox}=10^{-4}$

$$R_n = 10k / (V_{DD} - 1)$$

 

If $V_{DD}, |V_{SS}| < V_T$, the resistance is extremely high!!!

Switches (continues)

 


$$C_{GS,GD} = C_{OX} WL_D + \frac{1}{2} C_{OX} WL$$

$$C_{BS,BD} = \frac{1}{2} \frac{C_{j0} WL}{\sqrt{1 + \frac{2\phi_F}{V_{SB}}}} + C_{jBS}$$

$$\text{mobile - charge} = C_{OX} WL (V_{GS} - V_T)$$

 - **C_{GS} and C_{GD} are Linear polysilicon capacitors, introduce offset voltage.**
- **$C_{SB,DB}$ are non-linear capacitors, introduce harmonic distortion components.**
- **Mobile charge introduces gain errors and harmonic distortion components.**



Operational Transconductance Amplifier


PRACTICAL CONSIDERATIONS:

- **DC-gain.** The inverting input is not a real virtual ground. $v_{\text{invert}} = v_o / A_{\text{dc}}$


- **Settling time.** C1 must be discharged during phase 1. The main limitation is due to limited output current and phase margin.

- **Clock feedthrough.** Can be alleviated by using especial clocking schemes.

 - **Noise.** In most of the practical cases the dominant noise components are due to the Switches!!!



Switched-Capacitor Integrator Analysis

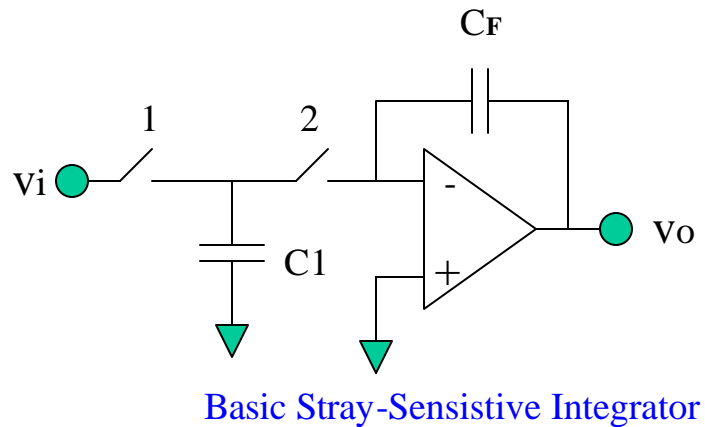


Charge conservation Principle:
 Charge injected by C1 is equal to the charge absorbed by CF ($\Delta Q_{C1} = \Delta Q_{CF}$)

$$\Delta V_0 C_F = -\Delta Q_{C1}$$


Phase 1 $t_0 < t \leq t_0 + T/2$

Phase 2 $t_0 + T/2 < t \leq t_0 + T$

 

$$\Delta V_0 = -\frac{C_1}{C_F} v_i(t_0 + NT/2)$$

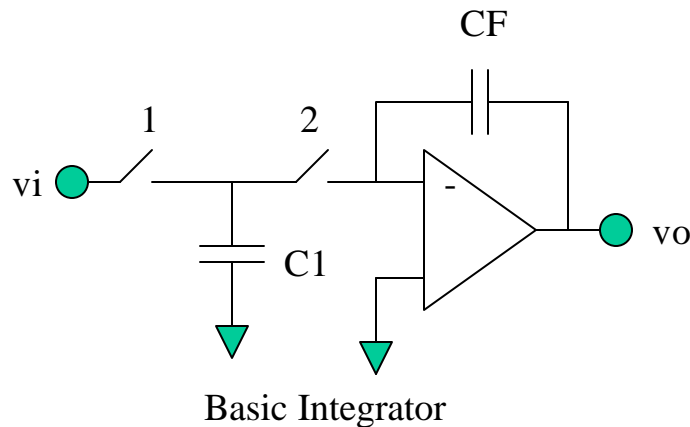Switched-Capacitor **Stray-Sensitive** Integrator Analysis



Phase 1 $t_0 < t \leq t_0 + T/2$

$$v_{C1}(t) = v_i(t)$$

$$v_{CF}(t) = v_{CF}(t_0)$$

$$v_{C1}(t_0 + NT/2) = v_i(t_0 + NT/2) \quad v_{CF}(t_0 + NT/2) = v_{CF}(t_0)$$

Phase 2 $t_0 + T/2 < t \leq t_0 + T$

Charge conservation Principle:


Charge injected by C1 is equal to the charge absorbed by CF ($DQ_{C1} = DQ_{CF}$)

$$[(0 - 0)C_1 - (v_i(t_0 + T/2) - 0)C_1] + [(0 - v_0(t))C_f - (0 - v_0(t_0 + T/2))C_f] = 0$$

Solving for phase 2 ($t=t_0+T$)

$$H(z) = -\frac{C_1}{C_f} \frac{z^{-1/2}}{1 - z^{-1}}$$

 Switched-Capacitor Integrators : Stray-Insensitive Integrators



Backward Integrator

Charge conservation ==> Phase 1

$$(v_i(nT) - 0)C_{in} + [(v_0(nT) - 0)C_f - (v_0(nT - T/2) - 0)C_f] = 0$$


Phase 2

$$0 = (v_0(nT - T/2) - 0)C_f - (v_0(nT - T) - 0)C_f$$

Solving for phase 1

$$v_i(nT)C_{in} - [v_0(nT) - v_0(nT - T)]C_f = 0$$
 
$$H(z) = -\frac{C_{in}}{C_f} \frac{1}{1 - z^{-1}}$$



Forward Integrator

Charge conservation ==> Phase 1

$$(0 - v_i(NT - T/2))C_{in} + [(v_0(nT))C_f - (v_0(nT - T/2))C_f] = 0$$

Phase 2


$$0 = C_f v_0(nT - T/2) - C_f v_0(nT - T)$$

$$v_{cin}(NT - T/2) = v_i(NT - T/2)$$


$$v_i(nT - T/2)C_{in} - [v_0(nT) - v_0(nT - T)]C_f = 0$$

$$H(z) = \frac{C_{in}}{C_f} \frac{z^{-1/2}}{1 - z^{-1}}$$

Switched-Capacitor Backward Integrator

 

Backward Integrator

 

phase 2

C_{in} is discharged ($v_{ci}=0$)
and v_{out} is constant

phase1

$$\Delta Q_{C_{in}} = C_{in} V_i$$

C_{in} is charged ($v_{ci}=v_i$)


$$\Delta Q_{C_f} = C_f (V_o(nT) - V_o(nT - T/2))$$

$$(v_i(nT) - 0)C_{in} + [(v_o(nT) - 0)C_f - (v_o(nT - T/2) - 0)C_f] = 0$$


or

$$v_o(nT) = v_o(nT - T) - \frac{C_{in}}{C_f} v_i(nT)$$

Switched-Capacitor Backward Integrator

 

Backward Integrator

 

phase 1

$$v_0(nT) = v_0(nT - T) - \frac{C_{in}}{C_f} v_i(nT)$$


$$H^{oo}(Z) = \frac{v_0^o(z)}{v_i^o(z)} = -\frac{C_{in}}{C_f} \frac{1}{1 - Z^{-1}}$$

phase2

$$v_0(nT + T/2) = v_0(nT)$$

$$H^{eo}(Z) = \frac{v_0^e(z)}{v_i^o(z)} = \frac{Z^{-1/2} v_0^o(z)}{v_i^o(z)} = -\frac{C_{in}}{C_f} \frac{Z^{-1/2}}{1 - Z^{-1}}$$

 Switched-Capacitor Integrators: Fundamental limitations



$$H(z=1) = \infty$$

dc gain


$$H(z=-1) = -C_{in}/C_f$$

Minimum gain


$$H^{oo}(Z) = -\frac{C_{in}}{C_f} \frac{1}{1 - Z^{-1}}$$

$$Z = e^{j\omega T}$$

| H(Z) behaves as an integrator for $f < f_s/4$

 

Backward (series) integrator: Why is stray insensitive???

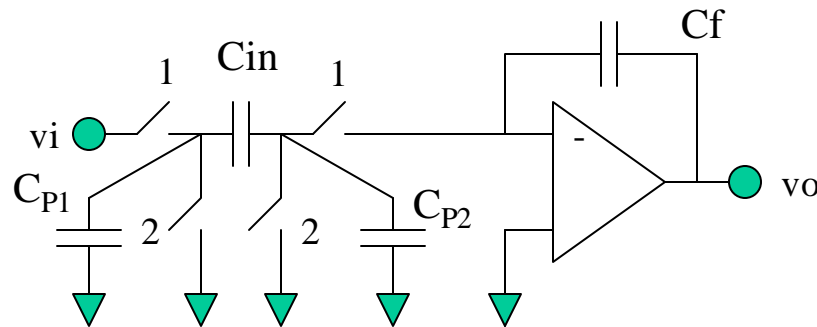

phase2

C_{in} , C_{P1} and C_{P2} are discharged
(initial conditons=0)

phase 1

C_{in} and C_{P1} are connected to V_i
 C_{P2} is connected to the virtual
ground (initial conditons=0)


NOTE THAT

- **CP1 IS CHARGED BY v_i**
- **CP2 IS CONNECTED TO GROUND OR VIRTUAL GROUND** (provided that the gain of the OPAM is large enough)

- **BOTH CP1 AND CP2 DO NOT INJECT ANY CHARGE TO CF.**

$$H^{oo}(Z) = \frac{v_0^o(z)}{v_i^o(z)} = -\frac{C_{in}}{C_f} \frac{1}{1-Z^{-1}}$$

Why SC-Circuits are important??

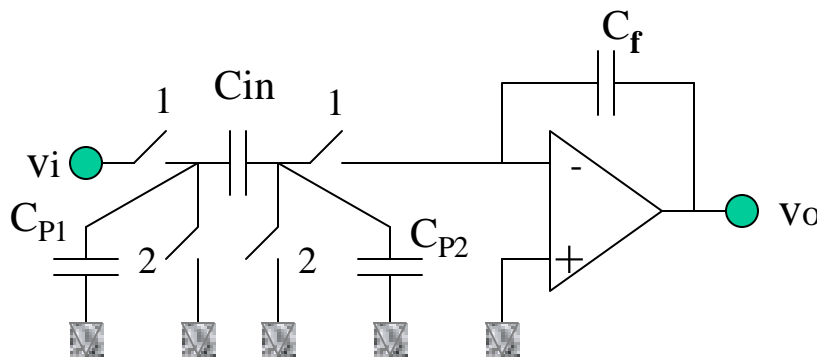

- **Little sensitive to parasitics** (due to the use of local feedback)



- **High precision (0.2-1 %)** (function of capacitor ratios and clock frequency)

$$H^{00}(Z) = - \left[\frac{C_{in}}{C_f} \right] \frac{1}{1 - Z^{-1}}$$

- **Reduced Silicon-Area** (double poly or metal-metal capacitors can be easily implemented in CMOS).

- **OPAMPS (VCVS) ARE NOT REQUIRED; OTAS ARE FASTER** (Resistors are simulated by switches and capacitors).

 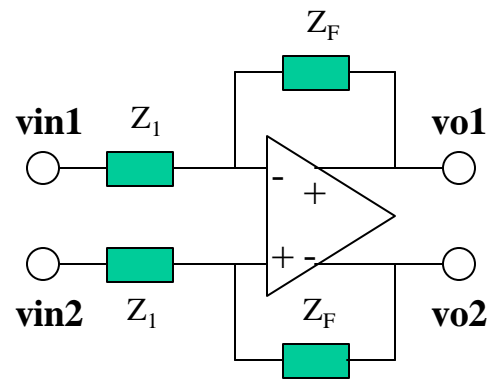
Fully-Differential Filters: CMFB Principle



$$v_{cm} = \frac{v_{o1} + v_{o2}}{2}$$

- A common-mode feedback loop must be used.
- **BASIC IDEA:** A circuit with very small impedance for the common-mode signals but be transparent for the differential signals.
- Differential GBW similar to the GBW of the CMFB
- Minimum power consumption

 Fully-Differential Filters: CMFB Principles




- A voltage controlled current source in a unity gain configuration represents a grounded impedance.


BASIC PRINCIPLE:

- The loop works for the common-mode signals.
- Ideally, the differential signals are not sensed

| **common-mode impedance=1/gm**

 

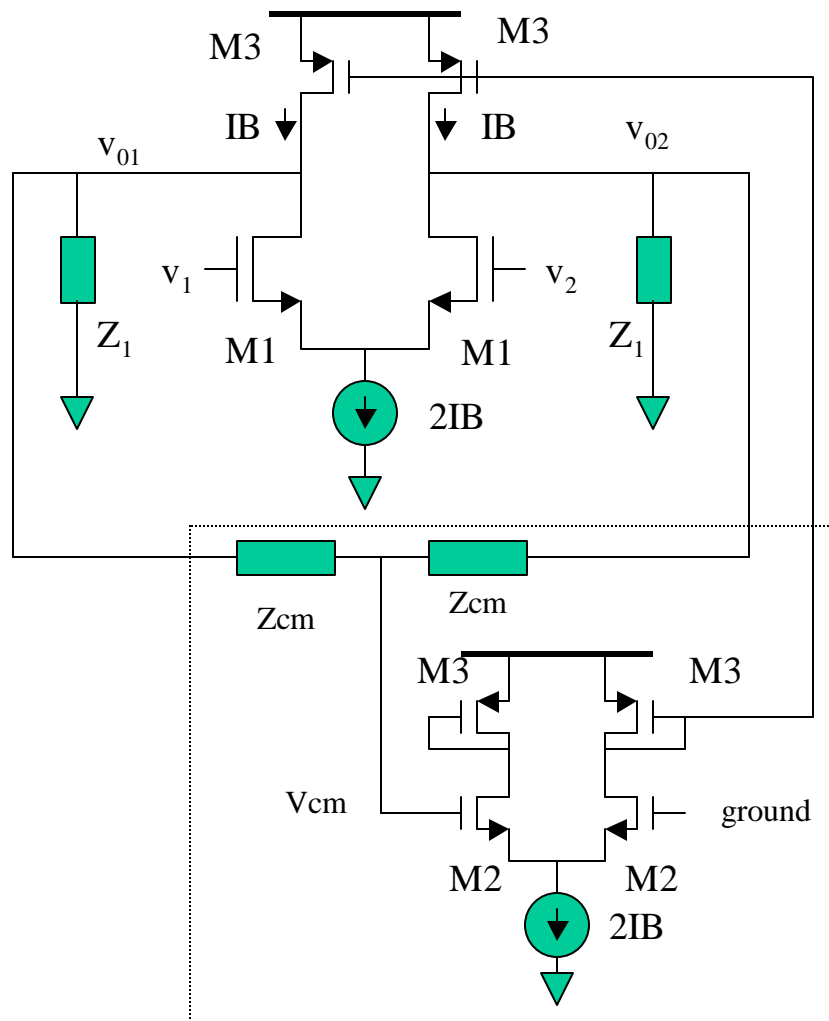Fully-Differential Filters: CMFB Principles




CMFB Characteristics:

- | Transconductance gain= $g_{m2}/2$
- | dominant pole at the output
- | At least 2 additional poles in the loop
- | Z_{cm} reduces the OTA dc gain, affecting the differential gain
- | NOTE THAT V_{cm} IS FORCED TO THE GROUND LEVEL.
- | **DC OFFSET IS AROUND I_{off}/g_{m2}**

CMFB

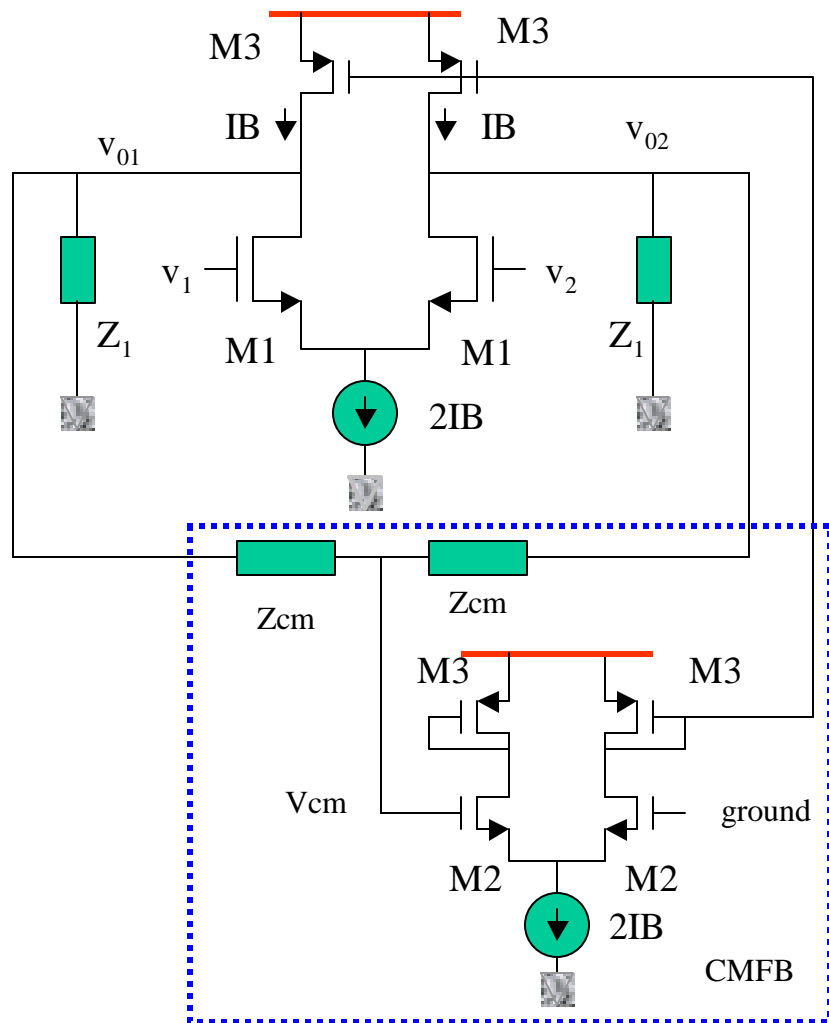
Fully-Differential Filters: CMFB Principles




Common-mode stability:

- 1 pole at vcm ($1/RC$)
- 1 pole at gate of M3 (g_{m3}/C_{P3})
- 1 pole at the output (g_{o1}/C_1)

$| \text{dc gain} = g_{m2}R_{o1}$

 


Fully-Differential Filters: OPAMP

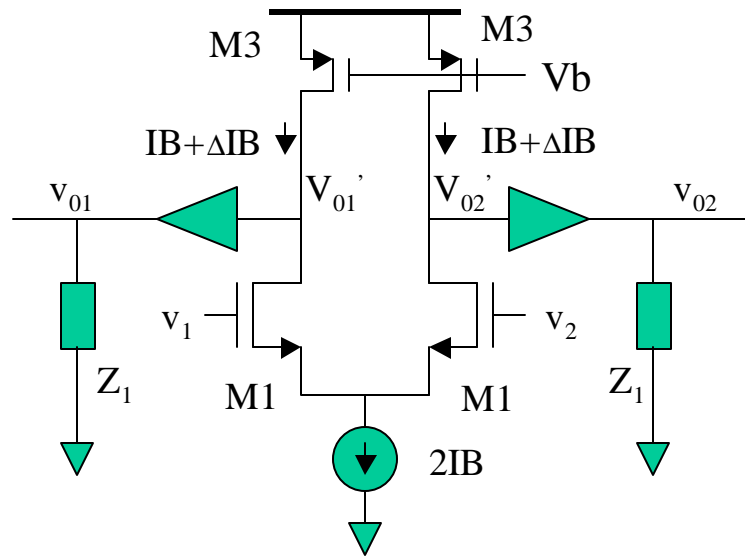

If ΔIB is positive transistors M3 eventually will be biased in triode region (small resistance)


- dc gain is drastically reduced
 - THD increases
 - The common-mode output impedance is the parallel of the equivalent output resistance (M1 and M3) and the parasitic capacitors. For large dc gain, the output impedance at nodes v_{01}' and v_{02}' are further increased.
- ΔIB produces a dc offset of $R_{out} \Delta IB$.

Fully-Differential Filters: OP AMP

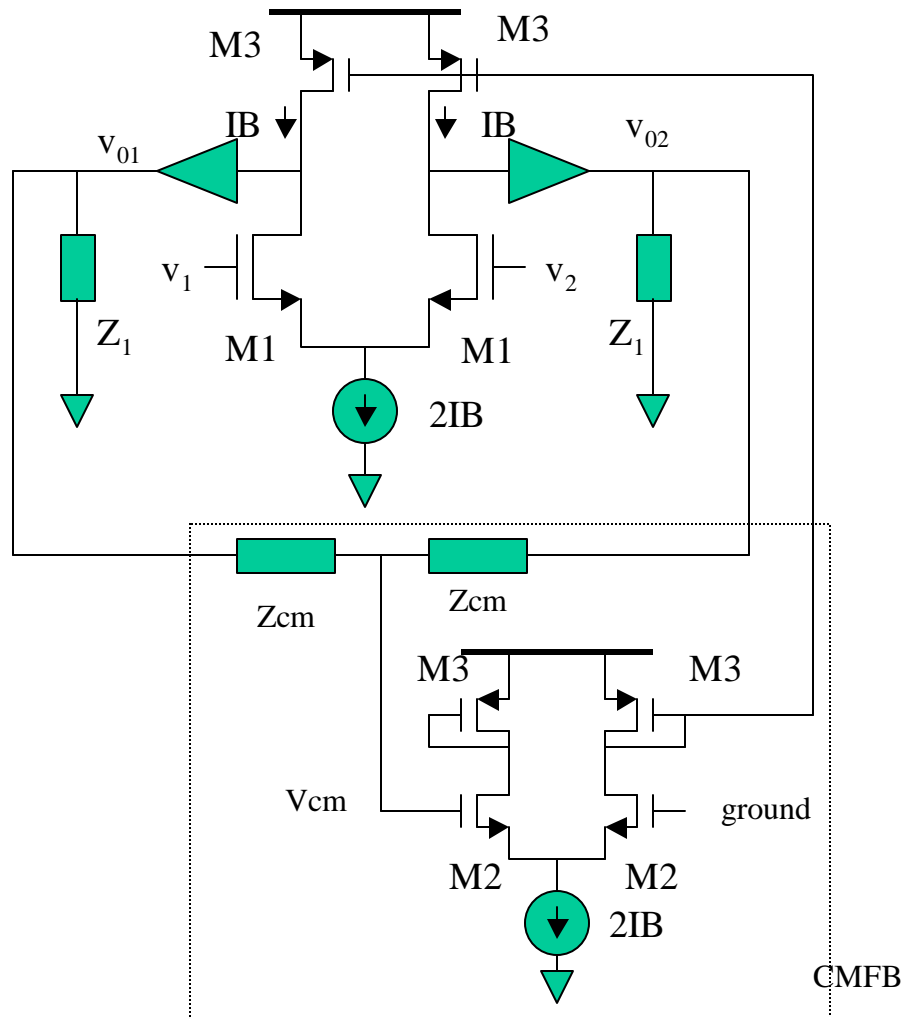

The stability conditions are exactly the same for OTA's and OPAMP's:


 
- 1 pole at v_{cm} ($1/RC$)
- 1 pole at gate of $M3$ (g_{m3}/C_{P3})
- 1 pole at the output (g_{o1}/C_1)
- **In OPAMP's you can use resistors as common-mode detector due to the buffers**
- $dc\ gain = g_{m2}R_{o1}$




Pseudo-Differential SC Amplifier

$$V_{OUT} = (C_1/C_2) V_{IN}$$

 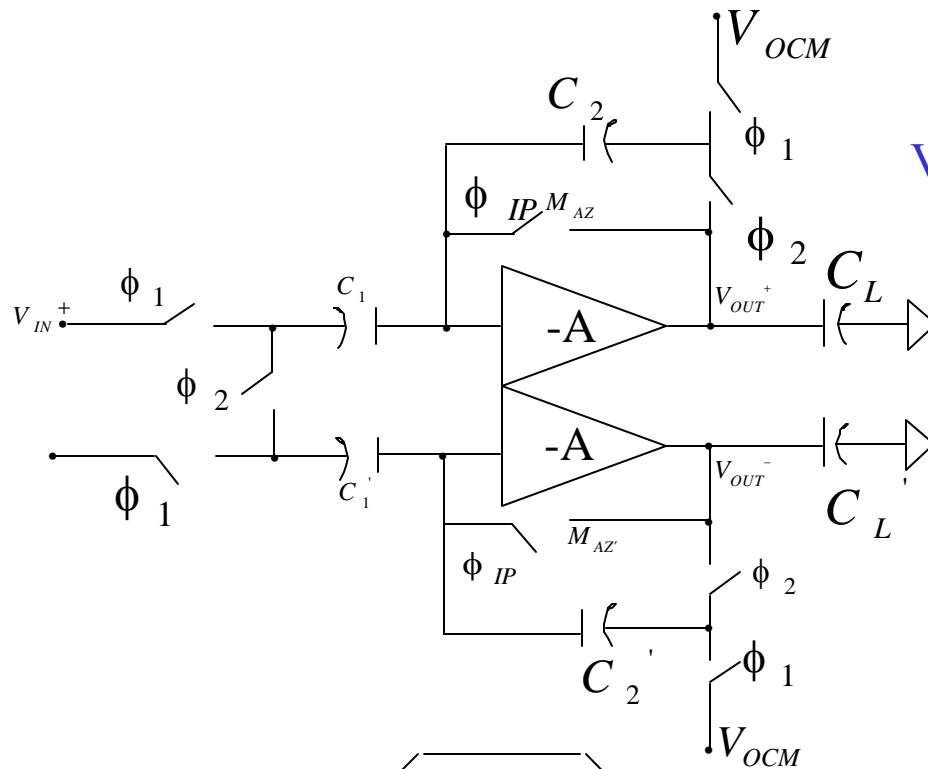
$$V_{OUT}/V_{IN} = (C_1/C_2) / (1 + (C_1 + C_2)/AC_2)$$



 


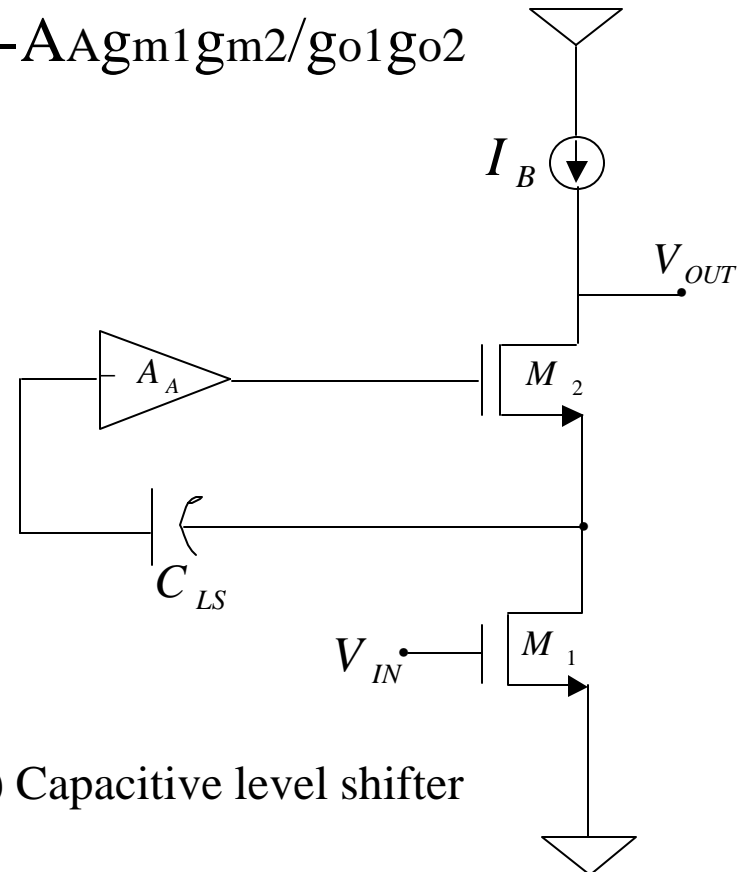
(a) Cascode transconductor with gain enhancement

$$A = -A_A g_{m1} g_{m2} / g_{o1} g_{o2}$$





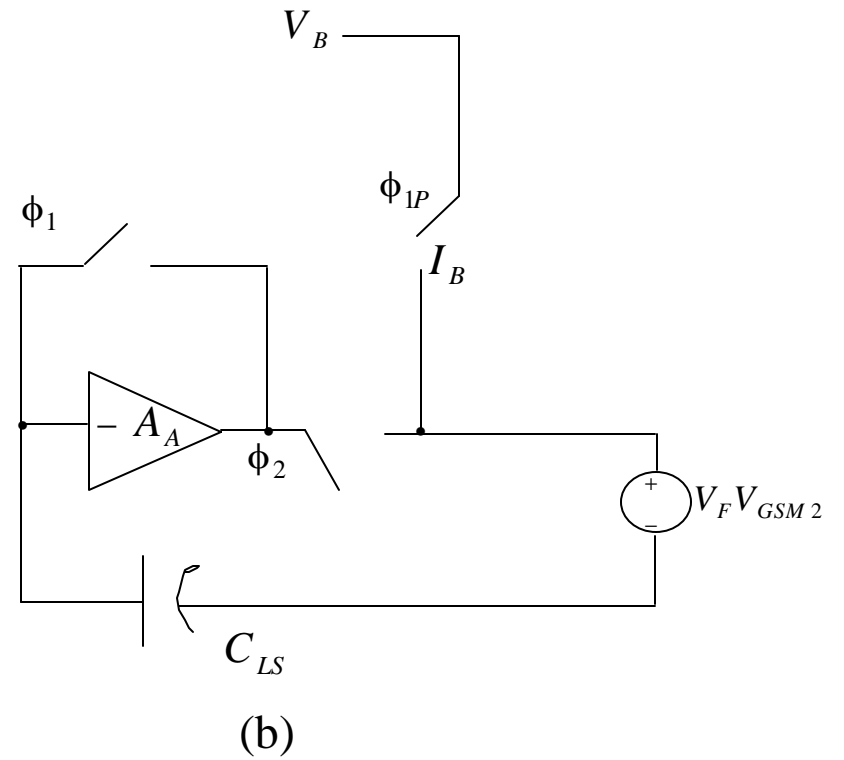 (b) Capacitive level shifter


Cascode transconductor with gain-enhancement



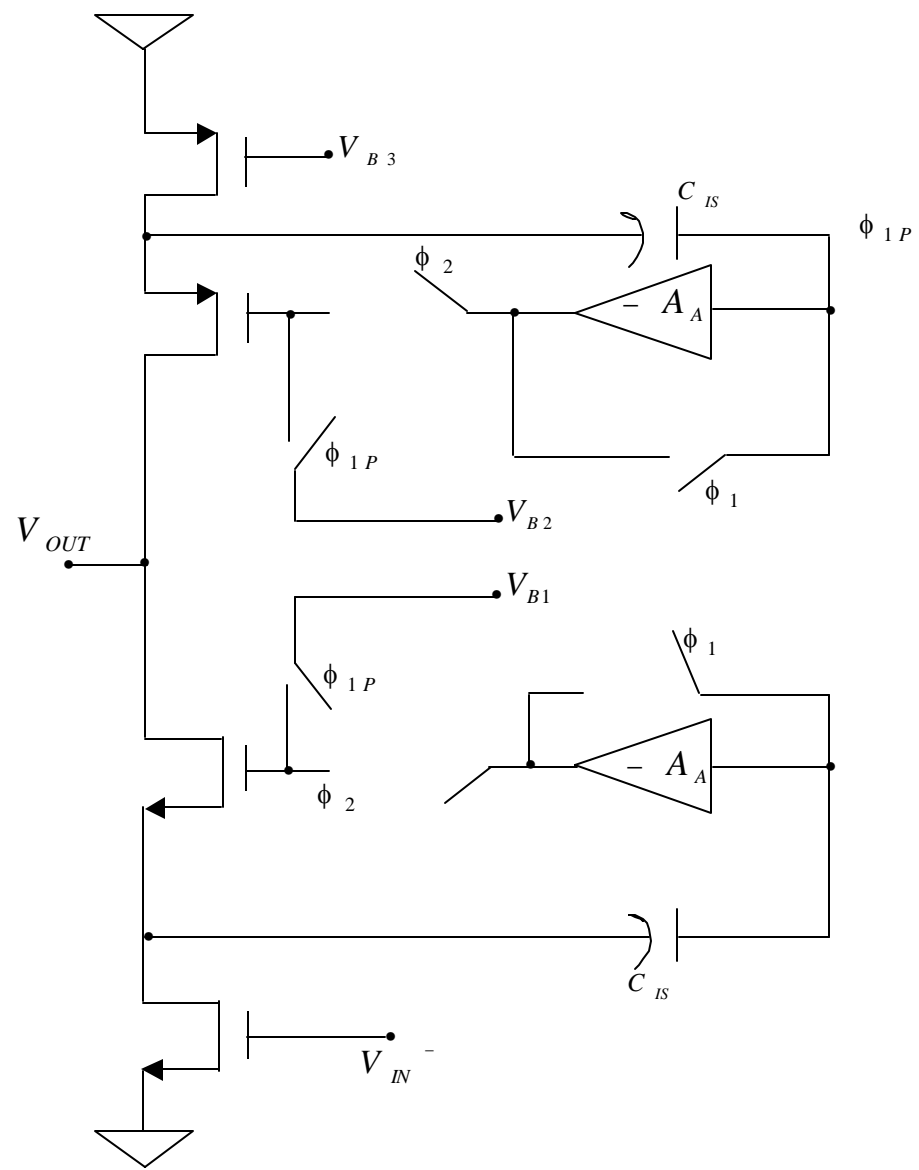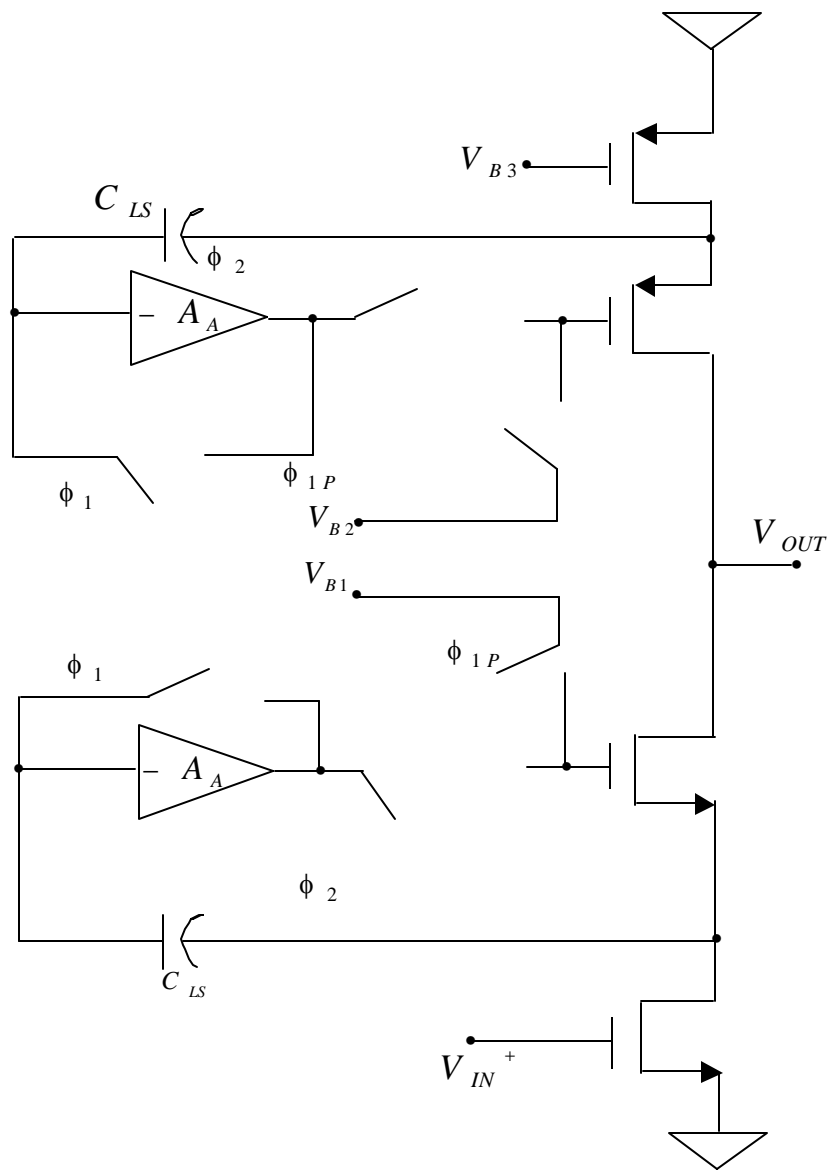Proposed capacitive level-shifting scheme



(a)

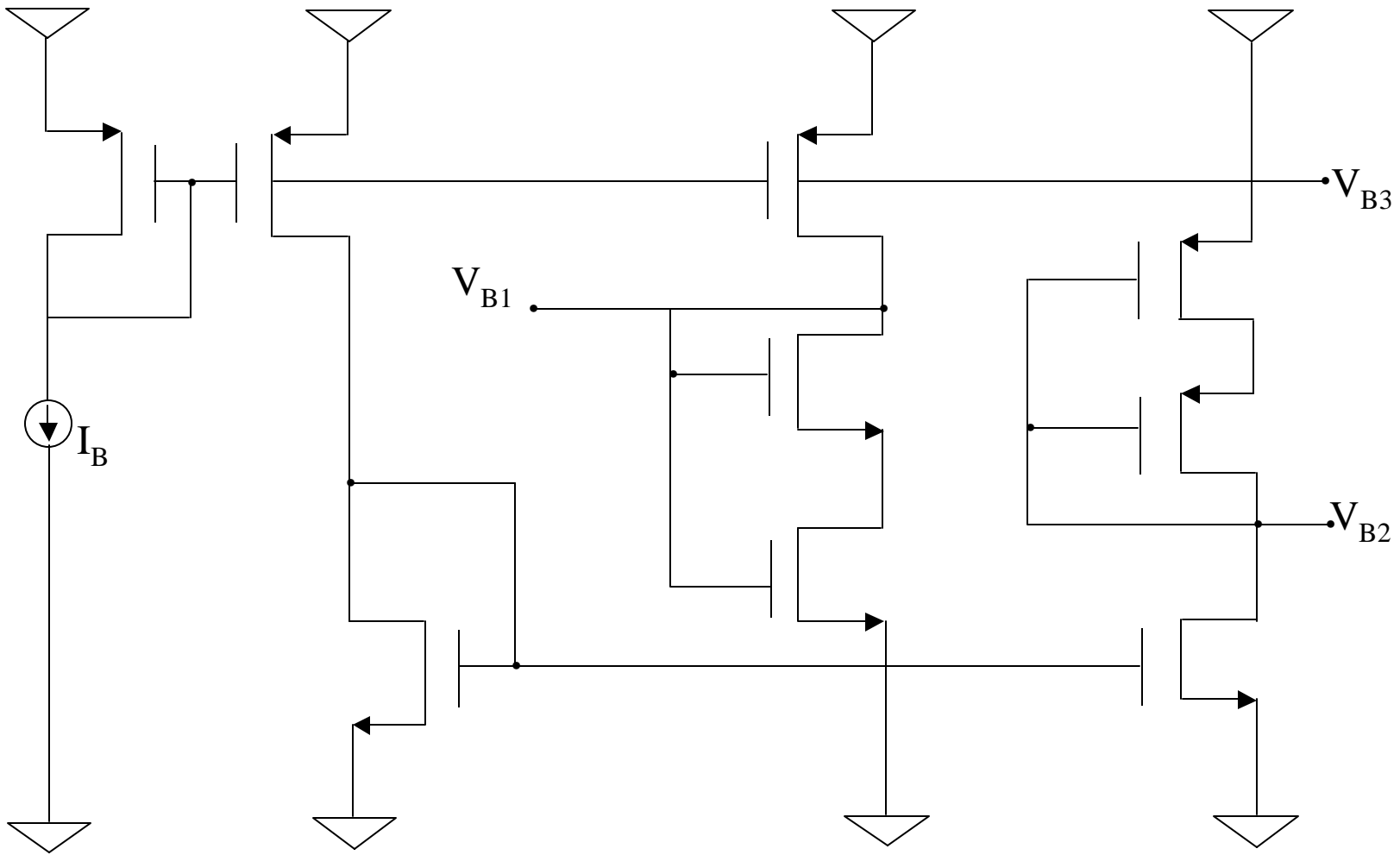


(b)

Fig. 4 (a) Pseudo-Differential core amplifier and (b) the biasing circuit

TABLE I
SUMMARY OF SIMULATED PERFORMANCE

Power Supply	1.8V
Supply Current	1.25mA
Open-Loop Gain	>100dB
U.G. Frequency	135MHz
Phase Margin	56°
Input Noise	22nV(Hz) ^{1/2}
Closed-Loop Gain	2
Gain Error	<.05%
Max. Sampling Rate	5MS/sec.
Differential Swing	1.6V

 

 


Fig.7. Settling behavior of the differential and single-ended outputs ($V_{DD}=1.8V$, $V_{IN}=800mV$).

 


Fig.8. Settling behavior of the differential and single-ended outputs ($V_{DD}=1.5V$, $V_{IN}=100mV$).

 


Fig.9. The frequency spectrum of the differential output.

References:

[1] The Circuits and Filters Handbook (chapter 81), Wai-Kai Chen, Editor, CRC and IEEE-Press, 1995.

[2] Analog Integrated Circuits and Systems, D. A. Johns and K. Martin, McGraw-Hill, 1997.

[3] Low-Voltage Low Power Integrated Circuits, E. Sánchez-Sinencio and A. Andreou, IEEE Press, 1999

[4] Switched Capacitor Circuits, P. E. Allen and E. Sánchez-Sinencio, Van Nostrand and Reinhold Co. 1984