



TRANSCONDUCTANCE AMPLIFIER TOPOLOGIES AND NON-IDEALITIES



- **Architectures and Macromodels***
- **Linearized OTAs**
- **OTA Non-Idealities**

}	Input impedance
	Frequency dependent transconductance
	Non-linear transconductance
	Output impedance
- Applications, i.e., OTA-C
Filters, Oscillators, and VGA

* Reference :

E. Sánchez-Sinencio and M.L. Majewski, " A Nonlinear Macromodel of Operational Amplifiers in the Frequency Domain", *IEEE Trans. Circuits and Systems* , Vol. CAS-26, No.6, pp 395-402, June 1979


OPERATIONAL TRANSCONDUCTANCE AMPLIFIER

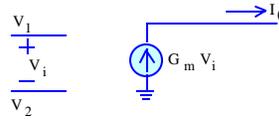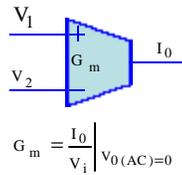

IDEAL MODEL


$$G_m = \frac{I_0}{V_i} \Big|_{V_0(AC)=0}$$

How do you simulate G_m ?

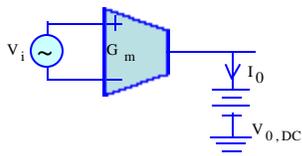


Φ_E is the phase difference between the actual G_m phase and the ideal phase.

$$\omega_p = 2\pi f_{3dB}$$

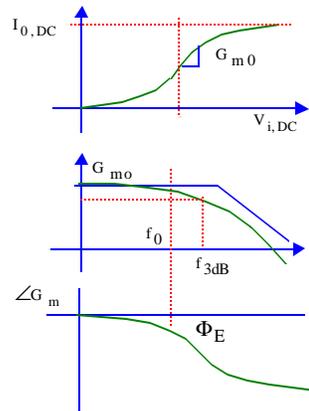


A Linear CMOS OTA Macromodel

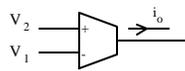

$$g_m = \frac{g_{m0}}{1 + \frac{s}{\omega_p}} \quad ; \quad \omega_p = \frac{1}{R_1 C_p}$$




OTA Macromodel Representation

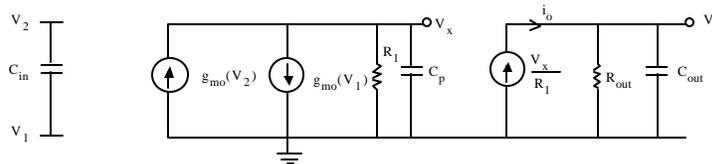

Real OTA Macromodel

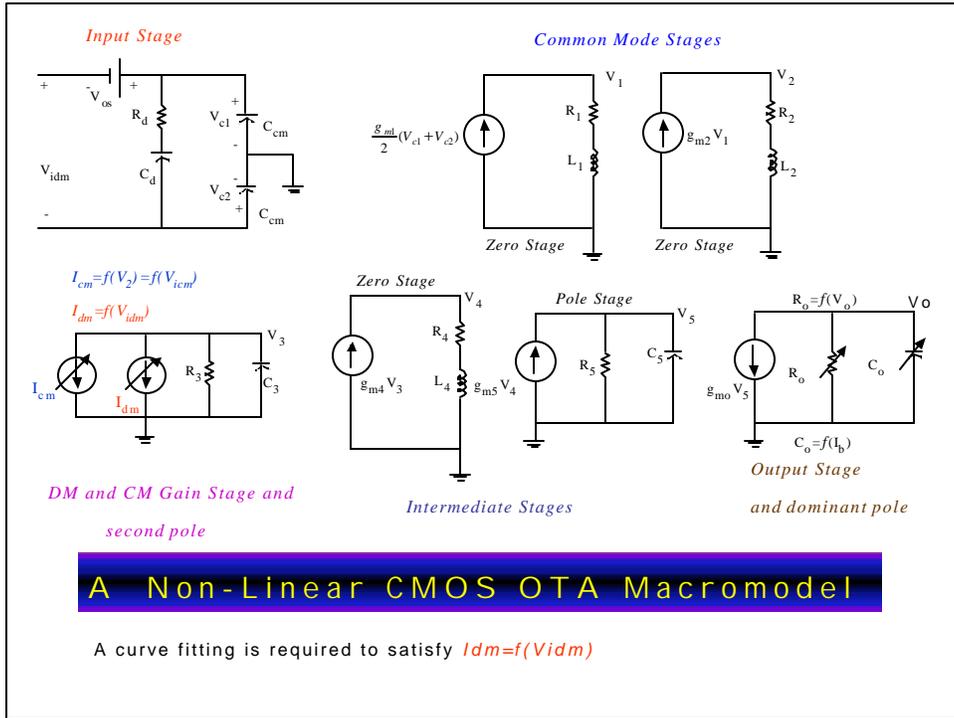Reference:
A nonlinear macromodel for CMOS OTAs Gomez, G.J.; Embabi, S.H.K.; Sanchez-Sinencio, E.; Lefebvre, M. Circuits and Systems, 1995. ISCAS '95., 1995 IEEE International Symposium on Volume: 2, 1995 Page(s): 920 -923 vol.2




CALCULATED PARAMETER VALUES FOR NON-LINEAR MACROMODEL

Element	Value
C_{cm}	27.88 fF
C_d	72.70 fF
R_d	2128.50 Ω
$R_1 = R_2 = R_3 = R_4 = R_5$	1K Ω
$g_{m1} = g_{m2} = g_{m3} = g_{m4} = g_{m5}$	1mmhos
L_1	125.60 μ H
L_2	57.38 μ H
C_3	2.83 pF
L_4	Not used
C_5	2.05 pF
R_o	2.17M Ω
C_o	109.88 fF
I_{dm}	$g_{m1m} = 590.04 \mu$ A/V
I_{cm}	$g_{mcm} = 56.41 \eta$ A/V
V_{os}	-1.44mV



SIMULATION DATA

Parameter	Simulated Value
$G_{m,dm}$ DM Transconductance	596.04 $\mu\text{A/V}$
$G_{m,cm}$ CM Transconductance	56.41 $\mu\text{A/V}$
$A_{v,dm}$ DM V/V Gain @ DC	1239.40 @ 62.2dB
CMRR CM Rejection Ratio	10565.95 @ 80.4dB
$R_{o,cm}$ Output Resistance	2.17M Ω
$\angle F_x$ Phase Error @ 1MHz	1.75°
ω_{p1} Dom. Pole (2 μf_{p1})	2 $\mu\text{f}666.95 \text{ KHz}$
ω_{p2} 2 nd pole (2 μf_{p2})	2 $\mu\text{f}56.16 \text{ MHz}$
ω_{p3} 3 rd pole (2 μf_{p3})	2 $\mu\text{f}77.69 \text{ MHz}$
ω_{z1} Zero (2 μf_{z1})	2 $\mu\text{f}77.94 \text{ MHz}$
$\omega_{z,cm1}$ 1 st CMZero (2 $\mu\text{f}_{z,cm1}$)	2 $\mu\text{f}813.67 \text{ KHz}$
$\omega_{z,cm2}$ 2 nd CMZero (2 $\mu\text{f}_{z,cm2}$)	2 $\mu\text{f}2.77 \text{ MHz}$
Z_{dm} DM Z_{in} @ Real part	1112.10 Ω
Z_{dm} DM Z_{in} @ Imag.	-1.58 E09
Z_{cm} CM Z_{in} @ LF	2.85 E09
$\angle Z_{cm}$ CM Z_{in} Phase	90°

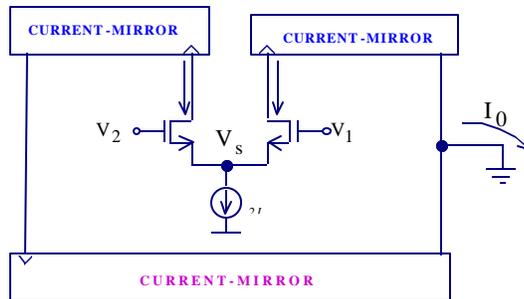Basic OTA (three current-mirrors): Non-linearity



$$\begin{aligned}
 \left. \begin{aligned} I_1 &= \beta(V_1 - V_s - V_T)^2 \\ I_2 &= \beta(V_2 - V_s - V_T)^2 \\ I_1 + I_2 &= I_{SS} \end{aligned} \right\} \Rightarrow V_s = \frac{V_1 + V_2 - 2V_T}{2} \pm \sqrt{\frac{I_{SS}}{2\beta} - \left(\frac{\Delta V}{2}\right)^2} \quad \begin{aligned} \beta &= \frac{\mu C_{ox} W}{2L} \\ g_m &= \sqrt{2I_{SS}\beta} \end{aligned} \\
 I_0 = I_1 - I_2 &\Rightarrow I_0 = \Delta V \sqrt{2I_{SS}\beta} \sqrt{1 - \frac{\beta}{2I_{SS}} (\Delta V)^2}
 \end{aligned}$$

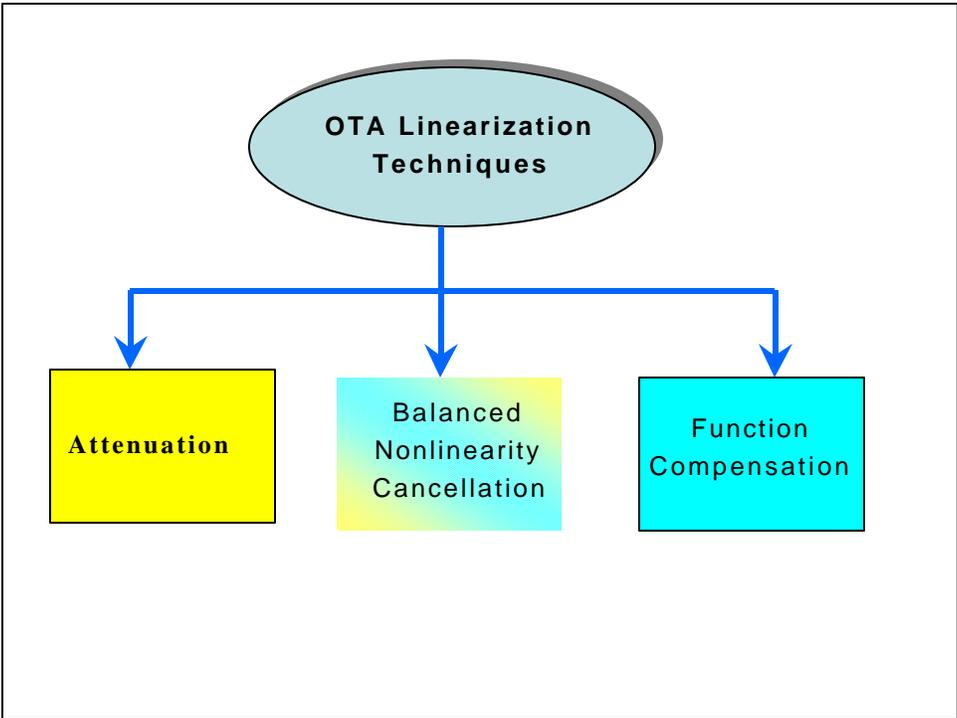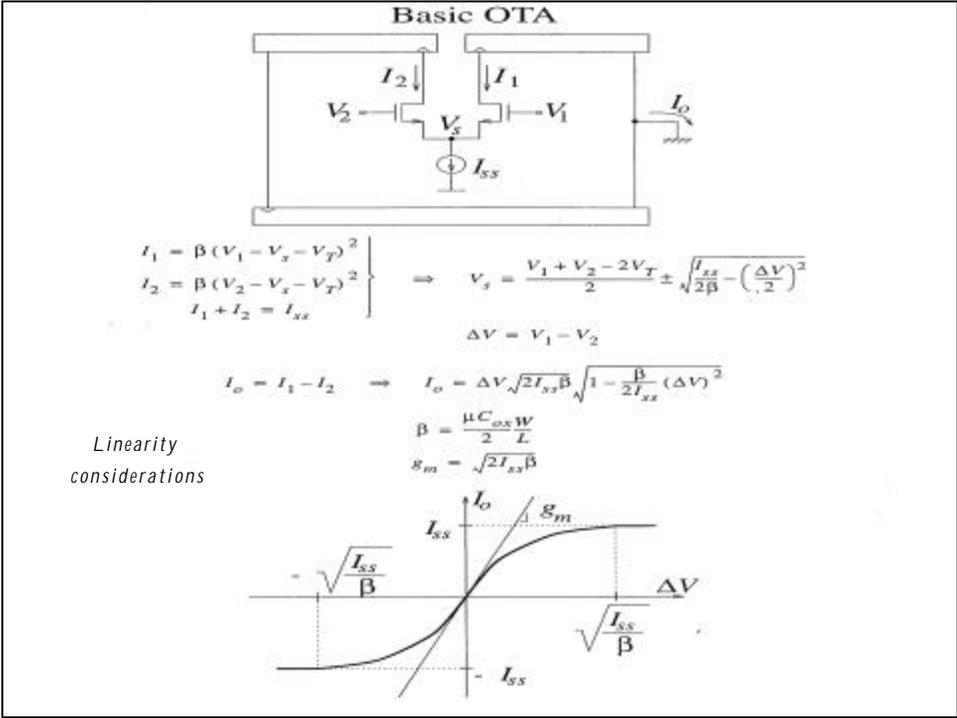

Remarks on Linearization Techniques

ATTENUATION


- > Overall Gm is reduced by the attenuation factor a
- > Non-idealities of the attenuation network affect the overall transconductance amplifier performance
- > Relative input noise increase by a
- > Input offset is proportional to a
- > Dynamic range can be modified via tradeoffs.

Balanced Nonlinearity Cancellation

Type I :

$$V_{in}^+ = V_1 = V_A + V/2$$

$$V_{in}^- = V_2 = V_A - V/2$$

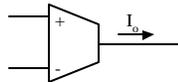

$$\begin{aligned}
 I_0(V_1, V_2) &= \sum_{i=1}^{\infty} a_i (V_1^i - V_2^i) \\
 &= a_1 (V_1 - V_2) + a_2 (V_1^2 - V_2^2) \\
 &\quad + a_3 (V_1^3 - V_2^3) + \dots
 \end{aligned}$$

$$\begin{aligned}
 I_0(V) &= V(a_1 + 2a_2 V_A + 3a_3 V_A + \dots) \\
 &\quad + \frac{1}{4} V^3 (a_3 + 4a_4 V_A + 10a_5 V_A + \dots) \\
 &\quad + \frac{1}{16} V^5 (a_5 + 6a_6 V_A + \dots)
 \end{aligned}$$


For small a_3, a_4, a_5, \dots

$$I_0 \cong g_m V$$

where

$$g_m = a_1 + 2a_2 V_A^1 + 3a_3 V_A^2 + \dots$$

Balanced Nonlinearity Cancellation

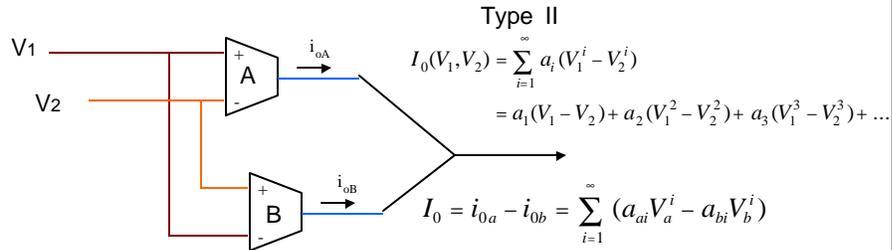

Particular cases:

For matched transconductors


$$a_{ai} = a_{bi} = a_i$$

$$V \equiv V_1 - V_2$$

$$I_0 = 2(a_1V + a_3V^3 + a_5V^5 + \dots)$$

Assume each OTA has the following type II non-linearity description:

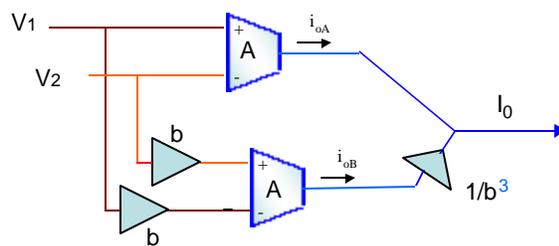
$$i_{oA} = A V_{in} (1 - a V_{in}^2) = a_1 V_{in} - a_2 V_{in}^3$$



Equal Transconductance gains can be used, but one of them modified at the input and output. Then the linearized output current yields:


$$I_o = A \left(1 - \frac{1}{b^2}\right) V_{in}$$

Function Compensation

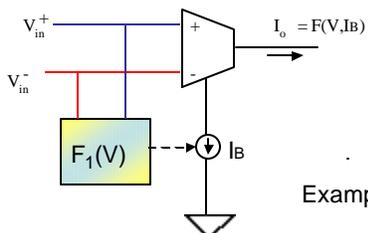

Let $I_B = F_1(V) + I_o$
 Then $I = F[V, F_1(V) + I_o]$
 Pick F_1 such that
 $I = V F_2(I_o)$

Example:

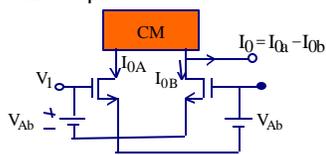


Balanced Configuration

Nedungadi Transconductor

[A. Nedungadi and T. R. Viswanathan, "Design of Linear CMOS Transconductor Elements," IEEE Transactions on Circuits and Systems, vol. CAS-31, No. 10, pp. 891-894, October 1984]

Unbalanced Differential Pair

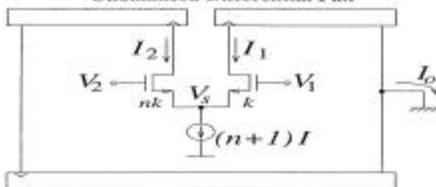

$$\begin{cases} I_1 = k(V_1 - V_s - V_T)^2 \\ I_2 = nk(V_2 - V_s - V_T)^2 \\ I_1 + I_2 = (n+1)I \end{cases} \Rightarrow V_s^2 - 2V_s \left(\frac{V_1 + nV_2}{n+1} - V_T \right) + \frac{(V_1 - V_T)^2 + n(V_2 - V_T)^2}{n+1} = \frac{I}{k}$$

$$V_s = \frac{V_1 + nV_2 - (n+1)V_T}{n+1} - \sqrt{\frac{I}{k} \frac{n\Delta V^2}{(n+1)^2}} \Rightarrow$$


$$\Rightarrow \begin{cases} I_1 = k \left[\frac{n\Delta V}{n+1} + \sqrt{\frac{I}{k}} \sqrt{1 - \frac{kn\Delta V^2}{(n+1)^2 I}} \right]^2 \\ I_2 = nk \left[\frac{-\Delta V}{n+1} + \sqrt{\frac{I}{k}} \sqrt{1 - \frac{kn\Delta V^2}{(n+1)^2 I}} \right]^2 \end{cases}$$

Range:

$$\begin{cases} I_1 = (n+1)I \\ I_2 = 0 \end{cases} \Rightarrow \Delta V = \sqrt{\frac{I}{k}(n+1)}$$


$$\begin{cases} I_1 = 0 \\ I_2 = (n+1)I \end{cases} \Rightarrow \Delta V = -\sqrt{\frac{I}{k}\left(1 + \frac{1}{n}\right)}$$

The Cross-Coupled Quad Transconductor

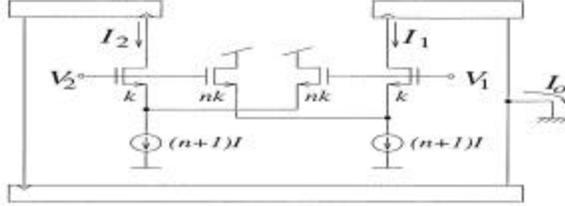

$$\begin{aligned}
 I_1 &= k \left[\frac{n\Delta V}{n+1} + \sqrt{\frac{I}{k}} \sqrt{1 - \frac{kn\Delta V^2}{(n+1)^2 I}} \right]^2 \\
 I_2 &= k \left[\frac{-n\Delta V}{n+1} + \sqrt{\frac{I}{k}} \sqrt{1 - \frac{kn\Delta V^2}{(n+1)^2 I}} \right]^2 \\
 \Rightarrow I_0 = I_1 - I_2 &\Rightarrow \begin{cases} I_0 = g_m \Delta V \sqrt{1 - \beta \Delta V^2} \\ g_m = \frac{4n}{n+1} \sqrt{Ik} \quad , \quad \beta = \frac{k}{I} \frac{n}{(n+1)^2} \end{cases} \\
 \text{Range: } |\Delta V| &\leq \sqrt{\frac{I}{k} \left(1 + \frac{1}{n}\right)} \\
 \text{For } \Delta V = \sqrt{\frac{I}{k} \left(1 + \frac{1}{n}\right)} &\Rightarrow I_0 = \frac{4n}{n+1} I
 \end{aligned}$$

Squarer

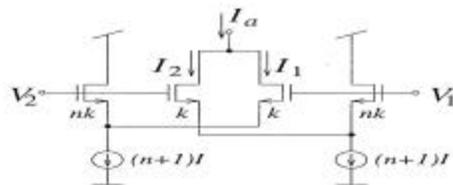

$$\begin{aligned}
 I_1 &= k \left[\frac{n\Delta V}{n+1} + \sqrt{\frac{I}{k}} \sqrt{1 - \frac{kn\Delta V^2}{(n+1)^2 I}} \right]^2 \\
 I_2 &= k \left[\frac{-n\Delta V}{n+1} + \sqrt{\frac{I}{k}} \sqrt{1 - \frac{kn\Delta V^2}{(n+1)^2 I}} \right]^2 \\
 \Rightarrow I_a = I_1 + I_2 &= 2k \frac{n(n-1)}{(n+1)^2} \Delta V^2 + 2I \quad , \quad \Delta V \leq \sqrt{\frac{I}{k} \left(1 + \frac{1}{n}\right)}
 \end{aligned}$$

Nedungadi Transconductor

Transistors M1 and M2 form a simple differential pair biased by

$$I_{ss} = aI - (aI - I_o) = I_o = 2k \frac{n(n-1)}{(n+1)} \Delta V^2 + 2I$$

Consequently,

$$I_o = \Delta V \sqrt{2kI_{ss} - k^2 \Delta V^2} = \Delta V \sqrt{k^2 \Delta V^2 \left(4\gamma \frac{n(n-1)}{(n+1)^2} \right) + 4kI} \quad \gamma = \frac{k}{k'}$$

If $4\gamma n(n-1) - (n+1)^2 = 0 \Rightarrow I_o = 2\Delta V \sqrt{kI} \quad \left\{ \begin{array}{l} s_m = 2\sqrt{kI} \\ |\Delta V| \leq \min \left(\sqrt{\frac{I}{k}} \left(1 + \frac{1}{n} \right), 2\sqrt{\frac{I}{k}} \right) \end{array} \right.$

Examples:

$$\gamma = 1 \Rightarrow n = 1 + \frac{2\sqrt{3}}{3} = 2.155$$

$$n = 3 \Rightarrow \gamma = \frac{(n+1)^2}{4n(n-1)} = \frac{2}{3}$$

$$aI - I_o \geq 0 \Leftrightarrow \left\{ \begin{array}{l} \Delta V_{max}^2 = \frac{I}{k} \left(\frac{n+1}{n} \right) \rightarrow a \geq \frac{4n}{n+1} \\ \Delta V_{max}^2 = \frac{I}{k} \rightarrow a \geq 2 \left[\frac{(1+4\gamma)n^2 + 2n(1-2\gamma) + 1}{(n+1)^2} \right] \end{array} \right.$$

Distortion Analysis

$i_d = i_d(v_{in})$ Suppose that i_d is a non-linear function, then

$$i_d = I_D + \frac{\partial i_d}{\partial v_{in}} \Big|_Q v_{in} + \frac{1}{2} \frac{\partial^2 i_d}{\partial v_{in}^2} \Big|_Q v_{in}^2 + \frac{1}{6} \frac{\partial^3 i_d}{\partial v_{in}^3} \Big|_Q v_{in}^3 + \dots$$

for $v_{in} = V \sin(\omega t)$

$$i_d \cong I_D + \frac{1}{4} \frac{\partial^2 i_d}{\partial v_{in}^2} \Big|_Q V^2 + \frac{\partial i_d}{\partial v_{in}} \Big|_Q V \sin(\omega t) + \frac{\partial^3 i_d}{\partial v_{in}^3} \Big|_Q \frac{V^3}{8} + \dots$$

$$+ \frac{1}{4} \frac{\partial^2 i_d}{\partial v_{in}^2} \Big|_Q V^2 \sin(2\omega t) + \frac{1}{24} \frac{\partial^3 i_d}{\partial v_{in}^3} \Big|_Q V^3 \sin(3\omega t) + \dots$$

CONTINUOUS-TIME FILTERS


Transconductance $g_m = \frac{\partial i_d}{\partial v_{in}} \approx \frac{\partial i_d}{\partial v_{in}} \Big|_Q + \frac{\partial^2 i_d}{\partial v_{in}^2} \Big|_Q \frac{V^2}{8} + \dots$

Second Harmonic Distortion $HD_2 \approx \frac{1}{4} \frac{\frac{\partial^2 i_d}{\partial v_{in}^2}}{\frac{\partial i_d}{\partial v_{in}}} \Big|_Q V$


Third Harmonic Distortion $HD_3 \approx \frac{1}{24} \frac{\frac{\partial^3 i_d}{\partial v_{in}^3}}{\frac{\partial i_d}{\partial v_{in}}} \Big|_Q V^2$

Third Intermodulation Distortion $IM_3 = 3 * HD_3$

Differential Pair as a V-I converter

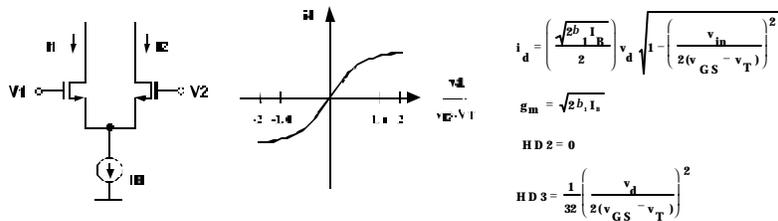

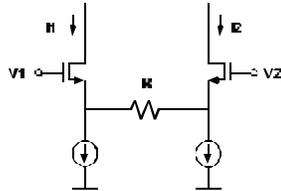Differential Pair with Source Degeneration




$$n = \frac{1}{1 + g_m R}$$

$$i_d = \left(\frac{\sqrt{2} b_1 B}{2} \right) \frac{v_d}{n} \sqrt{1 - \left(\frac{v_{in}}{2n(V_{GS} - V_T)} \right)^2}$$

HD 2 = 0 **Ideally**

$$HD 3 = \frac{1}{32 n^2} \frac{v_{in}^3}{(V_{GS} - V_T)^2}$$

BASIC INTEGRATOR: Fundamental Equations

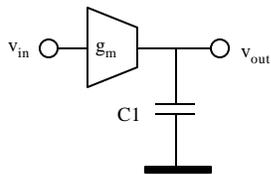

$$g_m \cong \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_T) \cong \sqrt{2 \mu_n C_{OX} \frac{W}{L} I_D}$$

$$HD3 \cong \frac{1}{32} \left(\frac{V_{in}}{V_{GS} - V_T} \right)^2$$

Mobility degradation:


$$\mu_n \cong \left(\frac{\mu_0}{1 + \theta (V_{GS} - V_T)} \right) \left(\frac{1}{1 + \frac{\theta V_{in}}{1 + \theta (V_{GS} - V_T)}} \right)$$

$$HD3 \cong \frac{1}{4} \left(\frac{\theta V_{in}}{1 + \theta (V_{GS} - V_T)} \right)^2$$

NOISE:

$$v_n^2 = \frac{16kT}{3g_m} (1 + NF)$$

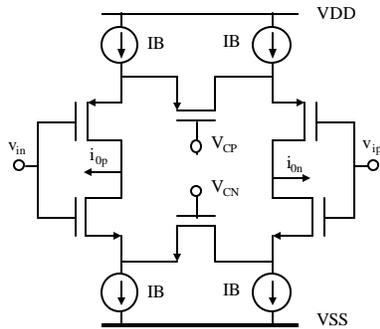OTA based on Complementary Differential Pairs



TRANSCONDUCTANCE:

$$G_m = \frac{g_{mn}}{1 + N_N} + \frac{g_{mp}}{1 + N_P}$$

DISTORTION:

$$HD3 \cong \frac{1}{32} \left(\frac{V_{in}}{(V_{GS} - V_T)(N+1)} \right)^2$$


OUTPUT RESISTANCE:

$$R_{out} \approx \frac{g_{mn} r_{on} R_N}{2} \parallel \frac{g_{mp} r_{op} R_P}{2}$$



DC GAIN:

$$A_V \approx A_{VN}$$


OTA Results: 0.35 μ m Process

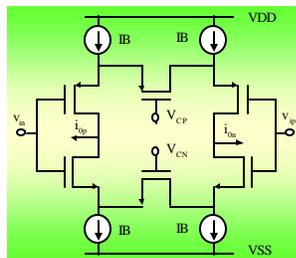

Transistor	W, L	Bias current
MN	200, 0.6 μ m	200 μ A
MCN	15, 0.6 μ m	0 μ A
MN	200, 0.6 μ m	200 μ A
MCN	30, 0.6 μ m	0 μ A

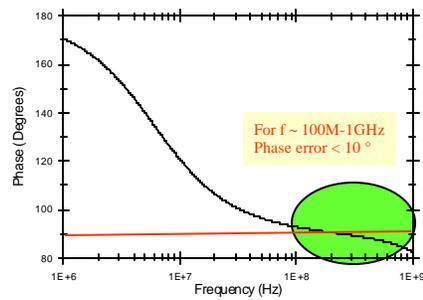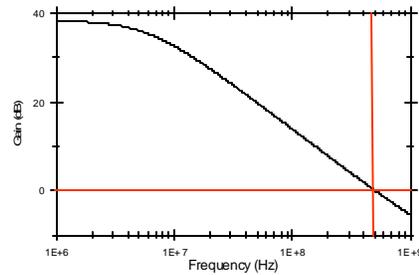

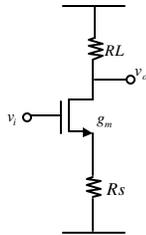
Wide Output and Good Linearity Observations



N-driver Transconductor

$$G_m = \frac{g_m}{1 + g_m R_s} = \frac{1}{\frac{1}{g_m} + R_s}$$
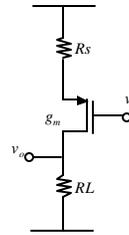
$$A_v = -G_m R_L = \frac{-R_L}{\frac{1}{g_m} + R_s}$$




P-driver Transconductor

- In order to make A_v or G_m independent of g_m , it is required that $R_s \gg 1/g_m$
- Large R_s take up large area and have large parasitic capacitances which limit the amplifier bandwidth.
- It would be desirable to have A_v (G_m) independent of g_m with small R_s

Next we introduce a wideband voltage amplifier, however a similar approach might be used to derive a transconductance amplifier whose G_m could be nearly $1/R$ without requiring a large g_m associated with driver transistor.

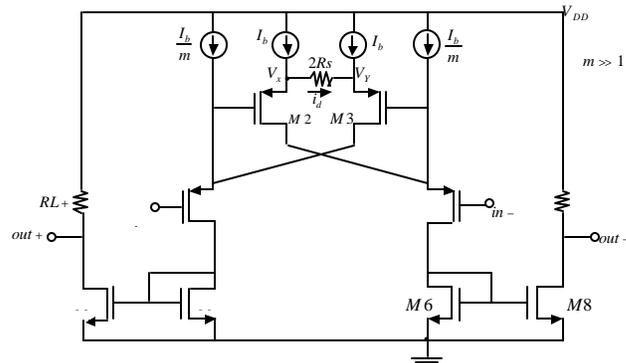
Wide Output Swing and Improved Linearity Amplifier



- This circuit is capable to cancel the effect of g_{m1} , g_{m4}
- We need to force the DC components of V_x and V_y to be equal, such that the current through $2R_s$ is only a function of the differential input $v_{in}^+ - v_{in}^- = v_d$, thus i_d becomes $v_d/2R_s$.
- Condition to satisfy

$$v_{g_{s1}} + v_{g_{s2}} = v_{g_{s4}} + v_{g_{s3}} \Rightarrow V_x = V_y$$

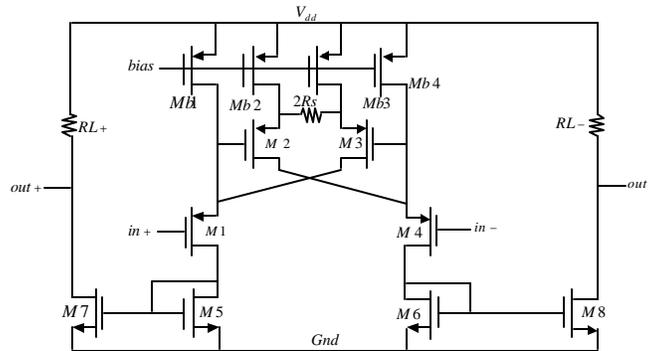Amplifiers with Wide Output Swing and Good Single-Ended Linearity A Circuit Implementation.



Resistively loaded MOS amplifier with g_m cancellation.


$$V_{gs1} + V_{gs2} = V_{gs3} + V_{gs4}$$

$$i_{2RS} = (v_{in}^+ - v_{in}^-) / 2R_S = v_d / 2R_S$$

$$\text{If } I_{b1,b4} \ll I_{b2,b3} \text{ then } A_v \cong \frac{R_L (W/L)_7}{R_S (W/L)_5}$$

A Bipolar Amplifier version is next shown.

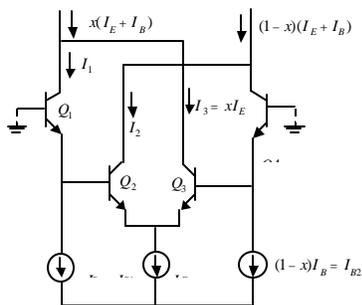
This Circuit is called Gilbert Gain Cell.



$$\frac{I_2}{I_3} = \frac{I_{B2}}{I_{B1}} = \frac{I_4}{I_1}$$

$$I_{o1} = (I_1 + I_3) - (I_2 + I_4)$$
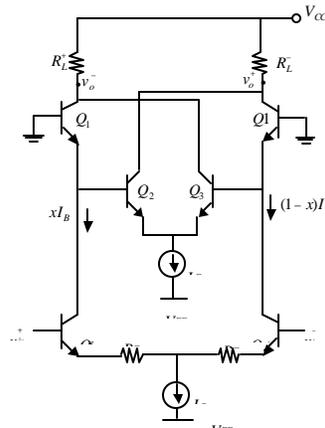
$$A_v = \frac{I_o}{I_{in}} = \frac{I_B + I_E}{I_B}$$



$$A_v = \frac{v_o}{v_{in}} = \frac{R_L}{R_E} \left(1 + \frac{I_E}{I_B} \right)$$


The dominant pole is placed at

$$w_p = \frac{w_T}{\dots}$$

Reference

A.B. Grebene, "Bipolar and MOS Analog Integrated Circuit Design", John Wiley & Sons, New York 1984.

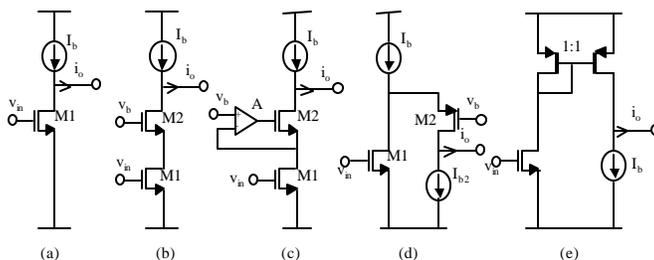Single-input Transconductor Implementations



Single Input (a) Negative Simple Transconductor, (b) Cascode Transconductor, (c) Enhanced Transconductor, (d) Folded-Cascode Transconductor, (e) Positive Simple Transconductor.

- Observe that:
 $g_m = f(I_b)$, the exact relation is a function of the transistor region of operation.
- Note that output impedance of (a) is only $1/g_{ds1}$ and (b) and (c) implementations have larger output impedances.

Properties of Simple Transconductors


Structure/ Figure	R_{out}	Min V_{DD}^*
Simple/1(a)	$\frac{1}{g_{ds1}}$	$\sqrt{\frac{2I_B}{k}} + V_{sat,I_B}$
Cascode/1(b)	$\frac{g_{m2}}{g_{ds1} g_{ds2}}$	$(1+m)\sqrt{\frac{2I_B}{k}} + V_{sat,I_B}$
Enhanced/1(c)	$\frac{A g_{m2}}{g_{ds1} g_{ds2}}$	$(1+m)\sqrt{\frac{2I_B}{k}} + V_{sat,I_B}$
Folded/1(d)	$\frac{g_{m2}}{g_{ds1} g_{ds2}}$	$\sqrt{\frac{2I_B}{k}} + V_{TP} + V_{sat,I_B}$

* The bottom devices of the cascode pairs have an aspect ratio of $(W/L)_1/(W/L)_2 = m^2$. k is a technological parameter determined by the mobility, and the gate oxide; V_{sat,I_B} is the saturation voltage for the I_B current source.

A Transconductance Amplifier with $G_m = 1/R$


An option to have a transconductance proportional to $1/R$ without requiring a large g_{m2}

g_{m2}

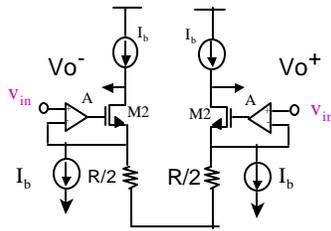

Active Frequency Compensation Transconductor

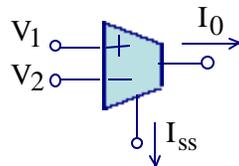
[J. Ramirez-Angulo and E. Sanchez-Sinencio, "Active Compensation of Operational Transconductance Amplifier Filters Using Partial Positive Feedback," IEEE Journal of Solid-State Circuits, vol. 25, No. 4, pp. 1024-1028, August 1990]



$$I_0 = g_m (V_1 - V_2)$$

$$g_m(s) = g_{m0} \left(1 - \frac{s}{\omega} \right)$$

ω depends on I_{SS}

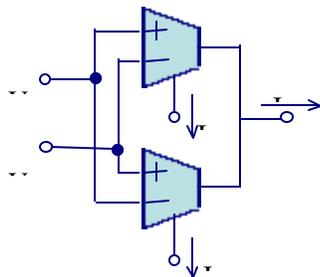


$$I_0 = (g_{mP}(s) - g_{mN}(s)) \Delta V = g_{meff}(s) \Delta V$$

$$g_{meff}(s) = g_{meff0} \left[1 - \frac{s}{\omega_{eff}} \right]$$

$$g_{meff0} = g_{mPo} - g_{mNo}, \quad \omega_{eff} = \frac{g_{meff0}}{\frac{g_{mPo}}{\omega_P} - \frac{g_{mNo}}{\omega_N}}$$

It is possible to make

Passive OTA Excess Phase Compensation

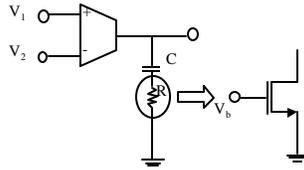


How to determine the value of RC ?


The R is implemented with a transistor operating in the triode (ohmic) region.

The zero generated by the RC should cancel the dominant pole of $G_m(s)$.

Two-integrator biquads

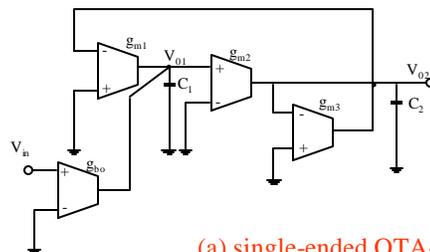

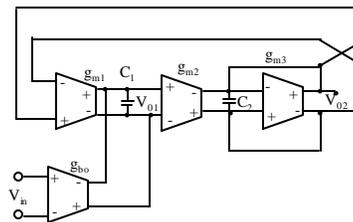(a) single-ended OTA-C Biquad with one input




(b)

Fully differential OTA-C Biquad

Analog and Mixed Signal Center, TAMU

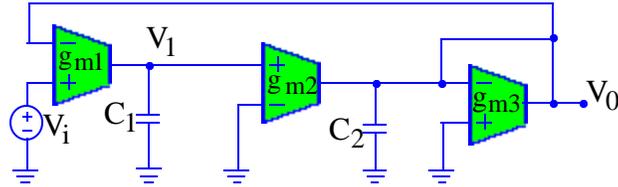OTA Specifications in Open Loop Applications



$$V_1 = \frac{1}{sC_1} g_{m1} (V_i - V_0) \quad (1)$$

$$V_0 = (g_{m2} V_1 - g_{m3} V_0) \frac{1}{sC_2} \quad (2)$$

(1) into (2)

$$(sC_2)V_0 = \left[g_{m2} \frac{g_{m1}}{sC_1} (V_i - V_0) - g_{m3} V_0 \right]$$

$$V_0 \left[sC_2 + \frac{g_{m1}g_{m2}}{sC_1} + g_{m3} \right] = \frac{g_{m1}g_{m2}}{sC_1} V_i$$

$$H_{LP}(s) = \frac{V_0}{V_i} = \frac{g_{m1}g_{m2}}{s^2 C_1 C_2 + sC_1 g_{m3} + g_{m1}g_{m2}} = \frac{\frac{g_{m1}g_{m2}}{C_1 C_2}}{s^2 + s \frac{g_{m3}}{C_2} + \frac{g_{m1}g_{m2}}{C_1 C_2}}$$

$$\omega_o^2 = \frac{g_{m1}g_{m2}}{C_1 C_2} \quad , \quad BW = \frac{\omega_o}{Q} = \frac{g_{m3}}{C_2}$$

$$Q = \frac{1}{g_{m3}} \sqrt{\frac{g_{m1}g_{m2}C_2}{C_1}} = \frac{C_2 \omega_o}{g_{m3}}$$

Now let's assume the transconductance is characterized by:

$$g_m = g_{m0} e^{-s/\omega_p} \cong g_{m0} \left(1 - s/\omega_p\right) \text{ for } \omega_p \ll \omega_o.$$

Under this condition the excess phase can be expressed as $\phi_E \cong \omega_o/\omega_p$.

Note that ideally $\phi_E = 0^\circ$.

then,

$$H_{LP}(s) = \frac{g_{m1} g_{m2} (1 - s/\omega_{p1})(1 - s/\omega_{p2})}{s^2 C_1 C_2 + s C_1 g_{m3} (1 - s/\omega_{p3}) + g_{m1} g_{m2} (1 - s/\omega_{p1})(1 - s/\omega_{p2})}$$

$$D(s) = s^2 C_1 C_2 + s C_1 g_{m3} - s^2 \frac{C_1 g_{m3}}{\omega_{p3}} + g_{m1} g_{m2} \left[1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \right]$$

$$D(s) = s^2 \left\{ C_1 C_2 - \frac{C_1 g_{m3}}{\omega_{p3}} + \frac{g_{m1} g_{m2}}{\omega_{p1} \omega_{p2}} \right\} + s \left\{ C_1 g_{m3} - \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) g_{m1} g_{m2} \right\} + g_{m1} g_{m2}$$

Then the actual ω_{oa} and BW_a become

$$\omega_{oa}^2 = \frac{g_{m1} g_{m2}}{C_1 C_2 + \frac{g_{m1} g_{m2}}{\omega_{p1} \omega_{p2}} - \frac{C_1 g_{m3}}{\omega_{p3}}}$$

$$BW_a = \frac{\omega_{oa}}{Q_a} = \frac{C_1 g_{m3} - \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) g_{m1} g_{m2}}{C_1 C_2 - \frac{C_1 g_{m3}}{\omega_{p3}} + \frac{1}{\omega_{p1} \omega_{p2}}}$$

Let us also assume that $\omega_{p1} = \omega_{p2} = \omega_p$, then $\omega_{oa} \cong \omega_o$, thus,

$$BW_a = \frac{\omega_{oa}}{Q_a} = \frac{C_1 g_{m3} - \frac{2}{\omega_p} g_{m1} g_{m2}}{C_1 C_2 - \frac{C_1 g_{m3}}{\omega_p} + \frac{1}{\omega_p^2}} \cong \frac{C_1 g_{m3} - \frac{2}{\omega_p} g_{m1} g_{m2}}{C_1 C_2}$$

$$BW_a \cong \frac{g_{m3}}{C_2} - \frac{g_{m1} g_{m2}}{C_1 C_2} \cdot \frac{2}{\omega_{p1}} = BW - \omega_{oa}^2 \cdot \frac{2}{\omega_{p1}} = BW - \frac{2\omega_{oa}^2}{\omega_{p1}}$$

$$Q_a = \frac{\omega_{oa}}{BW_a} \cong \frac{1 \cdot \omega_{oa}}{\frac{g_{m3}}{C_2} - \frac{2}{\omega_{oa}} \cdot \frac{2}{\omega_{p1}}}$$

$$Q_a = \frac{\frac{C_2 \omega_{oa}}{g_{m3}}}{1 - \frac{C_2 \omega_{oa}}{g_{m3}} \cdot \frac{2\omega_{oa}}{\omega_{p1}}} = \frac{Q}{1 - \frac{Q_2 \omega_{oa}}{\omega_{p1}}} = \frac{Q}{1 - \frac{2\omega_{oa}}{\omega_{p1}} Q}$$

Alternatively, Q_a can be expressed in terms of the excess phase $\phi_E = \tan^{-1} \frac{\omega_o}{\omega_p} \cong \frac{\omega_o}{\omega_p}$ then

$$Q_a \cong \frac{Q}{1 - 2\phi_E Q} \cong Q(1 + 2\phi_E Q)$$

Furthermore, if $A_{vo} = g_m R_o$ is taken into account, then

$$Q_a = \frac{Q}{1 + \frac{2Q}{A_{vo}}}$$

If $A_{vo} = 500$

$$Q_a = \frac{Q}{1 + 4 \times 10^{-3} Q}$$

Notethat :

$$Q_a \downarrow \text{ when } A_{vo} \downarrow$$

$$BW_a \downarrow \quad Q_a \uparrow \text{ when } \phi_E \uparrow$$

Q	Q_a
1	0.996
5	4.902
10	9.6
50	41.667