

problem 1 solution:(i) a) two poles at $p_{1,2} = -\frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$

$$\text{TF: } H(s) = \frac{k}{(s-p_1)(s-p_2)} = \frac{k}{s^2 + \sqrt{2}s + 1}$$

$$\text{at } s=0 \quad H(s) \Big|_{s=0} = 1 \Rightarrow \underline{k=1}$$

$$\therefore \boxed{H(s) = \frac{1}{s^2 + \sqrt{2}s + 1}}$$

(b) two poles at $p_{1,2} = -\frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$
one zero at $z=0$

$$\text{TF: } H(s) = \frac{k s}{s^2 + \sqrt{2}s + 1}$$

$$\text{at } \omega=1: |H(s)| \Big|_{s=1} = 1 \Rightarrow \frac{k}{\sqrt{2}} = 1$$

$$\therefore \boxed{H(s) = \frac{\sqrt{2}}{1} \frac{s}{s^2 + \sqrt{2}s + 1}}$$

(c) Two poles at $p_{1,2} = -\frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$
double zero at $z=0$

$$\text{TF: } H(s) = \frac{k s^2}{s^2 + \sqrt{2}s + 1}$$

$$\text{at } \omega=1 \quad |H(s)| \Big|_{s=1} = 1 \Rightarrow \frac{k}{\sqrt{2}} = 1$$

$$\boxed{H(s) = \frac{\sqrt{2} s^2}{s^2 + \sqrt{2}s + 1}}$$

(d) two poles at $p_{1,2} = -\frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$
 two zeros at $z_{1,2} = \frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$

TF: $H(s) = k \frac{s^2 - \sqrt{2}s + 1}{s^2 + \sqrt{2}s + 1}$

at $\omega=0$ $|H(s)|_{s=0} = 1 \Rightarrow \underline{k=1}$

$$H(s) = \frac{s^2 - \sqrt{2}s + 1}{s^2 + \sqrt{2}s + 1}$$

(e) two ~~poles~~ poles at $p_{1,2} = -\frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$
 two zeros at $z_{1,2} = \pm j$


TF: $H(s) = k \frac{(s+j)(s-j)}{s^2 + \sqrt{2}s + 1} = k \frac{s^2 + 1}{s^2 + \sqrt{2}s + 1}$

at $\omega=0$ $|H(s)|_{s=0} = 1 \Rightarrow k=1$

$$\therefore H(s) = \frac{s^2 + 1}{s^2 + \sqrt{2}s + 1}$$


(1)

a)

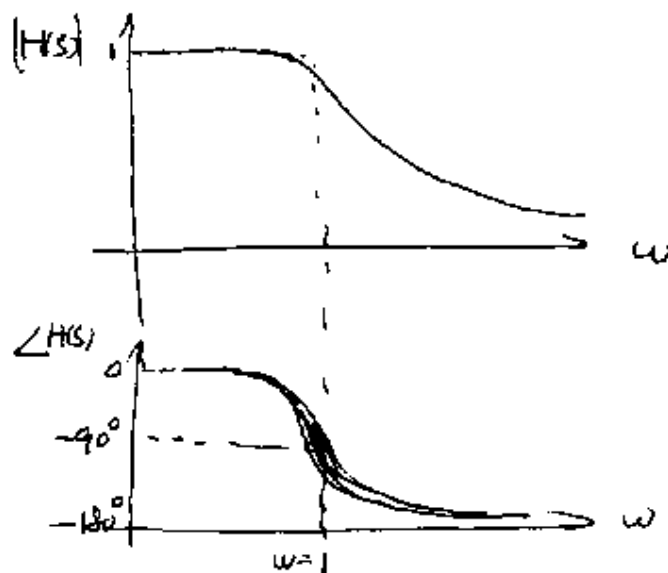


LP Filter

(b)

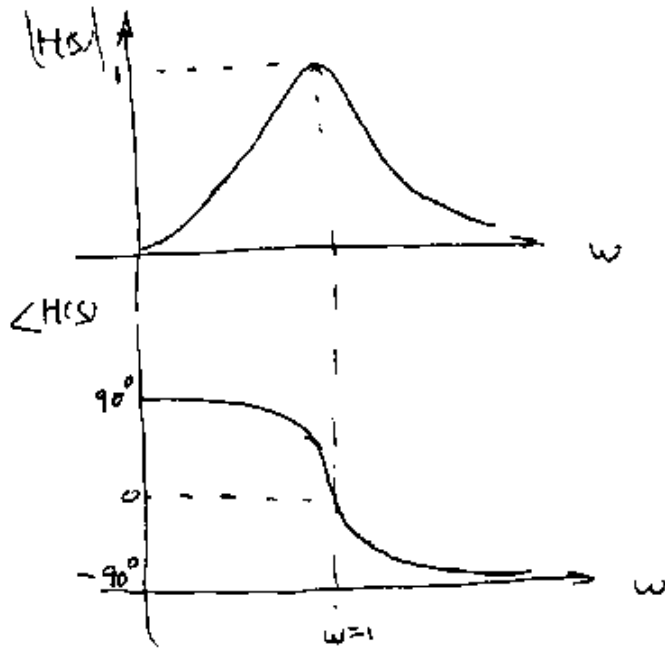


BP Filter

(c)

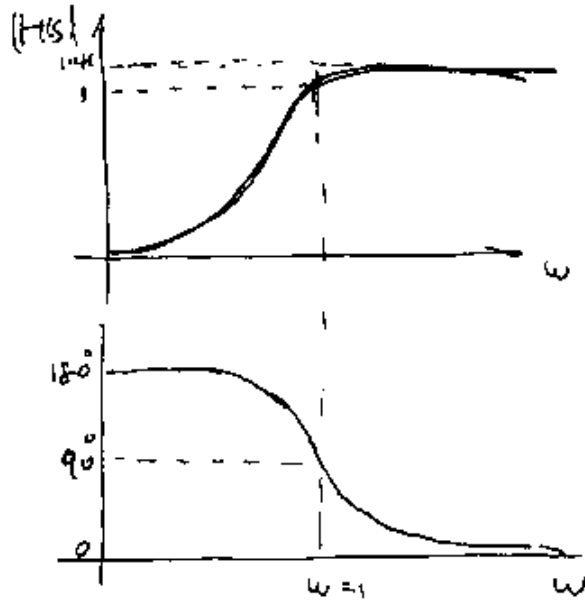


HP Filter

(d)

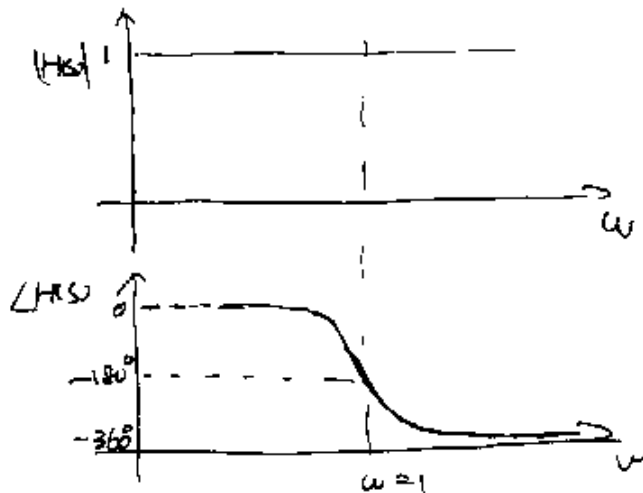


AP Filter

(e)

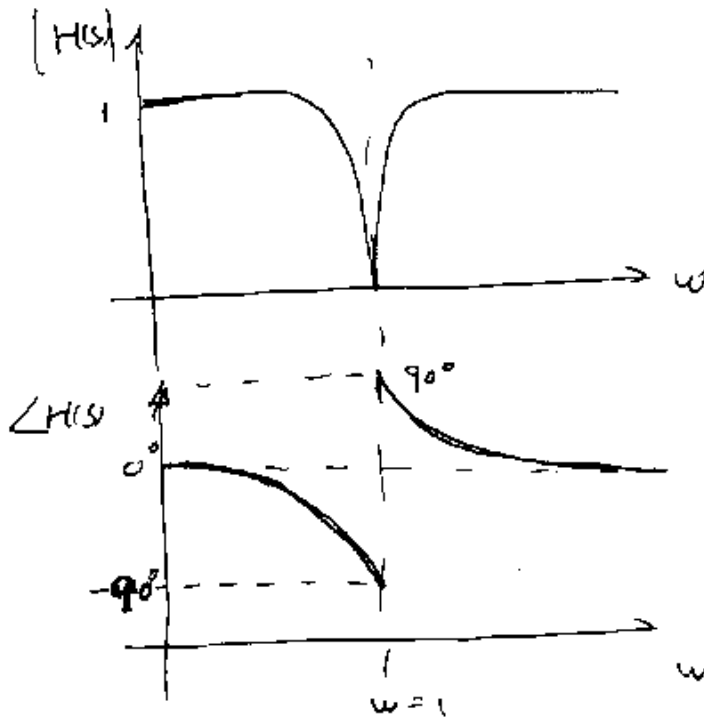

BS Filters

problem 2 solution

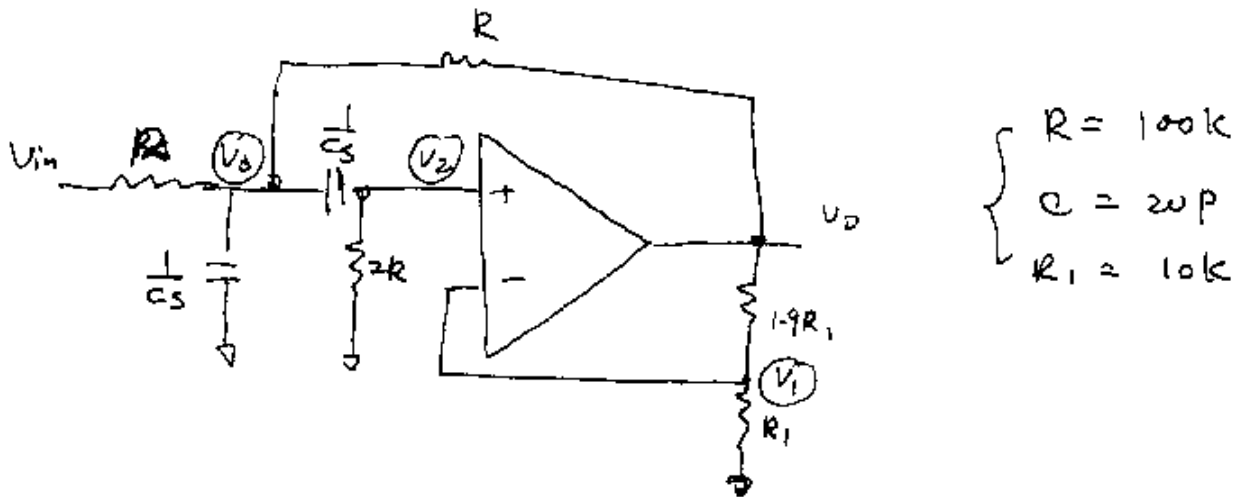

Set $\left\{ \begin{aligned} A &\equiv \frac{R_1 + 1.9R_1}{R_1} = 2.9 \\ \beta &\equiv RCs \end{aligned} \right. \leftarrow$

For ideal op. we have:

$$V_2 = V_1 = \frac{R_1}{R_1 + 1.9R_1} V_o = \frac{V_o}{A} \quad \text{(A)}$$

$$V_2 = V_3 \cdot \frac{2R}{2R + \frac{1}{Cs}} = V_3 \frac{2CRs}{2CR + 1} = V_3 \frac{2\beta}{2\beta + 1}$$

or
$$V_3 = \frac{2\beta + 1}{2\beta} \cdot \frac{V_o}{A} \quad \text{(B)}$$

For node V_3 :

$$\sum i = 0 \Rightarrow \frac{V_i}{R} + \frac{V_o}{R} + \frac{V_2}{\frac{1}{Cs}} = V_3 \left[\frac{1}{R} + \frac{1}{R} + \frac{1}{sC} + \frac{1}{sC} \right]$$

$$\Rightarrow V_i = -V_o - \beta V_2 + V_3 \beta [1 + \beta] \quad \text{(C)}$$

By (C) & (B) we have,

$$V_i = -V_o - \frac{\beta}{A} V_o + \frac{2\beta+1}{\beta} \frac{1}{A} \times [1+\beta] V_o$$

$$\Rightarrow V_i = \frac{1}{\beta A} [-\beta A + \beta^2 + (1+\beta)(2\beta+1)] V_o$$

$$\therefore \frac{V_o}{V_i} = \frac{\beta A}{1 + \beta^2 + (\beta - A)\beta}$$

or
$$\frac{V_o}{V_i} = \frac{A R C s}{1 + (R C)^2 s^2 + (\beta - A) R C s}$$


$$A = \frac{R_1 + 1.9 R_1}{R_1 + 1.9 R_1} = 2.9$$

$$\frac{V_o}{V_i} = \frac{2.9 R C s}{1 + (R C)^2 s^2 + \frac{R C}{10} s}$$


$$\omega_0 = \left(\frac{1}{R C}\right)^{\frac{1}{2}} = \frac{1}{100k \times 20p} = 500k \text{ rad/s}$$


$$\approx \frac{500k}{2\pi} \approx 80 \text{ KHz}$$

$$\underline{\underline{Q = 10}}$$

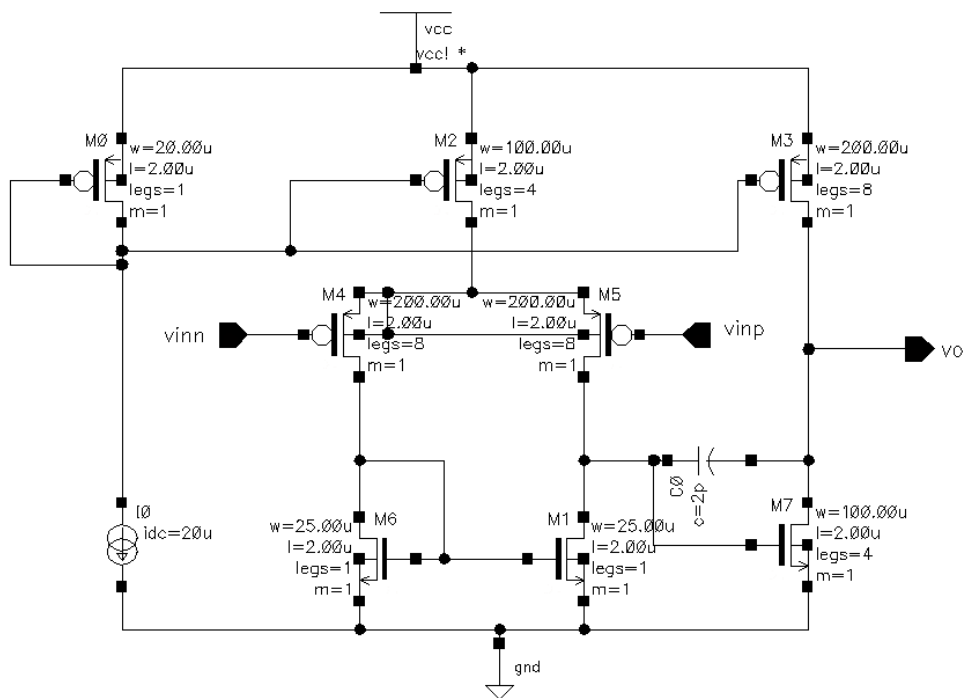


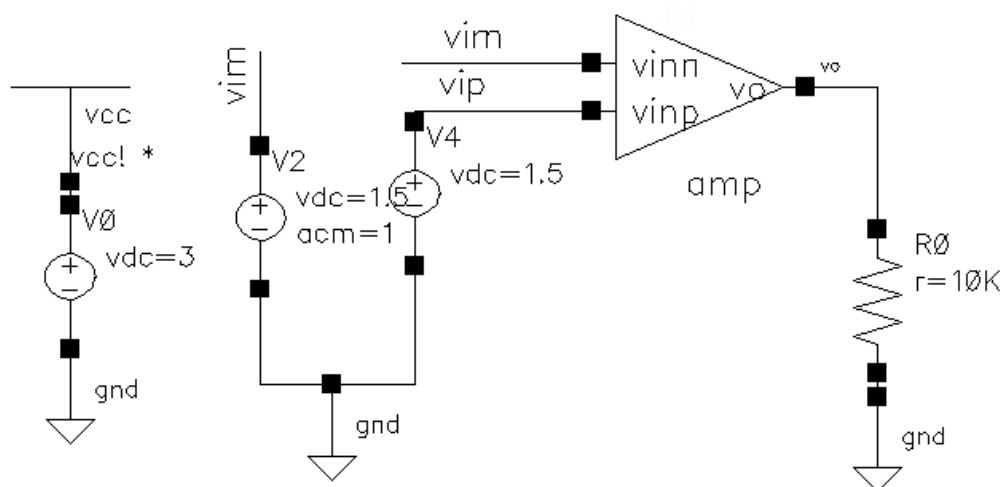Note that there is no negative bias. The following figure shows the test circuit of the opamp. The power supply is 3V, and we use $V_{cc}/2$ as the common mode voltage.




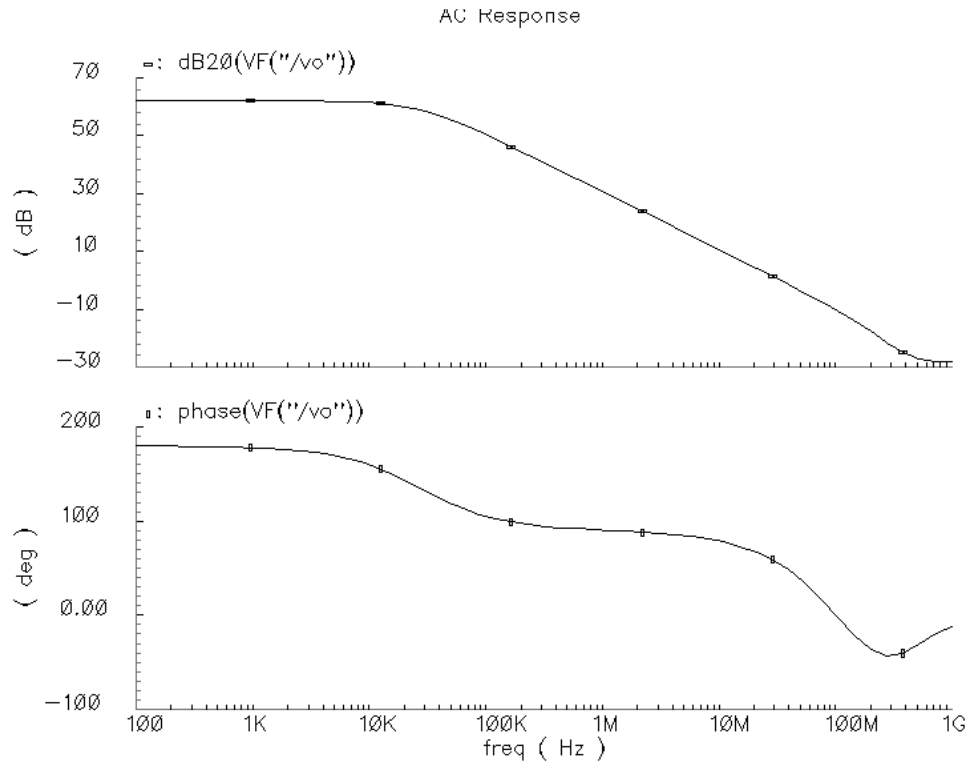

Bode plot of the opamp.

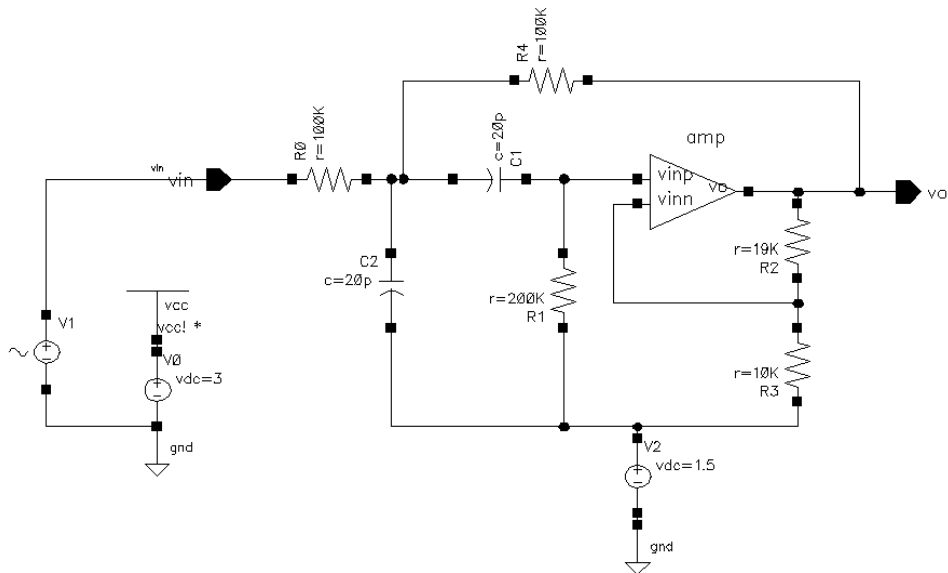

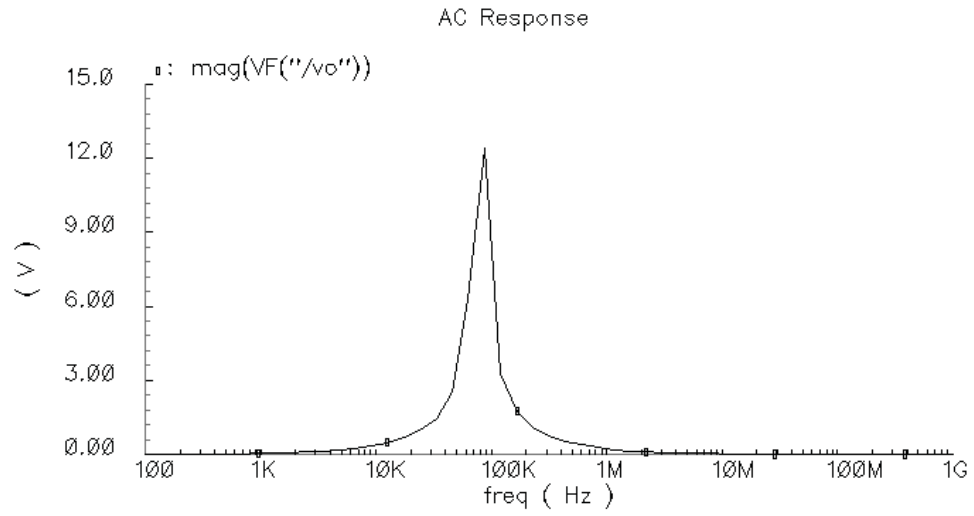Simulation circuit of the filter. Note that the reference of the circuit is $V_{cc}/2=1.5$.



Output character of the filter. The ac magnitude of the input signal is 1V.