

Subject: EEE598D Homework #3
 From: Dr. Hongjiang Song
 Due Date: February 12, 2002

A fully differential CMOS transconductor circuit is shown in Fig.1.

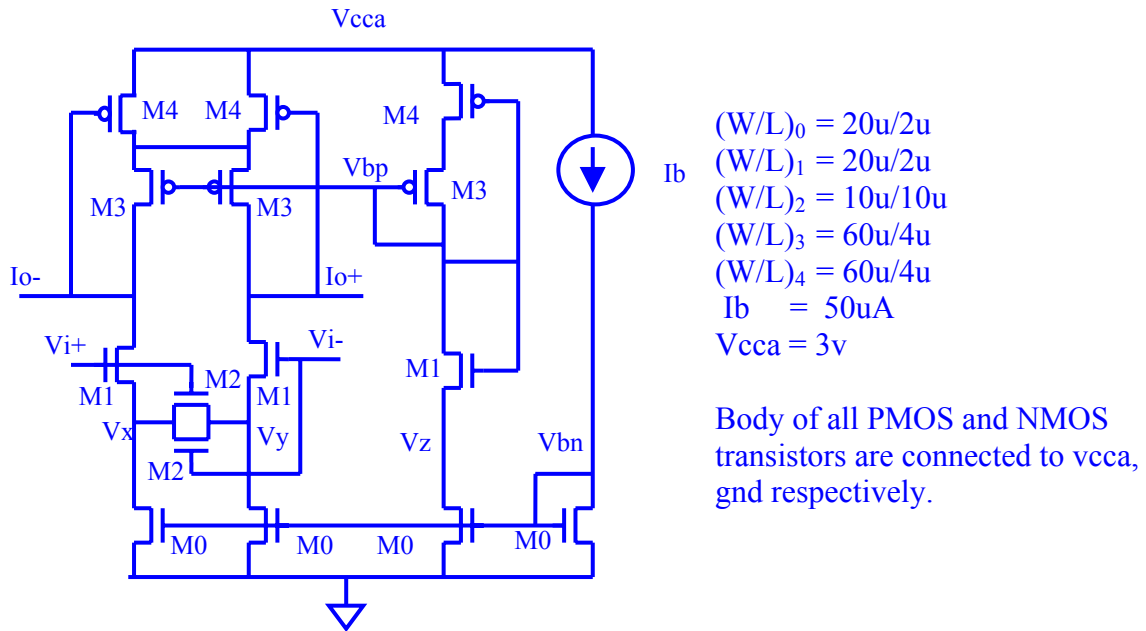


Fig.1 Fully differential CMOS transconductor circuit

Problem 1. Derive the expression of differential transconductance g_m of this circuit and calculate g_m for the 0.5 μm CMOS process (given in Homework#1). (Assuming 1.5v input common-mode voltage and neglecting body effects)

Problem 2. Simulate the differential g_m for the 1V peak-to-peak input voltage and a 1k resistive load across I^+ and I^- . Plot I (across R) and g_m vs. $(v_i^+ - v_i^-)$. Extract a_2 and a_3 from your simulation data using the curve fitting technique. Where a_2 and a_3 are non-linearity parameters defined as:

$$I^+ - I^- = I = g_m (V_i^+ - V_i^-) + a_2 (V_i^+ - V_i^-)^2 + a_3 (V_i^+ - V_i^-)^3$$