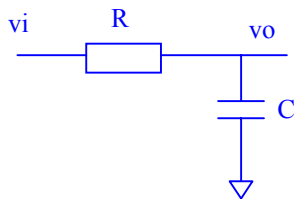


Subject: EEE598D Homework#4
From: Dr. Hongjiang Song
Due Date: February 19, 2002

Problem 1 (s-z- transformations)

For the lowpass continuous-time filter shown in Fig. 1, find the z-domain transfer functions $H(z)$ and plot gain and phase responses versus frequency $\log \omega$ ($0.0001\pi/T < \omega < \pi/T$) (i.e. BodePlots) under

- 1) Forward Euler
- 2) Backward Euler
- 3) Bilinear, and
- 4) LDI (or midpoint) transformations



$$H_A(s) \equiv \frac{V_o(s)}{V_i(s)} = \frac{p}{p + s}$$
$$p \equiv \frac{1}{RC}$$

(Assuming $2\pi/T = 100\text{p}$).

Problem2 (warm-up reading assignment for the SC filters)

For the rest of the course (homework/course project) we are going to use the SWITCAP program as one of the tools for SC circuit simulation. A manual/tutorial of SWITCAP can be download from

http://vlsi-libra.teipir.gr/w_flash/book5/switcap/tutor.htm

Read through this tutorial and answer the following questions:

- 1) What is SWITCAP used for?
- 2) What types of circuit components are used in SWITCAP?
- 3) What kind of analysis can SWITCAP do?

A DOS version of SWITCAP can be found at

<http://vlsi-libra.teipir.gr/anakoinosi.html>