

ROM

Types:
ROM
PROM
EPROM
EEPROM


3-94
أبراهيم عاصم

HOW ROM works

It consists of a decoder and OR gates.
In general Memory has address and Data lines.
We call a ROM with n address lines and m data lines $2^n \times m$ memory
This memory has n words, each word is m bits



3-95
أبراهيم عاصم

 

From the previous discussion its clear that each output of the ROM represents a SOP

Ex.

$$F_0 = \Sigma(1, 3, 5, 6, 7)$$

$$F_1 = \Sigma(0, 3, 4, 6, 7)$$

$$F_2 =$$

$$F_3 =$$

3-97
أبراهيم عاصم

Another example


Assume we want to build the Following Ckt that has two inputs and three outputs

$$F_0 = \Sigma(1,3)$$

$$F_1 = \Sigma(0,3)$$

$$F_2 = \Sigma(0,1,2)$$

 We can build this Ckt using a 4×3 ROM = $2^2 \times 3$ bit ROM
This ROM is built from a decoder, OR gates



Q. What is the Data stored in this ROM?

3-99

أبراهيم/أبو

BCD to Ex.3 Converter

What is the size of the ROM needed?

What will be the data stored?

BCD to 7 segment Converter

What is the size of the ROM needed?

What will be the data stored?

3-100
أبراهيم/أبو

Combinational vs. Sequential

Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- example: ticket counter
 - advances when you push the button
 - output depends on previous state
- useful for building "memory" elements and "state machines"

3-101
أبراهيم/أبو

Sequential Logic

Synchronous sequential circuits:

A system whose behavior can be defined from the knowledge of its signals at discrete instants of time.

Asynchronous sequential circuits: a system whose behavior depends on the order which its input signals changes at any instance of time

3-102
وراثي قسمان

 


Fig. 5-1 Block Diagram of Sequential Circuit

3-103
وراثي قسمان

 


Fig. 5-2 Synchronous Clocked Sequential Circuit

3-104
وراثي قسمان

Flip Flops



 


Fig. 5-3 SR Latch with NOR Gates


3-105
وراثي قسمان

 


3-106
أول فصل

 

3-107
أول فصل

 


3-108
أول فصل

 

 
3-109
أول فصل

Clearing the R-S latch

Suppose we start with output = 1, then change R to zero.



Output changes to zero.

 


Then set R=1 to "store" value in quiescent state.

 
3-110
أبراهيم/ABU

Setting the R-S Latch

Suppose we start with output = 0, then change S to zero.



Output changes to one.

 

Then set S=1 to "store" value in quiescent state.

3-111
أبراهيم/ABU

R-S Latch Summary

$$R = S = 1$$

- hold current value in latch

$$S = 0, R = 1$$

- set value to 1

$$R = 0, S = 1$$

- set value to 0

$$R = S = 0$$


- both outputs equal one
- final state determined by electrical properties of gates
- Don't do it!

3-112
أبراهيم/ABU

Gated D-Latch

Two inputs: D (data) and WE (write enable)

 - when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$



3-113
أبراهيم/ABU

Characteristic equations


Remember that the output depends on the inputs and the current state.

- First find the characteristic table
- Then derive the characteristic equation for the RS flip flop.

SR

	0	0	X	1
Q	1	0	X	1


$$Q(t+1) = S + R'Q$$

 

Qt	S	R	Q _{t+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

3-114
وراثن/أبوالحسن

Characteristic equation for D flip flop

 

(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	$Q = 0$, Reset state
1	1	$Q = 1$, Set state

(b) Truth table

Qt	D	Q _{t+1}
0	0	0
0	1	1
1	0	0
1	1	1

0	1
0	1

$$Q(t+1) = D$$


3-115
وراثن/أبوالحسن

J K flip flop

It's a refinement of RS flip flop , that defined the indeterminate states in RS.

In RS flip flop the state 11 is not allowed ,

 In JK flip flop the state 11 makes the flip flop changes (switches) its output.



3-116
وراثن/أبوالحسن


Problem in JK flip flop:

- When $J=1, K=1$ and the clock is 1 , $Q_{t+1}=Q'_t$
- Assume $Q=1$, it will flip to 0 then to 1 then to 0 and so on as long as the clock is 1.
- To avoid that the clock pulse (duration) must be less than the propagation delay of the Flip flop.
- But this is not a solution.
- The solution is to build a Master slave or edge triggered construction.

3-117
وراثن/أبوالحسن

Characteristic table and Equation

Q_t	J	K	Q_{t+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


$$Q(t+1) = JQ' + K'Q$$

3-118 وراثي قسمان


T flip flop

It's a single input version of the JK Flip flop

 T flip Flop has the same
Problem of JK when T=1



Q_t	T	Q_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q(t+1) = TQ' + T'Q$$

3-119 وراثي قسمان

 


Fig. 5-83 Clock Responses in Latch and Flip-Flop

3-120 وراثي قسمان

Master Slave D flip flop


 
 


Fig. 5-9 Master-Slave D Flip-Flop

3-121 وراثي قسمان

Master Slave RS flip flop

 

When $CLK = 0$, gates 2,3 are not working, gate 2=1, gate3=1 $\Rightarrow R=1, S=1$

\Rightarrow No change in the output.

If $D=0$; Gate 4=1, Gate1 =0.

If $D=1$; Gate 4=0, Gate1 =1.


IF $D=0 \Rightarrow$ Gate1=0, Gate4=1, Gate2=1, Gate3=1;
and CLK goes to 1

Gate 4=1, Gate 3=0, Gate1=0; Gate 2=1;

After the CLK being 1, if D changed to 1, this will not affect on Gate 4 , nor any other gates.

IF D=1 ➔ Gate1=1, Gate4=0, Gate2=1, Gate3=1;
 and CLK goes to 1
Gate 4=0, Gate 3=1, Gate1=1; Gate 2=0;
 After the CLK being 1, if D changed to 0, Gate 4 =1 , other gates will not affect by this change.

3-126
أول فصل

 


(a) Positive-edge (b) Negative-edge

Fig. 5-11 Graphic Symbol for Edge-Triggered D Flip-Flop


3-127
أول فصل

JK flip Flop from D flip flop

 

(a) Circuit diagram
Fig. 5-12 JK Flip-Flop

3-128
أول فصل

 

(a) From OR flip-flop
(b) Logic D flip-flop

(c) Graphic symbol

Fig. 5-13 T T' flip-flop

3-129
أول فصل

Analysis of sequential circuit

The behavior of a seq. ckt is determined from

- a) Inputs
- b) Outputs
- c) States of its flip flop


Both outputs and next state are function of input and present state.

From a seq. ckt diagram , we will find the

- a) state table
- b) State diagram

3-130
أول فصل من

Example

 

3-131
أول فصل من


State Table

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
AB	AB	AB	Y	Y
00	00	01	0	0
01	11	01	0	0
10	10	00	0	1
11	10	11	0	0

 3-132
أول فصل من

State diagram

The state table can be represented graphically using the state diagram. Transition from a state to state is shown as arrow labeled with two values (Input/output)



3-133
أول فصل من

State equation

State equation (or application equation) is an expression that shows the relation for the next state of each flip flop as a function of the present state and the inputs,

Method 1: using the characteristic equation of the flip flop

$$\begin{aligned}A(t+1) &= S + R'Q \\&= X \cdot B + (X \cdot B')'A \\&= X \cdot B + (X' + B) \cdot A \\&= X' \cdot B + X \cdot A + A \cdot B \\B(t+1) &= S + R'Q \\&= X \cdot A' + (X' \cdot A)' \cdot B \\&= X \cdot A' + X \cdot B + A' \cdot B\end{aligned}$$

3-134
أول فصل من AABU

State equation

Method 2:

From the state table.

$$\begin{aligned}A(t+1) &= (A'B + AB' + AB) \cdot X' + ABX \\&= A'BX' + AB'X' + ABX' + ABX \\&= BX' + AX' + AB\end{aligned}$$

3-135
أول فصل من AABU

6.7 Design procedure

1. Build the state diagram
2. Build the state table
3. Assign binary values for each state
4. Determine the number of flip flops needed and assign a symbol for each flip flop
5. Choose the type of flip flop to be used (we will use JK)
6. From the state table derive the excitation and output tables
7. Simplify the flip flop functions
8. Draw the logic diagram

3-136
أول فصل من AABU


The following formulas for JK flip flop inputs will help us

- 0 to 0 J=0, K=X (don't care)
- 0 to 1 J=1, K=X
- 1 to 0 J=X, K=1
- 1 to 1 J=X, K=0

3-137
أول فصل من AABU

 Example 1

Design a circuit that works as a counter from 0 to 3 if the input x is 1 and stay in the same state if x is 0



3-138
أبريل/أبريل ٢٠١٨

State table

AB	X=0	X=1
00	00	01
01	01	10
10	10	11
11	11	00

We have 4 states so we need 2 flip flops

3-139
أبريل/أبريل ٢٠١٨

Excitation table

A B X	Next state		flip flop inputs			
	A	B	JA	KA	JB	KB
0 0 0	0	0	0	X	0	X
0 0 1	0	1	0	X	1	X
0 1 0	0	1	0	X	X	0
0 1 1	1	0	1	X	X	1
1 0 0	1	0	X	0	0	X
1 0 1	1	1	X	0	1	X
1 1 0	1	1	X	0	X	0
1 1 1	0	0	X	1	X	1

Now we need to simplify the equation of each flip flop input

3-140
أبريل/أبريل ٢٠١٨

0	0	1	0
x	x	x	X

$$JA=Bx$$

x	x	x	x
0	0	1	0

$$KA=Bx$$

0	1	x	X
0	1	x	x

$$JB=x$$

x	x	1	0
x	x	1	0

$$KB=x$$

3-141
أبريل/أبريل ٢٠١٨

Example 2


Design a circuit that works as a down counter from 3 down to 0 if the input x is 1 and stay in the same state if x is 0

3-142
أبراهيم عاصم

Example 3

Design a sequential Ckt that generate the following sequence 000, 001, 010,100 , using JK flip flops

This circuit has 4 states

 

3-143
أبراهيم عاصم

Example 4

Repeat example 1 using RS flip flop

1) How RS Flip flop works

0 to 0 S=0, R=X (don't care)

0 to 1 S=1, R=0

1 to 0 S=0, R=1

1 to 1 S=X, R=0

2) Build the Excitation table, then simplify the equations that represents R and S for each flip flop.

3-144
أبراهيم عاصم

Excitation table

A B X	A B	Next state				flip flop inputs
		SA	RA	SB	RB	
0 0 0	0 0	0	X	0	X	
0 0 1	0 1	0	X	1	0	
0 1 0	0 1	0	X	X	0	
0 1 1	1 0	1	0	0	1	
1 0 0	1 0	X	0	0	X	
1 0 1	1 1	X	0	1	0	
1 1 0	1 1	X	0	X	0	
1 1 1	0 0	0	1	0	1	

Now we need to simplify the equation of each flip flop input


3-145
أبراهيم عاصم

<table border="1"> <tr><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>X</td><td>X</td><td>0</td><td>X</td></tr> </table>	0	0	1	0	X	X	0	X	<table border="1"> <tr><td>X</td><td>X</td><td>0</td><td>X</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td></tr> </table>	X	X	0	X	0	0	1	0
0	0	1	0														
X	X	0	X														
X	X	0	X														
0	0	1	0														
SA=	RA=																
<table border="1"> <tr><td>0</td><td>1</td><td>0</td><td>X</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>X</td></tr> </table>	0	1	0	X	0	1	0	X	<table border="1"> <tr><td>X</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>X</td><td>0</td><td>1</td><td>0</td></tr> </table>	X	0	1	0	X	0	1	0
0	1	0	X														
0	1	0	X														
X	0	1	0														
X	0	1	0														
SB=	RB=																

3-146

 
Example 5

Design an up_down counter that counts from 0 to 6, depending on the input value, if $x=0$ it counts down, if 1 it counts up




3-147

أبراهيم/أبوالفضل

 

Non-Standard Counters

 - Counters are sometimes defined that count in an order other than standard numerical order.
- The state machine below is for a *gray code* counter in which one bit changes at a time.




أبراهيم/أبوالفضل


Complete Example

A blinking traffic sign

 - No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)
- When the input is 0, No lights on



Traffic Sign State Diagram

 

Traffic Sign Truth Tables

Outputs
(depend only on state: $S_1 S_0$)

		Lights 1 and 2			Lights 3 and 4			Light 5		
		Z	Y	X	Z	Y	X	Z	Y	X
S_1	S_0	0	0	0	0	0	0	0	0	0
0	1	1	0	0	1	0	0	1	0	0
1	0	1	1	0	0	1	1	0	1	1
1	1	1	1	1	0	0	0	0	0	1

Whenever $In=0$, next state is 00.


Next State: $S_1' S_0'$
(depend on state and input)

In	Switch		$S_1' S_0'$	
	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

3-152

أول فصل

Traffic Sign Logic

 

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-2 on next slide.

Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

3-154

AABU/أبراهيم